

Poly - Phase Ckt

$\phi \rightarrow \text{phase}$

Page No.:
Date:
(13 - 15) marks
NEW LINK

Generation of a three-phase (3- ϕ) supply:

When the three identical coils are placed with their axis at 120° apart from each other & rotated in uniform magnetic field, a sinusoidal voltage is generated across each coil. This is a basic of 3- ϕ alternator shown in fig(a) aside.

Here, besides these are two, ~~the fig. aside shows~~ Here, ~~these are~~ ^{the fig. aside shows} 3- ϕ , two pole alternator. It has 3 sets of coil aa' , bb' & cc' symmetrically mounted on rotor such that their axis are at 120° from each other.

When rotor are rotated in anti-clock wise dirⁿ at a const angular velocity ~~omega~~ radian per sec, generate sinusoidal voltage across each coil.


All three coil rotate at the same velocity ($\omega = 2\pi f$) & generated voltage have the same freq. since the coil are identical. The generated voltage have same magnitude but their phase difference of 120° betⁿ these voltage.

$$V_{aa'} = V_m \sin \omega t$$

$$V_{bb'} = V_m \sin (\omega t - 120^\circ)$$

$$V_{cc'} = V_m \sin (\omega t - 240^\circ)$$

$$= V_m \sin (\omega t + 120^\circ)$$

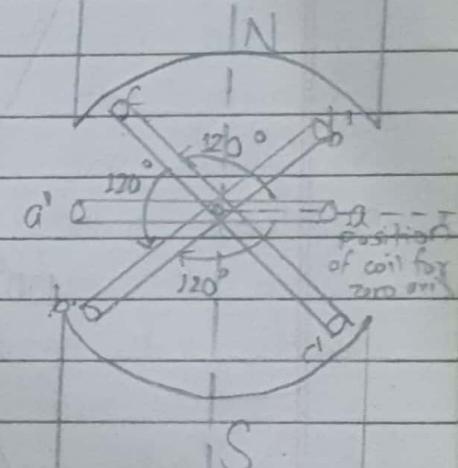

fig(a). Generation of 3- ϕ supply

In polar form,

$$V_{aa'} = V \angle 0^\circ$$

$$V_{bb'} = V \angle -120^\circ$$

$$V_{cc'} = V \angle -240^\circ \text{ or } V \angle +120^\circ$$

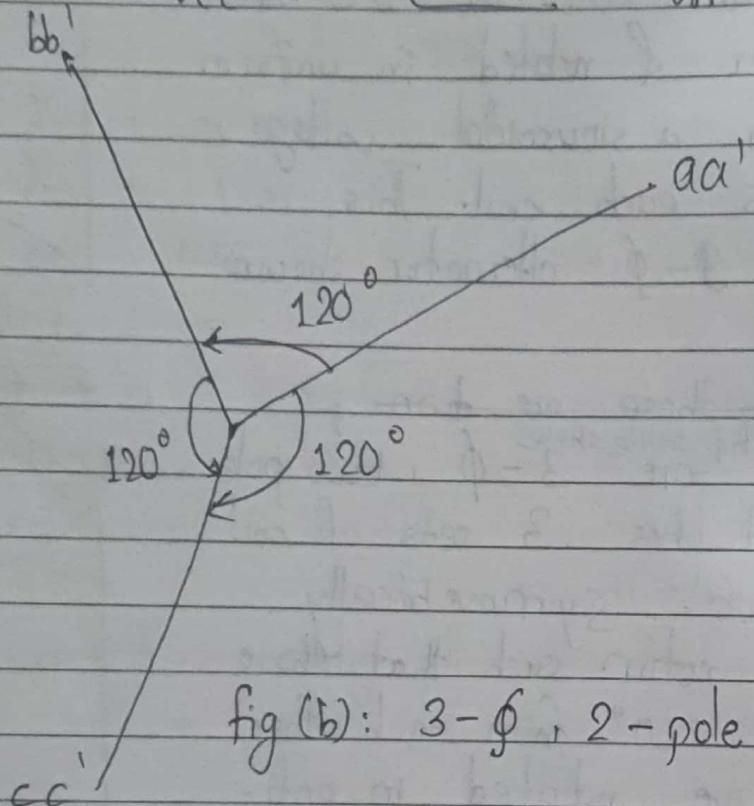


fig (b): 3-φ, 2-pole attenuator

The voltage waveform is as shown in fig(c). below:

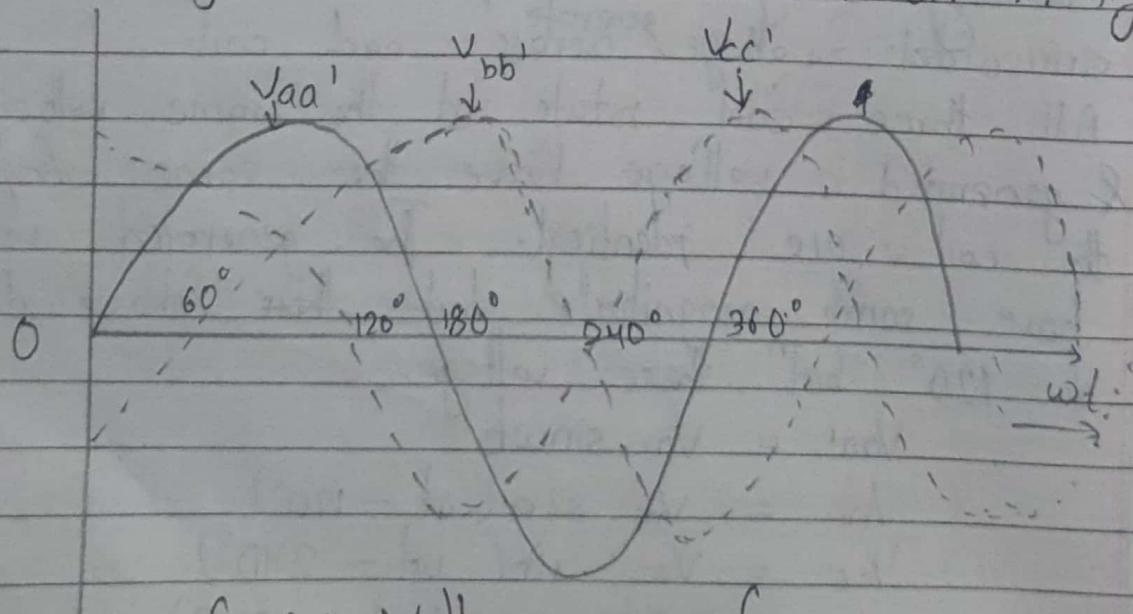


fig (c): Voltage waveform

It is seen that $V_{aa'}$ leads $V_{bb'}$ by 120° & $V_{bb'}$ leads $V_{cc'}$ by 120° . Also, the three voltage reach their position maximum value in the order $V_{aa'}, V_{bb'} \& V_{cc'}$. The order in which the phase voltage reach their maximum value is called the phase sequence for arrangement shown in fig (c) above. If the coil are rotating in anticlockwise dirⁿ, the phase sequence is a, b, c abc. If the coil is rotating in clockwise dirⁿ, the voltage reach their position max^m value in order $V_{cc'}, V_{bb'} \& V_{aa'}$. In this case, the phase sequence is cba or acb. Thus, the phase sequence determine the dirⁿ of rotation.

Advantage of 3-Φ over 1-Φ

~~most imp
V. Imp~~

It is observed that the poly-phase especially 3-Φ system has many advantage over 1-Φ system, both from utility point of view as well as from the consumer point of view. Some advantages are as follows:

- 1) The power of 1-Φ ckt is pulsating when pf. of ckt is unity but, 3-Φ power supply by each phase is pulsating torque. Total power is balanced 3-Φ ckt is constant at every instant of time. Because 3-Φ have more absolutely uniform torque.
- * 3Φ motor have uniform torque, whereas 1-Φ motor passes pulsating torque (except commutating motor).

- * 3- ϕ motors are more compact; whereas 1- ϕ motor requires more space for conveying the same power.
- * Power in polyphase never falls to zero; whereas it may fall to zero in 1- ϕ system.
- 2) A poly-phase Transmission line requires less conductor than 1- ϕ .
- 3) Poly-phase are self-starting but single-phase are not self-starting.
- 4) For given frame-size, 3- ϕ motor or 3- ϕ generator produced more output than 1- ϕ motor (generator).
- 5) ~~Effective~~ Efficiency of 3- ϕ generator is higher than 1- ϕ generator.

In general, we can conclude that operating characteristics of 3- ϕ apparatus are superior than the 1- ϕ apparatus. Control equipment are smaller, cheaper, lighter in wt. & more efficiency, therefore 3- ϕ ckt is of great importance.

Difference between 1- ϕ over 3- ϕ system.

For, 1- ϕ system:

- i) It requires more copper for transmitting the power.
- ii) Power may fall to zero value.
- iii) Single phase ^{have} fluctuating torque.
- iv) 1- ϕ motor passes no starting torque so that it needs additional starting device.
- v) 1- ϕ motor requires more space.
- vi) 1- ϕ generator can not start in parallel.
- vii) Transmission system or distribution system of 1- ϕ power is costly.

- viii) Less efficient.
- ix) Less efficiency.
- x) Output of 1- ϕ generator is low.
- x) 1- ϕ are less costly.

For, 3- ϕ system:

- i) It requires less copper for transmitting the power.
- ii) Power never falls to zero '0'.
- iii) It has uniform torque.
- iv) 3- ϕ motor can be self-start.
- v) 3- ϕ motor are more compact.
- vi) 3- ϕ can be started in parallel.
- vii) Transmission system or distribution of 3- ϕ power is cheaper.
- viii) More efficient.
- ix) Efficiency is very high (for generator).
- x) Output of poly-phase m/c machine is very high.
- xi) Polyphase are costly (little).
- Polyphase generator is large in size, more economical in operation.

Phase Sequence:

The order in which the phase voltage reach as obtained their maximum value is called the phase sequence.

Here, the sequence of the voltage in $3-\phi$ are in the order $V_{RR}' - V_{YY}' - V_{BB}'$ & they undergo change one after other is above maintained order, this is called the phase sequence. It can be observed that this sequence depend on the rotation of field. If field system is rotated in anti-clockwise direction, then the sequence of the voltage in $3-\phi$ is in order $V_{RR}' - V_{BB}' - V_{YY}'$.

Briefly, we say that the sequence is RBY.


Now, the eqⁿ can be written as

$$V_{RR} = V_m \sin \omega t$$

$$V_{YY} = V_m \sin(\omega t - 120^\circ)$$

$$V_{BB}' = V_m \sin(\omega t - 240^\circ) \text{ or } V_m \sin(\omega t + 120^\circ)$$

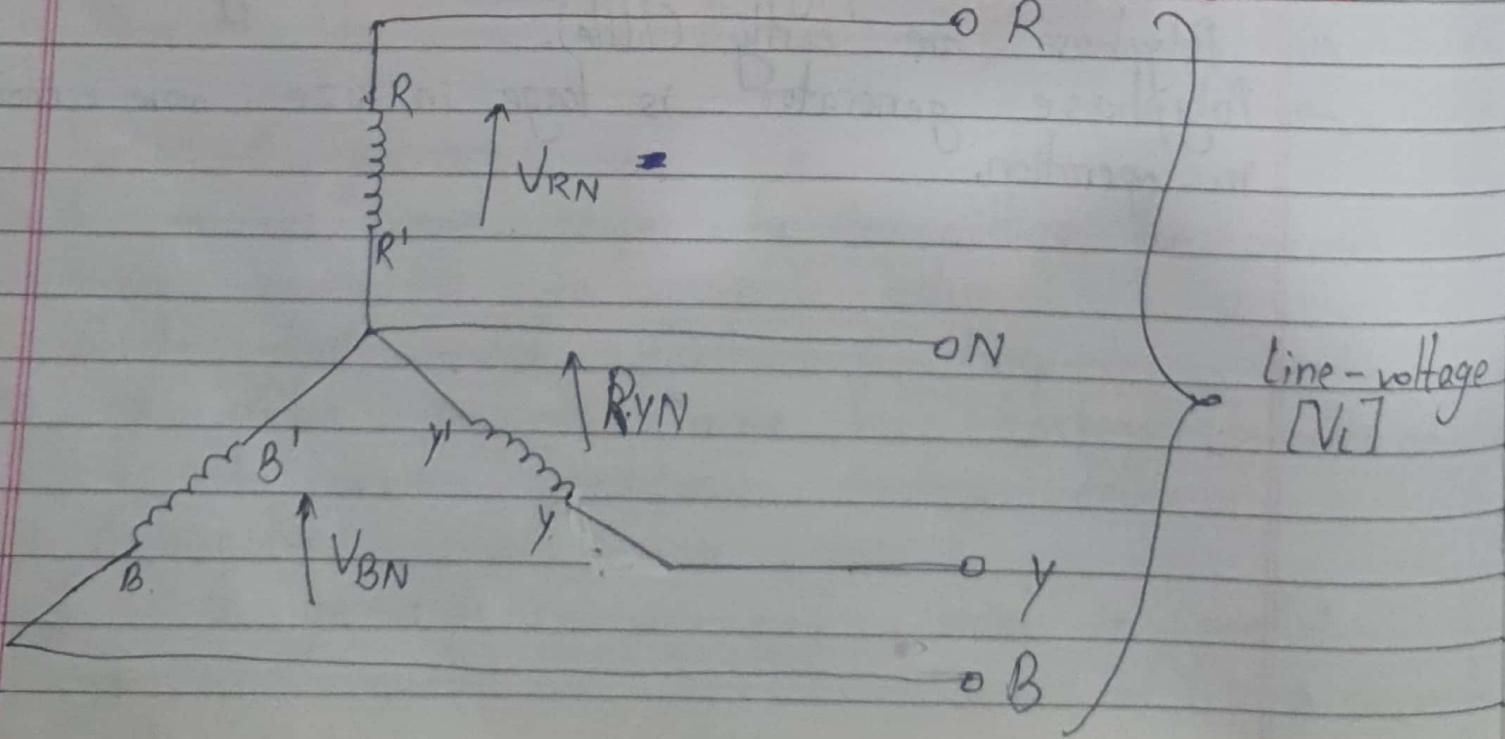Star Connections [Y connection] wye connection]



balanced load - having equal magnitude & phase angle.

Page No.: / /
Date: / /

Star connection formula:

$$\boxed{V_L = \sqrt{3} V_{ph}}$$

$$I_L = I_{ph}$$

Power consumed = $\sqrt{3} V_L \cdot I_L \cos\phi$

(V_L → line voltage)


I_L → line current

Delta connection formula:

$$\boxed{V_L = V_{ph}}$$

$$\boxed{I_L = \sqrt{3} I_{ph}}$$

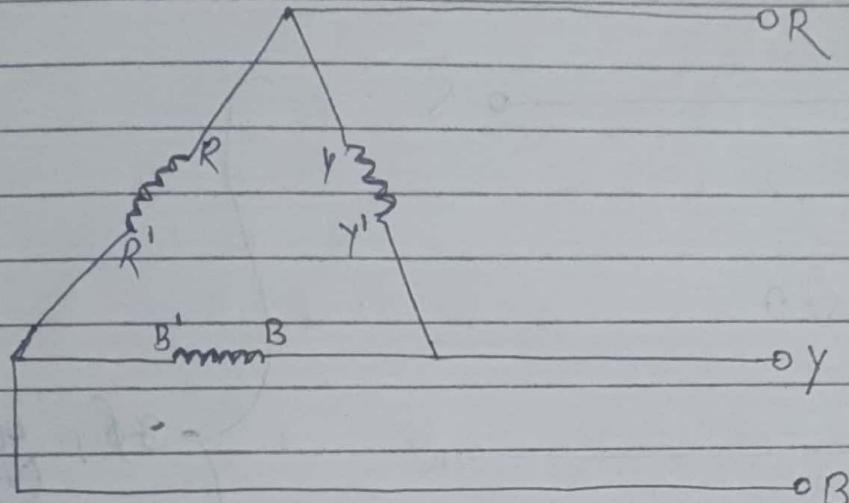Delta Connections (Mesh connection / Δ -connection):



$$V_L = V_{ph}$$


$$I_L = \sqrt{3} I_{ph}$$

Voltage, current, power for star-delta connection relation (self-study)

$$\cos\phi = \frac{R_{ph}}{Z_{ph}}$$

- 3.1) Three equal impedances each having the resistance of 8Ω inductive resistance of 6Ω are connected in series.
- (a) star (b) delta across $3\phi, 400V$ system. Find
 (i) phase current
 (ii) line current
 (iii) power consumed in each case.

solution:

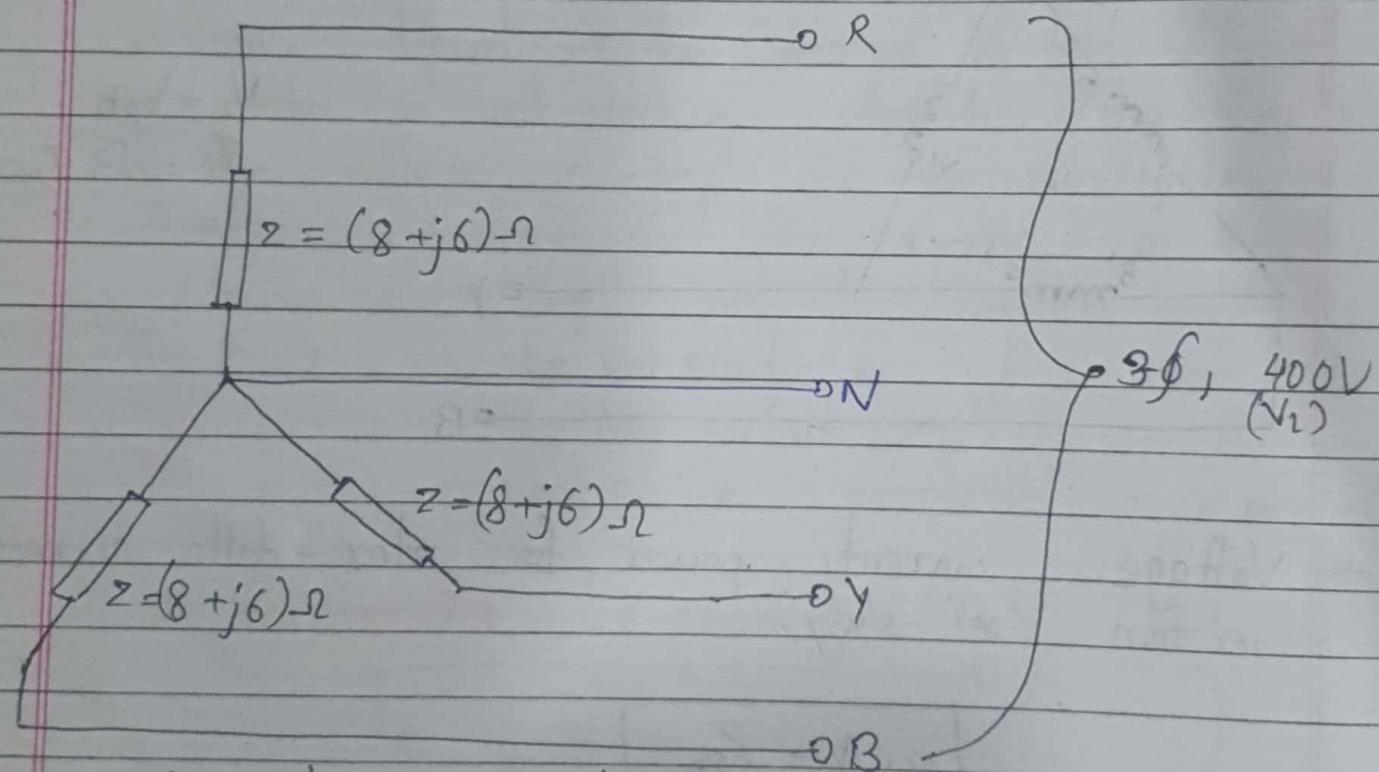

For star connection:

$$Z_{ph} = \sqrt{8^2 + 6^2} = 10\Omega$$

$$\therefore Z_{ph} = 10\Omega$$

Now,

$$V_L = \sqrt{3} V_{ph}$$

$$\text{or } \frac{400}{\sqrt{3}} = V_{ph}$$

$$\Rightarrow V_{ph} = 231V$$

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{231}{10} = 23.1 \text{ amp}$$

Also, $I_L = I_{ph} = 23.1 \text{ amp}$

power consumed = $\sqrt{3} V_L \cdot I_L \cos \phi$


$$= \sqrt{3} \times 400 \times 23.1 \times \cos \left(\frac{R_{ph}}{Z_{ph}} \right)$$

$$= \sqrt{3} \times 400 \times 23.1 \times \frac{8}{10}$$

$$= 12,803.32 \text{ watt}$$

$$= 12.8 \text{ kW}$$

For delta connection:

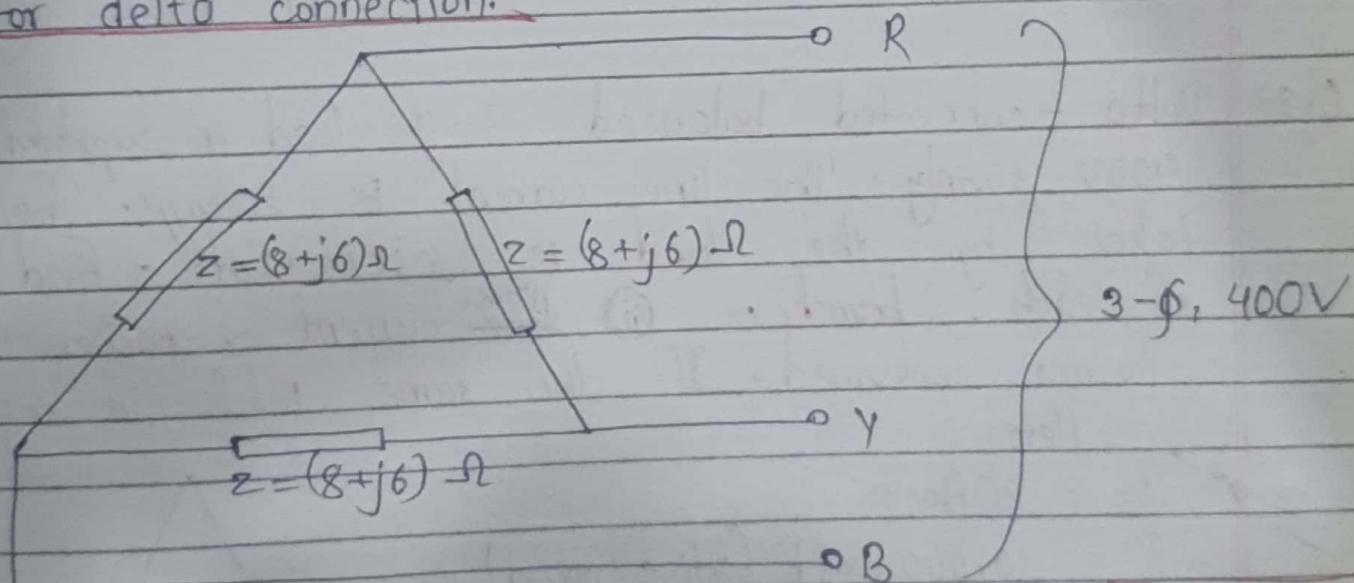

Here, $V_L = 400V$

$$Z_{ph} = \sqrt{8^2 + 6^2} = 10 \Omega$$

Now,

$$V_L = V_{ph} = 400V$$

$$\therefore V_{ph} = 400V$$

Again,

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{10} = 40 \text{ amp}$$

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$\begin{aligned} \text{So, } I_L &= \sqrt{3} I_{ph} \\ &= \sqrt{3} \times 40 \\ &= 69.28 \text{ amp} \end{aligned}$$

Again,

$$\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{8}{10} = 0.8$$

Now,

$$\begin{aligned} \text{power consumed} &= \sqrt{3} V_L \cdot I_L \cos \phi \\ &= \sqrt{3} \times 400 \times 69.28 \times 0.8 \\ &= 38,398.87 \text{ watt} \\ &= 38.39 \text{ kW} \end{aligned}$$

Q.2) Delta-connected balanced 3-φ load is supplied from 3-φ, 400V supply. The line current is 20 amp. The power taken by the load is 10,000 Watt. Find (i) impedance of each branch, (ii) ^{Phase} line current, power factor & power consumed. If the same load is connected to star.

Here,

~~$I_L = 20 \text{ amp}$~~

~~$P = 10,000 \text{ watt (active power)}$~~

for delta connection:

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

Now,


$$V_L = 400V$$

$$\Rightarrow V_{ph} = 400V$$

$$\text{Also, } I_L = \sqrt{3} I_{ph}$$

$$\Rightarrow 20 = \sqrt{3} I_{ph}$$
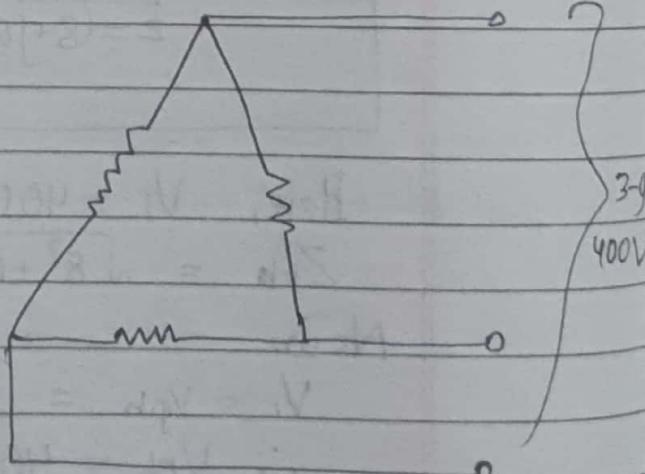
$$\Rightarrow I_{ph} = 11.52 \text{ amp}$$



$$\textcircled{1} \quad Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{11.52}$$

$$\therefore Z_{ph} = 34.6 \Omega$$

Now,

Power) $P = \sqrt{3} V_L \cdot I_L \cos \phi$

$$10000 = \sqrt{3} \times 400 \times 20 \times \cos \phi$$

$$\Rightarrow \cos \phi = 0.72$$

$$\textcircled{11} \quad \therefore \text{power factor} = \cos \phi = 0.72$$

for star connection:

$$V_L = 400V$$

So,

$$V_L = \sqrt{3} V_{ph}$$

$$\Rightarrow 400 = \sqrt{3} V_{ph}$$

$$\Rightarrow V_{ph} = 230.94V$$

Now,


$$I_L = 20 \text{ amp}$$

$$\Rightarrow I_{ph} = 20 \text{ amp} \quad [\because I_L = I_{ph}]$$

Again,

$$\textcircled{1} \quad Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{230.94}{20}$$

$$= 11.55 \Omega$$

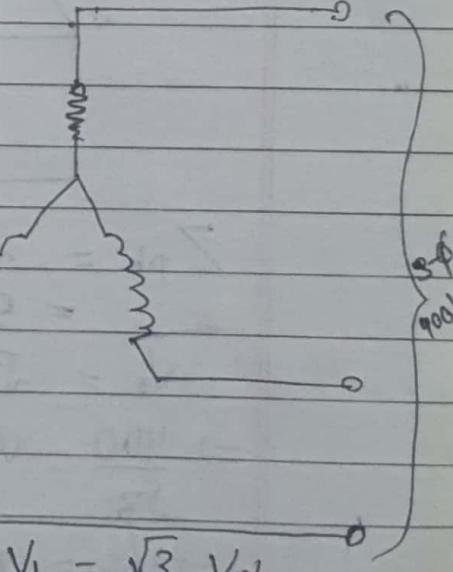

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$


\textcircled{11} power factor:

$$P = \sqrt{3} V_L \cdot I_L \cos \phi$$

$$10000 = \sqrt{3} \times 400 \times 20 \times \cos \phi$$

$$\Rightarrow \cos \phi = 0.72$$

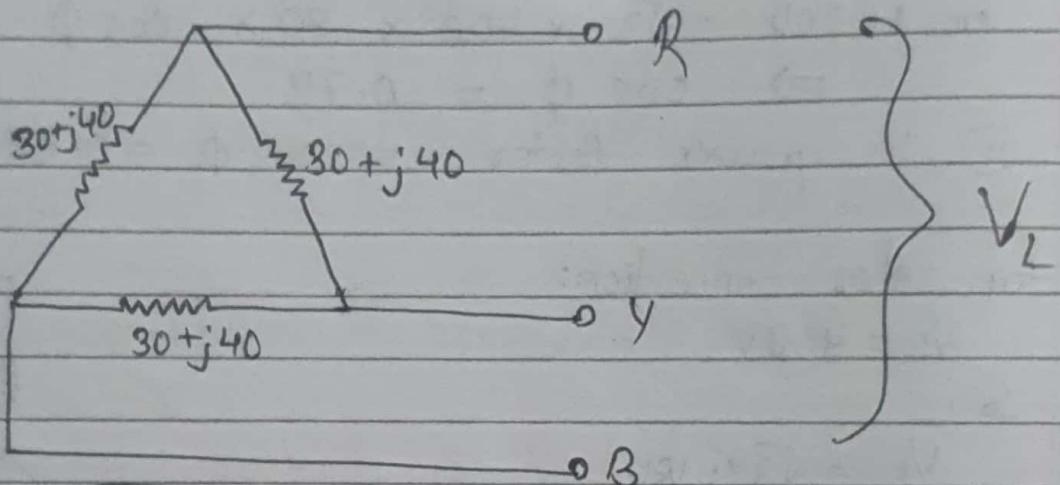- Q. 3) The three equal impedance $(30 + j40)\Omega$ are connected in star and balanced 3- ϕ , 400V supply is connected across this load. Find the (i) current flowing through load, (ii) power consumed by each phase (iii) p.f. of load.



$$Z_{ph} = \sqrt{(30)^2 + (40)^2} \\ = 50$$

$$V_1 = \sqrt{3} V_{ph}$$

$$\Rightarrow \frac{400}{\sqrt{3}} = V_{ph}$$

$$\Rightarrow V_{ph} = 230.94$$

Now,

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$= \frac{230.94}{50}$$

$$= 4.61 \text{ amp}$$

$$I_{ph} = I_L = 4.61 \text{ amp}$$

$$\rightarrow \text{Power consumed} = \sqrt{3} V_{ph} I_L \cos \phi \\ = \sqrt{3} \times 400 \times 4.61 \times \frac{R_{ph}}{Z_{ph}} \\ = \sqrt{3} \times 400 \times 4.61 \times \frac{30}{50} \\ = 1916.34 \text{ watt}$$

$$\text{pf of load} = \cos \phi \\ = 0.6$$

4) The three 3- ϕ balance load connected in star drawn a total power of 20kW at 0.8, if lag. When connected to 3- ϕ , 400V, 50Hz supply, calculate

- (i) resistance of coil
- (ii) inductance of coil

Here,

$$P = 20\text{ kW} = 20000\text{ W}$$

$$V_L = 400\text{ V}$$

$$\cos \phi = 0.8$$

Now,

$$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$$

$$\Rightarrow 20000 = \sqrt{3} \cdot 400 \cdot I_L \cdot 0.8$$

$$\Rightarrow I_L = 36.08 \text{ amp}$$

$$I_{ph} = I_L = 36.08 \text{ amp}$$

Now,

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{\sqrt{3} \cdot 400}{36.08} = \frac{230.94}{36.08} = 6.4 \Omega$$

Again,

$$\cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$\Rightarrow R_{ph} = Z_{ph} \times 0.8 \\ = 6.4 \times 0.8 = 5.12$$

Also,

$$X_L = \sqrt{Z_{ph}^2 - R_{ph}^2} = 3.84 \Omega$$

So,

$$X_L = 2\pi f L$$

$$\Rightarrow L = \frac{3.84}{2\pi f} = 0.012 \text{ H} = 12.2 \text{ mH}$$

Q) Three equal impedances having the resistance 8Ω & inductive reactance 6Ω are connected in delta & connected to $230V$, $3-\phi$ - source, $3-\phi$ delta connected source then calculate (i) phase & line current of load (ii) pf (iii) power consumed.

Here,

$$R_{ph} = 8\Omega$$

$$X_L = 6\Omega$$

$$Z_{ph} = \sqrt{8^2 + 6^2} = 10\Omega$$

$$V_L = 230V$$

Now,

$$V_{ph} = 230V$$

$$\text{So, } I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230}{10} = 23A$$

$$\text{Also, } I_L = \sqrt{3} I_{ph} = 23 \times \sqrt{3} = 39.83A$$

$$\text{So, pf (cos } \phi) = \frac{R_{ph}}{Z_{ph}} = \frac{8}{10} = 0.8$$

$$\begin{aligned} \text{Power (P)} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 230 \times 39.83 \times 0.8 \\ &= +2696 \text{ watt} \quad 12693.71 \text{ watt} \\ &= 12.69 \text{ kW} \end{aligned}$$

$$\begin{aligned}\text{active power} &= \sqrt{3} V_L I_L \cos\phi \text{ (watt)} \\ \text{reactive } " &= \sqrt{3} V_L I_L \sin\phi \text{ (VAR)} \\ \text{apparent } " &= \sqrt{3} V_L I_L \text{ (VA)}\end{aligned}$$

Page No.: /
Date: / / NEW LINK

- 6) The balanced delta connected load of $(2+j3)$ Ω per phase is connected to balance 3ϕ , 440V supply. The phase current is 10 amp. Find the (i) active power (ii) reactive power (iii) apparent power.

Here,

$$Z_{ph} = \sqrt{2^2 + 3^2} = 3.60 \Omega$$

$$V_L = 440V$$


$$V_{ph} = 440V$$

Now,

$$I_{ph} = 10 \text{ amp}$$

$$I_L = \sqrt{3} I_{ph}$$

$$= 17.32 A$$

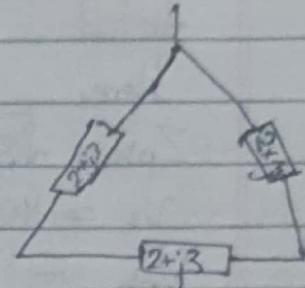

Again,

$$\begin{aligned}\text{(i) Active power} &= \sqrt{3} V_L I_L \cos\phi \\ &= \sqrt{3} \times 440 \times 17.32 \times \frac{2}{3.6}\end{aligned}$$

$$= 7333.19 \text{ watt}$$

$$\begin{aligned}\text{(ii) Reactive power} &= \sqrt{3} V_L I_L \sin\phi \\ &= \sqrt{3} \times 440 \times 17.32 \times \sqrt{1 - \cos^2(0.55)} \\ &= 126.70 \text{ VAR}\end{aligned}$$

$$\begin{aligned}\text{(iii) Apparent power} &= \sqrt{3} V_L I_L \\ &= \sqrt{3} \times 440 \times 17.32 \\ &= 13199.61 \text{ VA}\end{aligned}$$

Q. The balanced star-connected load of $(8+j6)$ per phase is connected to the balance 3- ϕ , 400V supply. Find the line current, power factor, power & total volts-amp.

Here,

$$Z_{ph} = \sqrt{8^2 + 6^2} = 10 \Omega$$

$$V_L = 400 \text{ V}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ V}$$

So,

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{10} = 23.09 \text{ A}$$

Now,


$$I_L = I_{ph} = 23.09 \text{ A}$$

$$\text{pf} = \cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{8}{10} = 0.8$$

$$\begin{aligned} \text{Power} &= \sqrt{3} \cdot V_L \cdot I_L \cos \phi \\ &= \sqrt{3} \times 400 \times 23.09 \times 0.8 \\ &= 12797.77 \text{ watt} \\ &= 12.79 \text{ kW} \end{aligned}$$

Also,
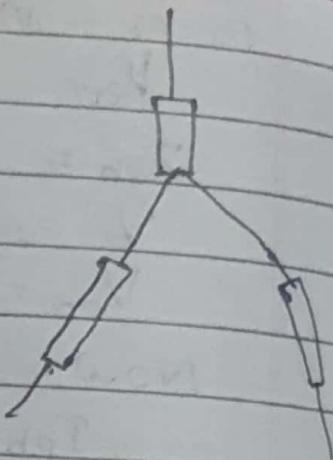
$$\begin{aligned} \text{Volts-amp} &= \sqrt{3} \cdot V_L \cdot I_L \\ &= \sqrt{3} \times 400 \times 23.09 \\ &= 15997.22 \text{ VA} \end{aligned}$$



Measurements of $3\text{-}\phi$ power:

1) One - wattmeter method

2) Two - wattmeter method

1) One - wattmeter method:

The measurement of power in in $1\text{-}\phi$ of $3\text{-}\phi$ balanced ckt where the star point is available. The current coil is connected in $1\text{-}\phi$ & the voltage or pressure coil connected betⁿ the star point i the reading on the wattmeter gives the power per phase.

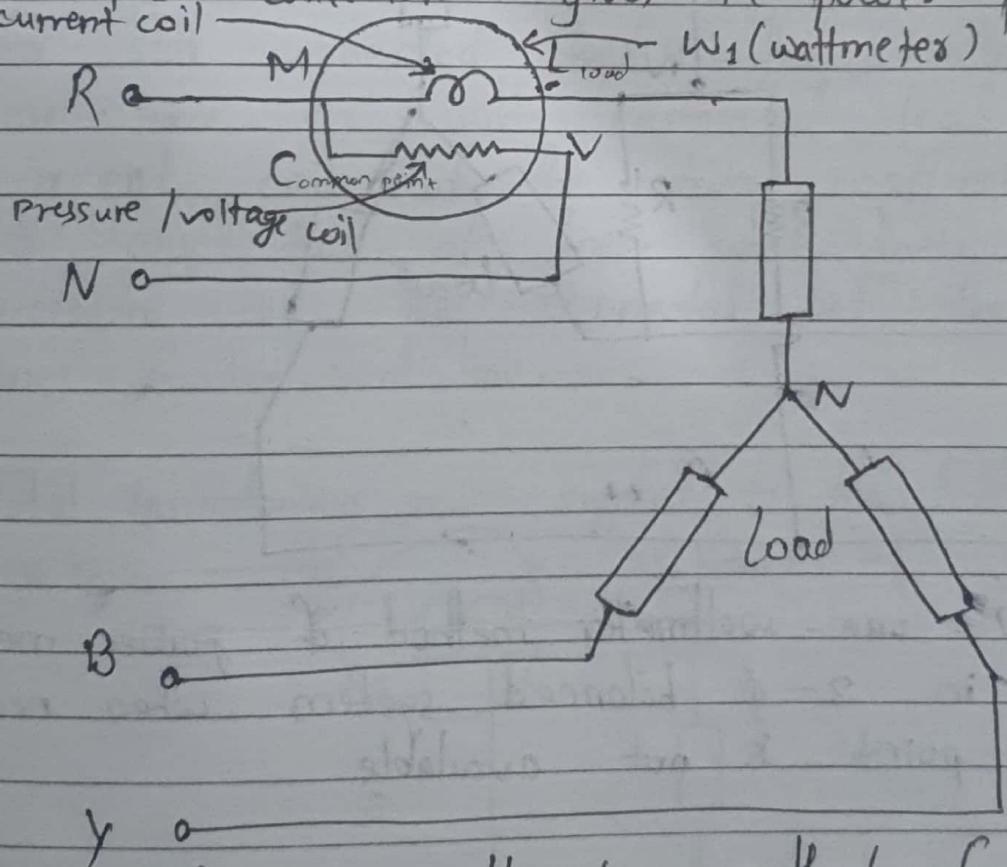


fig (a):-one wattmeter method of power - measurement

The 3- ϕ power gives three times the wattmeter reading. If the neutral point is not available & artificial neutral point N' is created by connecting two resistors R, R' shown in fig (b) below. The total power is given by 3 times wattmeter reading.

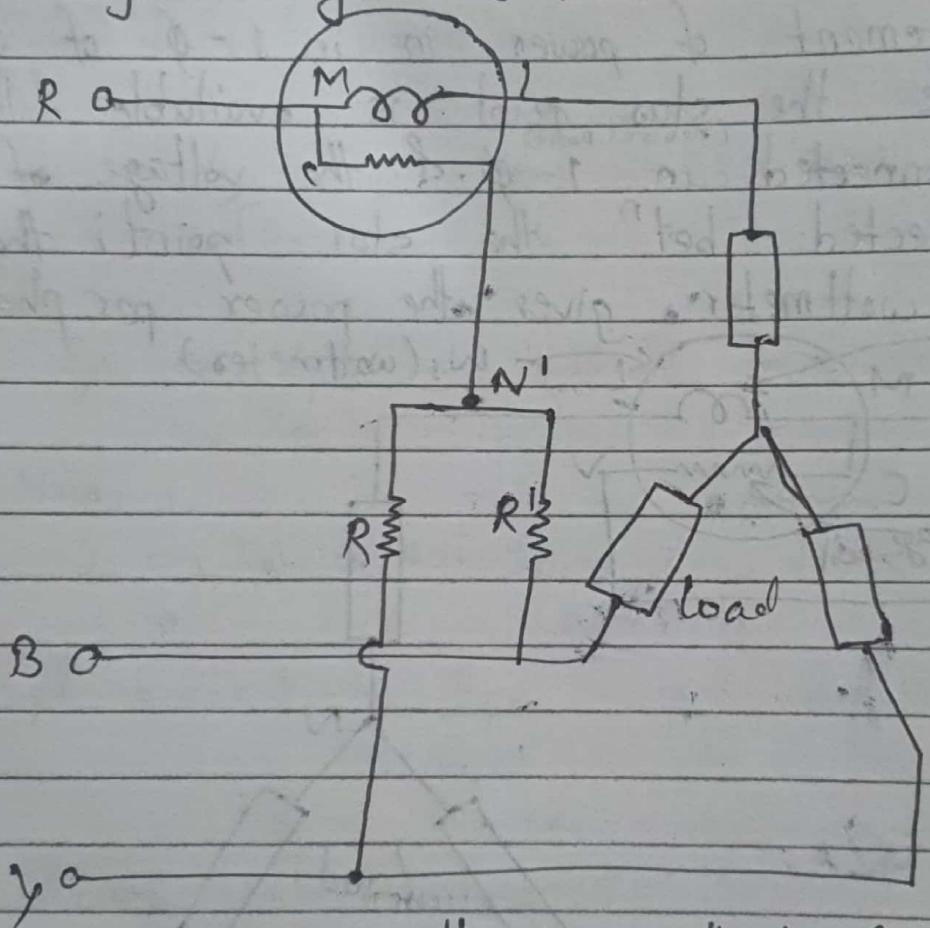


Fig (b) : one-wattmeter method of power measured in 3- ϕ balanced system, when neutral point is not available

* Volt-amp reactive of two

most
imp

one more
asked to
show


2) Two - wattmeter methods:

* volt - amp ~~resistance~~ reactive of two - wattmeter method
[self study]

for three phase, 3 - wire system; whether balanced or unbalanced ; star or delta connected, only two-wattmeter are required to measure the 3- ϕ power.

This is the most popular method of measuring the power.
In fig (a) below, the connection of 2-wattmeter for star connected load is shown. The wattmeter connection are same for delta connected load also. The current coil of the two - wattmeter are connected to any two of lines while their voltage coils or pressure coils are connected bet' the corresponding lines & the third line.

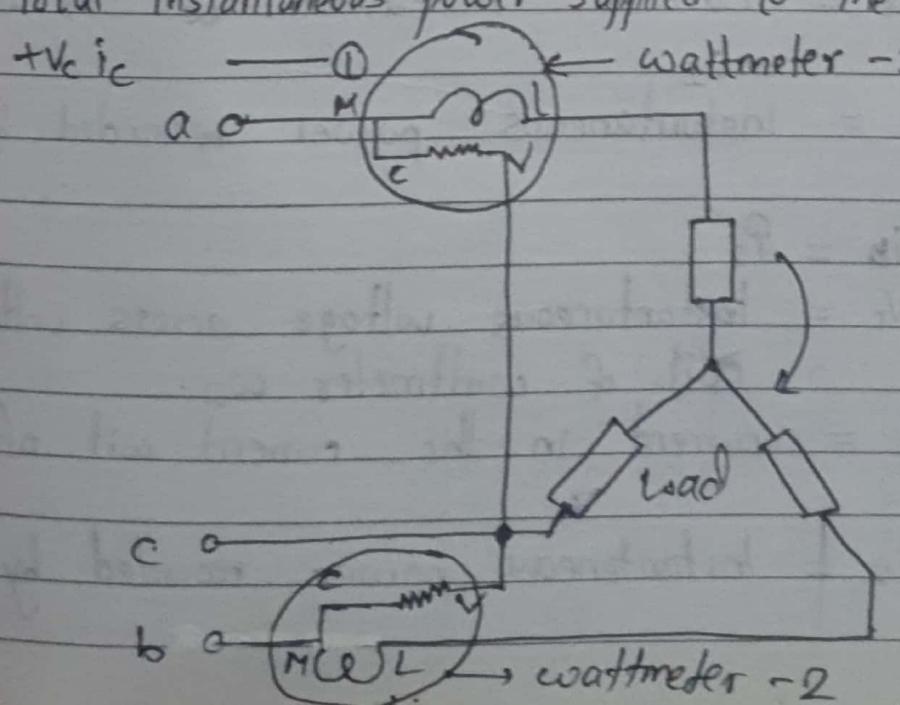Total Instantaneous power supplied to the load is $P = v_a i_a + v_b i_b + v_c i_c$



In a 3-wire system,

$$i_a + i_b + i_c = 0 \quad \text{--- (ii)}$$

Since, i_c is not flowing in either of wattmeter, we eliminate i_c .

From eqⁿ (i) & eqⁿ (ii),

$$i_c = -(i_a + i_b)$$

$$P = V_a \cdot i_a + V_b \cdot i_b - (i_a + i_b) V_c$$

$$P = V_a \cdot i_a + V_b \cdot i_b - i_a V_c - i_b V_c$$

$$P = i_a (V_a - V_c) + i_b (V_b - V_c) \quad \text{--- (iii)}$$

When,

$$(V_a - V_c) i_a = P_1$$

$$(V_b - V_c) i_b = P_2$$

$$\therefore P = P_1 + P_2$$

$$(V_a - V_c) i_a = P_1$$

Where,

$V_a - V_c$ = Instantaneous voltage across the voltage coil of wattmeter w_1 ,

i_a = current in current coil of wattmeter w_1

P_1 = Instantaneous power recorded by w_1 .

$$(V_b - V_c) i_b = P_2$$

where, $V_b - V_c$ = Instantaneous voltage across voltage coil of wattmeter w_2 .

i_b = current in the current coil of w_2

P_2 = Instantaneous power recorded by w_2 .

✓ Avg. voltage of φ = Avg. value of $P_1 + \text{Avg. value of } P_2$
 $P = \text{reading of } w_1 + \text{reading of } w_2$
 $\boxed{P = P_1 + P_2}$

Thus, the sum of the two-wattmeter reading gives the total three phase power in 3-wire system (Y or Δ connected) under all conditions of load whether balanced or unbalanced, Y or Δ connected.

$$\tan \phi = \sqrt{3} \cdot \frac{w_1 - w_2}{w_1 + w_2}$$

numerical using this formula

Electrical M/C

Transformer

→ Transformer is the electric static device which consists of two or more stationary electric ckt interlinked by the common magnetic ckt. for the purpose of transforming the electrical energy bet' them. The transfer of energy from one ckt to another ckt take place without change in frequency.

Consider the two coil, coil 1 & coil 2 wound on simple magnetic ckt shown in fig (a) below. The coil are insulated from each other & there is no electrical connection bet' them. Let T_1 & T_2 be no. of turns in coil 1 & coil 2 resp. When the source of ac voltage V_1 is applied to the coil 1 & coil 2, ac I_1 flow in it. This alternating current produce an alternating flux (Φ_m) in magnetic ckt. The mean path of this flux shown in fig (a) below. By the dotted line, this Φ_m links turn T_1 of coil 1 & indicates in alternating voltage E_1 by self induction.

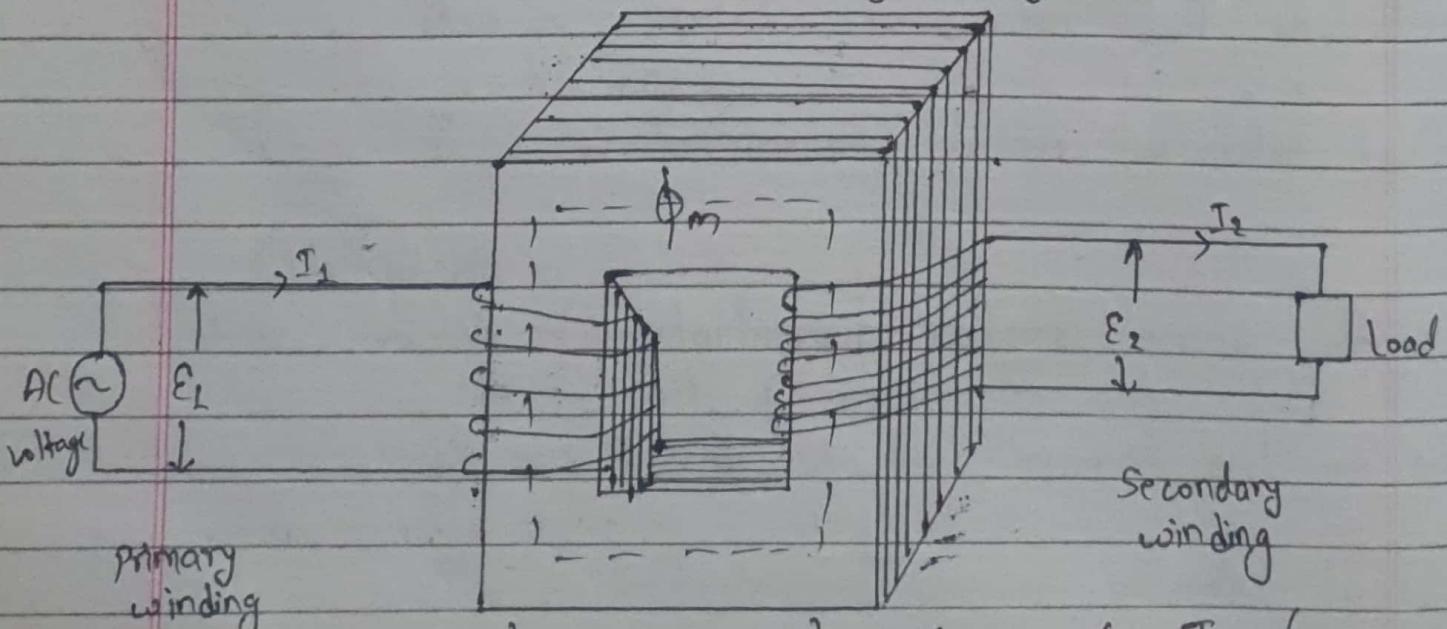


Fig (a) : Simple arrangement of 1- ϕ Transformer

* Simplifying Assumptions for Ideal Transformer:


- ① There is no losses either in electrical ckt or magnetic ckt.
- ② The whole magnetic flux (ϕ) is confined to magnetic ckt so there is no leakage flux.
- ③ The permeability of core is infinite.

All the flux produced by coil-1 also links N_2 turns of coil-2 and induces in them a voltage E_2 by mutual induction. If coil-2 end is connected to the load then alternating current will flow through it and energy will be delivered to the load. Thus electrical energy is transferred from coil-1 to coil-2 by common magnetic ckt. Since, there is no relative motion of coils, the freq. of the induction voltage of coil-2 is exactly the same as the freq. of applied voltage to coil-1.

Coil-1 which receives energy from the source ac supply is called primary coil or primary winding or simply primary.

Coil-2 which is connected to load & delivered energy to the load is called secondary life coil or secondary winding or simply secondary.

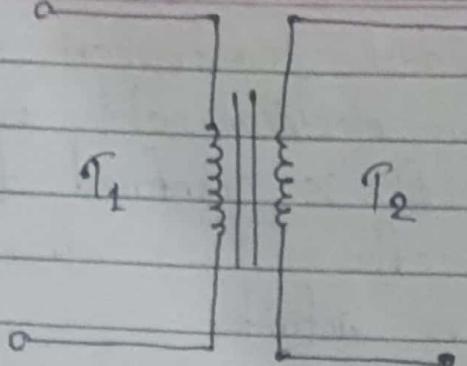The Δt symbol for two-winding transfer is



most imp

EMF Eqⁿ of Transformer

N_1 = No. of turns in primary coil

N_2 = No. of turns in secondary coil


ϕ_m = max^m flux in the core (wb)

$$\phi_m = B_m \cdot A$$

where, B_m = max^m flux density in the core

A = Area of core

f = freq. of ac input (Hz)

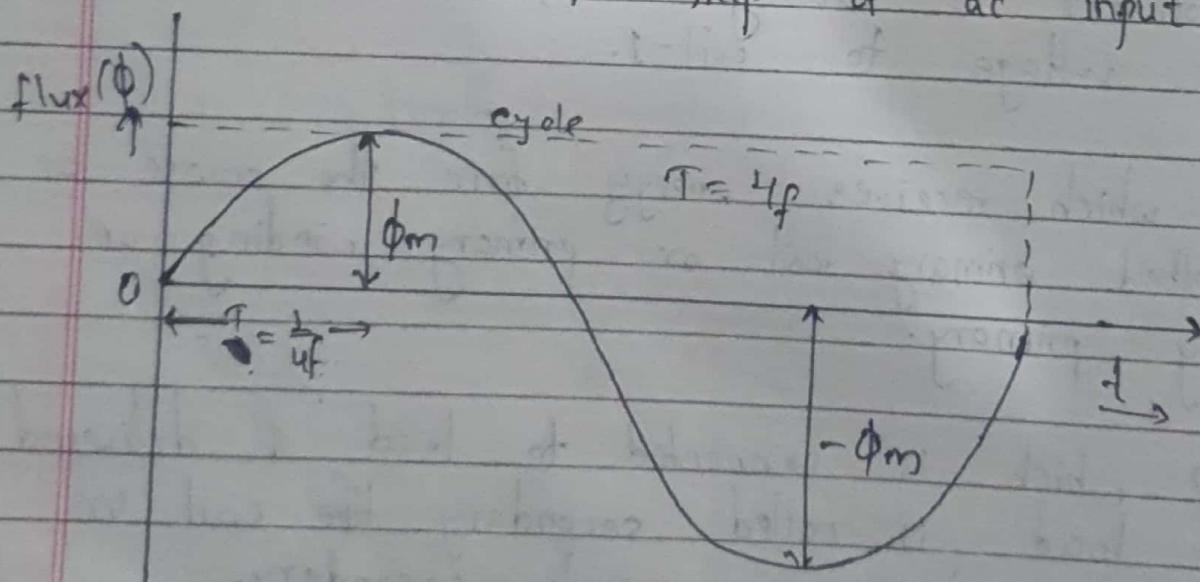

Since, flux increased from zero value to max^m value Φ_m in one quarter of cycle i.e. $T/4$ or $1/4f$ second. [T being time period of cycle],

Avg. rate of change of flux = $\frac{\phi_m}{4f} = 4f \phi_m$

If flux varies sinusoidally, the rms value of induced emf is obtained by multiplying the avg. value with form factor.

rms value = form factor \times avg. value

$$\therefore \text{Form factor} = \frac{\text{rms value}}{\text{avg. value}} = 1.11$$

$$\therefore \text{RMS value of emf / turn} = 1.11 \times 4 \phi_m f$$

Now,

rms value of induced emf in the whole primary winding,

$$E_1 = 4.44f \phi_m \cdot N_1 \quad \text{--- (i)}$$

Similarly,

rms value of induced emf in the whole secondary winding,

$$E_2 = 4.44f \phi_m \cdot N_2 \quad \text{--- (ii)}$$

In ideal transformer on No-load:

$$V_1 = E_1 \quad \&$$

$$V_2 = E_2$$

Transformer on No-load:

A transformer is said to be no load, when the secondary winding side is open ckt & primary winding is connected to sinusoidal alternating voltage V_1 . The alternating applied voltage will cause to flow of a.c. in the primary winding which creates the alternating flux. The primary input current I_o current under no-load condition supply.

- ① Iron loss in core [i.e. Hysteresis loss or eddy current loss].
- ② Copper loss (in primary) very small amount of loss.

Thus I_o lags 90° by V_1 .

No-load power input, $w_o = V_1 I_o \cos \phi_o$
where,

$\cos \phi_o$ = primary pf under no-load cond.
The primary current (I_o) has two components.

$$I_w = I_o \cos \phi_o$$

$$I_m = I_o \sin \phi_o$$

magnetising
component

(wattless comp)

active or working or iron loss
components (wattful amp.)


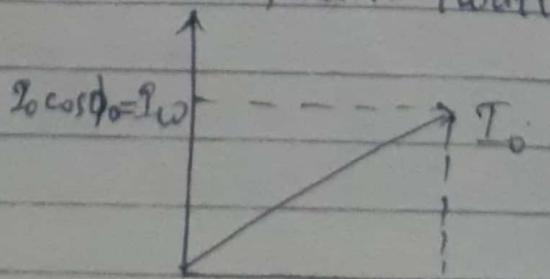


fig: no-load vector diagram

Transformer on load

The transformer is said to be loaded when second ckt of transformer is connected through impedance or load. The magnitude & phase of second current I_2 with respect to second terminal voltage will depend on characteristics of load i.e. the current I_2 will be in phase, lag behind & lead the terminal voltage V_2 resp. when the load is purely resistive, inductive & capacitive. The second current I_2 setup its own amp turn = $N_2 I_2$ creates its own flux Φ_2 creates by no-load current I_0 . The opposing second flux Φ_2 weakens the primary flux Φ_0 or back emf E_1 tends to be reduced. Hence, more current flows in primary & additional current be I_2 . It is known as the load current of primary current.

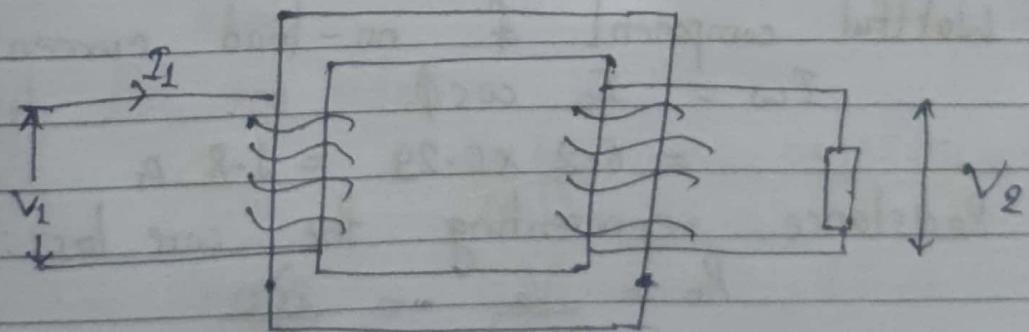

Test of Transformer

- (a) open ckt or no-load test (a.c. test)
- (b) short ckt or impedance test (s.c. test)

$$\eta = \frac{xxkVA \times 1000 \times Pf}{xxkVA \times 1000 \times Pf + I^2 P_c + P_i}$$

$$Cu_{loss} = \left(\frac{kVA \times 1000}{Scurrent \times HV} \right)^2 \times Sc.\text{power}$$

Page No.: Date: NEW LNK

Numericals

- Q. 1) Obtain the approx. eq. ckt. of a given 200/2000 V., 30 kVA transformer having the following test results:
- (i) o.c. Test [L.V side]: 200V, 6.2 A, 360 watt
 - (ii) s.c. Test [H.V. side]: 75V, 18 A, 600 watt.
- solution:

(i) O.C. Test [L.V side]:

$$\text{Primary voltage } V_o = 200 \text{ V.}$$

$$\text{No - Load current } I_o = 6.2 \text{ A}$$

$$\text{No - Load loss } P_o = 360 \text{ watt}$$

$$P_o = V_o I_o \cos \phi_o$$

$$360 = 200 \times 6.2 \cos \phi_o$$

$$\therefore \cos \phi_o = \frac{360}{200 \times 6.2} = 0.29$$

$$200 \times 6.2$$

$$\Rightarrow \phi_o = \cos^{-1}(0.29)$$

$$\Rightarrow \phi_o = 73.14$$

$$\therefore \sin \phi = 0.957$$

Wattful component of no-load currents:

$$I_w = I_o \cos \phi_o$$

$$= 6.2 \times 0.29 = 1.8 \text{ A}$$

Resistance representing the core loss:

$$R_o = \frac{V_o}{I_w} = \frac{200}{1.8}$$

$$\therefore R_o = 111.11 \Omega$$

Magnetizing components of no-load currents:

$$I_m = I_o \sin \phi_o$$

$$= 6.2 \times 0.95$$

$$I_m = 5.9 \text{ A}$$

Magnetizing resistance reactance

$$X_0 = \frac{V_0}{I_m} = \frac{200}{5.9} = 33.7 \Omega$$

$$\therefore X_0 = 33.7 \Omega$$

(ii) s.c. Test [H.V. side]: 75V, 18A, 600 watt.

$$\text{s.c. voltage (Vsc)} = 75V$$

$$\text{s.c. current (Isc)} = 18A$$

$$\text{losses (Psc)} = 600 \text{ watt}$$

Impedance of Transformer referred to H.V. side:-

$$Z_{02} = \frac{V_{sc}}{I_{sc}} = \frac{75}{18} = 4.167 \Omega$$

$$P_{sc} = I_{sc}^2 \times R_{02}$$

$$\approx 600 = (18)^2 \times R_{02}$$

$$\therefore R_{02} = 1.85 \Omega$$

Transformation ratio:

$$K = \frac{2000}{200} = 10$$

Transformation ratio:
$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{1}{K}$

Referred to 200 side:

$$Z_{01} = \frac{Z_{02}}{K^2} = \frac{4.167}{(10)^2} = 0.04167 \Omega = Z_{02} \left(\frac{N_1}{N_2} \right)^2$$


$$R_{01} = \frac{R_{02}}{K^2} = \frac{1.85}{(10)^2} = 0.0185 \Omega$$

$$\therefore X_{01} = \sqrt{(Z_{01})^2 - (R_{01})^2}$$

$$= \sqrt{(0.04167)^2 - (0.0185)^2}$$

$$X_{01} = 0.0373 \Omega$$

Approximate equivalent circuit:

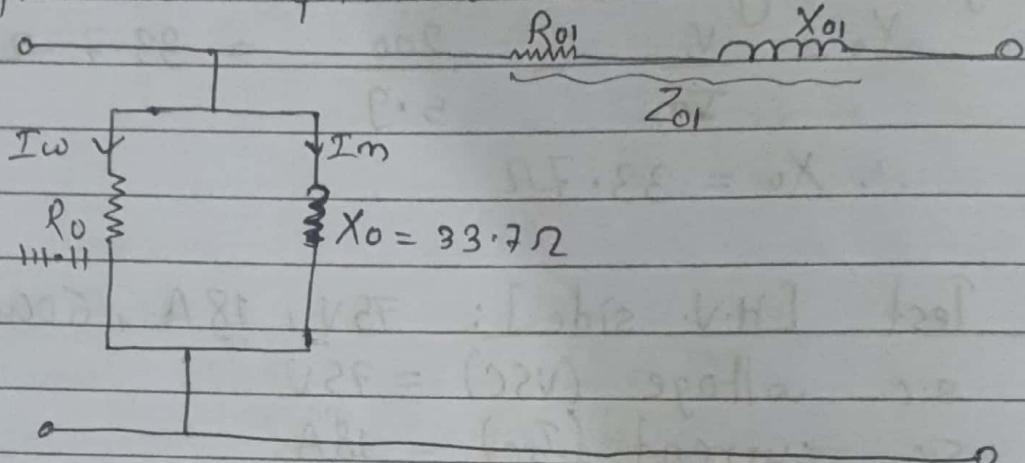

3 - ϕ Induction motor:

Working:


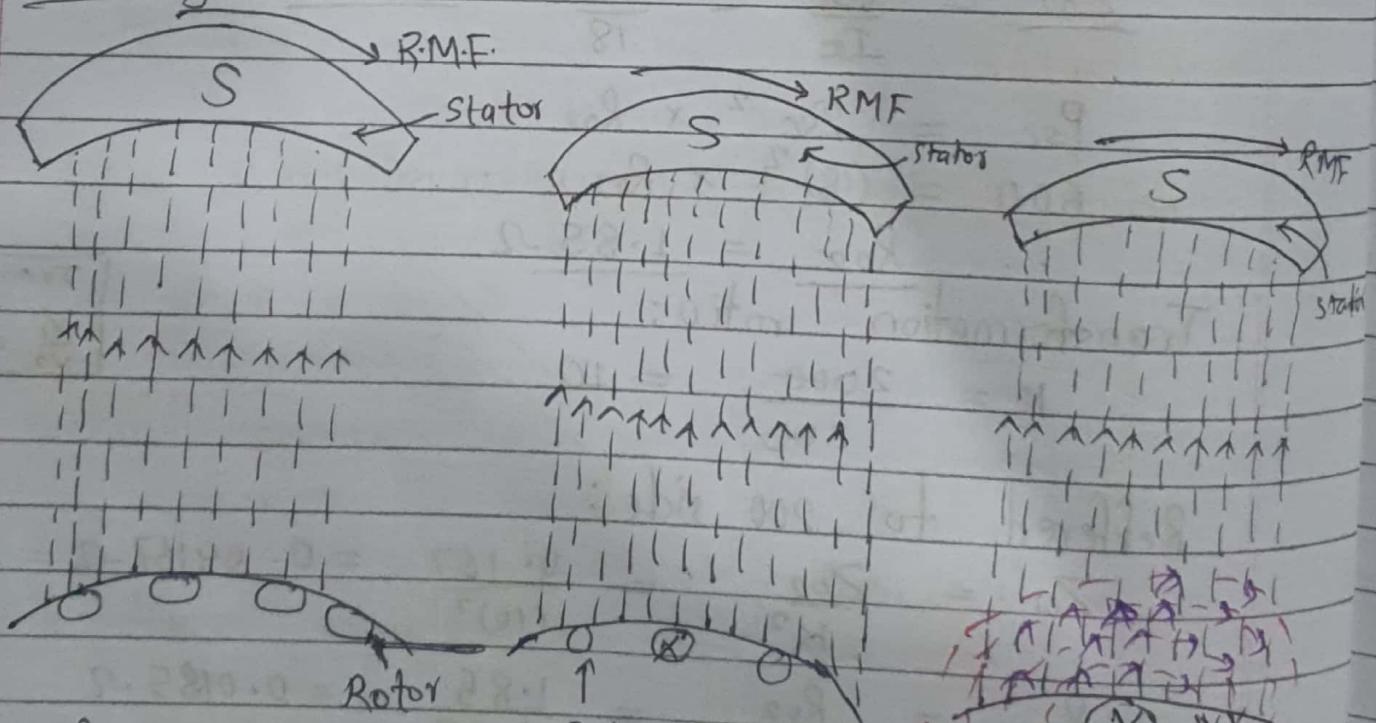



fig-(a)
motor conductors

fig (b)
induced current
in conductor

fig -(c)
flux - due to rotor
current

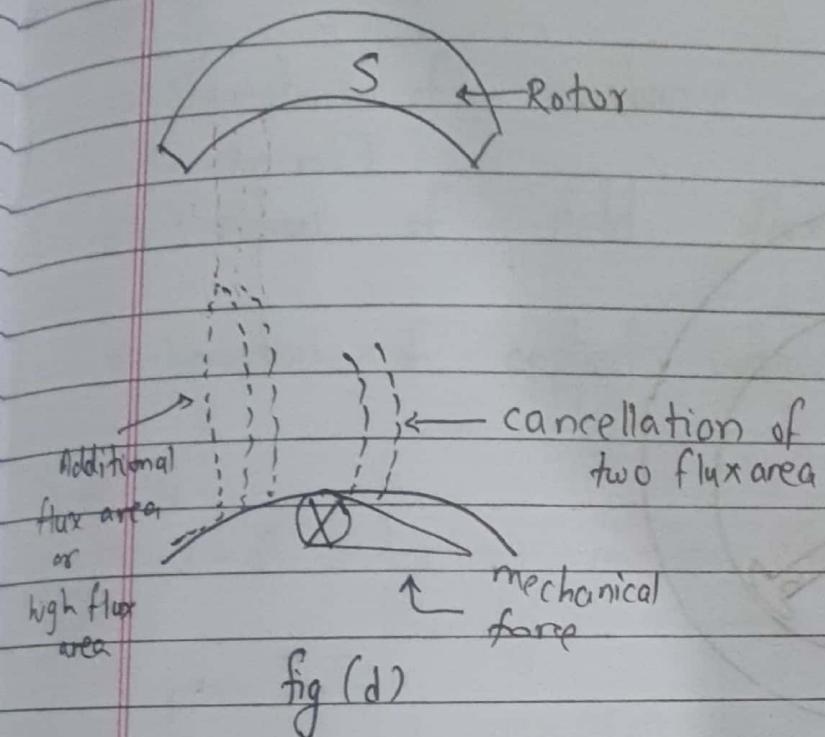

Working Principle of Synchronous (syn..) motor:

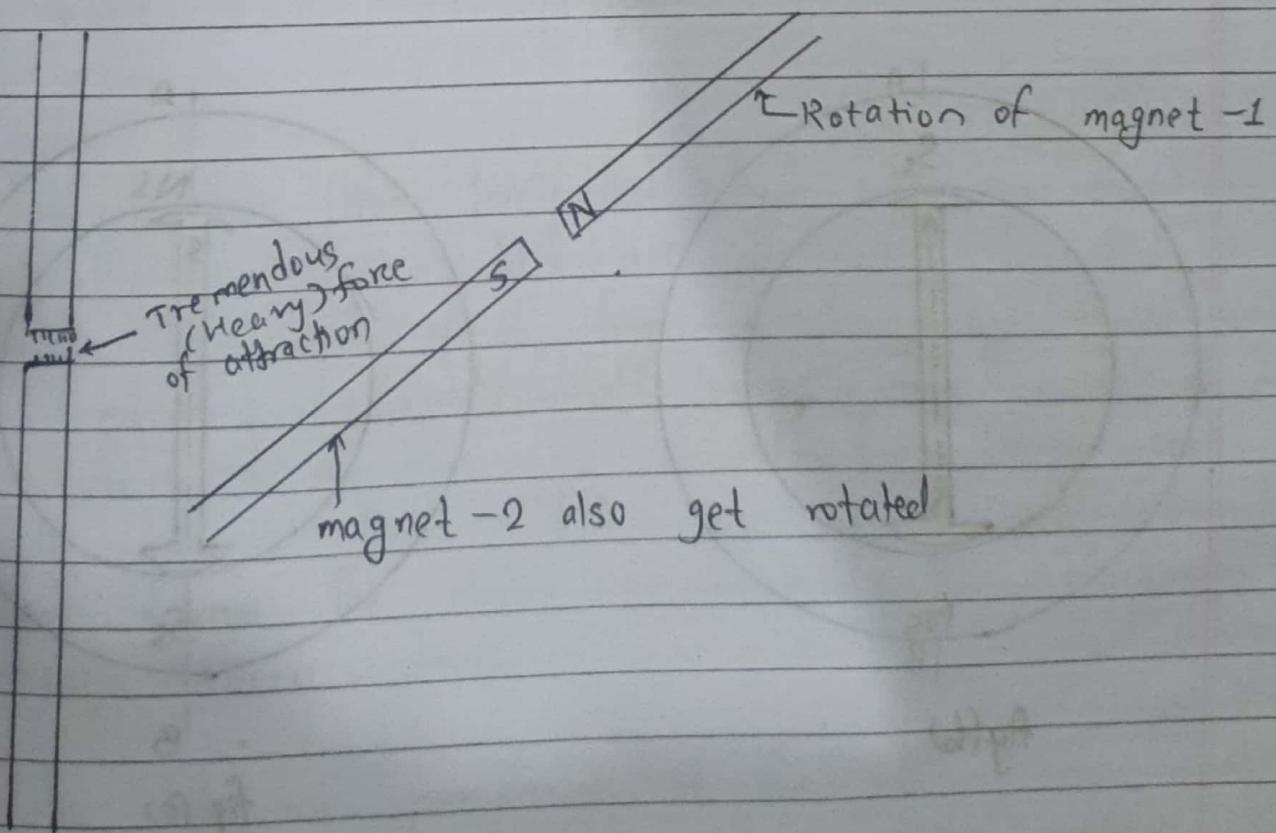

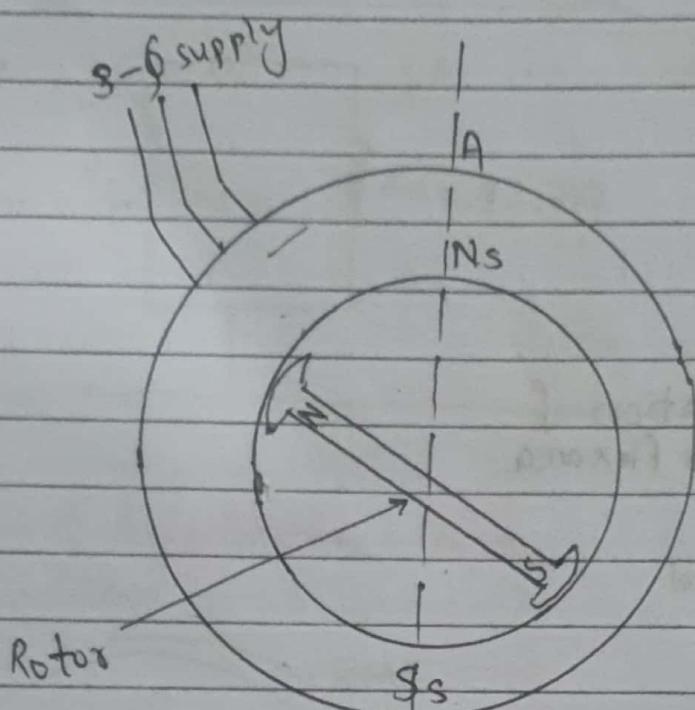


fig (a)

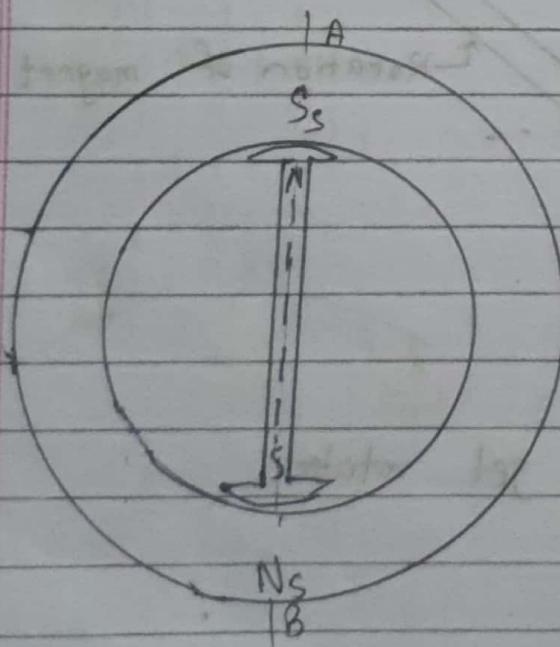


fig (b)

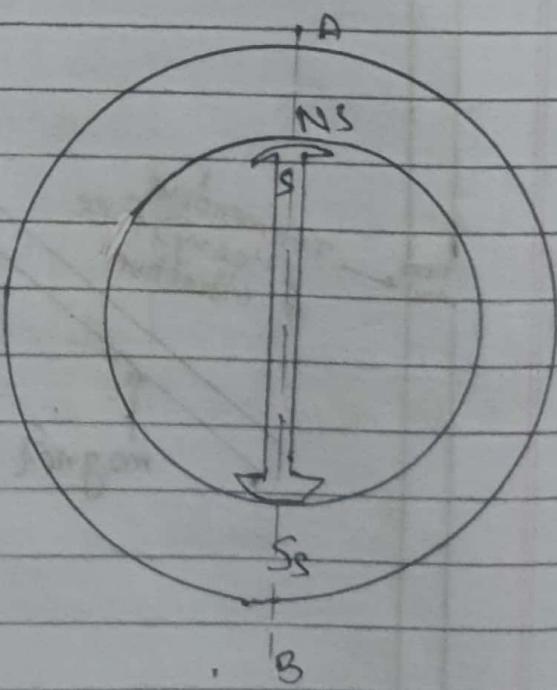


fig (c)

Speed ~~vs~~ Control of DC Motor:

- 1) Variation of resistance in the armature [Armature resistance control].
- 2) Variation of field flux (Φ) [field-resistance control]
- 3) Variation of applied voltage.

Q. #

3- ϕ induction motor Construction:

^{most imp} Basically, induction motor consists of two main parts:-

- 1) 3- ϕ winding which is called stator. [stationary part]
- 2) Rotor which is connected through mechanical load to shaft [i.e. rotating part]

1) Stator:

The stator has laminated type of construction made up of stampings which are 0.4mm to 0.5mm thick. Stator is built up of high-grade alloy-steel laminations to reduced eddy-current losses. The no's of stampings are stamped together to build the stator core. The built up is then fitted in casted or fabricated steel frame. The choice of materials for stampings is generally silicon-steel. ↳ finished plate

The slots on periphery of the stator core consist 3- ϕ winding, connected either ^{star to} core star or

delta connected 3-φ winding is called stator winding. The winding is excited by 3-φ supply, produces rotating magnetic field. The choice of no's of poles depends on the speed of rotating magnetic field required.

$$N_s \propto \frac{1}{P}$$

The radial ducts areas are provided for the cooling purpose.

→ tube or passage for air

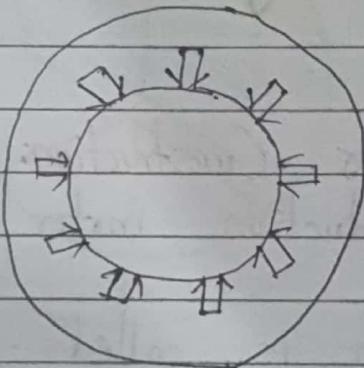


fig: stator lamination

ii) Rotor :


The rotor is placed inside the stator. The rotor core is also laminated in construction and uses as cast iron or same as stator materials. It is cylindrical with slots on its periphery. The Rotor winding or conductors is placed in the rotor slots.

There are two types of rotor construction in induction motors:

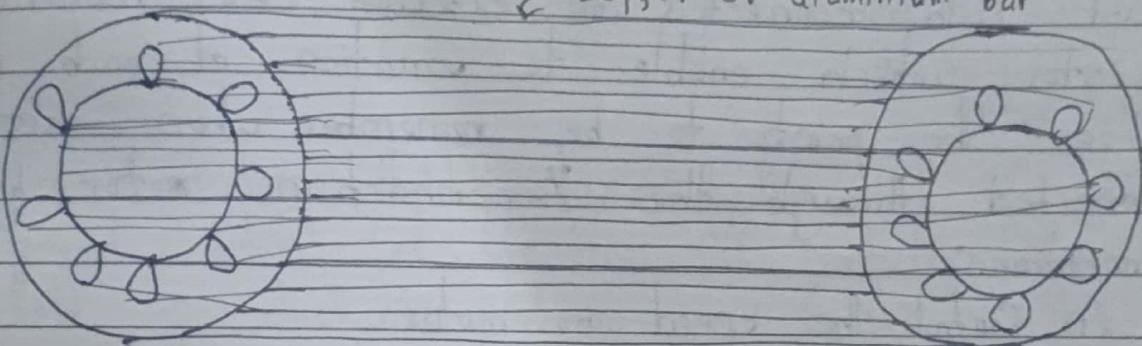
- (a) squirrel cage rotor
- (b) slip-ring or wound rotor
- (c) squirrel cage rotor :-

The rotor core is cylindrical and slotted on its periphery. The rotor consists of uninsulated

copper or aluminium bars called rotor conductor. The bars are placed in slots and each end of rotor bar is shortened by same materials. By same materials copper ring called end ring. The entire structure which looks like a cage, forming a closed electrical ckt. so the rotor is called the cage-rotor.



fig(a): Cage-type str of rotor

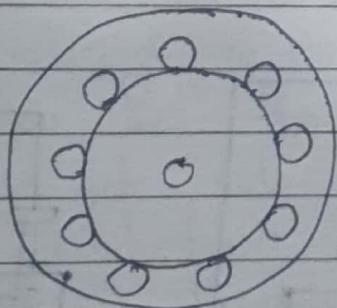

fig(b): Symbolic representation

The bars are permanently shorted to each other through end rings, entire rotor resistance is very small. Hence, the rotor is called short ckt rotor.

(b) Slip-ring or wound rotor :-

This type of construction rotor winding is exactly similar to the stator. The rotor carries a 3- ϕ star or delta connected distributed winding, wound

for some no. of poles as that of stator. The rotor winding are connected in series.

The slip-ring is mounted on the shaft with brushes are resting on it. The brushes are connected to the star connection, & the slip-ring mounted on the shaft with connected to external ckt resistance. The resistor which enable to variation of each rotor phase. - The points to be remember when resistor connected through the Y-connection motor by given connections:

- (i) Control the speed of motor
- (ii) Increasing current from the supply.

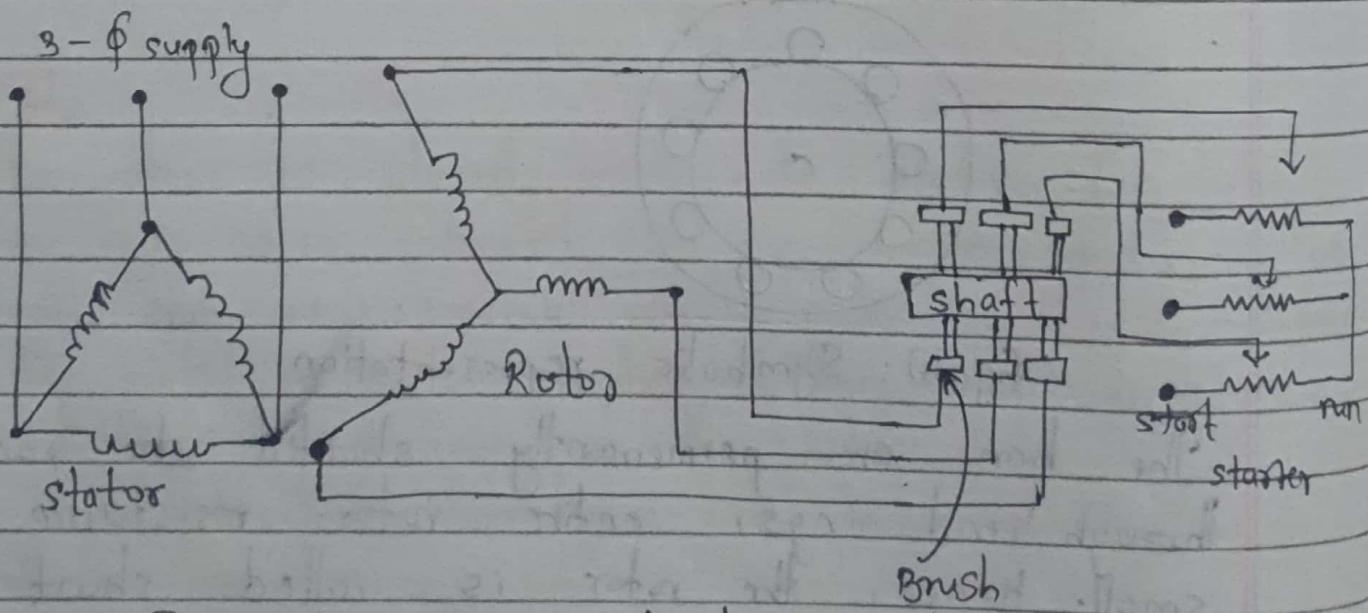


fig: Slip-ring induction motor

Working principle of 3-Φ Induction Motor:

Induction motor works on principle of electromagnetic induction when 3-Φ supply is given to the 3-Φ stator winding. A rotating magnetic field of constant magnitude is produced. The speed of this magnetic field is syn. speed [Ns] in r.m.p.

$$N_s = \frac{120f}{P}$$

where, f = supplied freq.
 P = no's of poles for which stator winding is wounded.

This rotating field is produced by the effect of rotating poles around rotor. Let direction of rotation of this rotating field is clockwise shown in fig (a)

Now, at this instant, rotor is stationary & stator flux, RMF is rotating so it's obvious that there exists a relative motion bet' the RMF and rotor conductor. Now the RMF gets cut by rotor conductor as RMF sweeps over rotor conductor. Whenever conductor cuts the flux, emf is induced in it. So emf gets induced in the rotor conductors called rotor induced emf. This is electromagnetic induction. As rotor form closed ckt, induced emf circulates current through rotor called rotor current. Let dir' of the current is going into the paper denoted by a cross as shown in fig.(b) above.

Any current carrying conductor produces its own flux. So rotor produces its flux called rotor flux. Assume the dir' of rotor flux ~~so not~~ & rotor current is clockwise dir'. This dir' is easily determined using shown in fig.(c) above.

right hand thumb rule. Now, there are two fluxes, one RMF & other rotor flux. Both flux interact with each.

As flux lines acts as stretched rubber band, high flux density ~~area~~ area exerts a push on rotor from low flux density area so that rotor conductor force from that left to right. All rotor conductor experience a force, the overall rotor ~~experience~~ experiences a torque & start rotating.

Application of Induction Motor:

- i) Used in different types of fans.
- ii) Driving pumps in power stations.
- iii) Irrigation project, fertilizer complexes.
- iv) Driving compressions in the street mills, paper mills and crushers and coal conveyor.

Merits of Induction motor:

- i) It is rugged, unbreakable in constructions.
- ii) Simple design, low maintenance cost.
- iii) High overload capacity.
- iv) Sufficiently efficiency, so it's good.
- v) Starting operation is simple.

Demerits:

- i) Speed decreases with increases of load.
- ii) Low power factor.
- iii) Speed cannot be varied without sacrificing some of its efficiency.

- Syn. motor is a 3-Ø electrical motor that runs only at syn. speed. Therefore, a syn. motor runs either at syn. speed or not at all. While running if maintaining constant speed.
- Similar to DC motor, rotating part of motor requires DC supply + generate magnetic field.

Page No. NEW LINK

Construction of Synchronous motor:

It is similar to d.c. machine ~~like~~ where there is no constructional difference betⁿ generator & motor, there is no difference betⁿ construction of syn. motor & the alternator both being the syn. m/c.

The syn. motor construction is basically similar to rotating field type alternator. It consists of two parts:

- i) Stator → similar to Induction Motor, its stationary part (stator) is connected to 3-Ø supply.
- ii) Rotor

i) Stator:

It consists of 3-Ø star-delta connected winding. This is excited by 3-Ø phase a.c. supply.

ii) Rotor:

Rotor field winding ~~the~~ constructions of which can be salient [projected pole] or non-salient [cylindrical] type. Practically, most of the syn. m/c use salient i.e. projected pole type constructions. The field winding is excited by a separate dc supply through slip-ring.

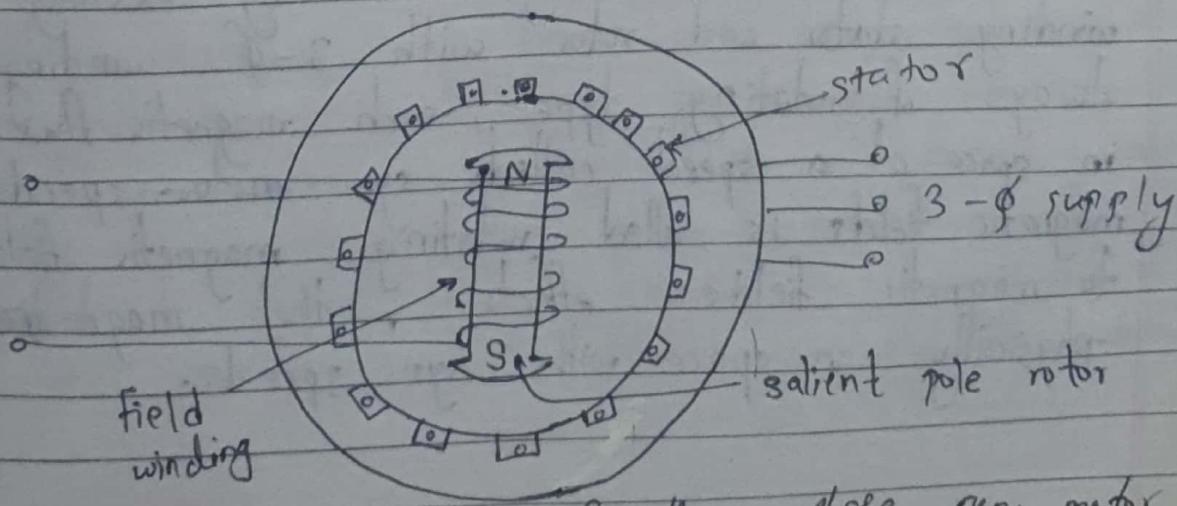


Fig: Schematic representation of three-phase syn. motor

most imp

Working Principle of Syn. motor:-

Syn. motor works on the principle of the magnetic locking. When other two unlike poles are brought near each other, if the magnets are strong, there exists a tremendous (heavy) force of attraction bet' those two poles in such condition the two magnets are said to be magnetically locked.

If one of the two magnets is rotated, the other also rotates in the same directions, with same speed due to force of attractions i.e. due to magnetic locking conditions.

So that, magnetic locking condition, there must exist unlike poles & magnetic force axes of two must be brought very close to each other. Let us see application of this principle in case of syn. motor.

Consider the 3- ϕ synchronous motor, whose stator is wound for 2 plates 2-poles, the magnetic fields are produced in the syn. motor by exciting both the winding stator and rotor with 3- ϕ winding is always of rotating type, such magnetic flux rotated in space at a speed called syn. motor speed. This magnetic field is called rotating magnetic fields. Due to magnetic fields effect, the magnets rotates physically in space with syn. speeds.

Due to magnetic fields effects, the magn.

The syn. speed of a stator rotating in magnetic field depends upon the supply freq. and no's of poles which stator winding is upward wound.

$$N_s = \frac{120f}{P}$$

for simplicity of understanding:-

Consider a two-pole stator, which makes in N_s & S_s & rotating at syn. speed say clockwise directions with rotor positions.

Two similar poles N [at rotor] & N_s [stator] as well as S & S_s will repel each other with results that rotor tends to rotates in the only clockwise directions, but half of period later, stator peaks, having rotated around interchange their position i.e. N_s is at points & S_s at point A. Under this, N_s attracts S & S_s attracts N. Hence rotor tends to rotate clockwise [which is just the reverse of the first direction] so that syn. motor restores at only one speed i.e. syn. speed. We find that due to continuous and rapid rotation of stator poles, the rotor is subjected to a torque which rapidly reversing i.e. quick succession. The rotor is subjected to torque which tends to move it first in one direction and then in opposite directions.

Now, consider the condition . The stator and rotor poles are attracting but is rotating clockwise with such a speed that it turn through one-pole pitch by the time the stator pole interchanging their position . Here again the stator & rotor poles attract each other . It means that if the rotor poles also shift their position along with the stator poles . They will continuously experience a unidirectional torque i.e. clockwise torque.

Uses of syn. motor:-


- i) Syn. motor used for const. speed power application in size above 20 H.P. & more often in size larger than 100 H.P.
- ii) Typical application are fan , blowers , d.c. generator , rolling mills , flour - mills , line - shaft , air & gas - compressor rubber - mills , mixers , crushers etc
- iii) Useful for power - factor control & pulp [soft] grinder & refineries , use in paper making industry.

Speed Control of a D.C. motor:-

- ^{most imp} (1) Variation of resistance in the armature [armature resistance control].
- (2) Variation of field flux (Φ) [field - resistance control].
- (3) Variation of applied voltage.

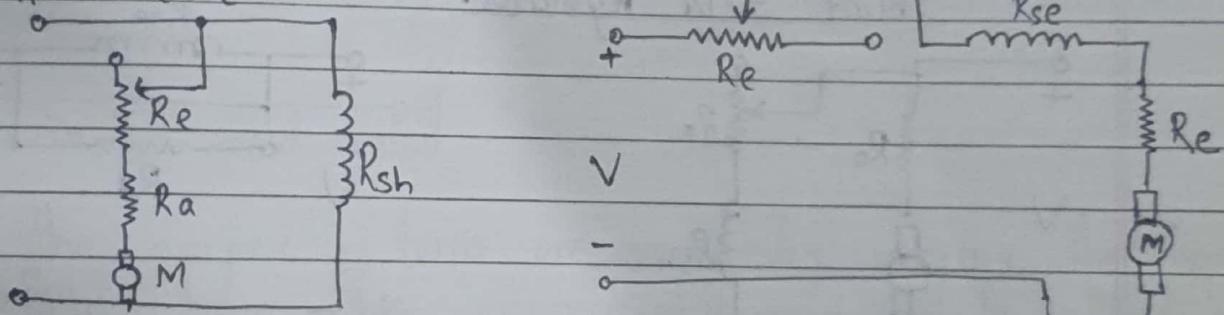1) Armature Resistance Control:

In this method, variable series [R_e] is ~~input~~ in the armature ckt. The voltage applied to the armature is varied.



fig(a): speed control of dc. shunt motor by armature control

fig (b): speed control of d.c. series motor by armature control

The simplest way to achieve this is to connect an external resistor in the armature ckt. By this method, only speed below the rated value can be obtained. As the value of the external resistor is increased, the speed decreases.

This method have following drawbacks:

- (i) Large amount of power is wasted in the external resistance R_e .
- (ii) Control. is limited to give speeds.
- (iii) The value of R_e , the speed reductions is not constant but varies with motor load.

This method is useful for small motor.

Speed / current char'':

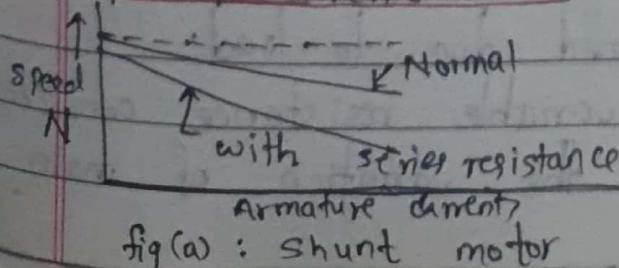


fig (a) : shunt motor

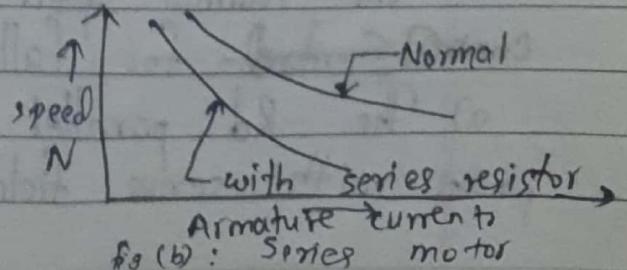


fig (b) : Series motor

Q2) Variation of field ϕ [field resistant control]:
 flux is produced by the field current control of speed by this method is obtained by control the field current.

In Shunt Motor:-

Connecting variable resistance [R_e] in the series with shunt field winding : R_e is called shunt field regulator

Shunt field regulator:-

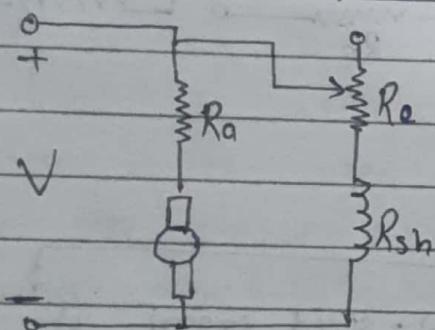


fig (a): speed control of
d.c. shunt motor with ϕ field

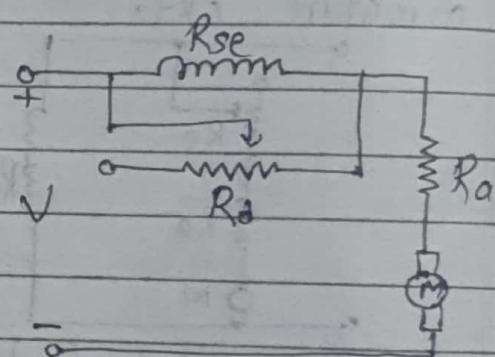


fig (b): Diverter is parallel with
the series field of d.c. m.

Shunt field current, $I_{sh} = \frac{V}{R_{sh} + R_e}$

$$R_{sh} \cdot R_e$$

The connection of R_e in the field reduces the field current & hence the flux ϕ is also reduced. The reduction in flux will result in an increase in the speed. The motor runs as speed ~~for~~ higher than the Normal speed.

control contact for fall the speed due to load:

- a) The R_d parallel variable resistance connected parallel with series field winding the variation of main

current in the series motor through the diverter [R_a]. Thus, the diverter reduces the currents flowing through the field winding. This reduces the flux or increased the speed.

b) The second method used a tapped field control.


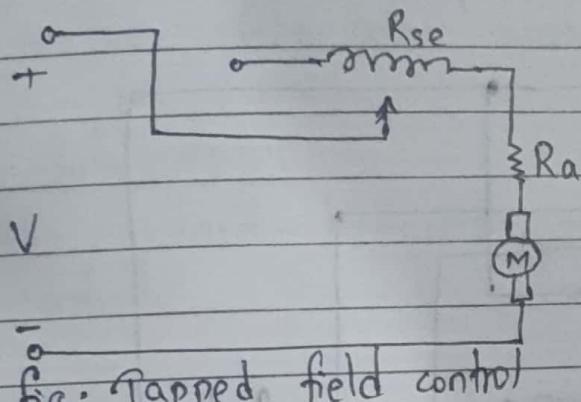


fig: Tapped field control

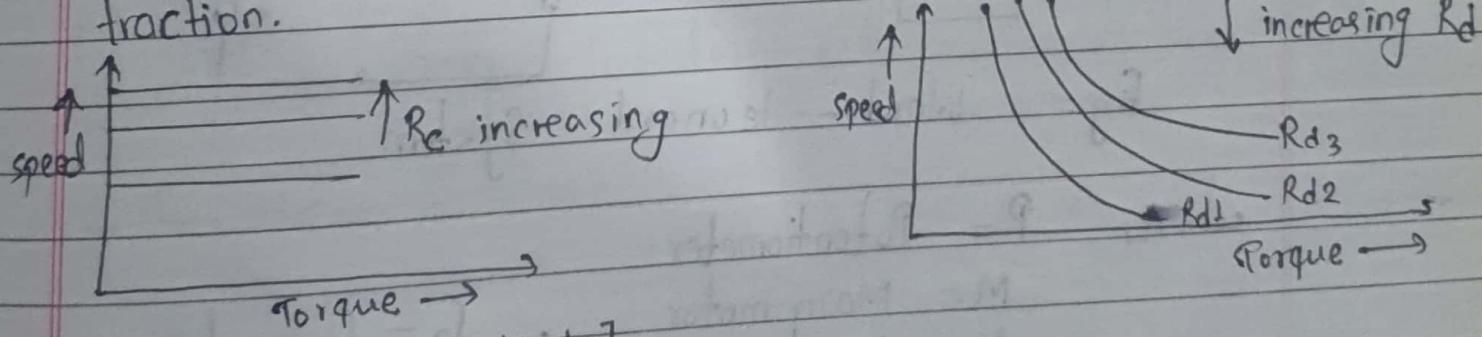Here the ampere - turns are varied by varying the number of field turns. This arrangement is used ~~to~~ in electric traction.



fig(a) : speed - torque [shunt motor]

Advantages:

- This method is easy.
- Shunt field current (I_{sh}) is very small so power loss is small.
- flux weakens so that speed is increasing.

3) Variation of applied Voltage:

for separately excited motors, speed control is obtained by varying the applied voltage to the armature in ward-leonard system. In this method [M] is main motor whose speed is to be controlled.

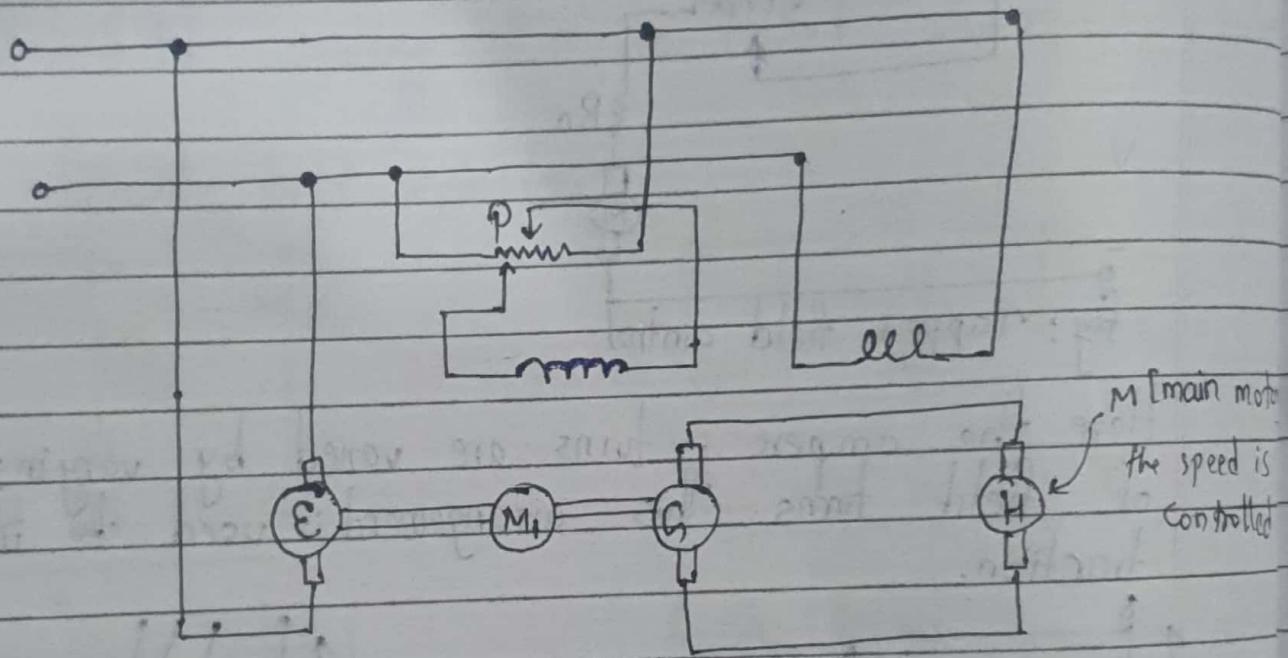


Fig: Ward - leonard System

where, P = Potentiometer

M = Main motor , G = Generator

M₁ = Auxiliary motor drives

Auxiliary motor drives the d.c. generator G. The field of G (generator) is separated from an excited E & the driving motor M, & the generator [G]. The purpose of small generator (E) is to supply voltage of generator to main motor field.

The output of G can be varied wide range by means of potentiometer. The variable voltage when applied direct to the main motor [M]. Wide range of speed to it. Generator field current can also be reversed by the potentiometer. Thus motor can be rotated in reverse dir". Motor - generator always run in same directions.

Advantage:

Ward-Leonard system offers smooth system speed control.

Drawbacks:

- i) Sum of extra m/c makes the system costly.
- ii) Overall efficiency is low, specially at light.
- iii) Large speed range as in motor driving rolling mills, colliery winder, etc.

D.C. Motor Problem:

Numericals

- Q. A 4kVA, 400/200V, 50Hz; single phase transformer has following test data:
 o.c. Test [W.V. side]: 200V, 1A, 64 watt
 s.c. Test [H.V. side]: 15V, 10A, 80 watt
- (a) Determine ckt referred to L.V. sides.
 (b) secondary load voltage on full-load at 0.8 p.f. lagging.
- solution:

O.C. Test [L.V. side]:

$$\text{Voltage } [V_o] = 200V$$

$$\text{No-load current } [I_o] = 1A$$

$$\text{No-load loss } [P_o] = 64 \text{ watt}$$

Now,

$$P_o = V_o I_o \cos \phi_o$$

$$64 = 200 \times 1 \times \cos \phi_o$$

$$\Rightarrow \cos \phi_o = 0.32$$

$$\Rightarrow \sin \phi_o = 0.9474$$

Wattfull component of no-load wment:

$$I_W = I_o \cos \phi_o$$

$$\therefore I_W = 1 \times 0.32 = 0.32 A$$

Magnetizing component of no-load current:

$$I_m = I_o \sin \phi_o = 1 \times 0.9474$$

$$\therefore I_m = 0.9474 A$$

Resistance representing the core loss:

$$R_o = \frac{V_o}{I_W} = \frac{200}{0.32} = 625 \Omega$$

Magnetising reactance:

$$X_0 = \frac{V_0}{I_m} = \frac{200}{0.0474} = 211.1 \Omega$$

$$X_0 = 211.1 \Omega$$

S.C. Test [H.V. sides]:

$$\text{s.c. ckt voltage } [V_{sc}] = 15 \text{ V}$$

$$\text{" " current } [I_{sc}] = 10 \text{ A}$$

$$\text{losses } [P_{sc}] = 80 \text{ watt}$$

Impedance of the ckt referred to H.V. side:

$$Z_{01} = \frac{V_{sc}}{I_{sc}} = \frac{15}{10} = 1.5 \Omega$$

$$[Z_{01} = 1.5 \Omega]$$

Also,

$$P_{sc} = I_{sc}^2 \times R_{01}$$

$$\therefore 80 = 10^2 \times R_{01}$$

$$\Rightarrow [R_{01} = 0.8 \Omega]$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} \\ = \sqrt{(0.375)^2 - (0.2)^2}$$

$$[X_{02} = 0.3179 \Omega]$$

$$V_2 = 193 - j2.675$$

Secondary load voltage = ?

$$I_2 = 4 \times 10^{-2} = 20 \text{ A}$$

$$200$$

$$\therefore [I_2 = 20 \text{ A}]$$

$$\cos \phi_2 = 0.8; \sin \phi_2 = 0.6$$

$$\therefore I_2 = 20 [0.8 - j0.6]$$

$$I_2 = 16 - j12$$

$$T_{02} = R_{02} + jX_{02}$$

$$= 0.2 + j0.3172$$

Secondary load voltage

$$V_2 = 193 - j2.675 = 200 - I_2 \cdot T_{02} \\ = 200 - (16 - j12)(0.375)$$

$$R_{02} = k^2 \cdot R_{01}$$

$$= (1/2)^2 \times 0.8$$

$$[R_{02} = 0.2 \Omega]$$

Transformer Problems

Page No.: / /
Date: / /

- Q. A 200 kVA, 1-φ Transformer with a voltage ratio 6350/660 V has the following winding resistance & reactances. $R_1 = 1.56 \Omega$

$$R_2 = 0.016 \Omega$$

$$X_1 = 4.67 \Omega$$

$$X_2 = 0.048 \Omega$$

Calculate the resistance & reactance of the transformer referred to the high voltage winding.

solution:

$$R_{01} = R_1 + R_2 \left[\frac{N_1}{N_2} \right]^2 \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{formula used}$$

$$X_{01} = X_1 + X_2 \left[\frac{N_1}{N_2} \right]$$

$$R_{01} = 1.56 + 0.016 \left[\frac{6350}{660} \right]^2 = 3.04 \Omega$$

$$X_{01} = X_1 + X_2 \left[\frac{N_1}{N_2} \right]^2 = 4.67 + 0.048 \left[\frac{6350}{660} \right]^2$$

$$= 8.912 \Omega$$

- Q. 1-φ 9300/400 V transformers has the following winding resistance & reactance.

$$R_1 = 0.7 \Omega$$


$$R_2 = 0.011 \Omega$$

$$X_1 = 3.6 \Omega$$

$$X_2 = 0.045 \Omega$$

The secondary is connected to coil having a resistance of 4.5Ω & inductive reactance 3.2Ω , calculate the secondary terminal voltage & the power consumed by the coil.

solution:

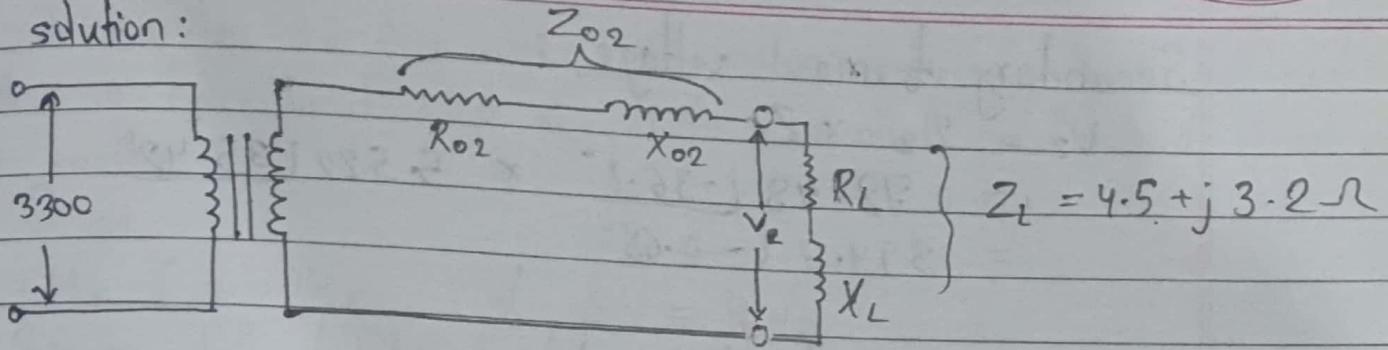

$$R_{02} = R_2 + R_1 \left[\frac{N_2}{N_1} \right]^2 = 0.011 + 0.7 \left[\frac{400}{3300} \right]^2$$

$$\therefore R_{02} = 0.0213 \Omega$$

$$X_{02} = X_2 + X_1 \left[\frac{N_2}{N_1} \right]^2 = 0.045 + 3.6 \left[\frac{400}{3300} \right]^2$$

$$\therefore X_{02} = 0.0979 \Omega$$

$$Z_{02} = R_{02} + X_{02} = 0.0213 + j 0.0979 \Omega$$

$$Z_L = 4.5 + j 3.2 = 5.522 \angle 35.45^\circ$$

Total impedance in the secondary:

$$Z = Z_{02} + Z_L$$

$$= 0.0213 + j 0.0979 + 4.5 + j 3.2$$

$$= 4.5213 + j 3.2979$$

$$= 5.696 \angle 36.1^\circ$$

$$I_2 = \frac{400 \angle 0^\circ}{Z}$$

$$I_2 = 400 \angle 0^\circ$$

$$5.696 \angle 36.1^\circ$$

$$I_2 = 71.48 \angle -36.1^\circ$$

Secondary terminal voltage :

$$V_2 = I_2 \times Z_L$$

$$= 72.48 \angle -36.1^\circ \times 5.522 \angle 35.42^\circ$$

$$= 394.7 \angle -0.68^\circ$$

Power consumed by coil:

$$P_L = I_2^2 \cdot R_L = (71.48)^2 \times 4.5$$

$$= 22992.26 \text{ watt.}$$

- Q. A 4-pole, 3- ϕ induction motor is supplied from 50Hz supply, determine its syn. speed on full load, its speed is observed to be 1410 rpm. Calculate its full load slip.

solution:

Given data are:

$$P = 4, f = 50 \text{ Hz}, N = 1410 \text{ rpm}$$

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm.}$$

full load absolute slip is given by

$$S = \frac{N_s - N}{N_s} \times 100$$

$$= \frac{1500 - 1410}{1500} \times 100 = 0.06$$

$$\therefore S = 0.06$$

$$\% S = 0.06 \times 100 = 6\%$$

$$[\% S = 6\%]$$

Q. A 4-pole, 3-φ, 50Hz star connected induction motor has a full load slip of 4%. Calculate full-load speed of the motor.

Given,

$$P = 4, f = 50\text{Hz}, \therefore S_{f1} = 4\%$$

S_{f1} = full load absolute slip = 0.04

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

Now,

$$S_{f1} = \frac{N_s - N_{f1}}{N_s} \quad \text{where } N_{f1} = \text{full-load speed of motor}$$

$$\therefore 0.04 = \frac{1500 - N_{f1}}{1500}$$

$$\Rightarrow N_{f1} = 1440 \text{ rpm}$$

This is full-load speed of the motor.

D.C. Motor Problems



Q. A 220 d.c. shunt motor draws a current of 40A at full-load & runs with speed of 1400 rpm. Calculate the value of resistance required to be inserted in the armature ckt so that speed drops to 1200 rpm at const. load. Given that $R_a = 0.02\Omega$, $R_f = 100\Omega$

solution:- Given ,

$$I_{a1} = 40\text{A}, N_1 = 1400 \text{ rpm}, V = 220\text{V}$$

$$N_2 = 1200 \text{ rpm}, R_a = 0.02 \Omega, R_f = 100 \Omega$$

Now,

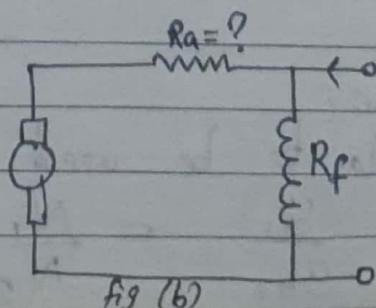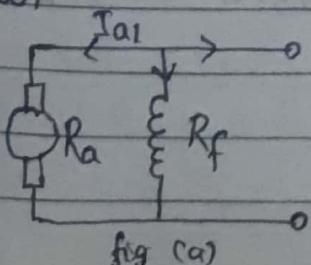

Note :

$$I_{a1} = I_{a2}$$

becz shunt
resistor is not
changed

$$E_{b1} = V - I_{a1} \cdot R_a = 220 - 40 \times 0.02 = 219.2$$

$$\begin{aligned} E_{b2} &= V - I_{a2} [R_a + R_x] \quad \text{where, } R_x = \text{unknown} \\ &= 220 - 40 [0.02 + R_x] \quad \text{resistance} \\ &= 220 - 40 \times 0.02 - 40 R_x \\ &= 219.2 - 40 R_x \end{aligned}$$

$$\frac{N_1}{N_2} = \frac{E_{b1}}{E_{b2}} \quad [\text{formula used}]$$

$$\frac{1400}{1200} = \frac{219.2}{219.2 - 40 R_x} \Rightarrow R_x = 0.75 \Omega$$

Q. A 240V shunt motor runs at 1450 rpm at full-load with armature current 11A. The total resistance of armature and brush is 0.6 ohm, if the speed to be reduced to 1000 rpm with the same armature current, calculate the value of resistance to be connected in series with the armature.

solution:

Given,

$$V = 240 \text{ V}$$

$$N_1 = 1450 \text{ rpm}$$

$$I_{a1} = 11 \text{ A}$$

$$R_x = ?$$

$$R_a = 0.6 \Omega$$

$$N_2 = 1000 \text{ rpm}$$

$$I_{a2} = 11 \text{ A} \quad [\text{same as earlier}]$$

$$E_{b1} = V - I_{a1} \cdot R_a = 240 - 11[0.6] = 233.4$$

$$\begin{aligned} E_{b2} &= V - I_{a2} [R_a + R_x] = 240 - 11[0.6 + R_x] \\ &= 233.4 - 11 R_x \end{aligned}$$

Now,

formula to be used is



$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\text{on } 233.4 = 1450 \\ 233.4 - 11 R_x \quad 1000$$

$$\text{on } 233400 = 1450 [233.4 - 11 R_x]$$

$$\text{on } 160 \cdot 96 - 233.4 = -11 R_x$$

$$\Rightarrow R_x = 6.58 \Omega$$

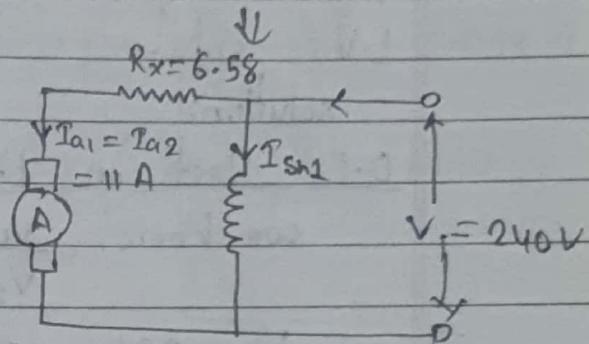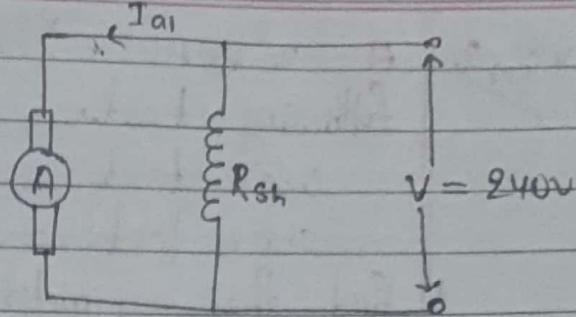

PU 2013 S

Q. A 220V dc shunt motor runs with 1000 rpm & an armature current of 40A. The resistance of armature is 0.5Ω, calculate the value of resistance to be centred in series so that the speed drops to 600 rpm.

Given data,

$$V = 220V, N_1 = 1000 \text{ rpm}, I_{a1} = 40A = I_{a2}$$

$$R_a = 0.5 \Omega, N_2 = 600 \text{ rpm}, R_x = \text{unknown resistance}$$

Now,

$$E_b1 = V - I_{a1} R_a = 220 - 40 \times 0.5 = 200V$$

$$E_b2 = V - I_{a2} [R_a + R_x] = 220 - 40 [0.5 + R_x] \\ = 200 - 40 R_x$$

so,

$$\frac{E_b1}{E_b2} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{200}{200 - 40 R_x} = \frac{1000}{600}$$

$$\Rightarrow R_x = 2 \Omega$$

fig. as above

Transformer

V.V
Imp. A. A 20 kVA, 800/100 A, 1-φ transformer gives the following test result.

O.C. test = 200V, 100A, 120 watt [H.V. side]

S.C. test = 25V, 35A, 320 watt [L.V side]

Find the parameters of equivalent ckt as referred to L.V. side.

solution:

O.C. Test on L.V. side :

$$\text{we know, } \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{200}{400} \quad [\text{Transformation ratio}]$$

$$V_1 = 200, I_o = 100A, \omega = 120 \text{ watt}$$

$$\therefore \cos \phi = \frac{\omega}{V_2 \cdot I_o} = 0.006$$

$$V_2 \cdot I_o$$

$$\sin \phi = \sqrt{1 - \cos^2 \phi} = \sqrt{1 - (0.006)^2} = 0.9999$$

$$I_m = I_o \sin \phi = 99.99 \text{ A}$$

$$I_w = I_o \cos \phi = 0.6 \text{ A}$$

$$X_{01} = \frac{V_1}{I_m} = \frac{200}{99.99} = 2.0 \Omega$$

$$R_{01} = \frac{V_1}{I_w} = \frac{200}{0.6} = 333.3 \Omega$$

S.C. Test on H.V. side :

$$V_{sc} = 25V, I_{sc} = 35A, \omega_{sc} = 320 \text{ watt}$$

$$R_{eq} = \frac{\omega_{sc}}{(I_{sc})^2} = \frac{320}{(35)^2} = 0.179 \Omega$$

$$Z_{eq} = \frac{V_{sc}}{I_{sc}} = \frac{25}{35} = 0.71 \Omega$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{(0.71)^2 - (0.179)^2}$$


$$\therefore X_{eq} = 0.68 \Omega$$

So, required parameter of eq. ckt, resistance & reactance referred to L.V. side:

$$R_L = R_{eq} \left(\frac{N_1}{N_2} \right)^2 = 0.179 \times \left(\frac{200}{400} \right)^2 = 0.044 \Omega$$

$$X_L = X_{eq} \left(\frac{N_1}{N_2} \right)^2 = 0.68 \times \left(\frac{200}{400} \right)^2 = 0.17 \Omega$$

Eq. ckt:

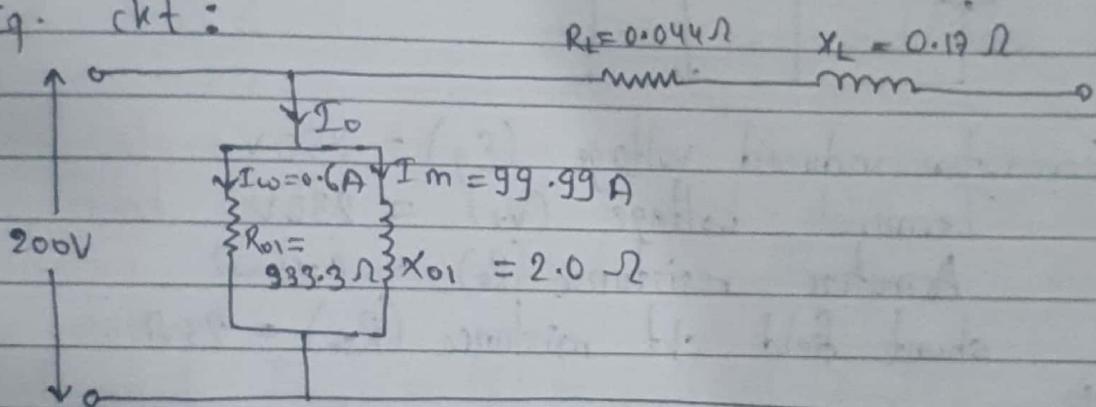

Q. A 4-pole d.c. shunt generator with lap-connected armature supplied a load of 100A at 200V. The armature-resistance is 0.1Ω & the shunt field resistance is 80Ω. Find the total armature current & emf generated:

Solution:

$$\text{Terminal voltage } (V_t) = 200V$$

$$\text{Load current } (I_L) = 100A$$

$$\text{Armature resistance } (R_a) = 0.1\Omega$$

$$\text{Shunt field resistance } (R_{sh}) = 80\Omega$$

$$\text{Shunt field current } (I_{sh}) = \frac{V_t - 200}{R_{sh}} = \frac{200 - 200}{80} = 0A$$

$$\text{Armature current } (I_a) = I_L + I_{sh}$$

$$= 100 + 0 = 100A$$

$$\text{Generated emf } (E_g)$$


$$= V + I_a R_a$$

$$= 200 + 100 \times 0.1$$

$$= 210V$$

Q. A shunt generator has induced voltage of 250V, when the m.k is loaded. The terminal voltage drops down to 230V. Determine the load current if the armature resistance is 0.05Ω & the field ckt resistance is 23Ω.

Solution:

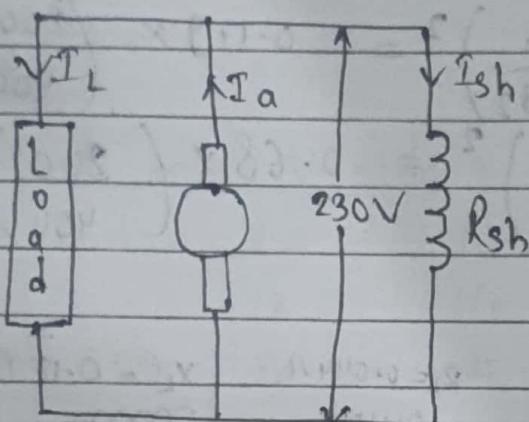

$$I_a = I_{sh} + I_L$$

Generator induced voltage (E_g) = 250V

Terminal voltage (V_t) = 230V

Armature resistance (R_a) = 0.05Ω

shunt field ckt resistance (R_{sh}) = 23Ω

Now,

$$\text{Armature current } (I_a) = \frac{E_g - V_t}{R_a} = \frac{250 - 230}{0.05} = 400 \text{ amp}$$

$$\text{shunt field current } (I_{sh}) = \frac{V_t}{R_{sh}} = \frac{230}{23} = 10 \text{ A}$$

$$\text{Armature current } (I_a) = I_L + I_{sh}$$

$$\therefore I_a - I_{sh} = I_L$$

$$\therefore I_L = 400 - 10 = 390 \text{ amp}$$

Transformer formula:

- 1) Equivalent resistance referred to primary $R_{eq} = R_1 + \left(\frac{N_1}{N_2}\right)^2 \cdot R_2$
- 2) Equivalent reactance referred to primary $X_{eq} = X_1 + \left(\frac{N_1}{N_2}\right)^2 \cdot X_2$
- 3) Equivalent resistance referred to secondary $R'_{eq} = R_2 + \left(\frac{N_2}{N_1}\right)^2 \cdot R_1$
- 4) Equivalent reactance referred to secondary $X'_{eq} = X_2 + \left(\frac{N_2}{N_1}\right)^2 \cdot X_1$

Overall Chapter Numericals

R-L, R-C & R-L-C series ckt Additional Problems

- 1) A resistance & inductance are connected in series across the voltage $V = 283 \sin 314t$. An expression of current is found to be $i = 4 \sin(314t - 45^\circ)$. Find the value of resistance, reactance, inductance & power factor.

solution:

$$\text{Supplied frequency (f)} = \text{coeff. of time (t)} = \frac{314}{2\pi} = 50 \text{ Hz}$$

$$\text{R.M.S. value of applied voltage (V)} = V_{rms} = \frac{283}{\sqrt{2}} = 200 \text{ V}$$

$$\text{RMS value of current (I)} = I_{rms} = \frac{4}{\sqrt{2}} = 2.82 \text{ A}$$

Phase angle (ϕ) = 45° lagging

Impedance of the ckt:

$$Z = \frac{V}{I} = \frac{200 \cdot 11}{\sqrt{2}} = 70.75 \Omega$$

Resistance of the ckt:

$$R = Z \cos \phi = 70.75 \cos 45^\circ = 50 \Omega$$

Reactance of the ckt.:

$$X_L = Z \sin \phi = 70 \cdot 75 \cos 45^\circ = 50 \Omega$$

$$X_L = 2\pi f L$$

$$50 = 2\pi \times 50 \times L$$

$$\therefore L = 0.159 H$$

Power factor:

$$pf = \cos \phi = \cos 45^\circ = 0.707 \text{ lagging}$$

- 2) If the load draws a current of 10A at 0.8 pf lagging when connected to 100V supply, calculate the value of real, reactive & apparent power. Also find the resistance of load.

Solution:

$$\text{Supply voltage (V)} = 100V$$

$$\text{Current (I)} = 10A$$

$$pf = \cos \phi = 0.8 \text{ (lagging)}$$

$$\text{Phase angle } (\phi) = \cos^{-1} (0.8) = 36.87^\circ \text{ (lagging)}$$

$$\text{Real power (P)} = VI \cos \phi \\ = 100 \times 10 \times 0.8 = 800 \text{ watt}$$

$$\text{Reactive power (Q)} = VI \sin \phi \\ = 100 \times 10 \times \sin (36.87^\circ) \\ = 600 \text{ VAR (lagging)}$$

$$\text{Apparent power (S)} = \sqrt{P^2 + Q^2} \\ = \sqrt{800^2 + 600^2} = 1000 \text{ VA}$$

$$\text{Load impedance (Z)} = \frac{V}{I} = \frac{100}{10} = 10 \Omega$$

$$\text{Resistance of load (R)} = Z \cos \phi = 10 \times 0.8 = 8 \Omega$$

3) A voltage $V(t) = 170 \sin(377t + 10^\circ)$ is applied to a ckt if causes a steady state current to find flow which is described by $i(t) = 14.14 \sin(377t - 20^\circ)$. Determine the variation of instantaneous power. Also find the avg. power delivered to ckt & power factor.

solution:

$$V(t) = 170 \sin(377t + 10^\circ)$$

$$i(t) = 14.14 \sin(377t - 20^\circ)$$

$$V_{\max} = 170 \text{ V}$$

$$I_{\max} = 14.14 \text{ A}$$

$$\text{Phase Angle } (\phi) = 10^\circ - (-20^\circ)$$

$$= 30^\circ \text{ (lagging)}$$

$$\text{Variation of instantaneous power} = \frac{1}{2} V_{\max} \cdot I_{\max} \cos(2\omega t - \phi)$$

$$= \frac{1}{2} \times 170 \times 14.14 \times \cos(2 \times 377t - 30^\circ)$$

$$= 1.202 \cdot \cos[754t - 30^\circ]$$

Average power delivered,

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi$$

$$= \frac{170}{\sqrt{2}} \times \frac{14.14}{\sqrt{2}} \times \cos 30^\circ$$

$$= 1.041 \text{ watt}$$

4) A voltage $V(t) = 150 \sin(2\pi f)t$, 50Hz is applied to series ckt considering of 10Ω resistance, 0.0318H inductance.

Determine: (a) the current $i(t)$ expression

(b) phase angle bet" voltage & current

(c) pf . (d) active power consumed

(e) max^m value pulsating energy.

solution:

$$\begin{aligned} V(t) &= 150 \sin(2\pi f)t \\ &= 150 \sin(2\pi \times 50)t \\ &= 150 \sin(100\pi t) \end{aligned}$$

$$\text{Resistance } (R) = 10 \Omega$$

$$\text{Inductance } (L) = 0.0318 \text{ H}$$

$$\text{Inductive reactance } (X_L) = 2\pi f \cdot L = 2\pi \times 50 \times 0.0318 = 10 \Omega$$

$$\text{Phase angle } (\phi) = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{10}{10}\right) = 45^\circ \text{ or } \frac{\pi}{4}$$

(lagging)

$$\text{Ckt impedance } (Z) = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 10^2} = 14.14 \Omega$$

$$\text{Max value of current } (I_{\max}) = \frac{V_{\max}}{Z} = \frac{150}{14.14} = 10.6 \text{ A}$$

(a) The current $i(t)$ expression $i(t) = I_{\max} \sin[100\pi t - \phi]$
 $= 10.6 \times \sin[100\pi t - \frac{\pi}{4}]$

(b) Phase angle bet' voltage & current
 $\phi = \frac{\pi}{4} = 45^\circ \rightarrow \text{(lagging)}$

(c) $\text{pf} = \cos \phi = \cos 45^\circ = 0.707 \text{ lagging}$

(d) Active power consumed $= VI \cos \phi$

$$= \frac{V_{\max}}{\sqrt{2}} \times \frac{I_{\max}}{\sqrt{2}} \times 0.707$$

$$= \frac{150}{\sqrt{2}} \times \frac{10.6}{\sqrt{2}} \times 0.707$$

$$= 562 \text{ watt}$$

(e) Max^m value pulsating energy

$$= \frac{1}{2} V_{\max} \cdot I_{\max} = \frac{1}{2} \times 150 \times 10 \cdot 6$$

$$= 79.5 \text{ VA}$$

5) A 50Hz sinusoidal voltage $= 311 \sin \omega t$ is applied to RL-series ckt. If the magnitude of resistance is 5Ω & that of inductance is 0.02 H :

(a) calculate the effective value of steady current & relative phase angle.

(b) obtain the expression for instantaneous value.

solution:

Peak value of applied voltage:

$$V_{\max} = 311 \text{ V}$$

RMS value of applied voltage

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}} = \frac{311}{\sqrt{2}} = 219.91 \text{ V}$$

Resistance of ckt:

$$R = 5 \Omega$$

Inductive reactance of ckt:

$$X_L = 2\pi f \cdot L = 2\pi \times 50 \times 0.02 = 6.28 \Omega$$

Impedance of the ckt:

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{5^2 + 6.28^2} = 8.03 \Omega$$

(a) Effective value of steady current:

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{219.91}{8.03} = 27.387 \text{ A}$$

$$\text{Phase angle } (\phi) = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{6.28}{5} \right) = 51.474 \text{ (lagging)}$$

Since, in R-L ckt current lags behind the applied voltage

$$\begin{aligned}
 (b) \quad i &= I_{\max} \cdot \sin(\omega t - \phi) \\
 &= 27.387 \times \sqrt{2} \sin(\omega t - 51.474^\circ) \\
 &= 38.73 \sin(\omega t - 51.474^\circ)
 \end{aligned}$$

(c) A coil of resistance 10Ω & inductance $0.02H$ is connected in series with another coil of resistance 6Ω & inductance $15mH$ across a $230V$, $50Hz$ supply, calculate

- (a) Impedance of the ckt
- (b) voltage drop across each coil
- (c) total power consumed by the ckt.

Solution:

$$R = 10\Omega$$

$$L = 0.02H$$

$$X_L = 2\pi f L$$

$$= 2\pi \times 50 \times 0.02$$

$$= 6.28 L$$

$$\text{mm} \quad \text{mm}$$

$$\leftarrow V_1 \rightarrow$$

$$R = 6\Omega$$

$$I = 15 mH = 15 \times 10^{-3} H$$

$$X_L = 2\pi f L$$

$$= 2\pi \times 50 \times 15 \times 10^{-3}$$

$$= 4.71 L$$

$$\text{mm} \quad \text{mm}$$

$$\leftarrow V_2 \rightarrow$$



$230V, 50Hz$

$$Z_1 = (10 + j 6.28)\Omega = 11.81 \angle 32.14^\circ$$

$$Z_2 = (6 + j 4.71)\Omega = 7.629 \angle 38.14^\circ$$

(a) Impedance of whole ckt:

$$\begin{aligned}
 Z &= Z_1 + Z_2 = (10 + j 6.28) + (6 + j 4.71)\Omega \\
 &= (16 + j 10.99)\Omega \\
 &= 19.414 \angle 34.5^\circ \Omega
 \end{aligned}$$

Current through the ckt:

$$I = \frac{V}{Z} = \frac{230 \angle 0^\circ}{19.41 \angle 34.5^\circ} = 11.847 \angle -34.5^\circ$$

(b) Voltage drop across coil-1:

$$V_1 = I Z_1 = 11.847 \angle -34.5^\circ \times 11.81 \angle 32.14^\circ \\ = 139.9 \angle -2.36^\circ$$

Voltage drop across coil-2:

$$V_2 = I Z_2 = 11.847 \angle -34.5^\circ \times 7.629 \angle 38.14^\circ \\ = 90.38 \angle -2.36^\circ V$$

(c) Total power consumed by the ckt:

$$P = VT \cos \phi = 230 \times 11.847 \times \cos 34.5^\circ \\ = 2246 \text{ watt} = 2.246 \text{ kW}$$

or,

Total power consumed by the ckt:

$$P = I^2 [R_1 + R_2] \\ = 11.847^2 [10 + 6] = 2246 \text{ watt} \\ = 2.246 \text{ kW}$$

fall
2019 PV


7) Two coil A & B are connected in series across 240V, 50Hz supply. The resistance of A & B is 5Ω & the Inductance of B is 0.015H. If input of supply is 3kW or 2kVAR find the inductance of A & resistance of B. Calculate the voltage across each coil.

solution:

$$\text{Input true power } (P) = 3 \text{ kW}$$

$$\text{Input reactive power } (Q) = 2 \text{ kVAR}$$
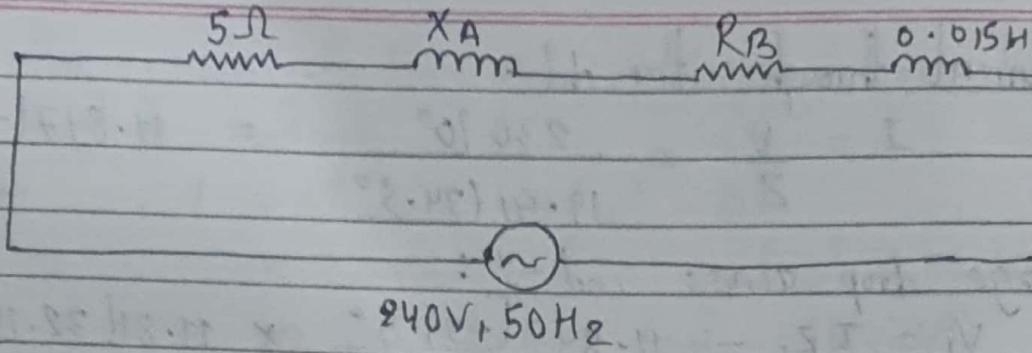
$$\text{Input apparent power } (S) = \sqrt{P^2 + Q^2} \\ = \sqrt{3^2 + 2^2} = 3.606 \text{ kVA}$$



Ckt current:

$$I = \frac{S \times 1000}{V} = \frac{3.606 \times 1000}{240}$$

$$\therefore I = 15.025 \text{ A}$$

Total resistance of the ckt:

$$R_T = R_A + R_B = \frac{P}{I^2} = \frac{3 \times 1000}{(15.025)^2} = 13.29 \Omega$$

Resistance of coil - B:

$$R_B = R_T - R_A = 13.29 - 5 = 8.29 \Omega$$

Impedance of the ckt:

$$Z = \frac{V}{I} = \frac{240}{15.025} = 15.97 \Omega$$

Total inductive reactance of the ckt:

$$\begin{aligned} X_{LT} &= \sqrt{Z^2 - R_T^2} \\ &= \sqrt{(15.97)^2 - (13.29)^2} \\ &= 8.86 \Omega \end{aligned}$$

$$Z^2 = R_T^2 + X_L^2$$

Inductive reactance of the coil - A:

$$X_A = X_{LT} - X_B$$

$$= 8.86 - 2\pi f L$$

$$= 8.86 - 314 \times 0.015$$

$$= 4.15 \Omega$$

$$X_B = X_L = 2\pi f L$$

$$= 314 \times 0.015$$

Inductance of coil - A:

$$2\pi f X_L = X_A$$

$$\therefore X_A = X_L = 2\pi f \cdot L$$

$$\Rightarrow L = \frac{X_A}{2\pi f} = \frac{4.15}{314} \quad [X_A = 4.15]$$

$$\Rightarrow L = 0.0132 \text{ H}$$

Voltage across coil - A:

$$V_A = I \times Z_A = I \sqrt{R_A^2 + X_A^2} \quad [Z_A = \sqrt{R_A^2 + X_A^2}]$$

$$= 15.025 \sqrt{5^2 + 4.15^2}$$

$$= 97.63 \text{ V}$$

Voltage across coil - B:

$$V_B = I \times Z_B = I \times \sqrt{R_B^2 + X_B^2}$$

$$= 15.025 \times \sqrt{8.29^2 + 4.71^2} = 143.25 \text{ V}$$

8) for a.c ckt, the voltage & current are given by

$$V = (200 \sin 377t) \text{ V}$$

$$I = 8 \sin (377t - 30^\circ) \text{ amp}$$

Determine the power factor, true power, apparent power & reactive power of the ckt. Also cross verify by Power Triangle.

solution:

$$V = 200 \sin 377t \text{ V}$$

$$I = 8 \sin (377t - 30^\circ) \text{ A}$$

$$\text{Phase angle } (\phi) = 30^\circ$$

RMS value of applied voltage:

$$V = \frac{V_{\max}}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.42 \text{ V}$$

RMS value of current:

$$I = \frac{I_{\max}}{\sqrt{2}} = \frac{8}{\sqrt{2}} = 5.65 \text{ A}$$

(a) Power factor = $\cos \phi = \cos 30^\circ = 0.866$ (lagging)

(b) True power (P) = $VI \cos \phi$


$$= 141.42 \times 5.65 \times 0.866 \\ = 692.82 \text{ watt}$$

(c) Apparent power (S) = $VI = 141.42 \times 5.65$
= 800 VA

(d) Reactive power (Q) = $VI \sin \phi$

$$= 141.42 \times 5.65 \times \sin 30^\circ \\ = 400 \text{ VAR}$$

By Power triangle:

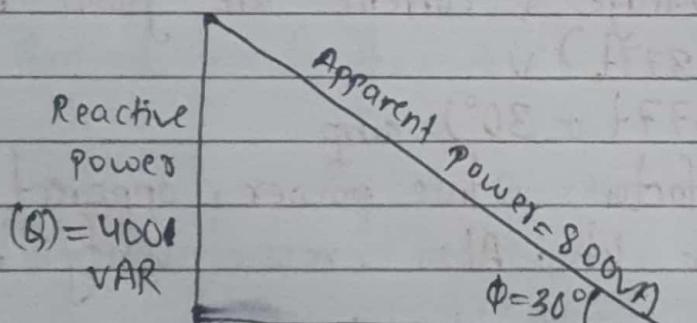

$$S = \sqrt{P^2 + Q^2} \\ = \sqrt{(692.82)^2 + (400)^2} \\ = 800 \text{ VA}$$

Phase angle $\phi = \tan^{-1} \left(\frac{Q}{P} \right)$

$$= \tan^{-1} \left(\frac{400}{692.82} \right) \\ = 30^\circ$$

- 9) The voltage applied to the ckt is $V = 100 \sin(\omega t + 30^\circ)$. Current flowing in the ckt is $I = 20 \sin(\omega t + 60^\circ)$. Determine the impedance, resistance, reactance, power factor of the ckt.

solution:

$$V = 100 \sin (\omega t + 30^\circ) \rightarrow \text{Voltage applied to the ckt}$$

$$i = 20 \sin (\omega t + 60^\circ) \rightarrow \text{current flowing in the ckt}$$

Current leads the applied voltage by $[60^\circ - 30^\circ]$ i.e. 30°

$$\text{ckt impedance } (Z) = \frac{V_{\max}}{I_{\max}} = \frac{100}{20} = 5 \Omega$$

$$\text{ckt Resistance } (R) = Z \cos \phi = 5 \times \cos 30^\circ = 4.33 \Omega$$

$$\text{ckt Reactance } (X) = Z \sin \phi = 5 \times \sin 30^\circ = 2.5 \Omega$$

[capacitive]

$$P_f = \cos \phi = \cos 30^\circ = 0.866 \quad [\text{lagging}]$$

$$\text{Power factor of ckt } (P) = V_{\text{rms}} \cdot I_{\text{rms}} \cos \phi$$

$$= \frac{V_{\max}}{\sqrt{2}} \cdot \frac{I_{\max}}{\sqrt{2}} \cdot \cos \phi$$

$$= \frac{100}{\sqrt{2}} \times \frac{20}{\sqrt{2}} \times \cos 30^\circ$$

$$\therefore P = 866 \text{ watt}$$

- 10) A supply of 400V, 50Hz is applied to a series R-C ckt. Find the value of C. If the power absorbed by the resistor be 500 watt at 150V. What is the energy stored in capacitor?

solution:

$$V = 400V$$

$$P = 500 \text{ watt}$$

$$\text{Voltage across resistor } (V_R) = 150V$$

Current through R-C. series ckt:

$$I = \frac{P}{V_R} \quad [\because P = I \cdot V_R]$$

$$= \frac{500}{150} = 3.33A$$

Voltage drop across capacitor:

$$V_c = \sqrt{400^2 - 150^2}$$

$$\therefore V_c = 370.8 \text{ V}$$

$$V^2 = V_R^2 + V_c^2$$

$$V_c = \sqrt{V^2 - V_R^2}$$

Capacitive reactance of the ckt:

$$X_c = \frac{V_c}{I} \quad \therefore V_c = I \cdot X_c$$

$$\therefore X_c = \frac{370.8}{3.33} = 111.30 \Omega$$

Capacitance of ckt:

$$C = \frac{1}{2\pi f \cdot X_c} = \frac{1}{314 \times 111.30}$$

$$\Rightarrow C = 28.6 \mu\text{F}$$

$$\therefore X_c = \frac{1}{\omega C}$$

$$\Rightarrow C = \frac{1}{\omega X_c}$$

Energy stored at capacitive

$$= \frac{1}{2} C \times V_{c \text{ max}}^2$$

$$= \frac{1}{2} \times 28.6 \times 10^{-6} \times (370.9 \times \sqrt{2})^2$$

$$= 3.934 \text{ J}$$

10) A series ckt has $R = 10 \Omega$, $L = 50 \text{ mH}$ & $C = 100 \mu\text{F}$ & supply is 200V, 50Hz, find

(a) Impedance

(b) Current

(c) Power

(d) pf

(e) voltage drop across each elements.

solution:

$$R = 10 \Omega ; L = 50 \text{ mH} = 0.05 \text{ H} ; C = 100 \text{ nF} = 10^{-9} \text{ F}$$

Inductive reactance of ckt:

$$X_L = 2\pi f \cdot L = 2\pi \times 50 \times 0.05 \\ = 15.7 \Omega$$

Capacitive reactance of ckt:

$$X_C = \frac{1}{2\pi f \cdot C} = \frac{1}{2\pi \times 50 \times 10^{-9}} \\ = 31.83 \Omega$$

$$(a) \text{ ckt impedance } (Z) = \sqrt{R^2 + (X_L - X_C)^2} \\ = \sqrt{(10)^2 + (15.7 - 31.83)^2} \\ = 18.979 \Omega$$

$$(b) \text{ ckt current } (I) = \frac{V}{Z} = \frac{200}{18.979} = 10.538 \text{ A}$$

$$\text{Phase angle of ckt } (\phi) = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \\ = \tan^{-1} \left(\frac{15.7 - 31.83}{10} \right) = -58.2^\circ$$

(c) Power of ckt:

$$P = VI \cos \phi \\ = 200 \times 10.53 \times \cos(-58.2^\circ) \\ = 1110.61 \text{ watt}$$

$$(d) \text{ pf} = \cos \phi \\ = \cos(-58.2^\circ) = 0.529 \text{ leading}$$

(e) Voltage drop across resistance (R) & each elements:

$$V_R = IR = 10.53 \times 10 = 105.38 \text{ V}$$

$$V_L = I \cdot X_L = 10 \times 15.7 = 157 \text{ V}$$

$$V_C = I \cdot X_C = 10 \times 31.83 = 318.3 \text{ V}$$

- 12) A voltage $v(t) = 150 \sin 1000t$ is applied across a series RLC ckt where, $R = 40 \Omega$, $L = 0.13H$, $C = 10\mu F$.
- compute rms value of steady state current
 - find rms voltage across the inductor.
 - find rms voltage across capacitor.
 - draw phasor diagram showing all voltage components
 - Determine the reactive power supplied by source.
- solution:

$$V_{max} = 150V$$

$$\omega = 1000 \text{ rad/sec}$$

RMS value of supply voltage

$$V_{rms} = \frac{V_{max}}{\sqrt{2}} = \frac{150}{\sqrt{2}} = 106V$$

$$R = 40\Omega$$

$$X_L = 2\pi f \cdot L = \omega L = 1000 \times 0.13 = 130\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \times 10 \times 10^{-6}} = 100\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(40)^2 + (130 - 100)^2}$$

$$\therefore Z = 50\Omega$$

(a) RMS value of steady state current:

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{106}{50} = 2.12A$$

$$\text{Phase angle } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left[\frac{130 - 100}{40} \right]$$

$$\phi = 36.87^\circ \text{ lagging}$$

(a) Voltage across inductor's resistance (R):

$$V_R = I_{\text{rms}} \times R = 2.12 \times 40 = 84.8 \text{ V} \text{ in phase with } I$$


(b) Voltage drop across inductor (L):

$$V_L = I_{\text{rms}} \times X_L = 2.12 \times 130 = 275.6 \text{ V leading current } I \text{ by } 90^\circ$$

(c) Voltage drop across capacitor (C):

$$V_C = I_{\text{rms}} \times X_C = 2.12 \times 100 = 212 \text{ V lagging current } I \text{ by } 90^\circ$$

(d) Phasor diagram:

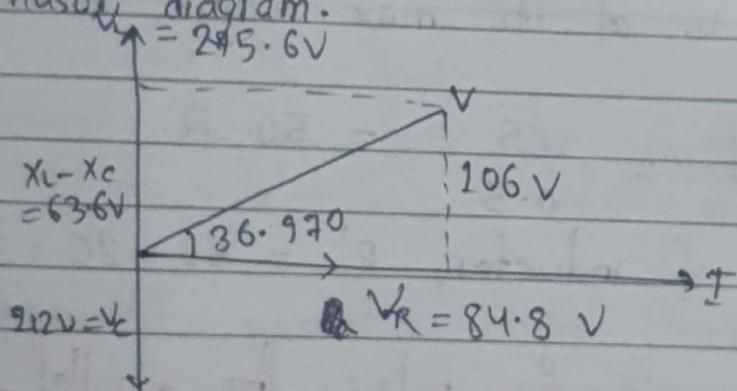

13) A 20Ω resistor is connected in series with an inductor, a capacitor & ammeter across a 25V variable freq supply when the freq. is 400Hz , the current is at its maximum value of 0.5A & potential difference across the capacitor is 150V , calculate (a) the capacitance of capacitor, (b) the resistance & inductance of inductor.

solution:

Voltage drop across capacitor C ,

$$V_C = 150 \text{ V}$$

Current through capacitor,

$$I = \text{supply current} = 0.5 \text{ A}$$

$$(a) \text{Capacitance } (C) = \frac{1}{2\pi f \cdot V_c} = \frac{1}{2\pi \times 400 \times 150} = 1.326 \mu F$$

Since current is at its max^m value, reactance is zero.

Inductive reactance of ckt = capacitive reactance of ckt

$$\Rightarrow X_L = X_C$$

$$\text{on } 2\pi f \cdot L = \frac{1}{X_C}$$

$$\Rightarrow X_C = \frac{1}{2\pi f \cdot C} = \frac{1}{4\pi^2 f^2 \cdot C} = \frac{1}{4\pi^2 \times (400)^2 \times 1.326 \times 10^{-6}}$$


$$\Rightarrow L = 1.326 \mu H \Rightarrow L = 0.1193 H$$

Since current is at its max^m value, reactance is zero

$$R = \frac{V}{I} = \frac{25}{0.5} = 50 \Omega$$

So, resistance of inductor, $R' = 50 - 20 = 30 \Omega$

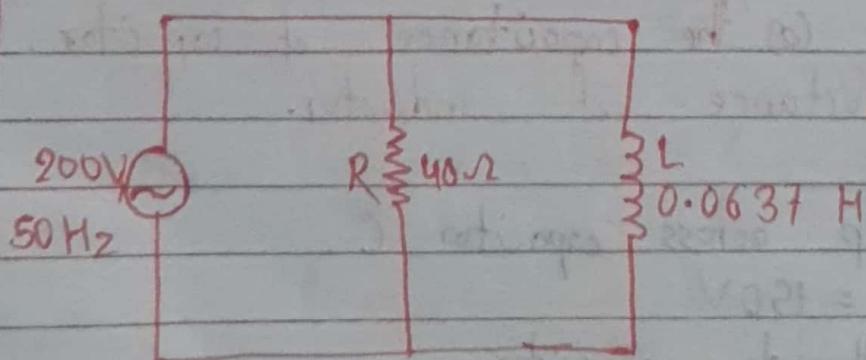- 14) The ckt shown in fig below, the parallel R-L arrangement connected across 200 volt, 50Hz ac supply. Calculate : (a) current drawn from supply
 (b) apparent power, (c) real power, (d) reactive power



solution:

Resistance of reactive resistive branch:

$$R = 40 \Omega$$

Inductive reactance of inductive branch:

$$X_L = 2\pi f \cdot L = 2\pi \times 50 \times 0.0637 = 20 \Omega$$

Current drawn by resistive branch:

$$I_R = \frac{V}{R} = \frac{200}{40} \quad \therefore V = I_R \cdot R$$

$$\therefore I_R = 5 A$$

Current drawn by inductive branch:

$$I_L = \frac{V}{X_L} = \frac{200}{20} \quad \therefore V = I_L \cdot X_L$$

$$\Rightarrow I_L = 10 A$$

(a) Current drawn from the supply:

$$I = \sqrt{I_R^2 + I_L^2} = \sqrt{5^2 + 10^2} = 11.18 \text{ amp}$$


(b) Apparent power: $S = V \times I$

$$= 200 \times 11.18 = 2236 \text{ VA}$$

(c) Real power, $P = V \cdot I_R = 200 \times 5$
 $= 1000 \text{ watt}$

(d) Reactive power, $Q = V \cdot I_L$
 $= 200 \times 10$
 $= 2000 \text{ VAR}$

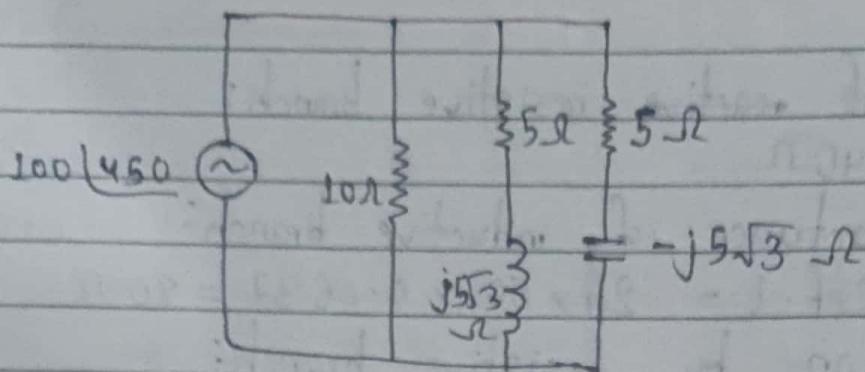- 15) Consider an electric ckt shown in fig. below, determine
 (a) the current & power consumed in each branch.
 (b) the supply current & pf.



solution:

$$I_1 = \frac{V}{R} = \frac{100 \angle 45^\circ}{10 \angle 0^\circ} = 10 \angle 45^\circ A$$

Current in inductive branch:

$$I_2 = \frac{V}{Z_2} = \frac{100 \angle 45^\circ}{5 + j5\sqrt{3}} = \frac{100 \angle 45^\circ}{10 \angle 60^\circ} = 10 \angle -15^\circ$$

Current in capacitive branch:

$$I_3 = \frac{V}{Z_3} = \frac{100 \angle 45^\circ}{5 - j5\sqrt{3}} = \frac{100 \angle 45^\circ}{10 \angle -60^\circ} = 10 \angle 105^\circ$$

Power consumed in resistive branch:

$$P_1 = I_1^2 R = 10^2 \times 10 = 1000 W = 1 kW$$

Power consumed in inductive branch:

$$P_2 = I_2^2 R_2 = 10^2 \times 5 = 500 \text{ watt}$$

Power consumed in capacitive branch:


$$P_3 = I_3^2 \cdot R_3 = 10^2 \times 5 = 500 \text{ watt}$$

Supply current:

$$\begin{aligned} I &= I_1 + I_2 + I_3 = 10 \angle 45^\circ + 10 \angle -15^\circ + 10 \angle 105^\circ \\ &= (7.0 + j7.0) + (9.6 - j2.5) + (-2.5 + j11) \\ &= (14.14 + j14.14) A \\ &= 20 \angle 45^\circ A \end{aligned}$$

- 16) For ckt shown in fig below, calculate the current in each branch
 b) total current taken, c) total power consumed by ckt
 (d) Reactive power consumed / generated (e) p.f. of the ckt.
 (f) phasor diagram of the ckt.

solution

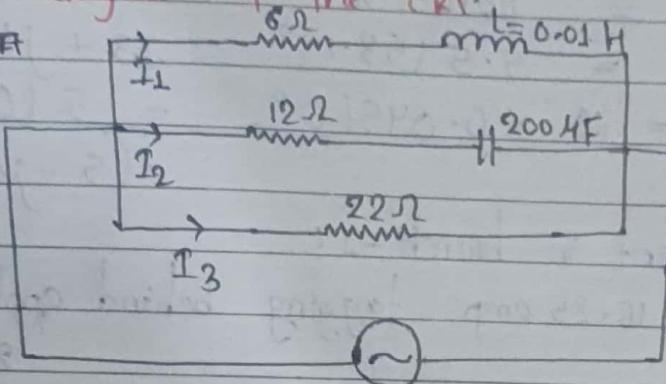

solution:

* 110V, 50Hz

$$X_L = 2\pi f \cdot L = 2\pi \times 50 \times 0.01 = 3.14$$

$$Z_1 = R_1 + j X_L = (6 + j 3.14)\Omega$$

$$Z_2 = R_2 + j X_C = (12 - j 15.92)\Omega$$

$$Z_3 = (22 + j 0)\Omega$$

$$X_C = \frac{1}{2\pi f \cdot C}$$

$$= \frac{1}{314 \times 200 \times 10^{-6}}$$

$$= -j 15.92$$

Admittance of Branch -1:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{6 + j 3.14} = \frac{6 - j 3.14}{(6)^2 + (3.14)^2} = \frac{6 - j 3.14}{45.85}$$

Admittance of Branch -2:

$$Y_2 = \frac{1}{Z_2} = \frac{1}{12 - j 15.92} = \frac{12 + j 15.92}{(12)^2 + (15.92)^2} = 0.03 + j 0.0415$$

Admittance of branch -3:

$$Y_3 = \frac{1}{Z_3} = \frac{1}{22 + j 0} = \frac{22 - j 0}{(22)^2 + (j 0)^2} = \frac{22}{484} = 0.045 \angle 0^\circ$$

$$I_1 = V Y_1 \quad \text{current in branch -1}$$

$$I_2 = V Y_2 \quad \text{" " branch -2}$$

$$I_3 = V Y_3 \quad \text{" " branch -3}$$

$$I_1 = 110 \angle 0^\circ \times 0.147 \angle -27.64^\circ$$

$$= 16.25 \angle -27.64^\circ$$

$$= (14.4 - j 7.54) \text{ amp}$$

$$I_2 = VY_2 = 110 \angle 0^\circ \times 0.05 \angle 53.13^\circ$$

$$= 5.5 \angle 53.13^\circ = 3.3 + j 4.4 \text{ amp}$$

$$I_3 = VY_3 = 110 \times 0.045 \angle 0^\circ = 5 \angle 0^\circ$$

$$= (5 + j 0) \text{ amp}$$

(a) Thus, current in branch -1:

$I_1 = 16.25 \text{ amp}$ lagging behind applied voltage by 27.64°

b Current in branch -2:

$I_2 = 5.5 \text{ amp}$ leading applied voltage by 53.13°

Current in branch -3:

$I_3 = 5 \text{ amp}$ in phase with applied voltage.

~~$$Y = Y_1 + Y_2 + Y_3$$~~

Total admittance of ckt:

$$Y = 0.1308 - j 0.668 + 0.03 + j 0.04 + 0.045$$

$$= 0.2063 - j 0.0285 = 0.208 \angle -7.866^\circ$$

(b) Total current taken:

$$I = VY = 110 \angle 0^\circ \times 0.208 \angle -7.866^\circ$$

$$= 22.88 \angle -7.866^\circ$$

i.e. Total current drawn:

$I = 22.88 \text{ amp}$ lagging behind the applied voltage by 7.866°

(c) Total power consumed by the ckt:

$$\begin{aligned} P &= VI \cos \phi \\ &= 110 \times 22.88 \times 0.99 \\ &= 2.493 \text{ kW} \end{aligned}$$


(d) Reactive power (Q):

$$\begin{aligned} Q &= VI \sin \phi \\ &= 110 \times 22.88 \times \sin(7.866) \\ &= 344.44 \end{aligned}$$


(e) Power factor consumed by the ckt:

$$pf = \cos \phi = \cos(7.866) = 0.99 \text{ lagging}$$

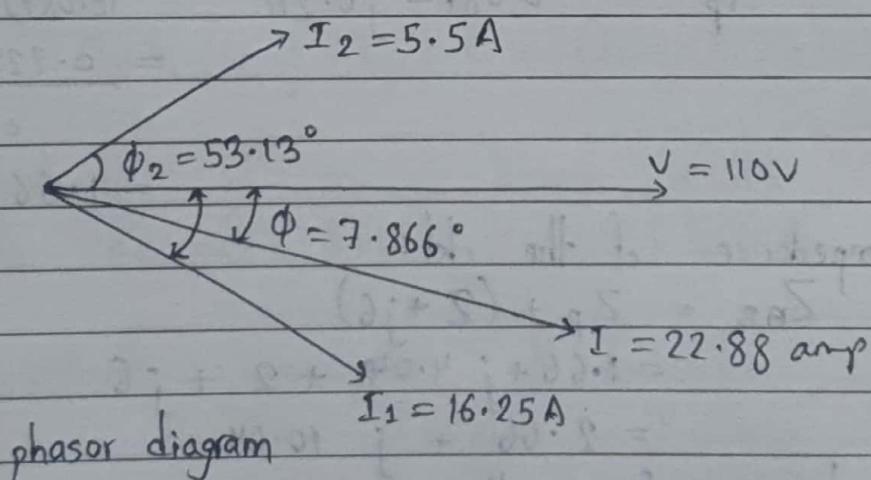(f) Phasor diagram: Voltage phasor has been taken as reference phasor.



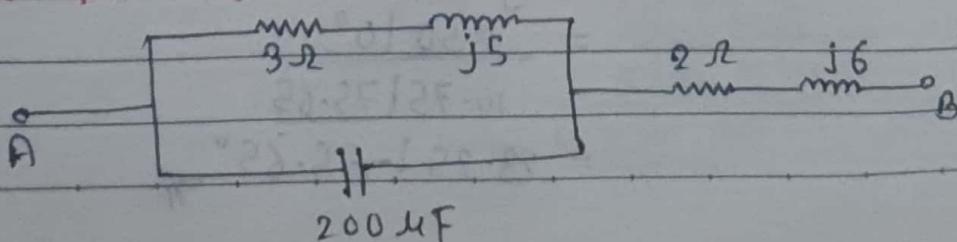- 15) A voltage of 250V at 50Hz is applied to the ckt drawn in fig below find the current drawn from the source.



solution:

Reactance of 900uF at 50Hz supply freq.

$$X_C = \frac{1}{2\pi f \cdot C} = \frac{1}{2\pi \times 50 \times 900 \times 10^{-6}} = 15.91 \Omega$$

Admittance of parallel branches:

$$\begin{aligned} Y_p &= \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{3+j5} + \frac{1}{j15.91} \quad [\because Y = \frac{1}{Z}] \\ &= \frac{3-j5}{9+25} + \frac{1}{j15.91} \\ &= 0.087 - j0.145 - j0.066 \\ &= (0.087 - j0.211) \Omega \end{aligned}$$

Impedance in parallel branch:

$$\begin{aligned} Z_p &= \frac{1}{Y_p} = \frac{1}{0.087 - j0.211} = \frac{0.087 + j0.211}{(0.087)^2 + (0.211)^2} \\ &= 0.228 \angle 67.59^\circ \\ &\quad 0.052 \end{aligned}$$

Total impedance of the ckt:

$$\begin{aligned} Z_{AB} &= Z_p + (2+j6) \\ &= 1.66 + j4.04 + 2 + j6 \\ &= 2.66 + j10.04 \end{aligned}$$

Current drawn from the source:

$$\begin{aligned} I &= \frac{V}{Z_{AB}} = \frac{250 \angle 0^\circ}{2.66 + j10.04} = \frac{250 \angle 0^\circ}{10.73 \angle 75.65^\circ} \\ &= \frac{250 \angle 0^\circ}{10.75 \angle 75.65^\circ} \\ &= 23.25 \angle -75.65^\circ \# \end{aligned}$$


18) In series - parallel ckt, the parallel branches A & B are in series with branch C. The impedances are

$$Z_A = (4 + j3) \Omega ; Z_B = (4 - j16/3) \Omega ,$$

$Z_C = 6 + j8 \Omega$, if the current $I_C = (25 + j0)$ amp, determine,

- (a) branch current & voltage,
- (b) total voltage,
- (c) phasor diagram.

Solution:

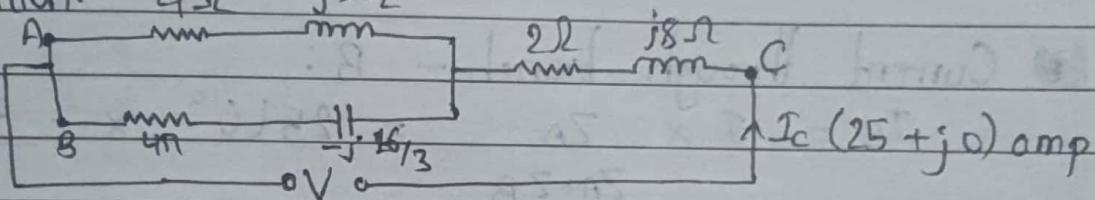

Impedance of branch A of parallel ckt:

$$Z_A = (4 + j3) \Omega = 5 (36.86^\circ) \Omega$$

Impedance of branch B of || ckt:

$$Z_B = (4 - j\frac{16}{3}) \Omega = (4 - j5.33) \Omega = 6.66 \angle -53.11^\circ$$

Impedance of series branch of C:

$$Z_C = (6 + j8) \Omega = 10 \angle 75.96^\circ$$

Equivalent impedance of || ckt:

$$\begin{aligned} Z_{AB} &= Z_A \cdot Z_B = 5 (36.86^\circ) \times 6.66 \angle -53.11^\circ \\ &= \frac{Z_A + Z_B}{Z_A \cdot Z_B} = \frac{5 (36.86^\circ) + 6.66 \angle -53.11^\circ}{5 (36.86^\circ)} \\ &= \frac{33.3 \angle -16.25^\circ}{(8 - j2.33) \Omega} \\ &= \frac{33.3 \angle -16.25^\circ}{8.33 \angle -16.23^\circ} \\ &= 4 \angle 0^\circ \Omega \end{aligned}$$

(a) Current through branch A:

$$\begin{aligned} I_A &= \frac{I}{Z_A + Z_B} = \frac{25 \angle 0^\circ \times 6.66 \angle -53.11^\circ}{8.33 \angle -16.23^\circ} \\ &= \frac{166.6 \angle -53.11^\circ}{8.33 \angle -16.23^\circ} \\ &= 19.98 \angle -36.88^\circ \end{aligned}$$

$$\begin{aligned} Z_A &= 4 + j3 \\ Z_B &= (4 - j5) \\ Z_A + Z_B &= (8 - j2) \\ &= 8.33 \angle -16.23^\circ \end{aligned}$$

Current through branch - B:

$$\begin{aligned} I_B &= \frac{I}{Z_A + Z_B} = \frac{25 \angle 0^\circ \times 5 \angle 36.86^\circ}{8.33 \angle -16.23^\circ} \\ &= \frac{125 \angle 36.86^\circ}{8.33 \angle -16.23^\circ} = 15 \angle 53.09^\circ \end{aligned}$$

Voltage drop across the parallel branch:

$$\begin{aligned} V_{AB} &= I \times Z_{AB} \quad [\because V = IZ] \\ &= 25 \angle 0^\circ \times 4 \angle 0^\circ \\ &= 25 \times 4 \angle 0^\circ = 100 \angle 0^\circ \end{aligned}$$

Voltage drop across series branch:

$$\begin{aligned} V_C &= I \cdot Z_C = 25 \angle 0^\circ \times 8.29 \angle 75.96^\circ \\ &= 206 \angle 75.96^\circ \end{aligned}$$

(b) Impedance of the whole ckt:

$$\begin{aligned} Z &= Z_{AB} + Z_C \\ &= (4 + j0) + (2 + j8) \\ &= 6 + j8 \Omega \\ \therefore Z &= 10 \angle 53.13^\circ \end{aligned}$$


Voltage across the whole ckt:

$$V = 12$$

$$= 25 \angle 0^\circ \times 10 \angle 53.13^\circ$$

$$= 250 \angle 53.13^\circ$$


(c) Phasor diagram:

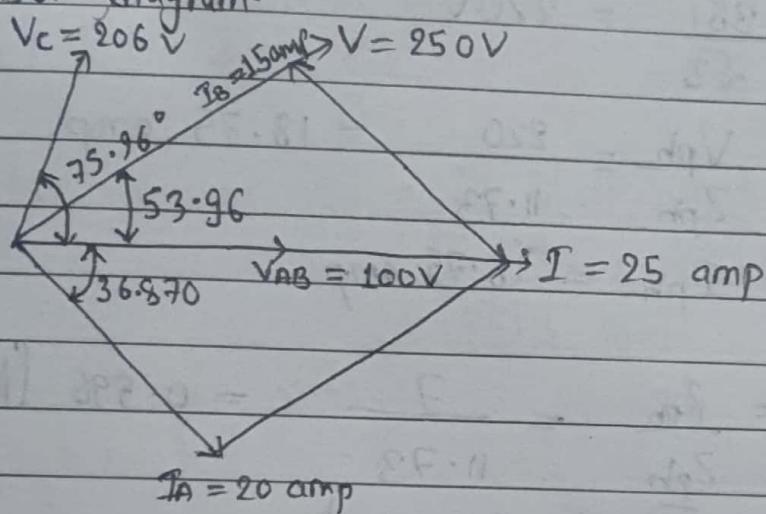

Star - delta Problems

- 1) Three similar coil each of resistance 7Ω & inductance 0.03H are connected in Δ (wye) (or star) to a 381V , $3-\phi$, 50Hz supply. Calculate: (a) line currents
(b) Total power

Solution:

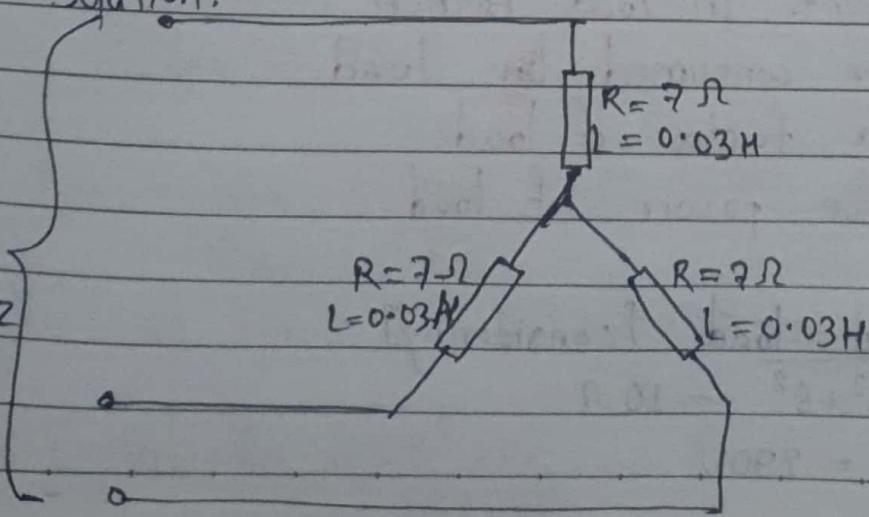

$$X_L = \omega L = 2\pi f \cdot L = 2\pi \times 50 \times 0.03 = 9.42 \Omega$$

for star

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$Z_{ph} = \sqrt{R^2 + X_L^2} = \sqrt{7^2 + (9.42)^2} = 11.73 \Omega$$

$$V_L = \sqrt{3} V_{ph}$$

$$\Rightarrow V_{ph} = \frac{381}{\sqrt{3}} = 220V$$

$$\text{Now, } I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{220}{11.73} = 18.75 \text{ amp}$$

$$I_L = I_{ph} = 18.75 \text{ amp}$$

Again,

$$\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{7}{11.73} = 0.596 \text{ [lag]}$$

$$\begin{aligned} \text{Power} &= \sqrt{3} V_L \cdot I_L \cdot \cos \phi \\ &= \sqrt{3} \times 381 \times 18.75 \times 0.596 \\ &= 7374.50 \text{ watt} \end{aligned}$$

2) A star-connected alternator supplied a delta connected load. The impedance of the load branch is $(8+j6)\Omega$ /phase. The line voltage is 230V. Determine:

- (a) Def current in load branch
- (b) power consumed by load
- (c) power factor of load
- (d) reactive power of load

solution:

Delta connected load. [considering]

$$Z_{ph} = \sqrt{8^2 + 6^2} = 10 \Omega$$

$$V_L = V_{ph} = 230V$$

$$(a) I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230}{10} = 23A$$

$$(b) I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 23 = 39.8A$$

$$P = \sqrt{3} V_L \cdot I_L \cos\phi$$

$$= \sqrt{3} \times 230 \times 39.8 \times 0.8$$

$$\therefore P = 12,684 \text{ watt}$$

$$(c) \cos\phi = \frac{Z_{ph}}{Z_L} = \frac{8}{10} = 0.8$$

$$\begin{cases} Z = 8+j6 = 10 \angle 36.86^\circ \\ \phi = 36.86^\circ \\ \cos\phi = 0.8 \end{cases}$$

$$(d) \text{Reactive power } (Q) = \sqrt{3} V_L \cdot I_L \cdot \sin\phi$$

$$= \sqrt{3} \times 230 \times 39.8 \times 0.6$$

$$= 9513 \text{ watt}$$

3) A 220V, 3-φ voltage is applied to balanced delta-connected 3-φ load of phase impedance $(15+j20)\Omega$

(a) find phasor current in each live

(b) what is power consumed per phase?


(c) what is the phasor sum of the three live current? What does it have this value?

solution:

$$V_{ph} = 220V$$

$$Z_{ph} = \sqrt{(25)^2 + (20)^2}$$

$$\therefore Z_{ph} = 25\Omega$$

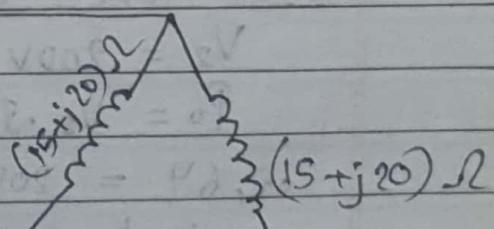

$$(a) I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{220}{25} = 8.8A$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 8.8 = 15.24A$$

$$(b) P = I_{ph}^2 \cdot R_{ph} = 8.8^2 \times 15$$

$$= 1162 \text{ watt}$$

Phasor sum would be zero because the three currents are equal in magnitude & have a equal phase difference of 120° .

Transformer Problems

1) A 4 kVA, $400/200$ V, 50Hz, 1- ϕ transformer has following test delta are given:

O.C. test [L.V. side]: $200, 1A, 64$ watt

S.C. test [H.V. side]: $15, 10A, 80$ watt

Determine

(a) ckt referred to L.V. side.

(b) secondary load voltage on full-load 0.8 pf lagging

solution:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{400}{200} = \text{transformation ratio}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{2}{1} = \text{transformation ratio}$$

O.C. Test [L.V. side]:

$$V_2 = 200V, I_0 = 1A, P_0 = 64 \text{ watt}$$

$$P_0 = V_2 \cdot I_0 \cdot \cos \phi_0$$

$$\text{or}, 64 = 200 \times 1 \times \cos \phi_0$$

$$\therefore \phi_0 = 71.33$$

$$\therefore \sin \phi = 0.94$$

Magnetizing component of no-load current:

$$I_m = I_0 \cdot \sin \phi_0$$

$$= 1 \times 0.94$$

$$= 0.94$$

Wattful component of no-load current:

$$I_w = I_0 \cdot \cos \phi_0 \\ = 1 \times 0.32 = 0.32$$

Magnetizing reactance:

$$X_{02} = \frac{V_2}{I_m} = \frac{200}{0.94} = 212.76 \Omega$$

Resistance representing the core loss:

$$R_{02} = \frac{V_2}{I_w} = \frac{200}{0.32} = 625 \Omega$$

S.C. Test [H.V. side]:

$$V_{sc} = 15V, I_{sc} = 10A, P_{sc} = 80 \text{ watt}$$

$$P_{sc} = I_{sc}^2 \cdot R_{eq}$$

$$\therefore 80 = (10)^2 \cdot R_{eq}$$

$$\Rightarrow R_{eq} = 0.8$$

$$Z_{eq} = \frac{V_{sc}}{I_{sc}} = \frac{15}{10} = 1.5 \Omega \quad [\because V_{sc} = I_{sc} Z_{eq}]$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{1.5^2 - 0.8^2}$$

$$\therefore X_{eq} = 1.26 \Omega$$


Equivalent ckt, ref° parameter (Resistance & reactance) referred to L.V. side

$$R_2 = R_{eq} \cdot \left(\frac{N_2}{N_1} \right)^2 = 0.8 \left(\frac{200}{400} \right)^2 = 0.2 \Omega$$

$$X_2 = X_{eq} \cdot \left(\frac{N_2}{N_1} \right)^2 = 1.26 \left(\frac{200}{400} \right)^2 = 0.315 \Omega$$

$$Z_2 = R_2 + j X_2 \\ = (0.2 + j 0.315) \Omega \\ = 0.37 (\text{at } 57.58^\circ)$$

Equivalent ckt:

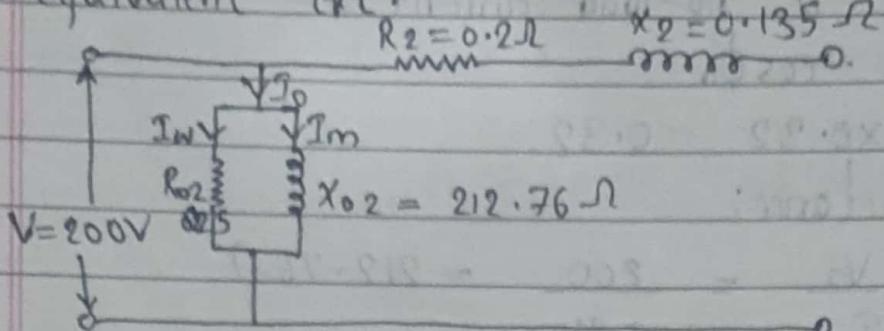

(b) Secondary load voltage (V_2) = ?

$$\text{Secondary full-load current } (I_2) = \frac{4 \times 10^3}{200} = 20 \text{ amp}$$

$$\cos \phi = 0.8 \text{ [lag]}$$

$$\therefore I_2 = 20 \angle -36.86^\circ$$

Secondary load voltage:

$$\begin{aligned} V_2 &= 200 - I_2 \cdot Z_2 \\ &= 200 - 20 \angle -36.86^\circ \times 0.37 \angle 57.58^\circ \\ &= 200 - 74.1 \angle 94.44^\circ \\ &= 200 - 74.1 \angle 20.72^\circ \end{aligned}$$

$$\therefore V_2 = 192.6V$$

Working Principle of Syn. Motor

→ When the 3-φ winding of a syn. motor is fed with a 3-φ supply, a rotating magnetic field is produced having constant magnitude which revolves around the stator with syn speed $N_s = 120f/p$. It is called syn. speed because it synchronizes to the power frequency.

→ Suppose at any instant N_s happens to face S. N_s tries to pull S in clockwise direction due to mutual attraction. The rotor takes little time to move since it has high inertia. Now,

the revolving pole N_s is replaced by S_s . Then S is repelled in the anticlockwise dirⁿ. Here, the high inertia ^{MAYUR} motor first moves in one direction & then in other direction in quick succession. As a

result, the rotor stays where it is. That's why syn. motor is not self starting.

→ However rotor can be made self starting with the help of squirrel cage when 3-φ supply is fed to stator winding. Then a rotating magnetic field is produced which induces an EMF in the damper winding. Now the syn. motor starts up as an induction motor. When it reaches near its syn. speed, the rotor poles get magnetized & start rotating at syn. speed in same dirⁿ. Here, the stator & rotor run at same speed. In fact, torque in a syn. motor never develop any other speed other than the syn. speed!

→ State Ohm's law and write its limitations:

It states that,

At constant temp', the current through an ideal resistor is directly proportional to the voltage applied across the resistor.

$$I \propto V \Rightarrow V = I R$$

The constant of proportionality is written as R & this is the resistance value of the resistor.

$$V = I R$$

Limitations of Ohm's law

- 1) This law cannot be applied to unilateral networks. A unilateral network has unilateral elements like diode, transistor, etc., which do not have some voltage current relation for both directions of current.
- 2) Ohm's law is also not applicable for non-linear elements. Non-linear elements are those which do not have current exactly proportional to the applied voltage, that means the resistance value of those elements changes for different values of voltage and current. Examples of non-linear elements are thyristor, electric arc, etc.