

Superposition Theorem

Statement:

The superposition theorem states that "In any linear networks containing two or more sources, the response in any element is equal to the algebraic sum of the response causes by individual source acting alone, while the other source are non-operative"; i.e.


i.e. while considering the effect of individual source, other ideal voltage source & other ideal current source in the network are replaced by short ckt & open ckt across their terminals.

This theorem is valid only for linear system.

Procedure


- 1) Remove the source Pick one source,
- 2) Remove the source,
- 3) Voltage - short ckt (s.c.)
Current - open ckt (o.c.)
- 4) Determine the individual response,
- 5) Sum of the response of reaction.

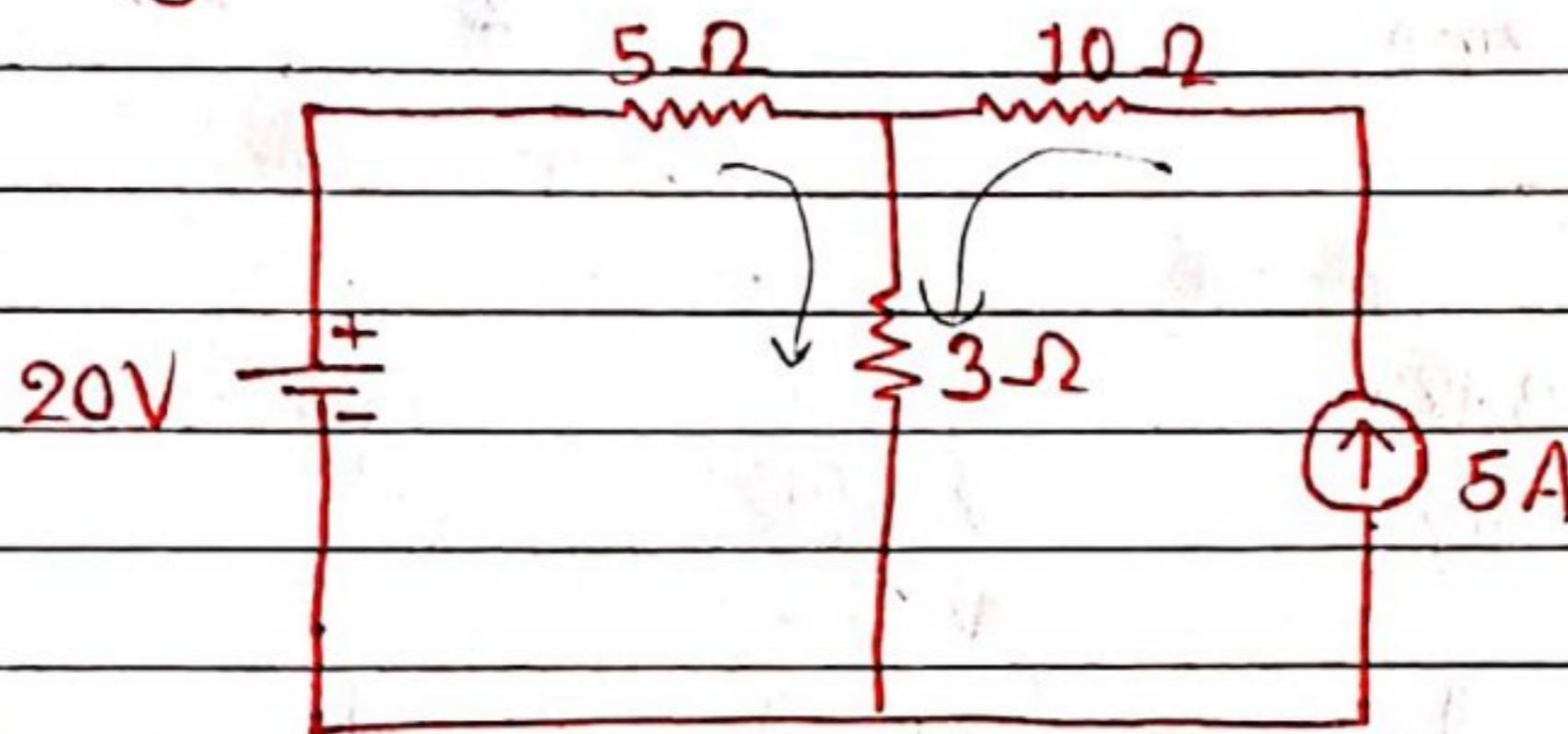Q.1) Use the superposition theorem, find the current passing through 3Ω resistor.



solution:-

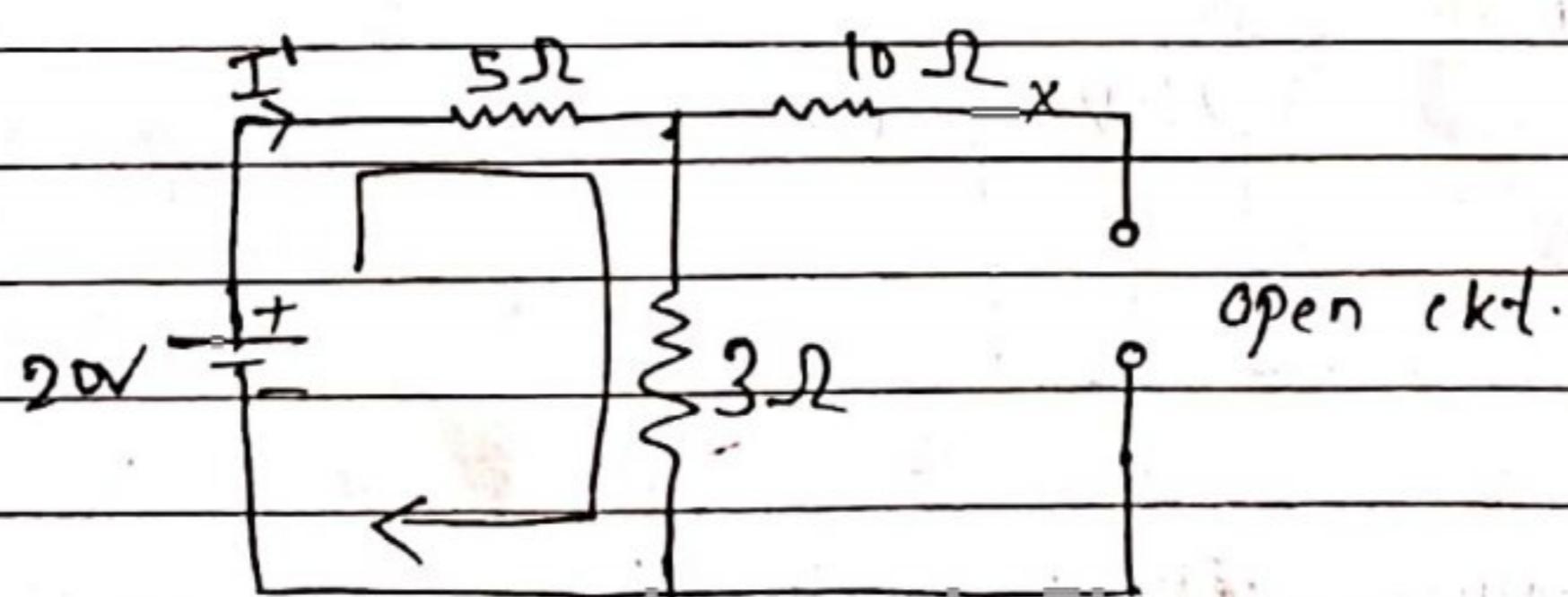
Case I: Consider the voltage source (20v):



$$I' = \frac{20}{5+3} = 2.5 \text{ A}$$

$$\Rightarrow I' = 2.5 \text{ A}$$

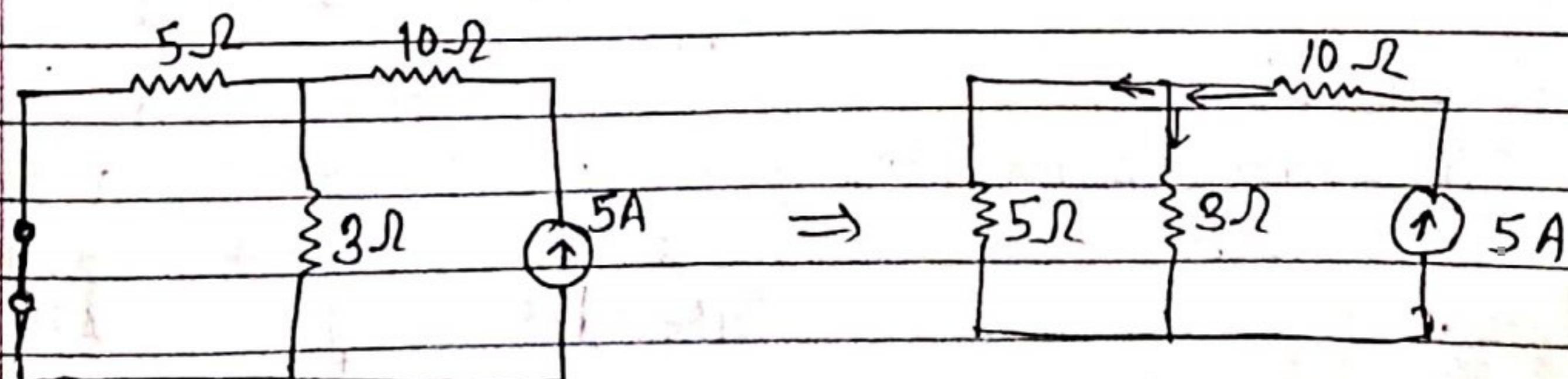Case II: Consider the current source (5A):



$$I'' = 5 * \frac{5}{3+5} = 3.125 \text{ amp}$$

[current division formula is used]

$$I'' = 3.125 \text{ amp}$$


$$I_2 = I_T \times \frac{R_1}{R_1 + R_2}$$

$$\therefore I = I' + I''$$

$$= 2.5 + 3.125$$


$$= 5.625 \text{ amp}$$

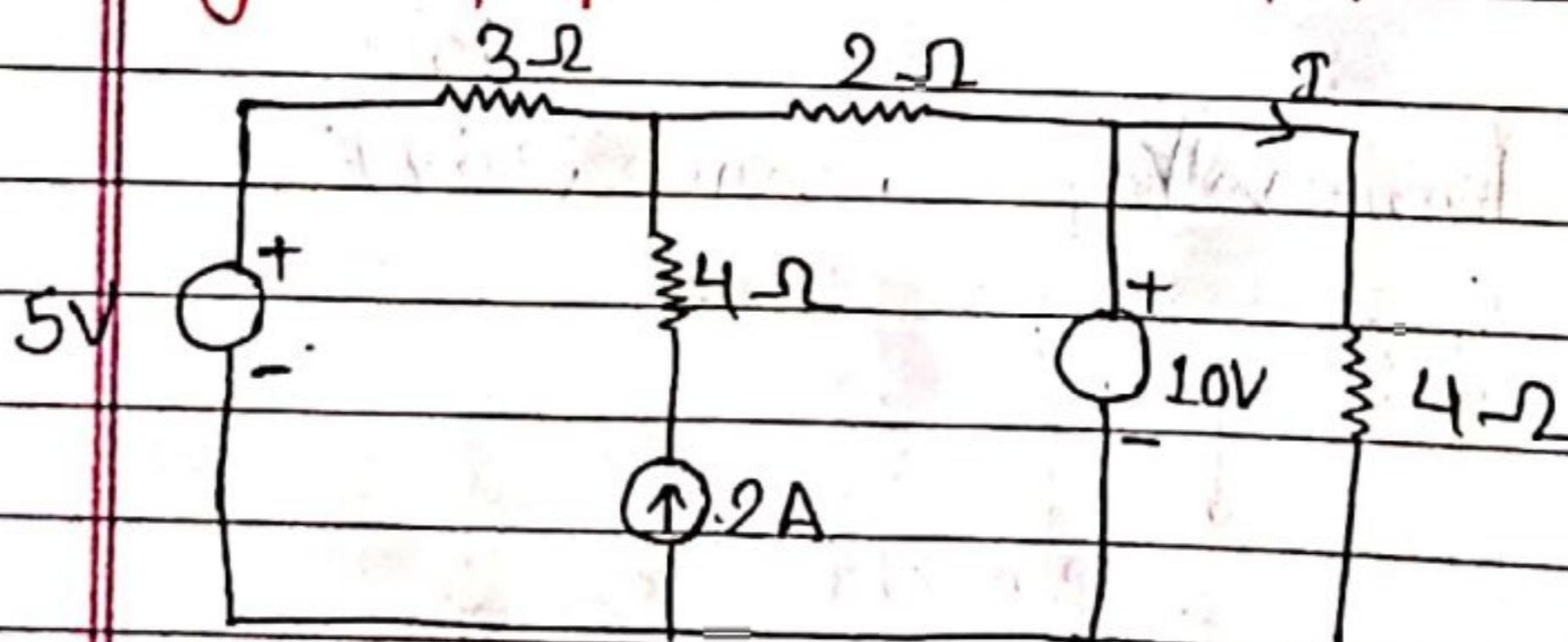Q.2) By superposition theorem, find the current in 4Ω resistor



Solution:

Step-1: 5V source acting alone:

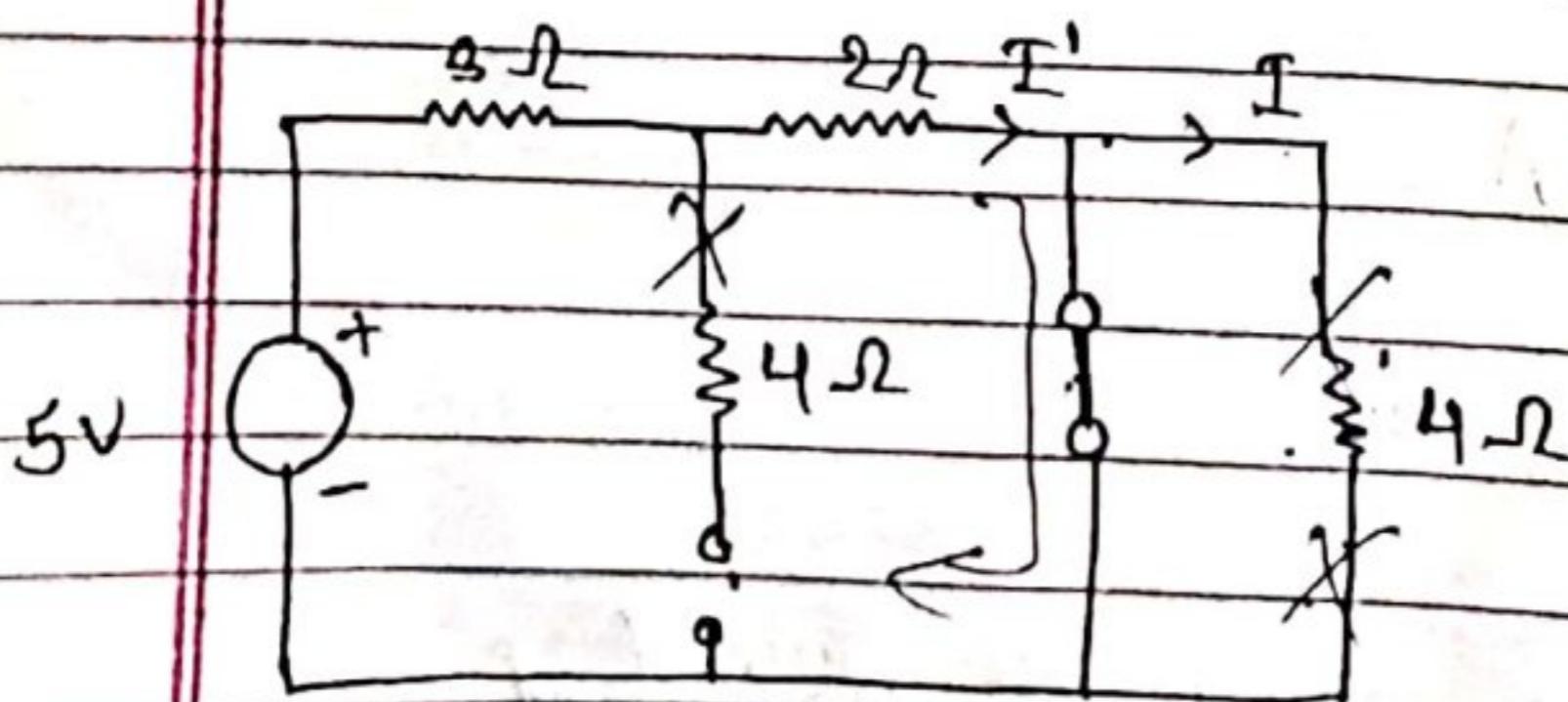

$$I' = \frac{5}{3+2} = 1 \text{ amp}$$


$$\therefore I' = 1 \text{ amp}$$

no current flows through 4Ω resistor

$$I' = 0$$

Step-2:

2A current source acting alone.

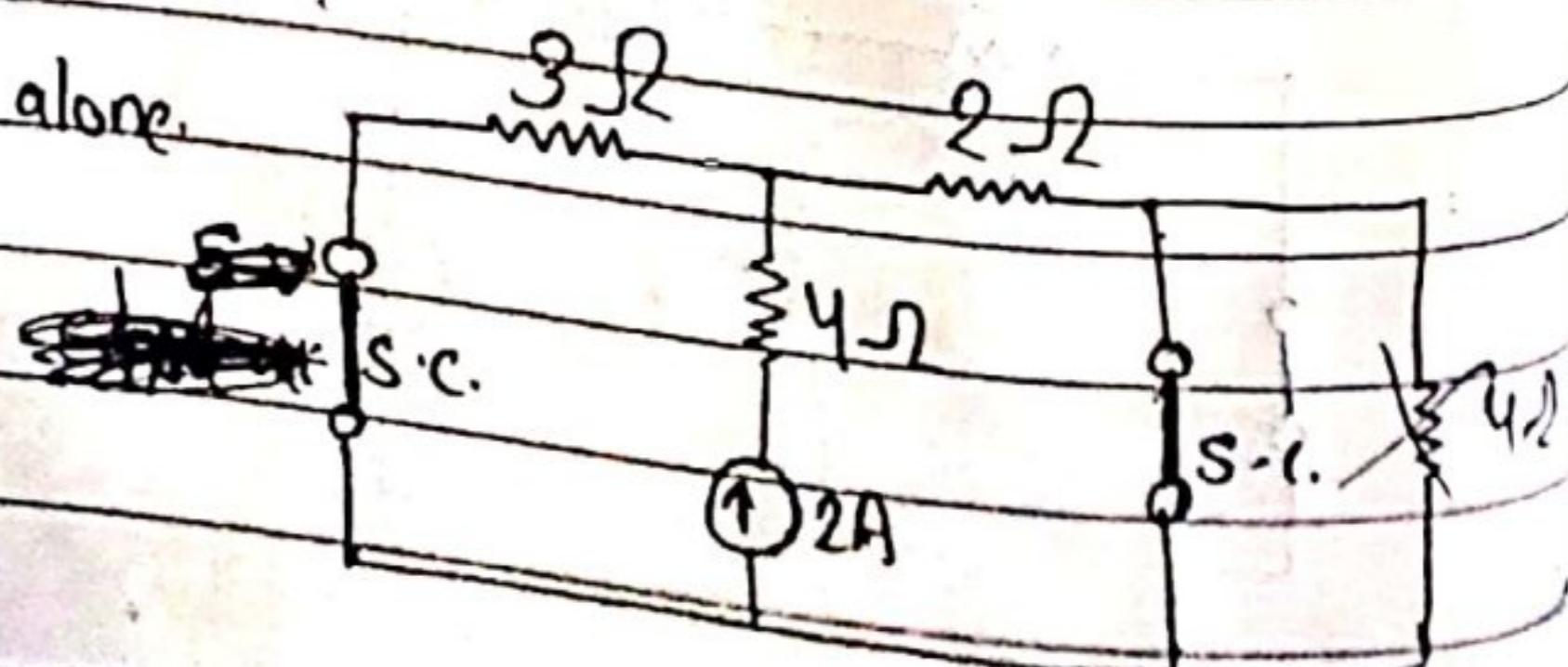

$$\Rightarrow \begin{array}{c} \text{Circuit Diagram: } \\ \text{A parallel combination of three resistors } 3\Omega, 2\Omega, \text{ and } 4\Omega. \\ \text{Current } I'' \text{ flows through the } 4\Omega \text{ resistor.} \end{array}$$

$$I'' = \frac{2 \times 3}{2+3}$$


$$= 1.2 \text{ amp}$$

$$\therefore I'' = 1.2 \text{ amp}$$

no current flows through 4Ω resistor.


Step - 3:

10V source acting along:

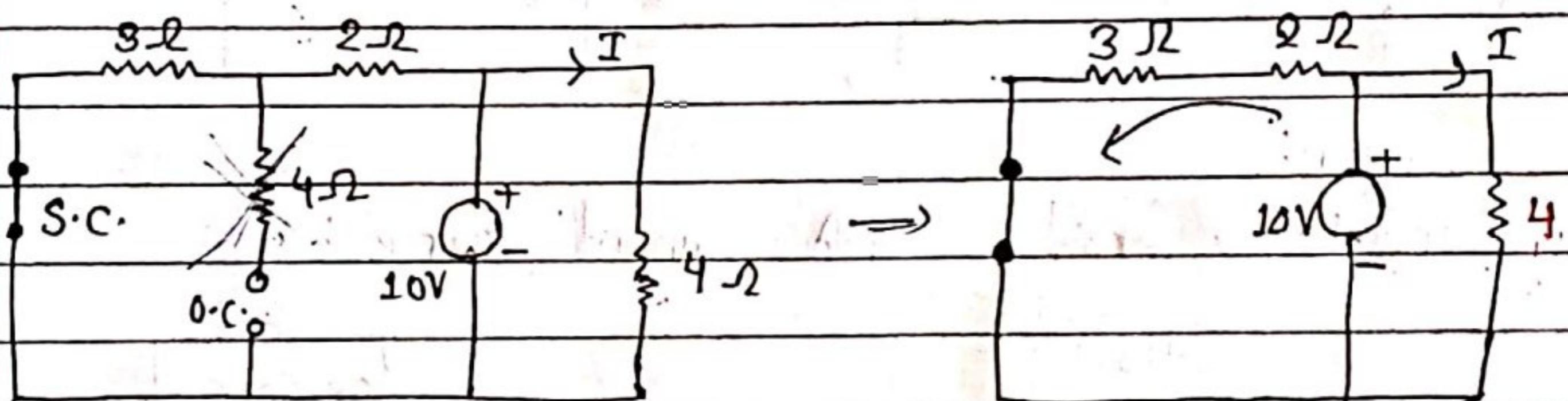

$$I'' = \frac{10}{3+2} = 2 \text{ amp}$$

$$\therefore I'' = 2 \text{ amp}$$

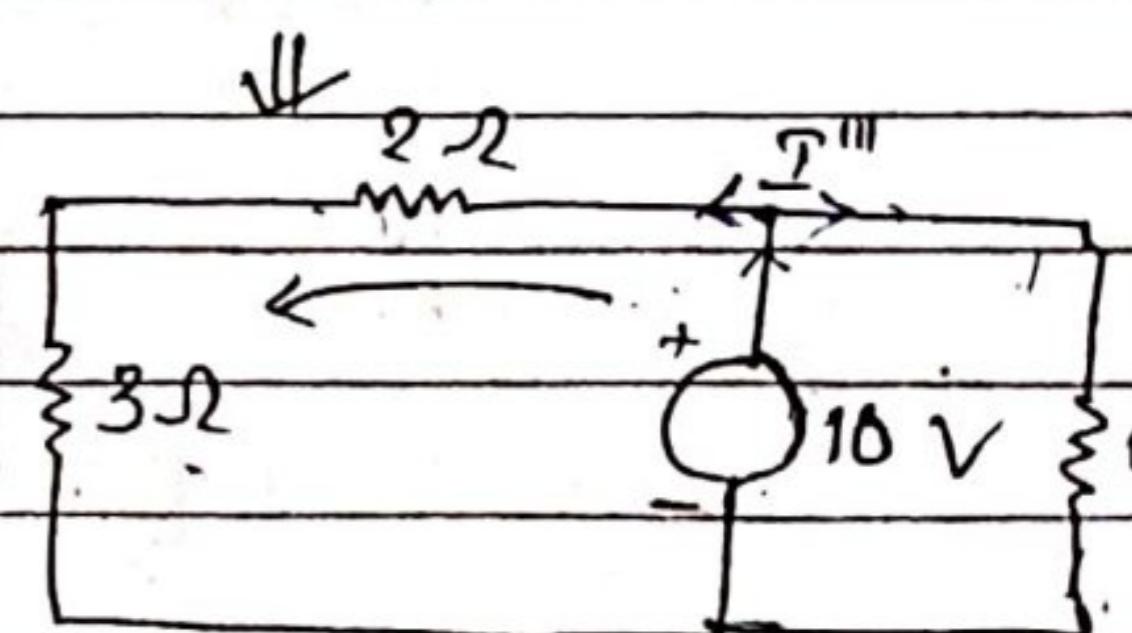

$$\therefore I = I' + I'' + I'''$$

$$= 1 + 1.2 + 2$$

$$= 4.2 \text{ amp}$$

$$I_T = \frac{V}{R}$$

$$= \frac{10}{2.22}$$

$$= 4.5$$


$$I''' = 4.5 \times \frac{5}{9}$$

$$= 2.5 \text{ amp}$$

$$I = I' + I'' + I'''$$


$$= 0 + 0 + 2.5 = 2.5 \text{ amp}$$

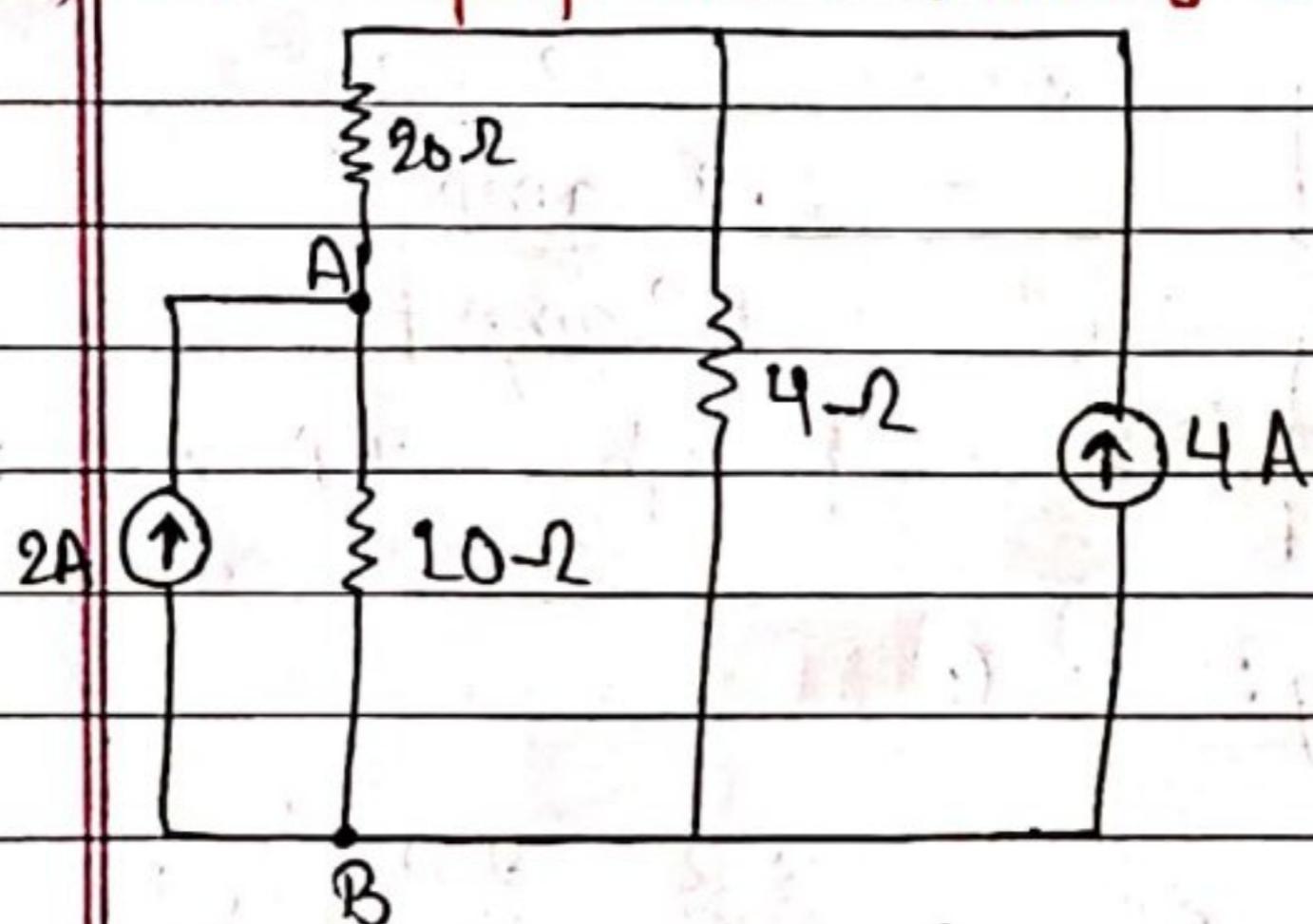Q.3) Use superposition theorem to find voltage across 10Ω resistor.



Solution:

Step - 1: Consider 2A current source :

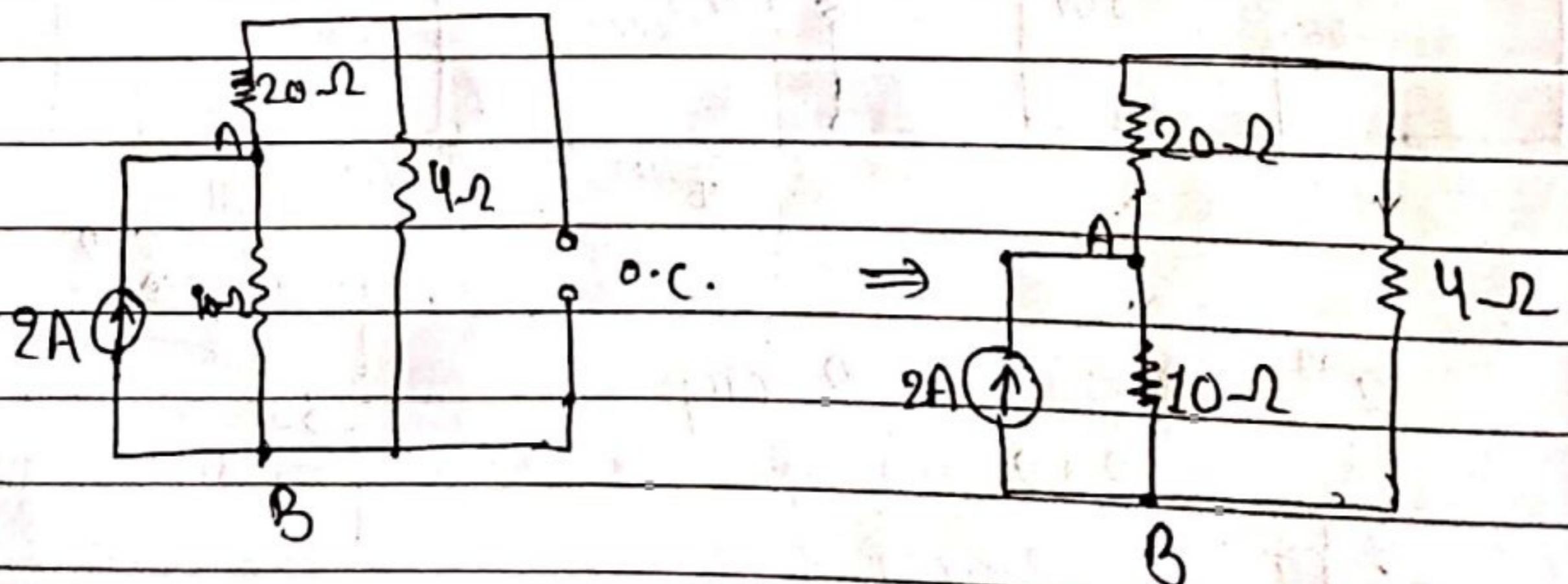


$$I_{AB} = 2 \times \frac{24}{24+10} = 1.41 \text{ amp}$$


$$\Rightarrow I_{AB}' = 1.41 \text{ amp}$$

$$V_{AB}' = 1.41 \times 10 = 14.1 \text{ V}$$

$$\Rightarrow V_{AB} = 14.1 \text{ V}$$

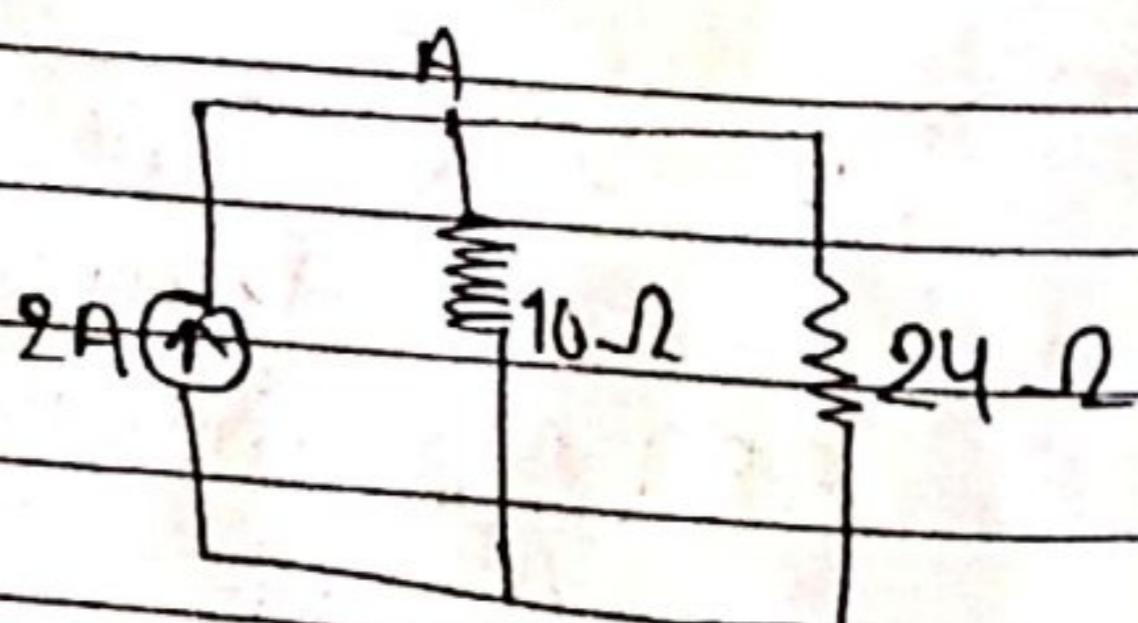


Step-2: Consider 4A current source.

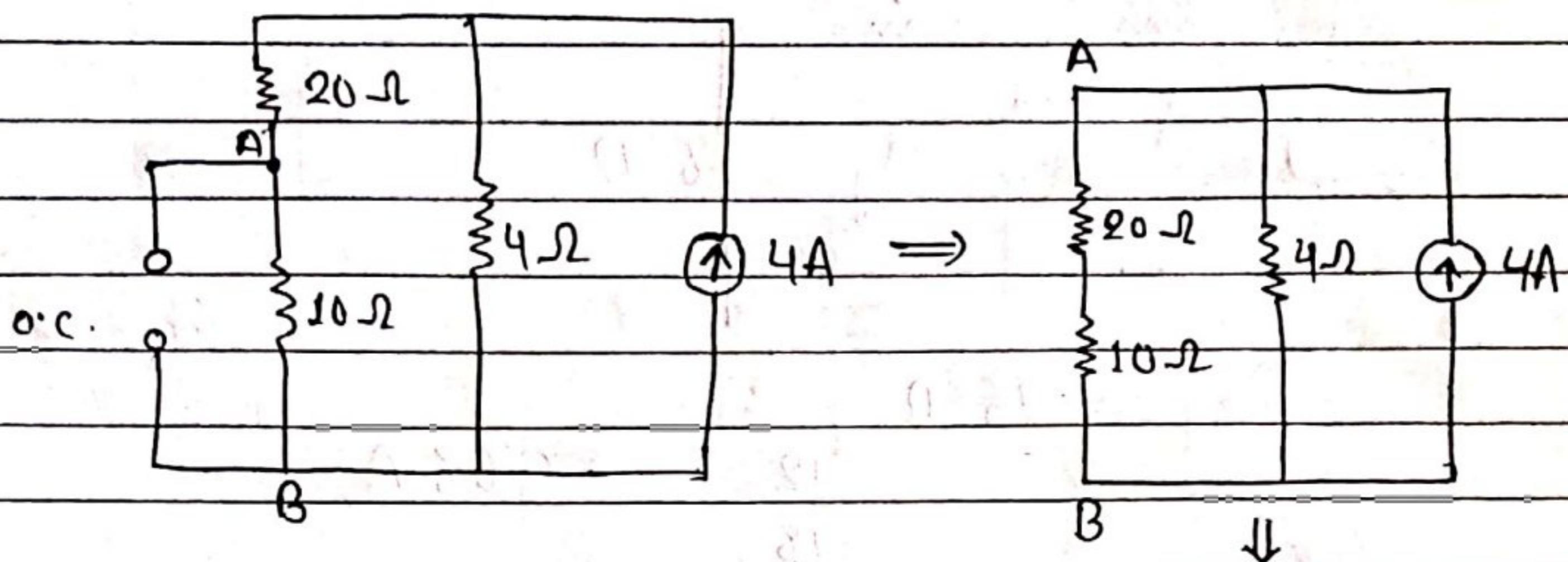

$$I_{AB}'' = 4 \times \frac{4}{30+4} = 0.470 \text{ amp}$$
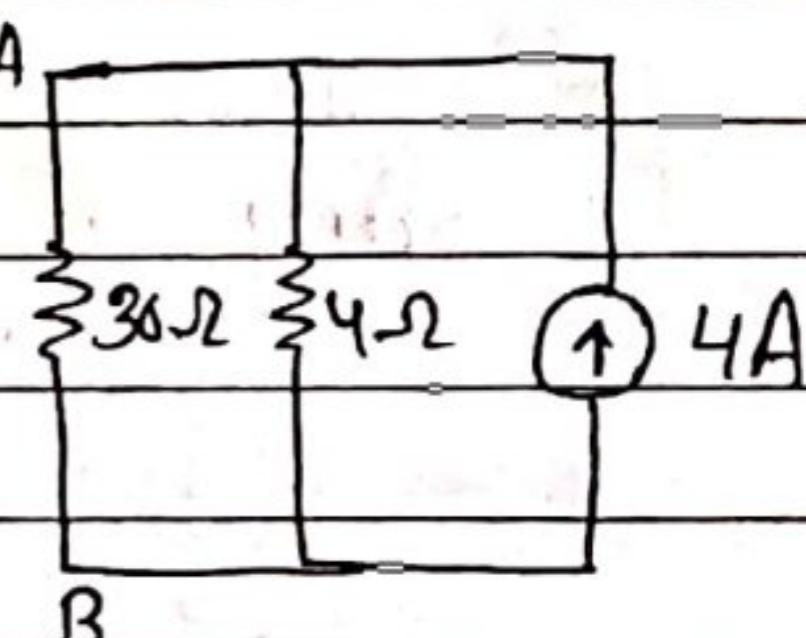
$$V_{AB}'' = 0.470 \times 10 = 4.70 \text{ V}$$




So,


$$V_{AB} = 14.1 \text{ V} + 4.7 \text{ V} = 18.8 \text{ V}$$

Q. 4) Determine the current flowing in 8Ω ~~the~~ resistor by superposition theorem:

Ans: 1.98 A

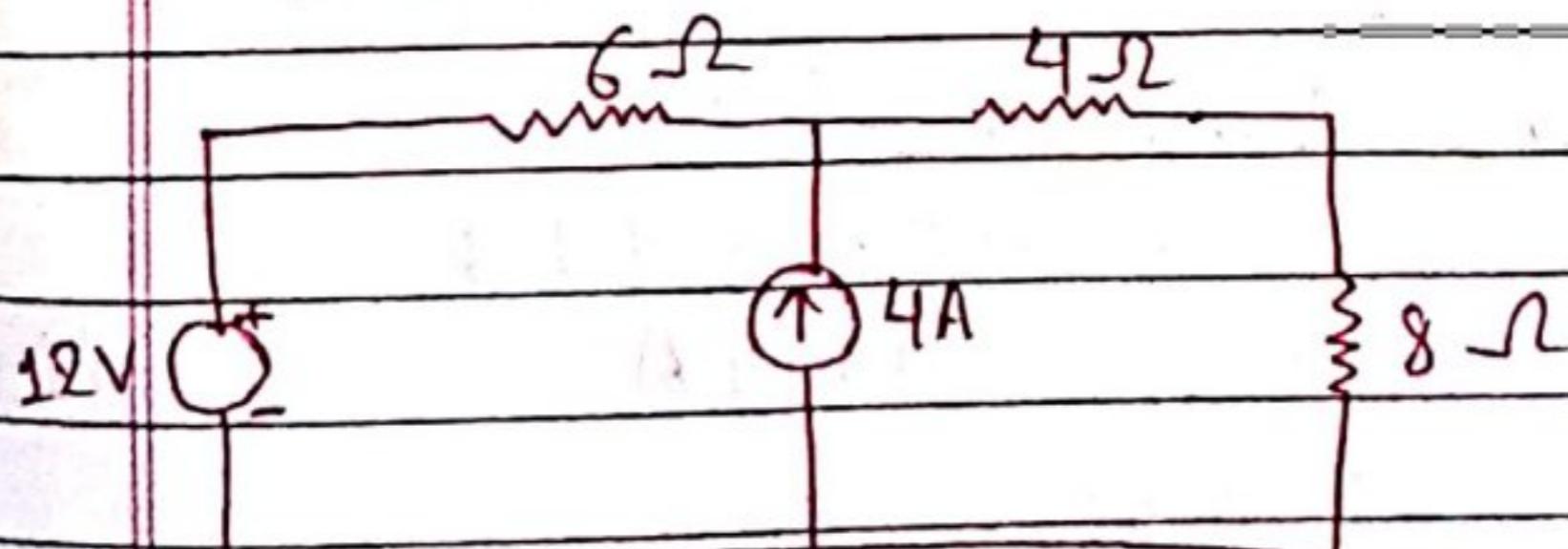

Here, taking $12V$,

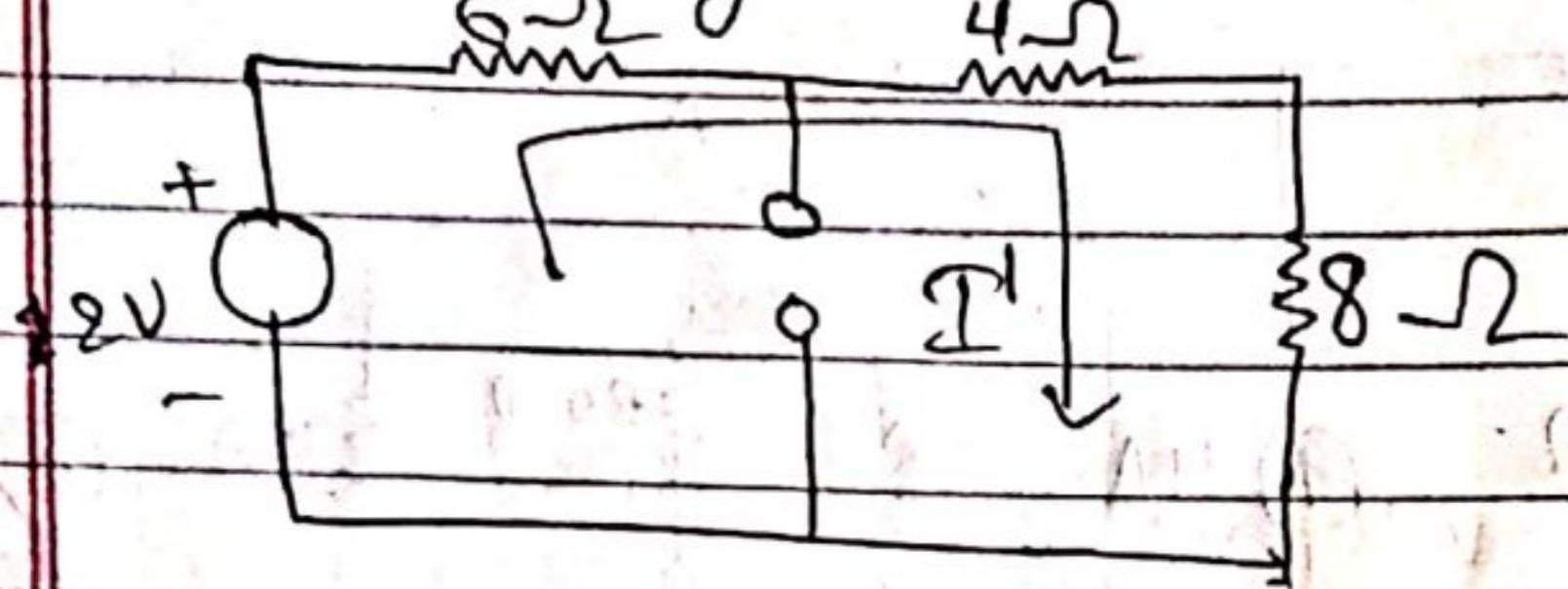


$$R_{eq} = 16\Omega$$

$$I' = \frac{V}{R} = \frac{12}{16} = 0.66A$$

Now,

Taking $4A$ current source,

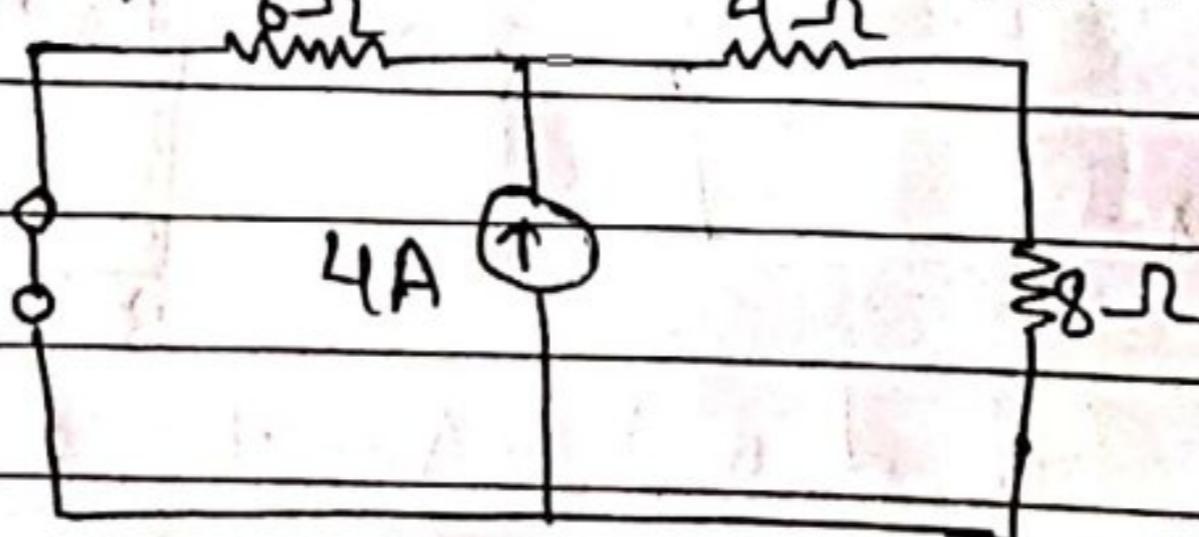


Using current division formula,

$$I'' = \frac{4 \times 6}{6 + 12} = 1.33A$$

$$\therefore \text{Current through } 8\Omega = I' + I''$$

$$= 0.66 + 1.33 \\ = 1.99A$$

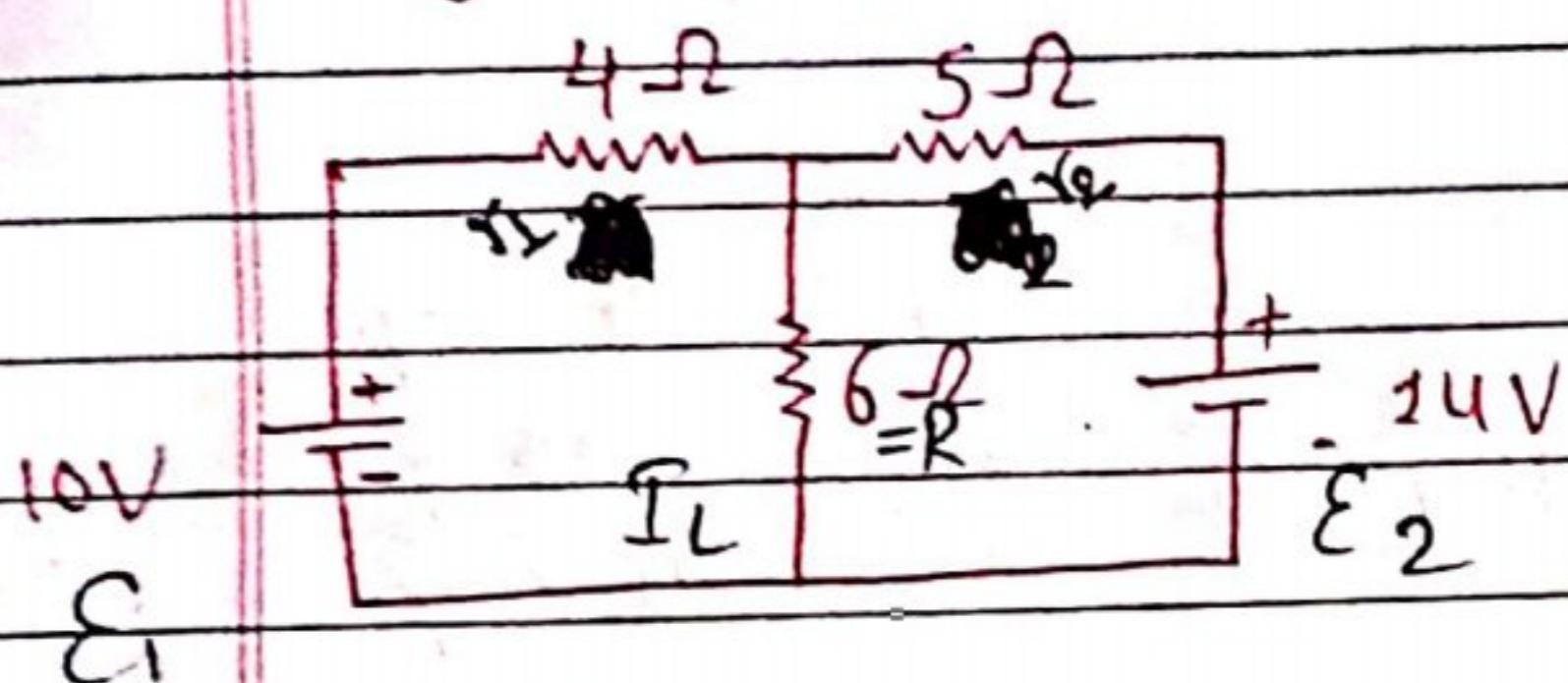Q.5) Using superposition theorem, find the current in 6Ω resistor




Ans: 1.42 Amps

$$I_L = \frac{E_1 R_1 + E_2 R_2}{R r_1 + r_1 r_2 + R r_2}$$

$$= \frac{10 \times 5 + 14 \times 4}{6 \times 4 + 4 \times 5 + 5 \times 6}$$

$$= 1.43 A$$

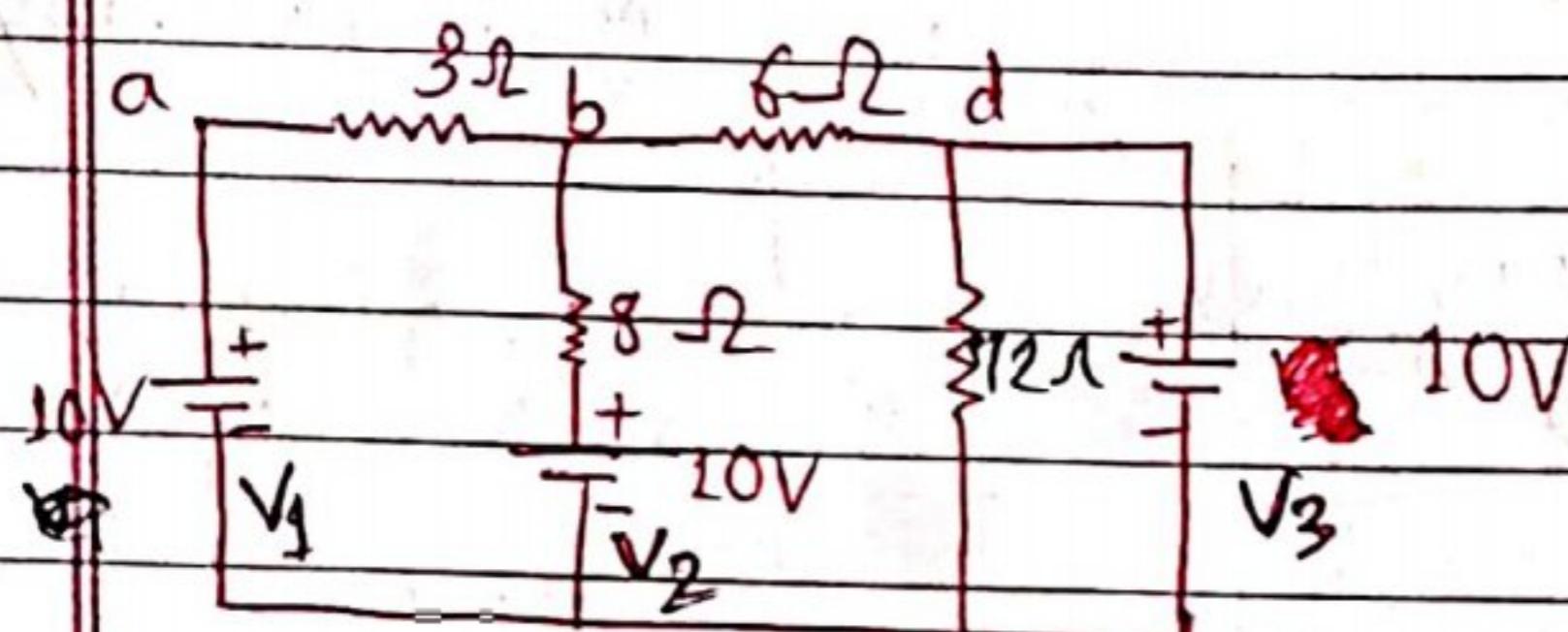Q.6) By superposition theorem, find the current in different branch of ckt.



Ans:


$$I_{ab} = 0 \text{ amp}$$

$$I_{bc} = 0 \text{ amp}$$

$$I_{bd} = 0 \text{ amp}$$

$$I_{dc} = 0.83 \text{ amp}$$

Taking 10V,

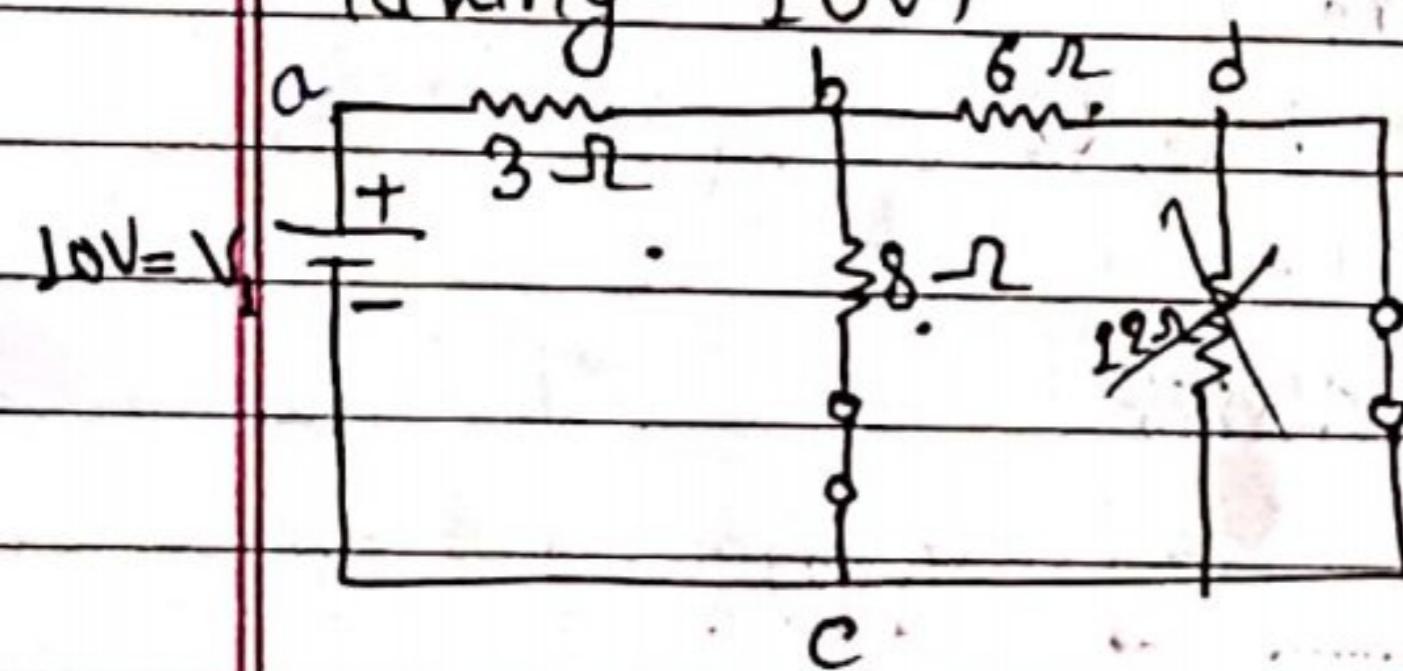

$$R_{eq} = 3 + \frac{8 \times 6}{8+6} = 6.42 \Omega$$

$$I_T = \frac{10}{6.42} = 1.55 \text{ A}$$


$$I'_{ab} = 1.55 \text{ A} \quad (\text{a to b})$$

$$I'_{bd} = \frac{1.55 \times 8}{8+6} = 0.88 \quad (\text{b to d})$$

$$I'_{bc} = \frac{1.55 \times 6}{8+6} = 0.66 \quad (\text{b to c})$$

$$I'_{cd} = 0.88 \quad (\text{d to c})$$

Taking 10V (V_2) voltage source:

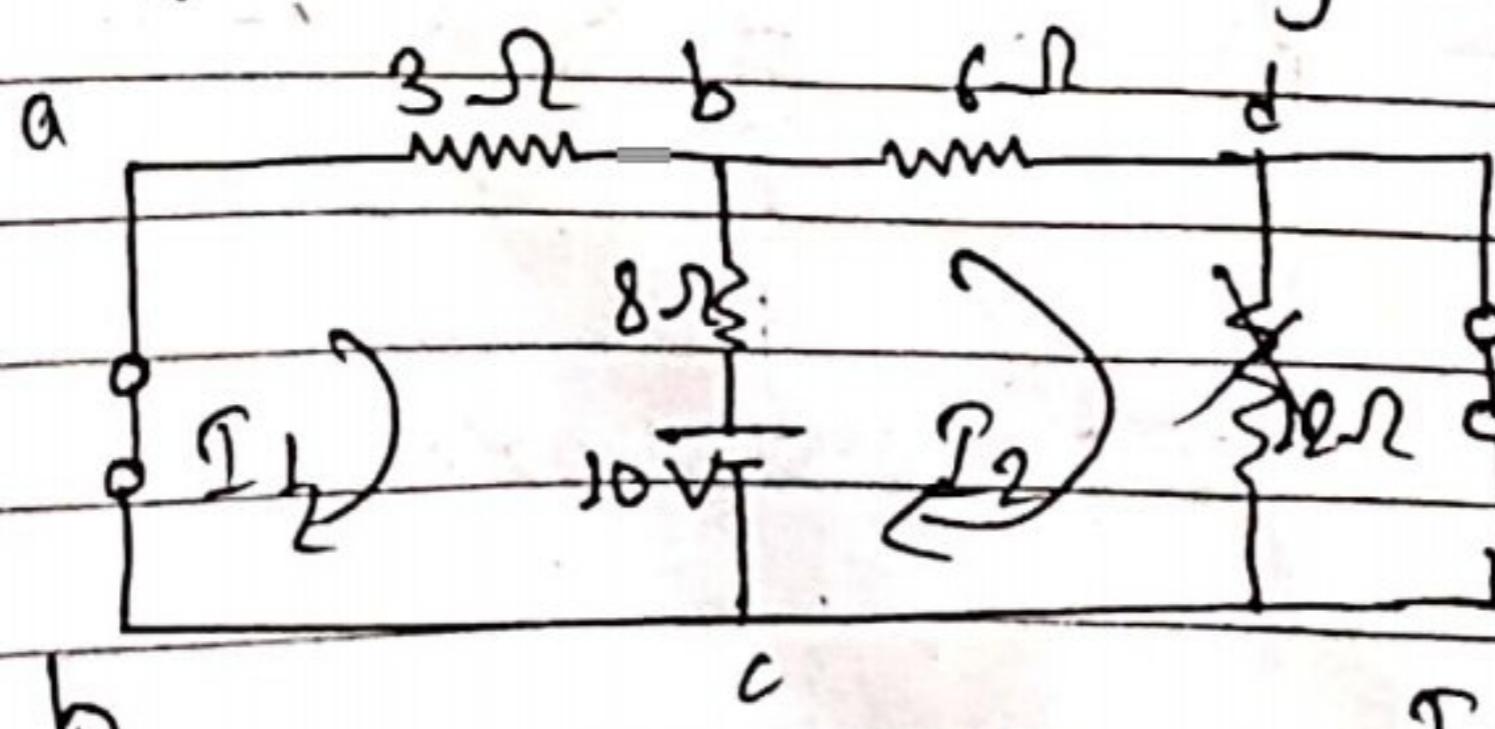

Loop I :

$$-3I_1 - 8(I_1 - I_2) - 10 = 0 \quad (1)$$

Loop II :

$$-6I_2 + 10 - 8(I_2 - I_1) = 0 \quad (2)$$


Solving (1) & (2),

$$I_1 = -0.6 \text{ A} \quad [\text{opposite dir.}]$$

$$I_2 = 0.33 \text{ A}$$

$$\begin{array}{l|l} I''_{ab} = 0.66 \text{ A (b to a)} & I''_{bd} = 0.33 \text{ (b to d)} \\ I''_{bc} = I_1 + I_2 \text{ (c to b)} \\ = 0.99 \text{ A} & I''_{dc} = 0.33 \text{ (d to c)} \end{array}$$

Taking 10 V (V_3) voltage source:

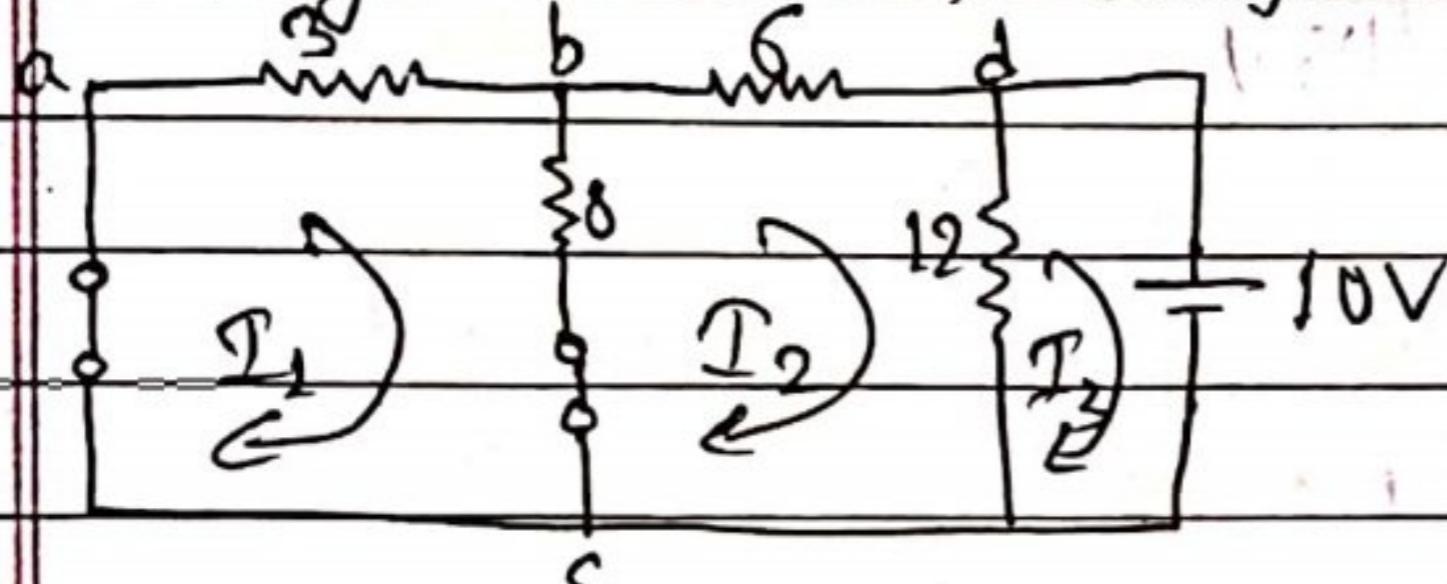

Loop I :

$$-3I_1 - 8(I_1 - I_2) = 0 \quad \text{--- (1)}$$

Loop II :

$$-6I_2 - 12(I_2 - I_3) - 8(I_2 - I_1) = 0 \quad \text{--- (2)}$$

Loop III :

$$-12(I_3 - I_2) - 10 = 0 \quad \text{--- (3)}$$

Solving,

$$I_1 = -0.88 \text{ A} \quad (\text{opposite dir?})$$

$$I_2 = -1.22 \text{ A} \quad (\text{" " "})$$

$$I_3 = -2.055 \text{ A} \quad (\text{" " "})$$

$$I'_{ab} = 0.88 \text{ A (b to a)}$$

$$I''_{bc} = (1.22 - 0.88) \text{ A} = 0.34 \text{ (b to c)}$$

$$I''_{bd} = 1.22 \text{ (d to b)}$$

$$I'''_{dc} = I'''_{cd} = 0.83 \text{ amp}$$

So,

$$I_{ab} = I'_{ab} + I''_{ab} + I'''_{ab}$$

$$= 1.55 - 0.66 - 0.88 = 0.01 \approx 0 \text{ A}$$


$$I_{bc} = I'_{bc} + I''_{bc} + I'''_{bc}$$

$$= 0.99 - 0.66 - 0.34 = 0.01 \approx 0 \text{ A}$$

$$I_{bd} = I'_{bd} + I''_{bd} + I'''_{bd}$$

$$= 1.22 - 0.88 - 0.33 = 0.01 \approx 0 \text{ A}$$

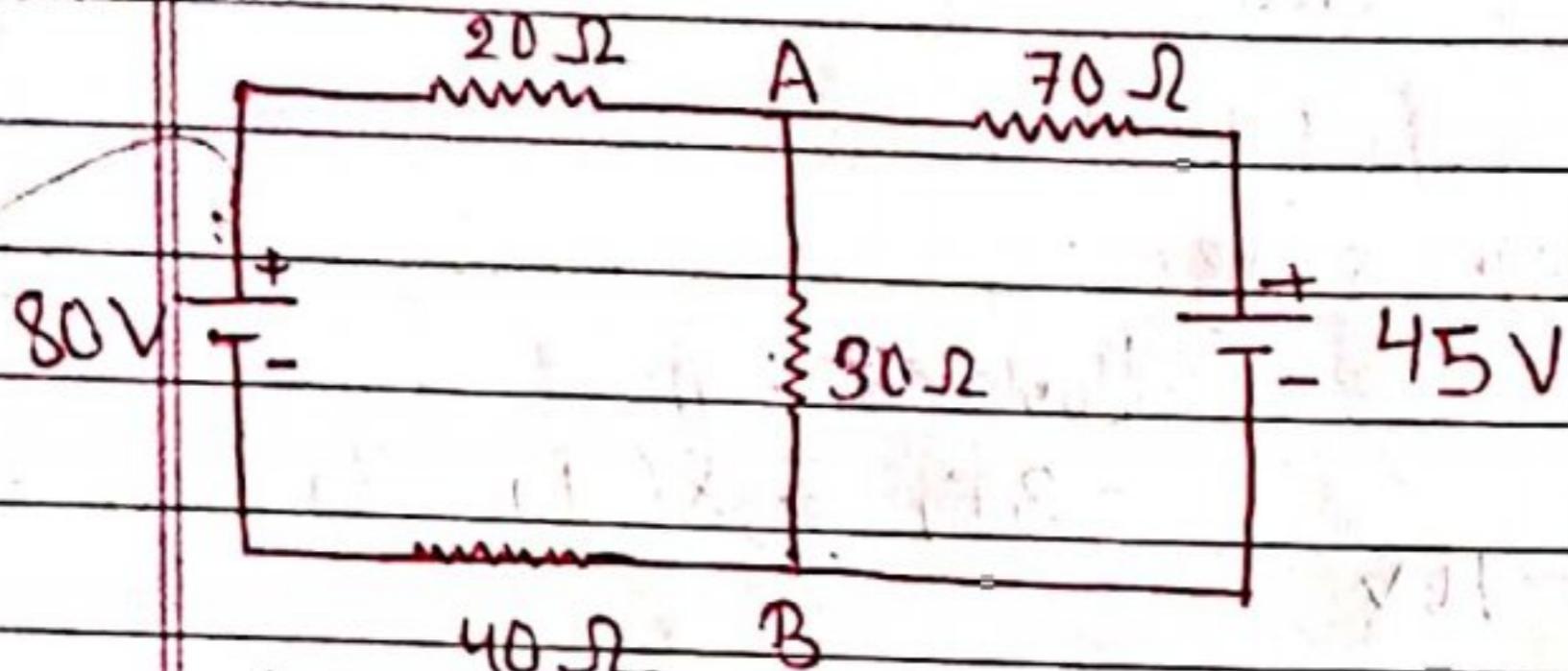
Q.7) Use the superposition theorem to find the current through the 30Ω resistor in a given circuit.



Ans:

$$I_{AB} = 1.024 \text{ amp}$$

Here,

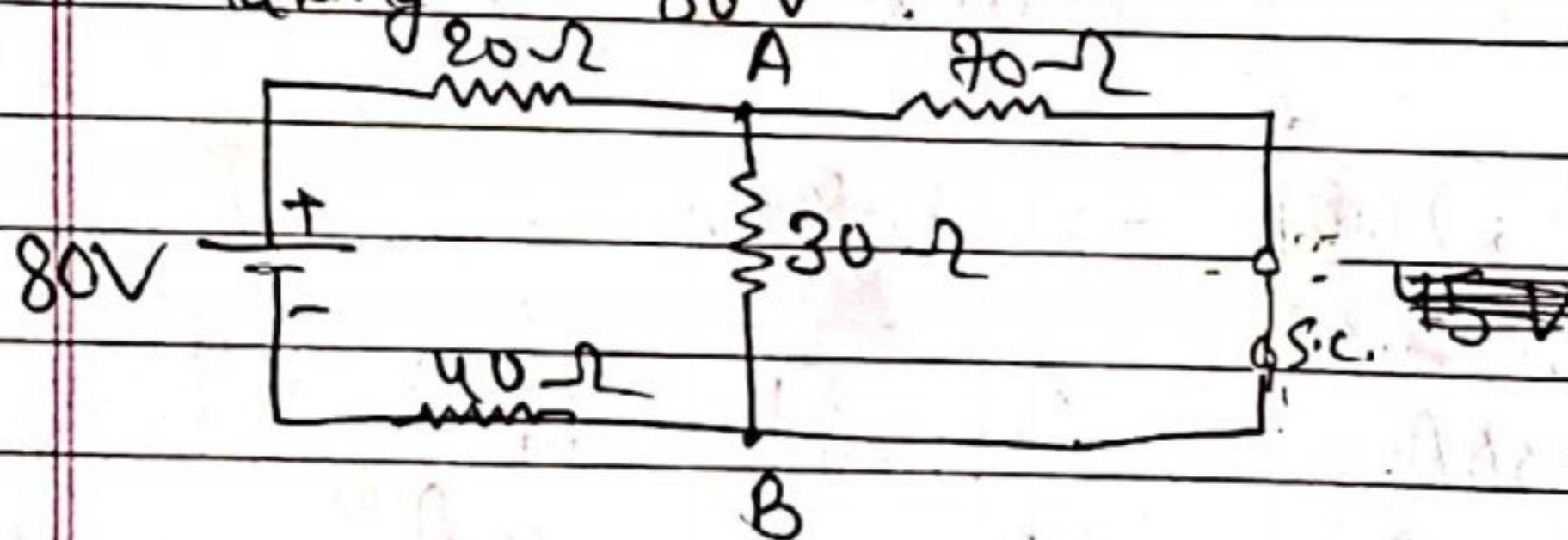
Taking $80V$:

$$R_{eq} = 20 + 40 + \frac{30 \times 70}{30 + 70} = 81 \Omega$$

$$I_T = \frac{80}{81} = 0.987 \text{ A}$$

$$I'_{AB} = I_T \times \frac{70}{30+70} = 0.686 \text{ (a to b)}$$

Now,

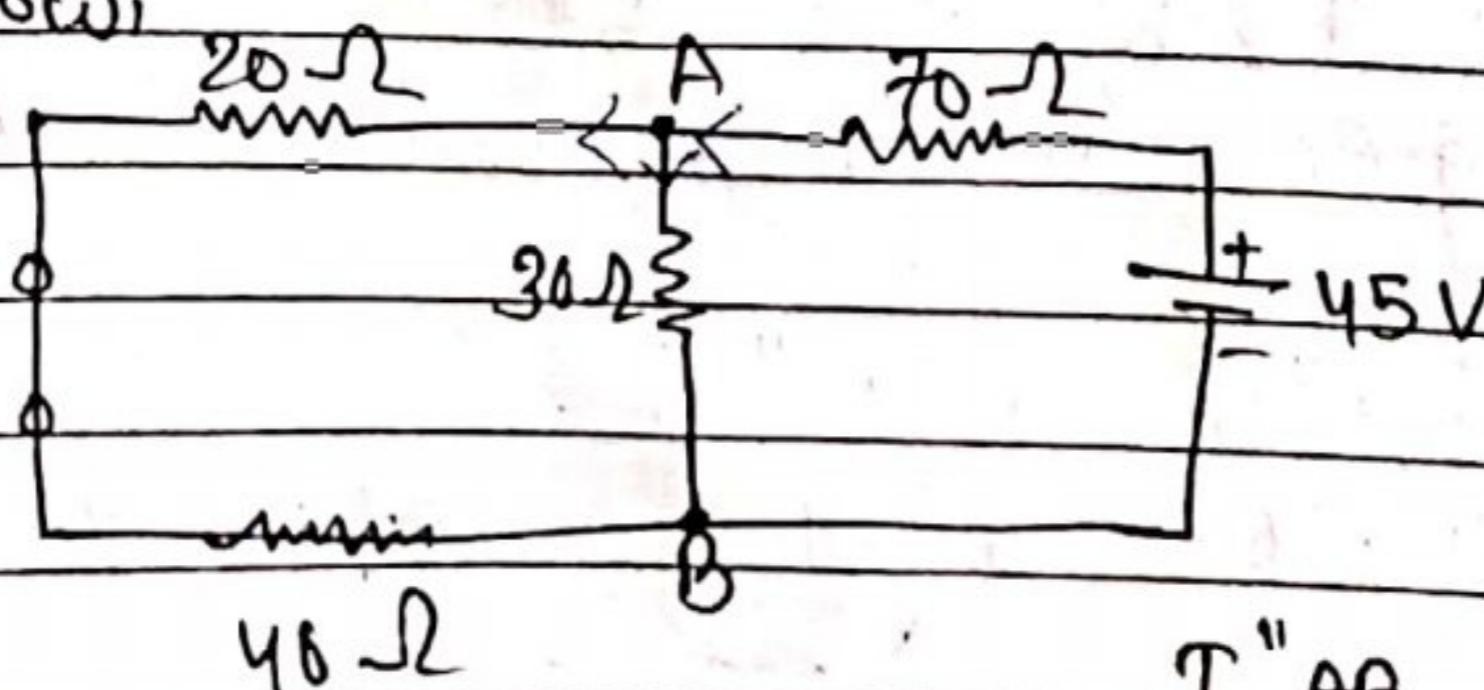


$$R_{eq} = 70 + \frac{30 \times 60}{30 + 60} = 90 \Omega$$

$$I_T = \frac{45}{90} = 0.5 \text{ A}$$


$$I''_{AB} = \frac{0.5 \times 60}{60 + 30} = 0.33 \text{ A (a to b)}$$

$$\therefore I_{ab} = I'_{ab} + I''_{ab} = 0.686 + 0.333 = 1.019 \text{ Amp}$$

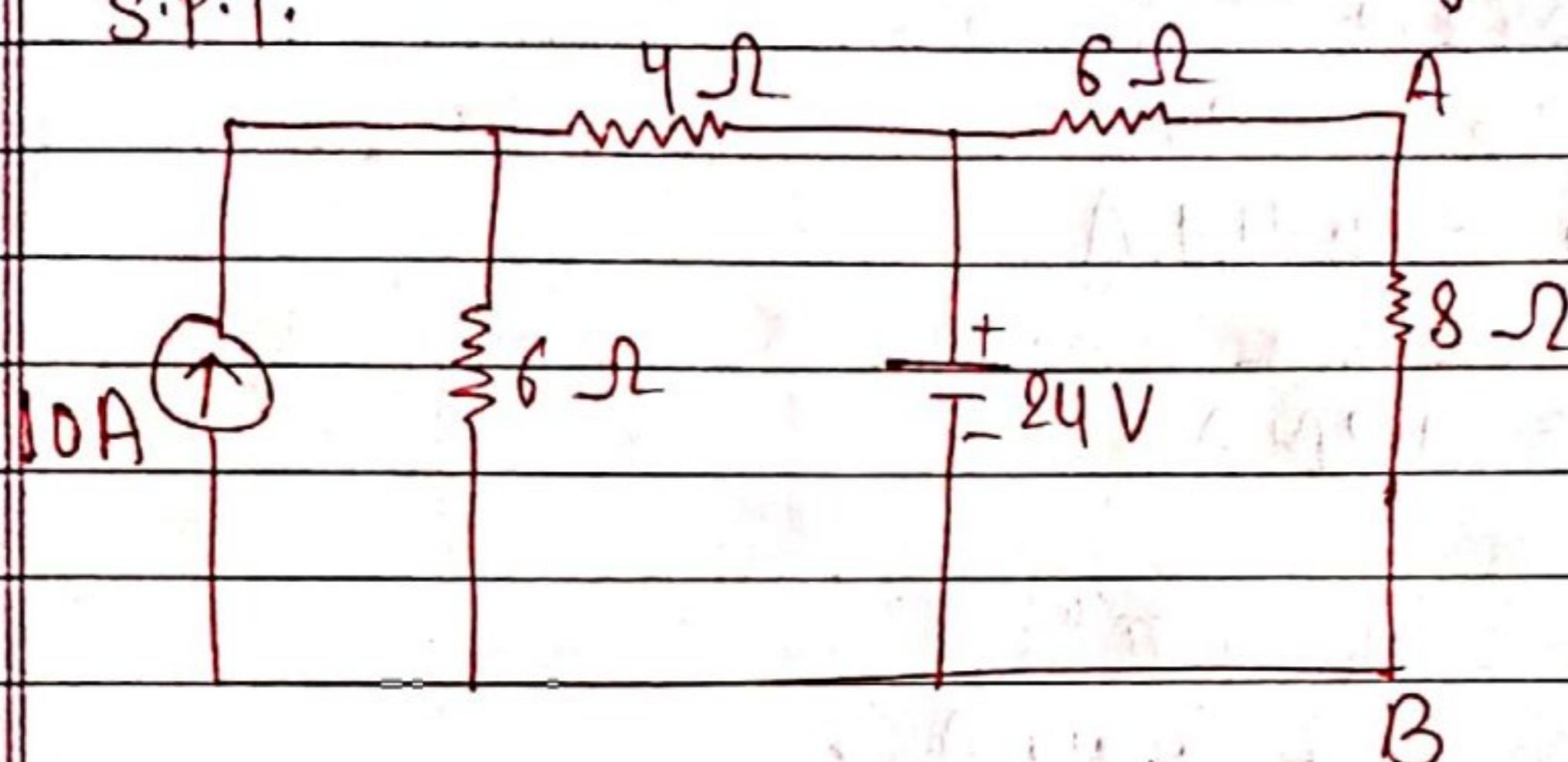Q. 8) Calculate the power consumed by 8Ω resistor using S.P.T.




Taking 10 A:

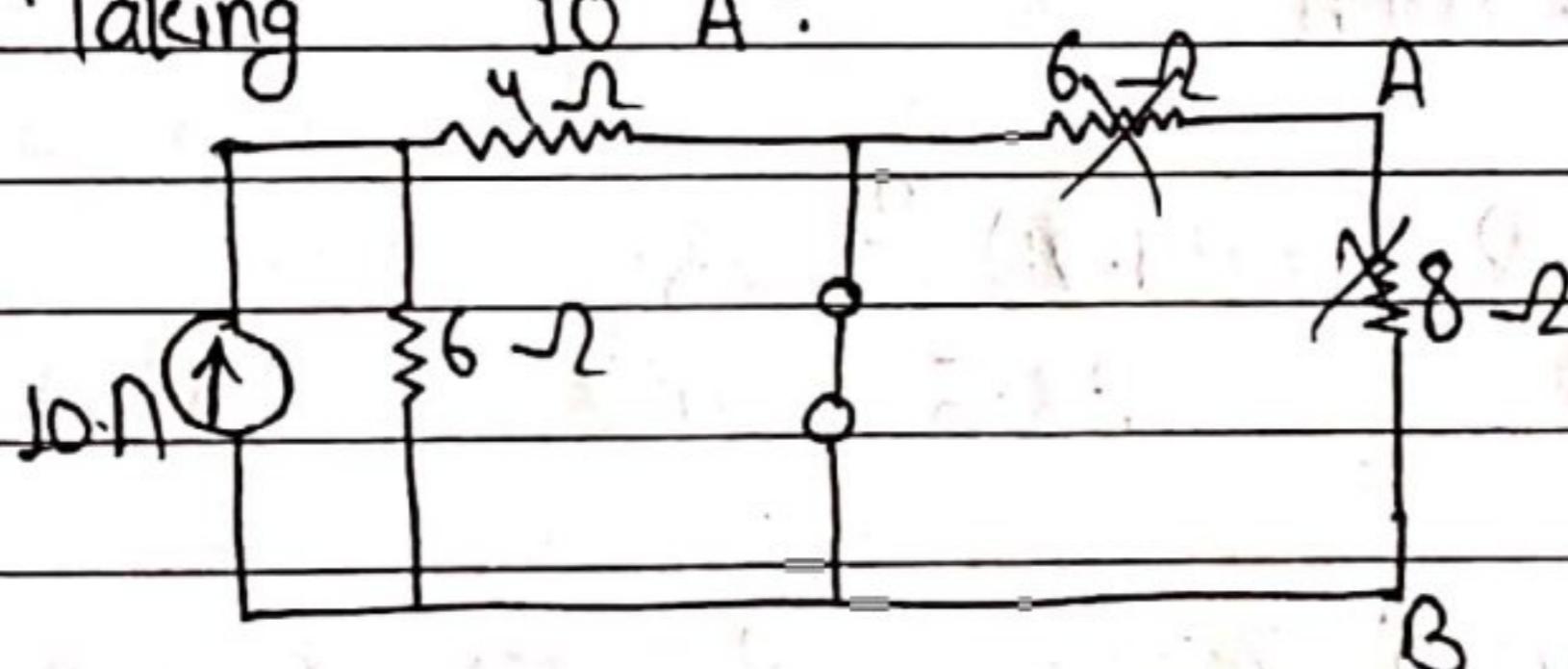

$$I'_{AB} = 0$$

Taking 24V:

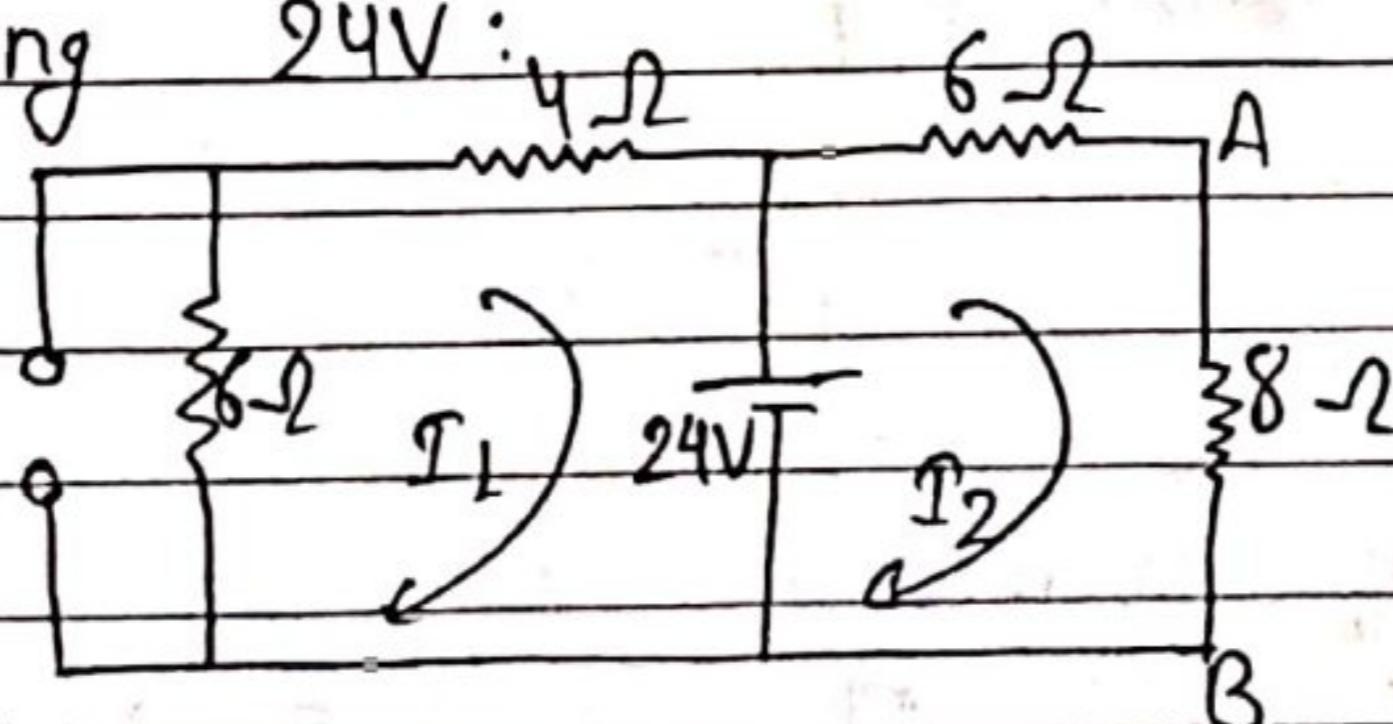

$$\text{Loop 1: } -6I_1 - 4I_1 - 24 = 0$$

$$\Rightarrow -10I_1 = 24$$

$$\Rightarrow I_L = -2.4 \text{ (opp. dir.)}$$

Also, loop-2:

$$-6I_2 - 8I_2 + 24 = 0$$

$$\Rightarrow -14I_2 = -24$$

$$\Rightarrow I_2 = 1.714 \text{ A}$$

$$\therefore I''_{ab} = 1.714 \text{ A}$$

$$\therefore I_{ab} = I'_{ab} + I''_{ab}$$


$$= 0 + 1.714 \text{ A}$$

$$= 1.714 \text{ A}$$


$$P_{ab} = (I_{ab})^2 \cdot R = (1.71)^2 \times 8$$

$$= 23.5 \text{ watt}$$

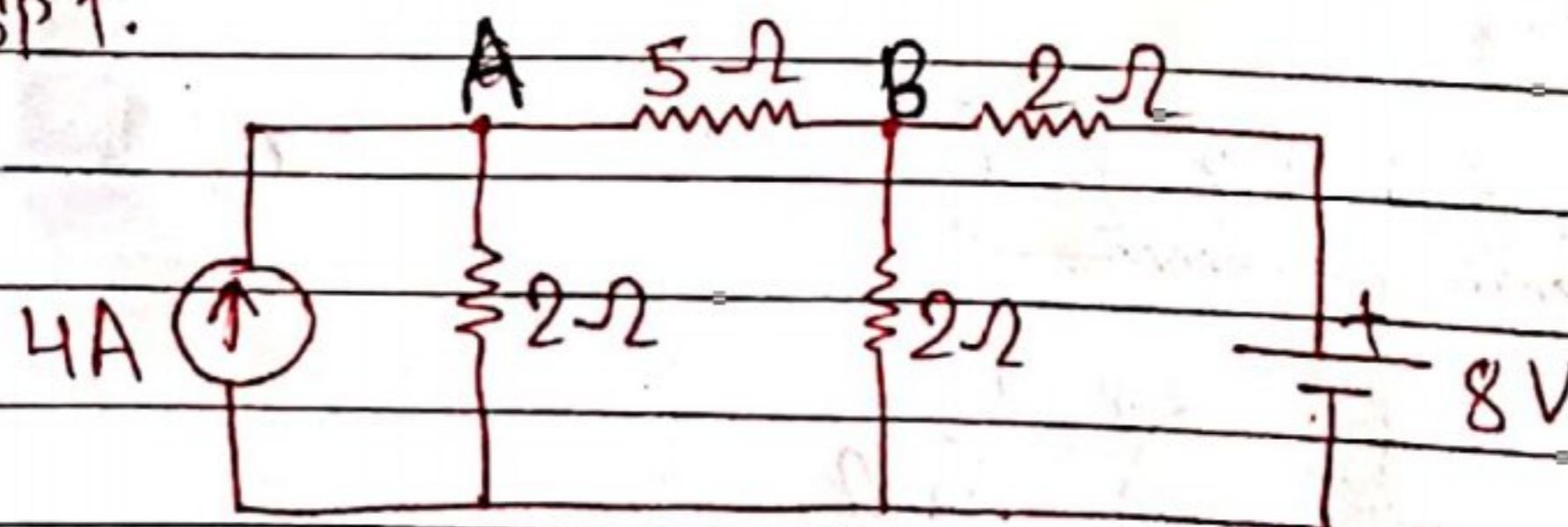Q. 9) find out the current through 5Ω resistor connected across the terminal AB in the given network. Using SPT.



Taking 4A current source:

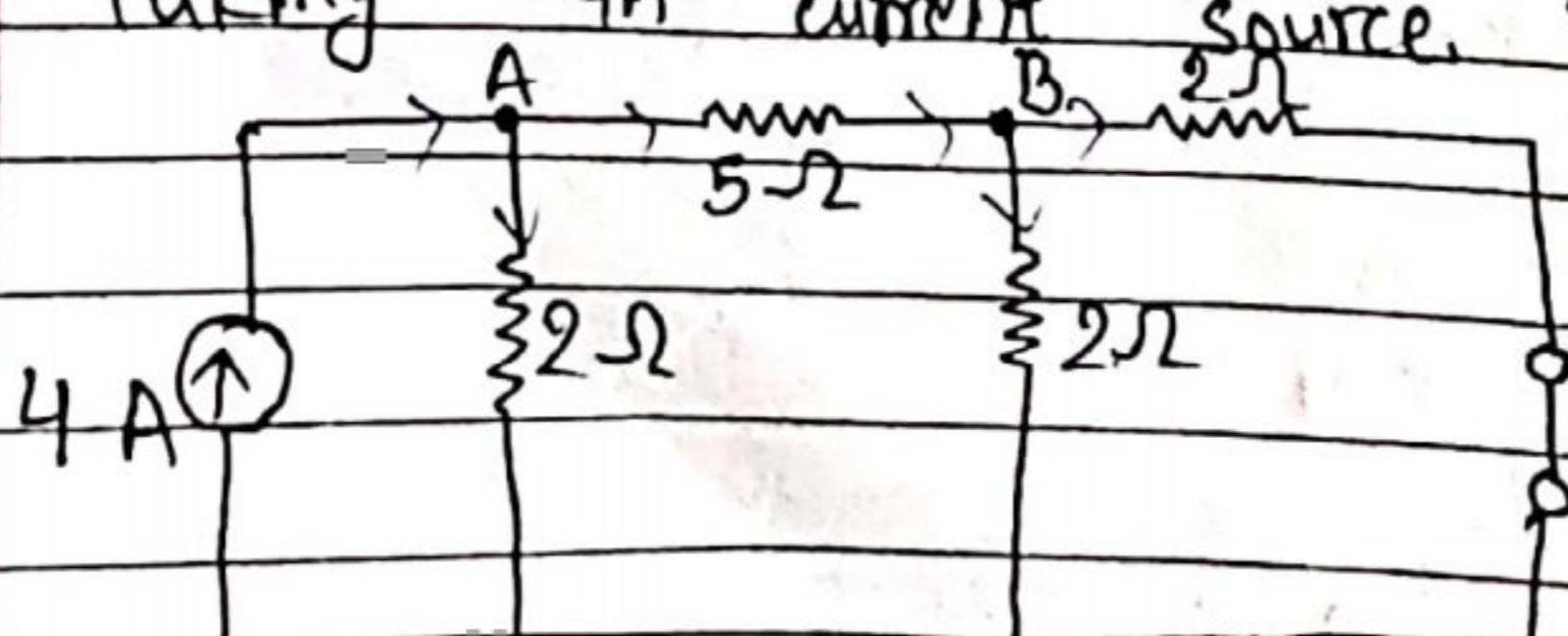


$$R_1 = \frac{2 \times 2}{2+2} = 1\Omega$$

$$R_2 = 5\Omega + 1\Omega = 6\Omega$$

$$I_T = 4 \text{ A}$$

$$I'_{AB} = \frac{I_T \times 2}{2+6} = \frac{4 \times 2}{2+6} = 1 \text{ Amp (A)}$$

Taking 8V (Voltage source)

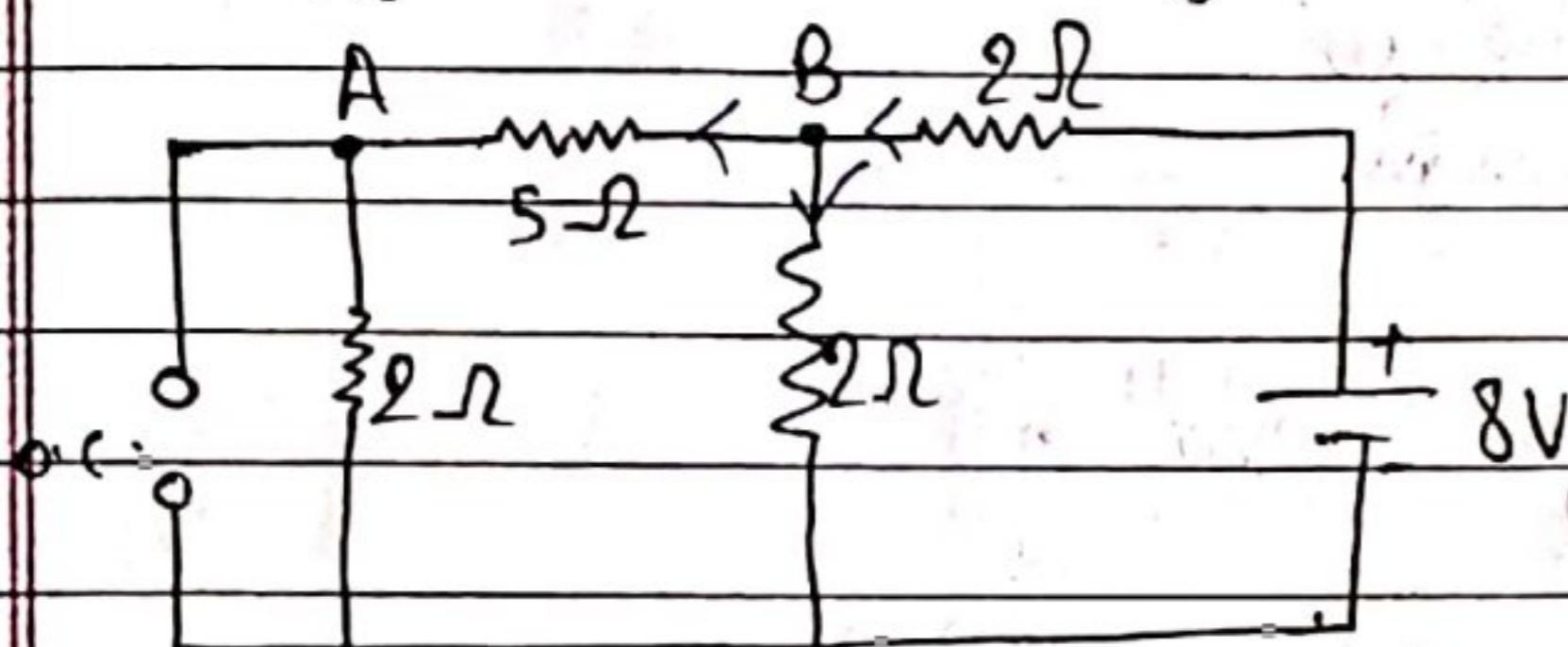

$$R_1 = 5\Omega + 2\Omega = 7\Omega$$

$$R_2 = \frac{7 \times 2}{7+2} = 1.5\Omega$$

$$R_{eq} = (2 + 1.5)\Omega = 3.5\Omega$$


$$I_T = \frac{8}{3.5} = 2.25A$$

$$I''_{AB} = \frac{2.25 \times 2}{7+2} = 0.5A \quad (\text{B to A})$$


$$\begin{aligned} \therefore I_{AB} &= I'_{AB} + I''_{AB} \\ &= 1A - 0.5A \\ &= 0.5A \end{aligned}$$

Q. 10) By using SPT, determine the current through 2Ω resistor in fig. given below:

2021
PV

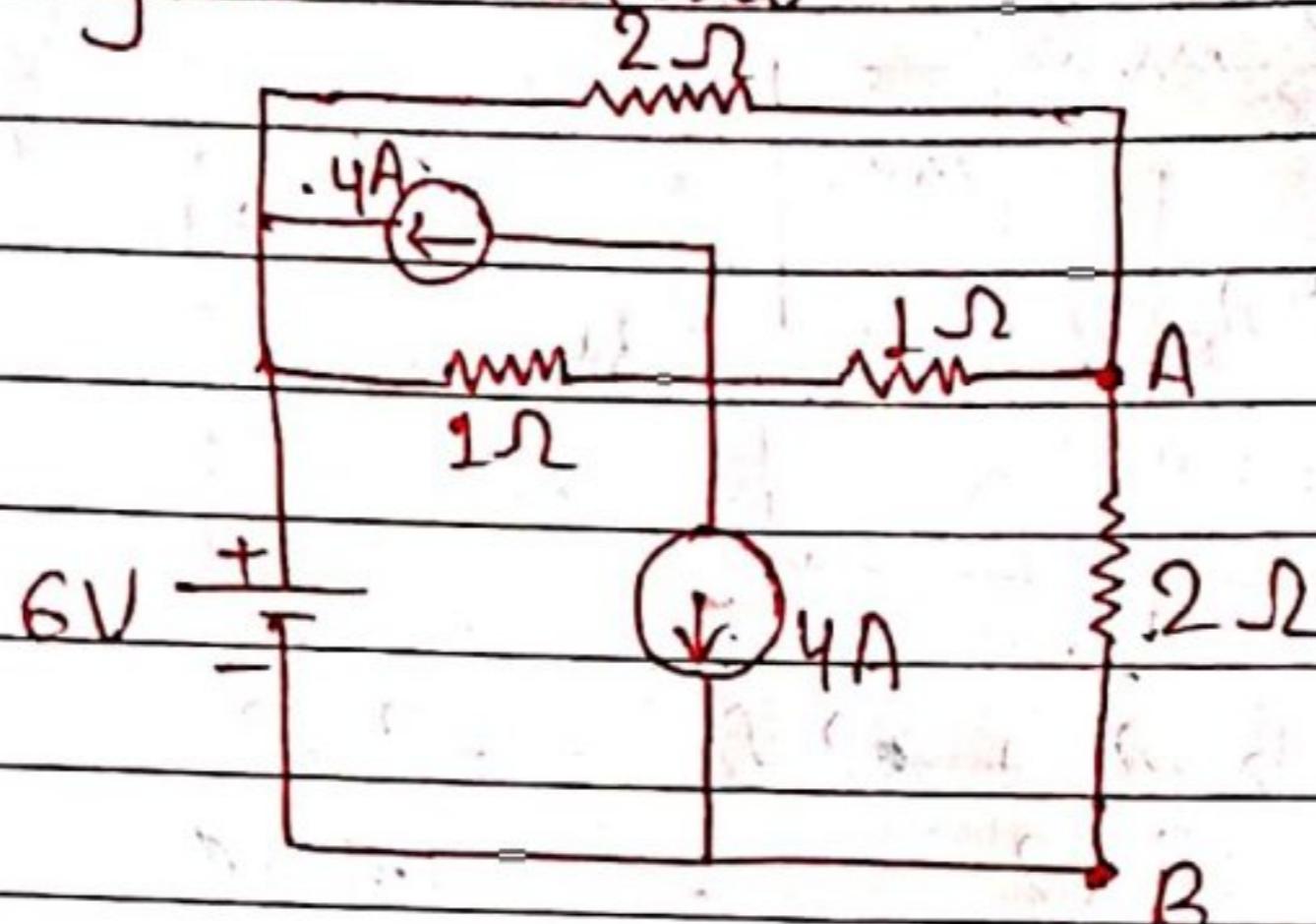

Taking $\frac{6V}{2\Omega}$:

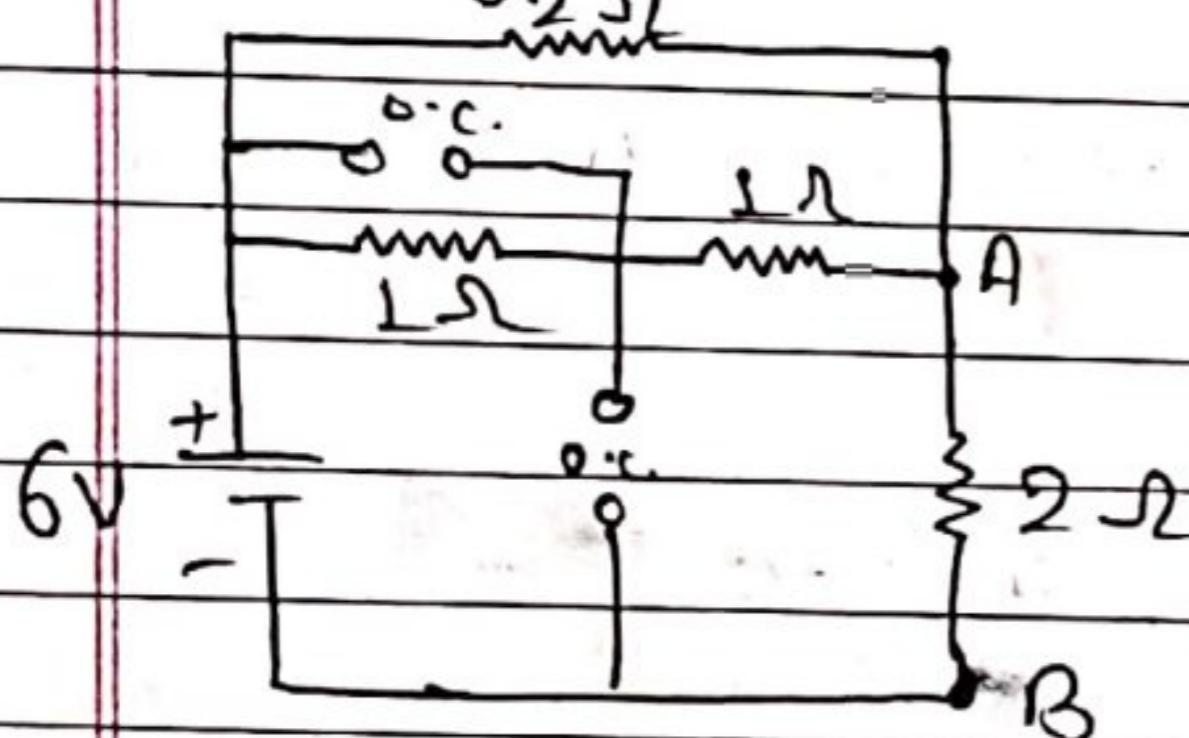

$$R_1 = 1 + 1 = 2\Omega$$

$$R_2 = 2 \times 2 = 1\Omega$$


$$R_{eq} = 1 + 2 = 3\Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{6}{3} = 2A$$

$$I'_{AB} = 2A \quad [A \text{ to } B]$$

Now,

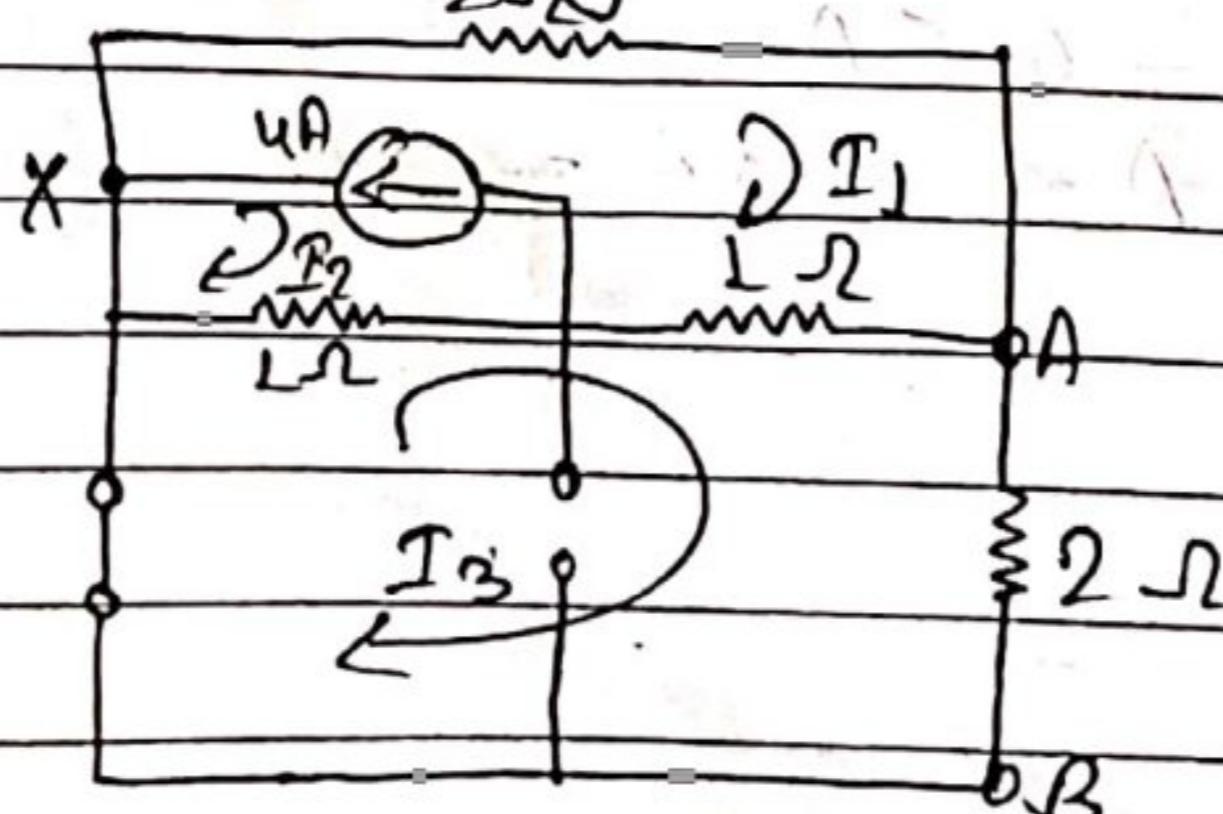Again taking $\frac{4A}{2\Omega}$ (\leftarrow)



At node X:

$$I_1 = I_2 + 4$$

$$\Rightarrow I_1 - I_2 = 4 \quad (1)$$

Now, taking combine loop $\textcircled{1} + \textcircled{2}$

$$-2I_1 - 1(I_1 - I_3) - 1(I_2 - I_2) = 0$$

$$\Rightarrow -2I_1 - I_1 + I_3 - I_2 + I_3 = 0$$

$$\Rightarrow -3I_1 - I_2 + 2I_3 = 0 \quad (2)$$

Again taking loop III,

$$-1(I_3 - I_2) - 1(I_3 - I_1) - 2I_3 = 0$$

$$\Rightarrow I_1 + I_2 - 4I_3 = 0 \quad \text{--- (III)}$$

Equating (I), (II) & (III),


$$I_1 = 0.66 \text{ A}, \quad I_2 = -3.33 \text{ A} \quad (\text{opp. dir}^n)$$

$$I_3 = -0.66 \quad (\text{opp. dir}^n)$$

$$\therefore I''_{AB} = 0.66 \quad (\text{B to A})$$

Now,

Taking 4A (↓)

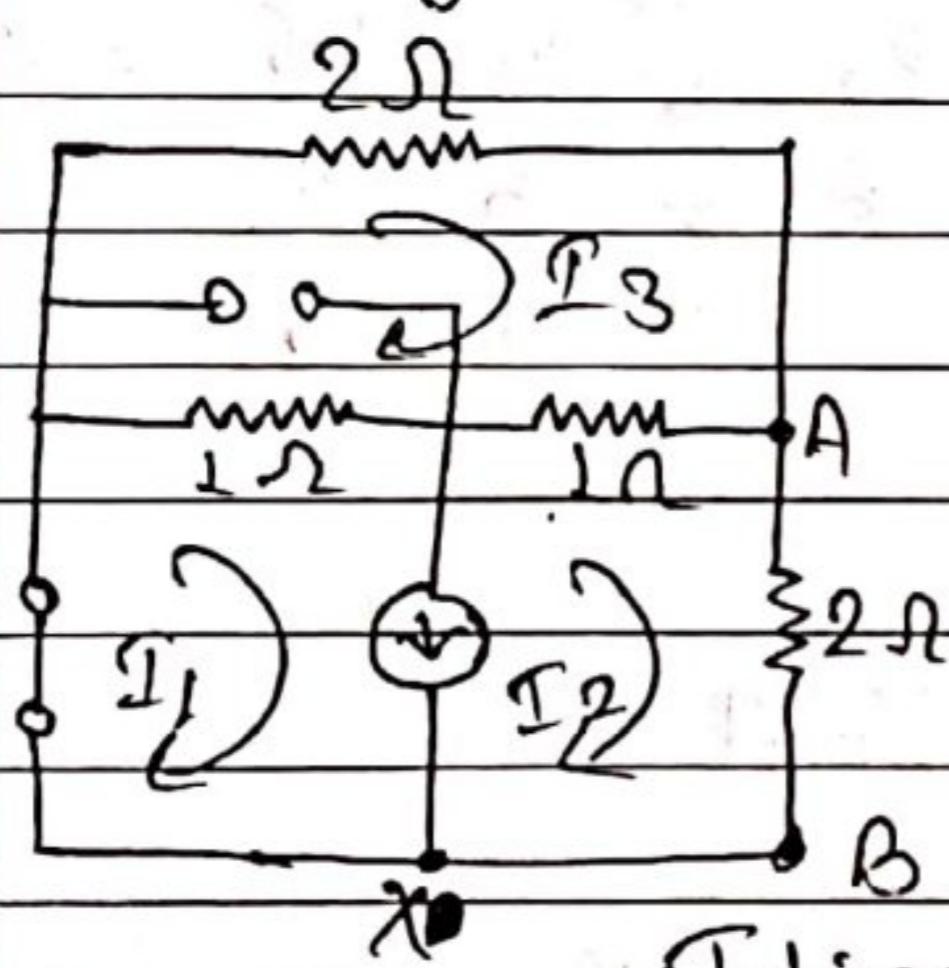

At node X:

$$I_1 = I_2 + 4$$

$$\Rightarrow I_1 - I_2 = 4 \quad \text{--- (I)}$$

Taking combine loop (I) & (II),

$$-1(I_1 - I_3) - 1(I_2 - I_3) - 2I_2 = 0$$

$$\Rightarrow -I_1 - 3I_2 + 2I_3 = 0 \quad \text{--- (II)}$$

Taking loop (III),

$$-2I_3 - 1(I_3 - I_2) - 1(I_3 - I_1) = 0$$

$$\Rightarrow I_1 + I_2 - 4I_3 = 0 \quad \text{--- (III)}$$


Equating (I), (II) & (III),

$$I_1 = 3.33, \quad I_2 = -0.66 \text{ A} \quad (\text{opp. dir}^n), \quad I_3 = 0.6 \quad (\text{opp. dir}^n)$$


$$\therefore I''_{AB} = 0.66 \quad (\text{B to A})$$

$$\begin{aligned} \therefore I_{AB} &= I'_{AB} + I''_{AB} + I'''_{AB} \\ &= 2 - 0.66 - 0.66 \\ &= 0.68 \text{ A} \end{aligned}$$

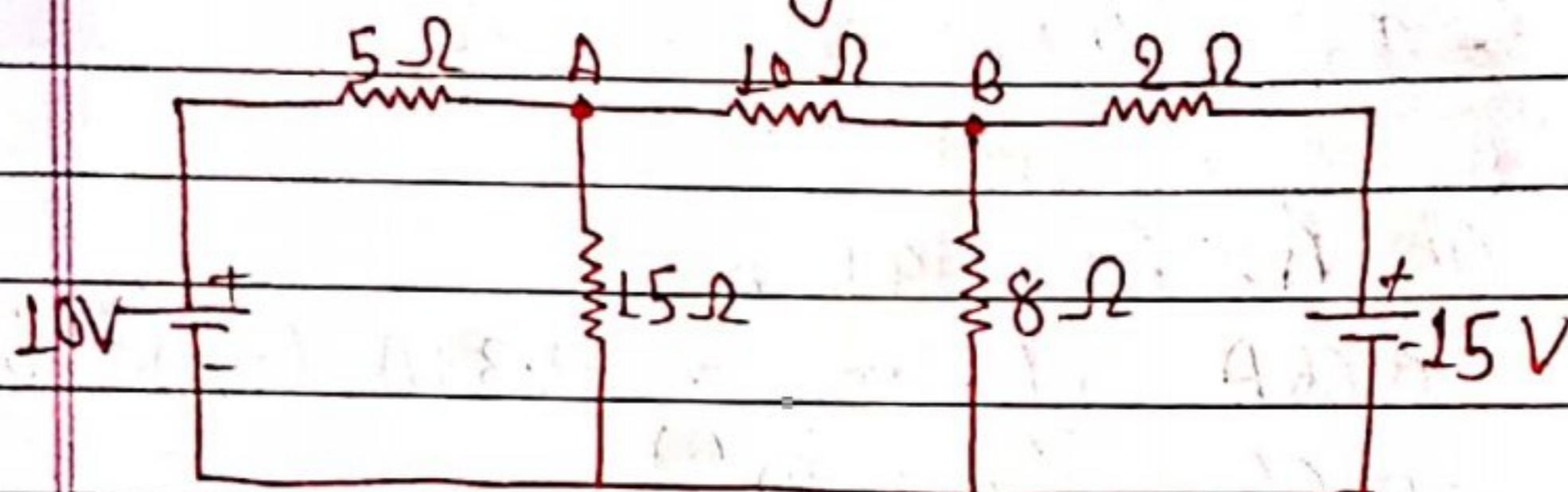Q. 11) Using SPT, to calculate the current through $10\ \Omega$ resistor
 QV fall
 20/3 fall of the following ckt shown below:



Taking 10 V,

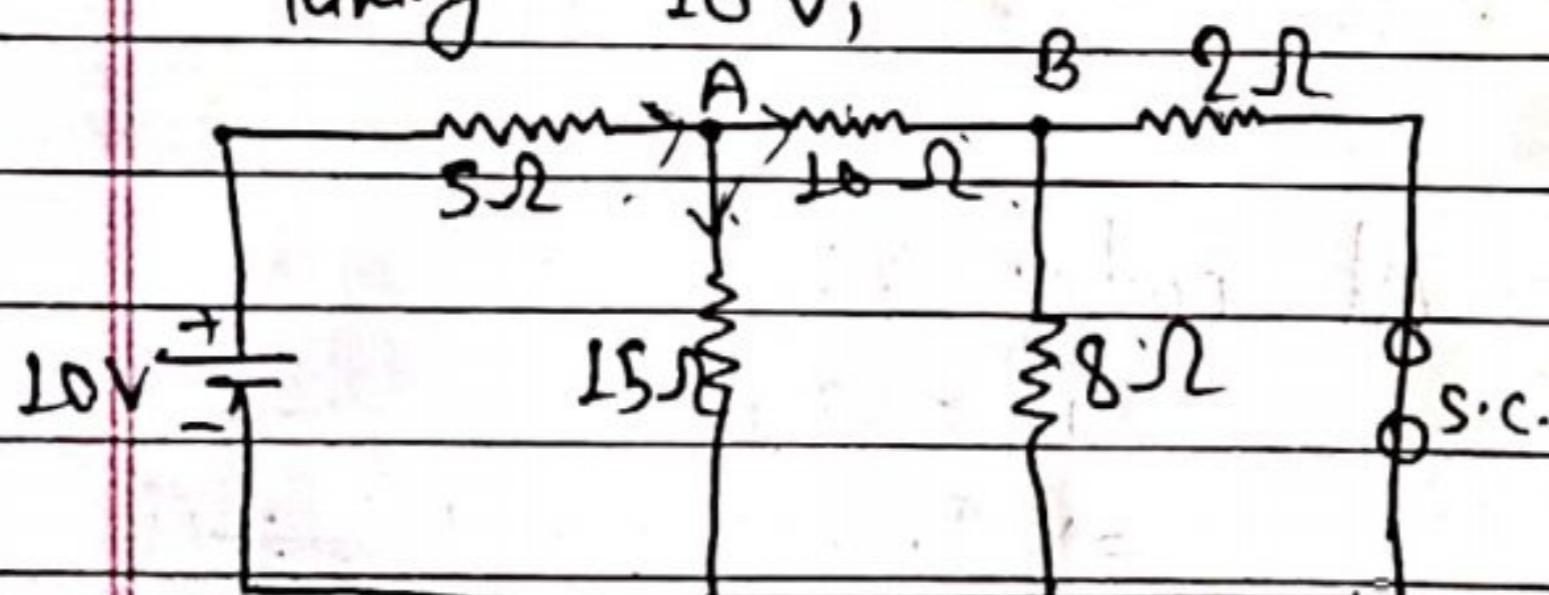

$$R_1 = \frac{8 \times 2}{8 + 2} = 1.6\ \Omega$$

$$R_2 = 10 + 1.6 = 11.6\ \Omega$$


$$R_3 = \frac{15 \times 11.6}{15 + 11.6} = 6.54\ \Omega$$

$$R_{eq} = 5 + 6.54 = 11.54\ \Omega$$

$$I_T = \frac{V}{R} = \frac{10}{11.54} = 0.866\ A$$

$$I_{AB} = \frac{0.866 \times 15}{15 + 11.6} = 0.488\ \text{Amp (A to B)}$$

Taking 15 V;

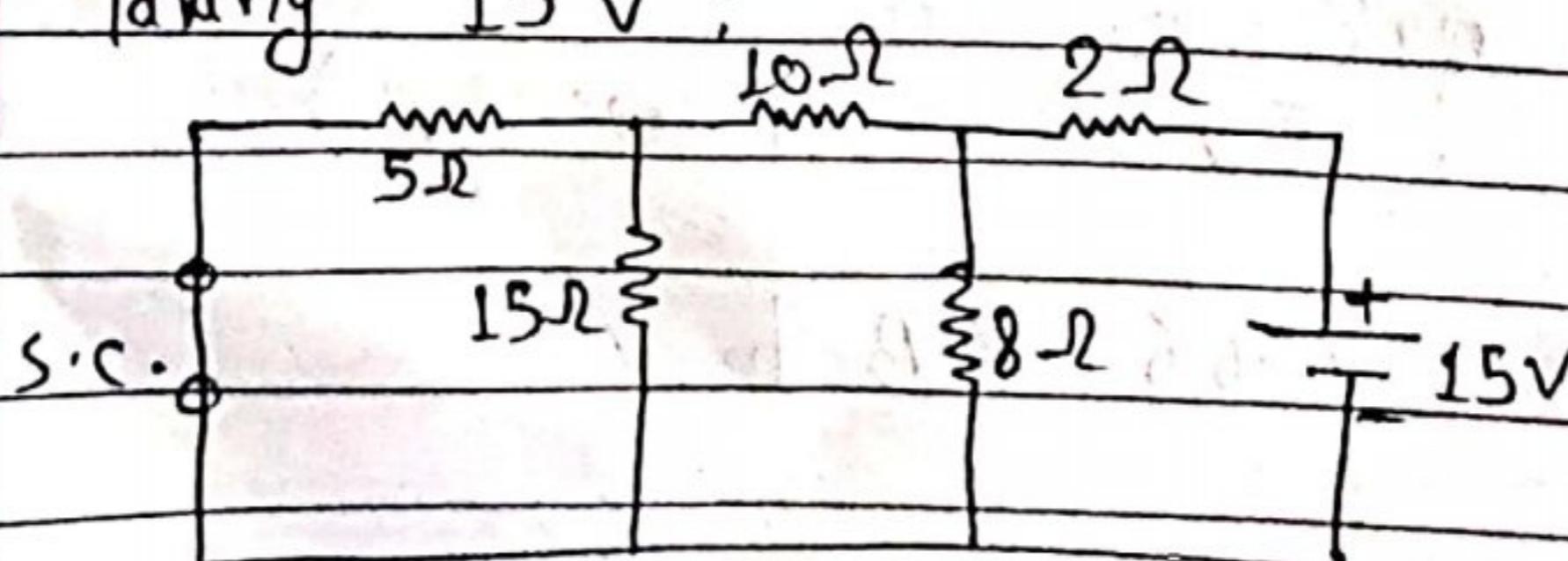

$$R_1 = 3.75\ \Omega$$

$$R_2 = 10 + 3.75 = 13.75\ \Omega$$

$$R_3 = 5.05\ \Omega$$


$$R_{eq} = 5.05 + 2 = 7.05\ \Omega$$

$$I_T = \frac{15}{7.05} = 2.125\ \Omega$$


$$I''_{AB} = \frac{2.12 \times 8}{13.75 + 8} = 0.78\ \text{Amp (B to A)}$$

$$\begin{aligned}\therefore I_{AB} &= I''_{AB} - I'_{AB} \\ &= 0.78 - 0.488 \\ &= 0.29 \text{ Amp}\end{aligned}$$

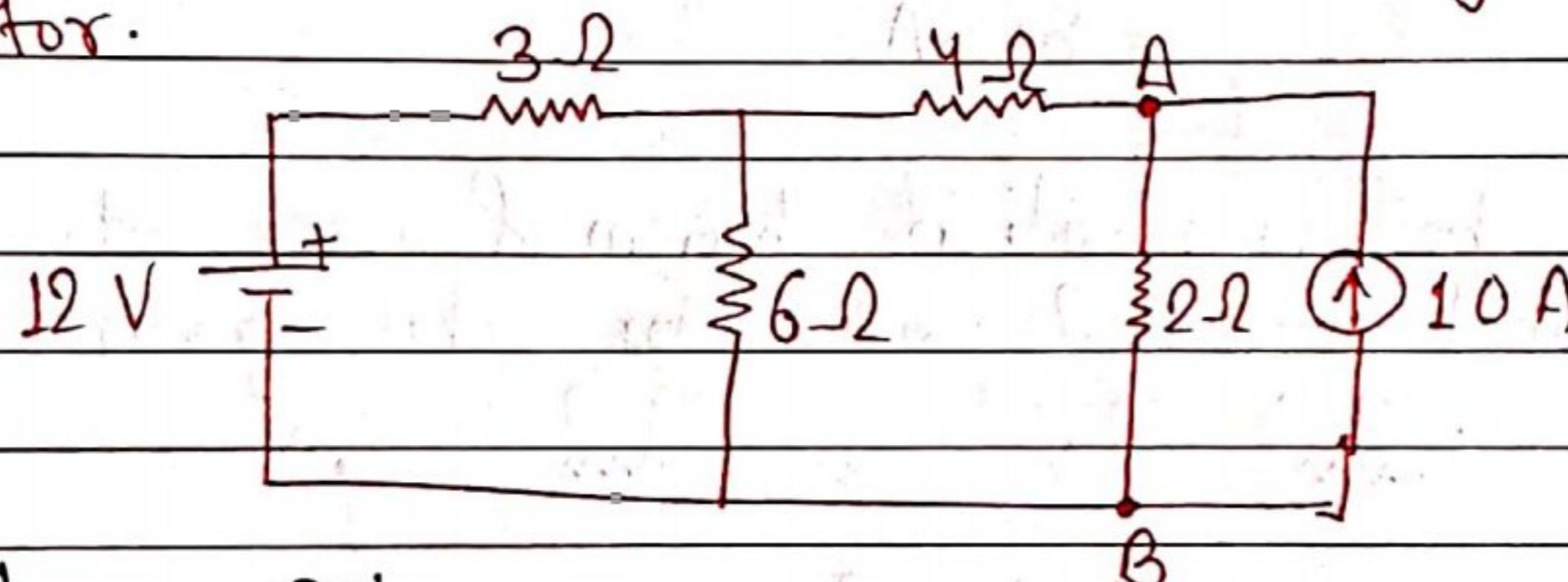Q.18 Using SPT, calculate the current flowing through 2Ω resistor.



Taking 12V,

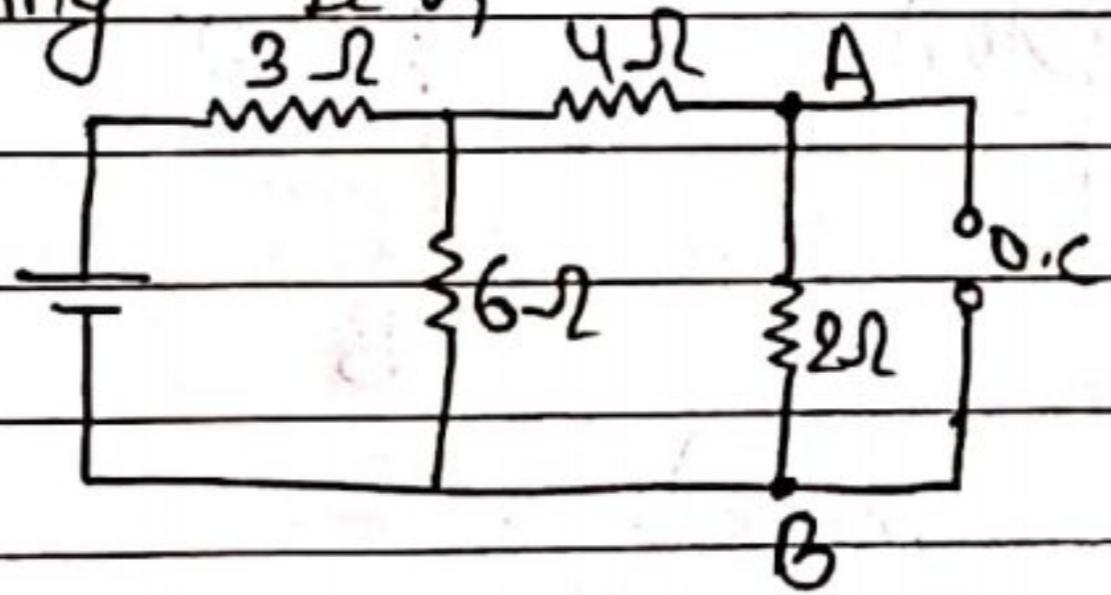

$$R_1 = 4 + 2 = 6\Omega$$


$$R_2 = \frac{6 \times 6}{6+6} = 3\Omega$$

$$R_{eq} = 3 + 3 = 6\Omega$$

$$I_T = \frac{V}{R} = \frac{12}{6} = 2A$$

$$\therefore I'_{AB} = \frac{2 \times 6}{6+6} = \frac{12}{12} = 1A \text{ (A to B)}$$

Taking 10A current source:

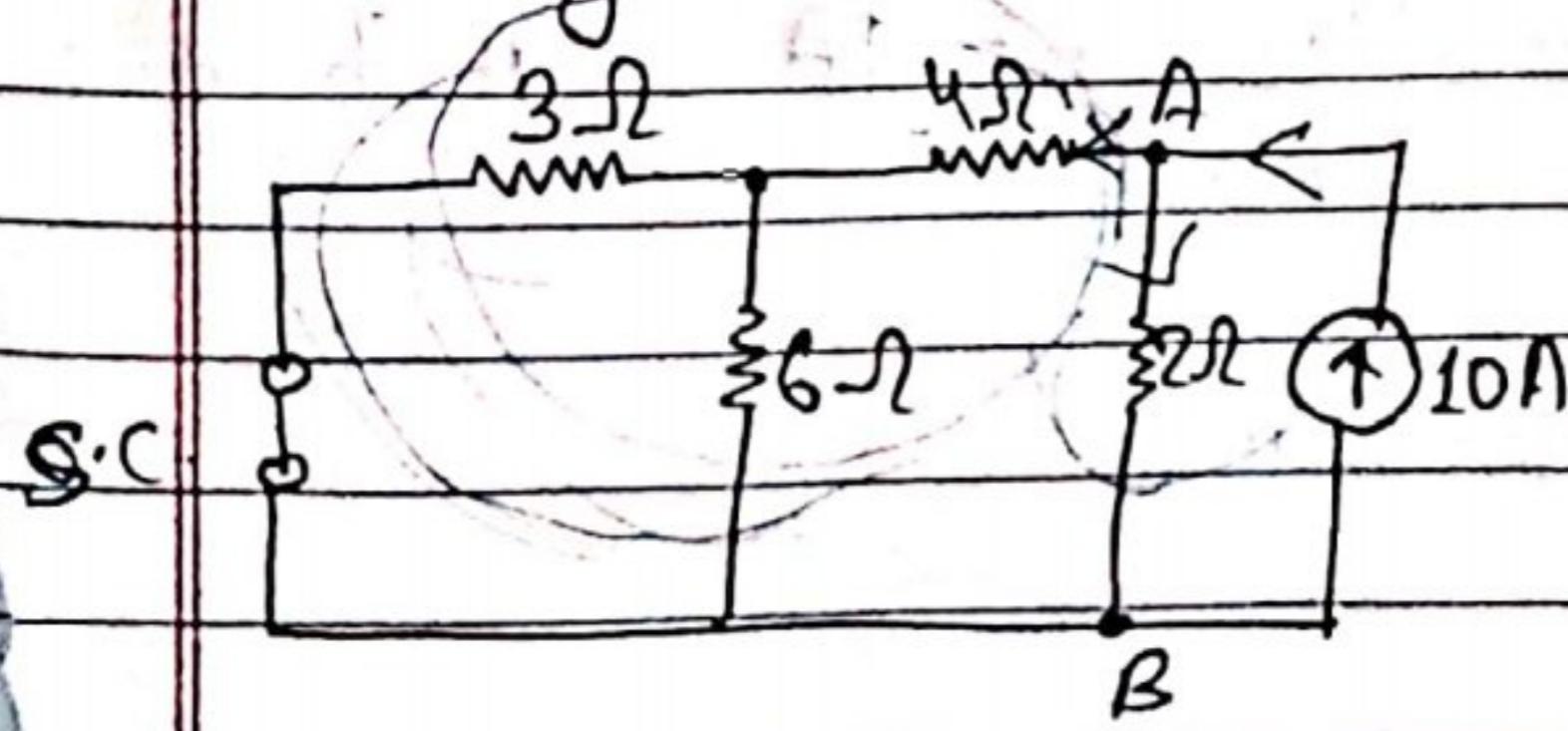

$$R_1 = \frac{3 \times 6}{3+6} = 2\Omega$$

$$R_2 = 2 + 4 = 6\Omega$$

$$I_T = 10 A$$


$$I'_{AB} = \frac{I_T \times R_{opp.}(R_2)}{R_2 + R_{AB}} = \frac{10 \times 6}{6+2} = 7.5 \text{ A} \quad (\text{A to B})$$

$$\therefore I_{AB} = I'_{AB} + I''_{AB}$$


$$= 1 \text{ A} + 7.5 \text{ A}$$

$$= 8.5 \text{ A}$$

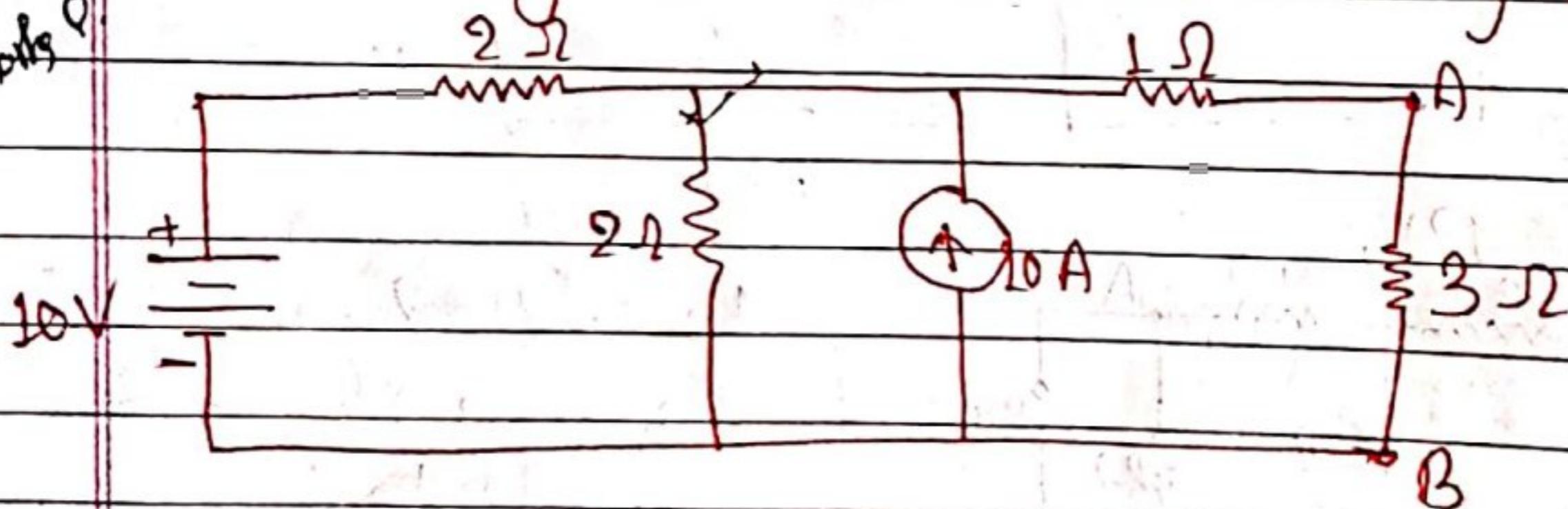13) State the superposition theorem & use it to find power consumed by 3Ω resistor for ckt given below:



Taking 10V (voltage source):

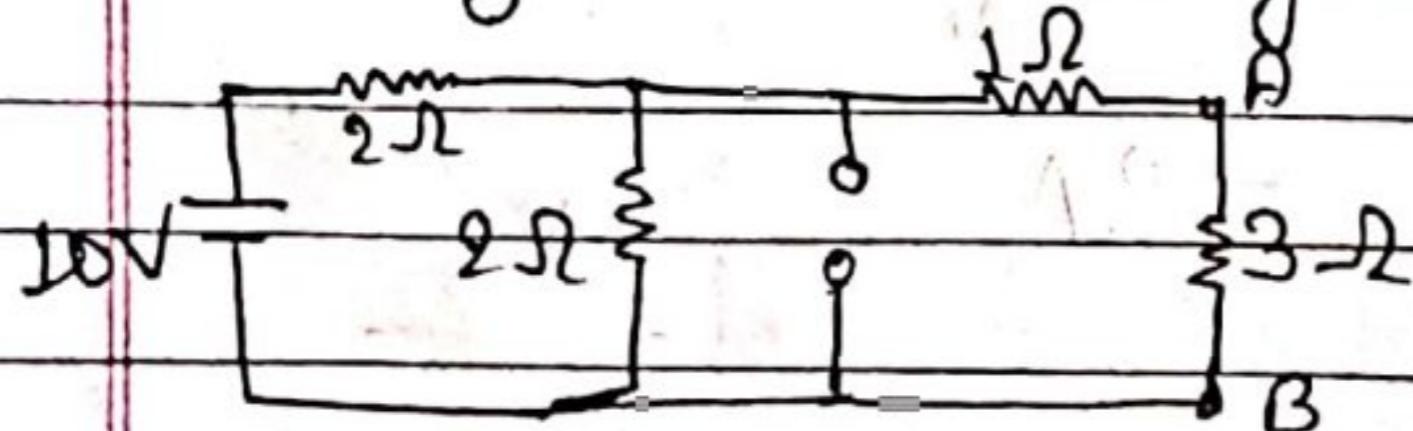

$$R_1 = 1\Omega + 3\Omega = 4\Omega$$


$$R_2 = \frac{2 \times 4}{2+4} = 1.33 \Omega$$

$$R_{eq} = 2 + 1.33 = 3.33 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{10}{3.33} = 3 \text{ A}$$

$$I'_{AB} = \frac{I_T \times 2}{2+4} = \frac{3 \times 2}{2+4} = 1 \text{ A} \quad (\text{A to B})$$

Taking 10A current source

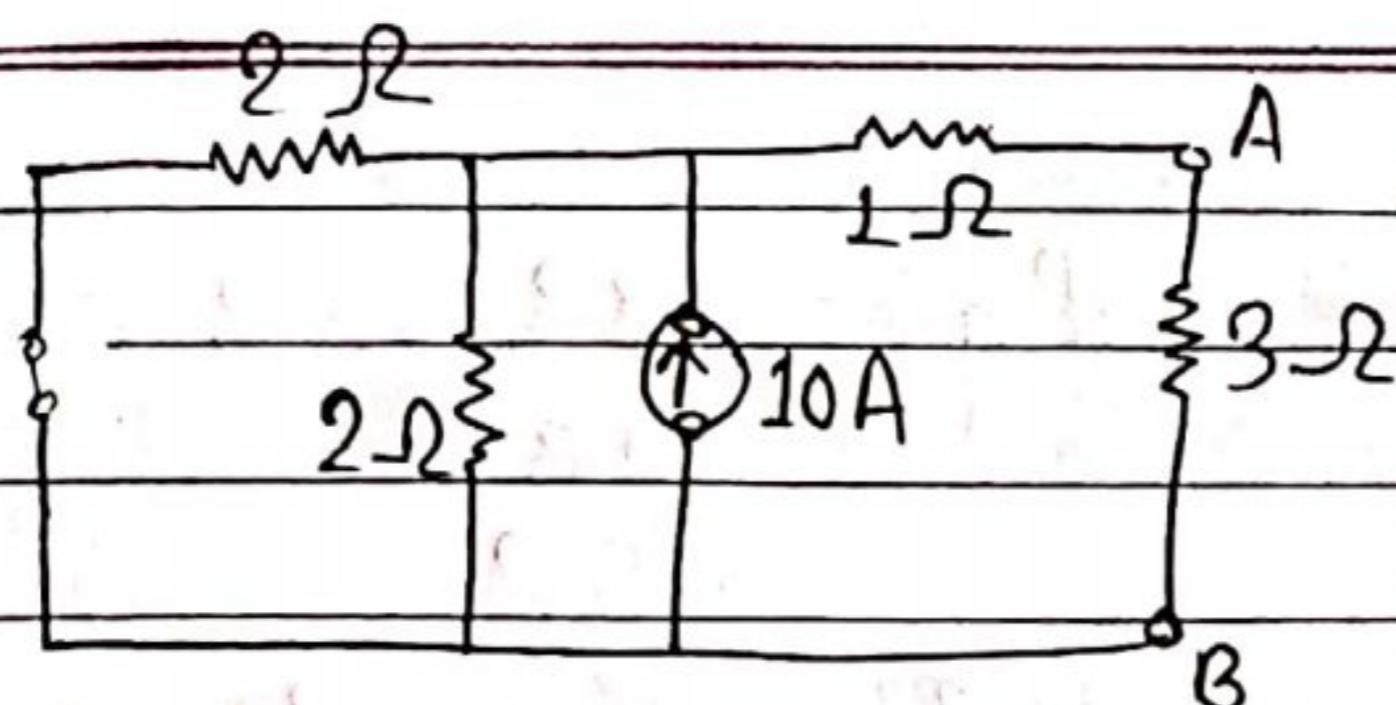

$$R_1 = 1\Omega + 3\Omega$$

$$R_1 = \frac{2 \times 2}{2+2} = 1\Omega, R_2 = 1+3 = 4\Omega.$$


$$I_T = 10A$$

$$I'_{AB} = \frac{10 \times 1}{1+4} = \frac{10}{5} = 2A \text{ (A to B)} \quad [\text{current division}]$$


$$\therefore I_{AB} = I'_{AB} + I''_{AB} \\ = 1 + 2 = 3A$$

$$\therefore P_{AB} = (I_{AB})^2 \cdot R_{AB} \\ = 3^2 \cdot 3 \\ = 27 \text{ watt}$$

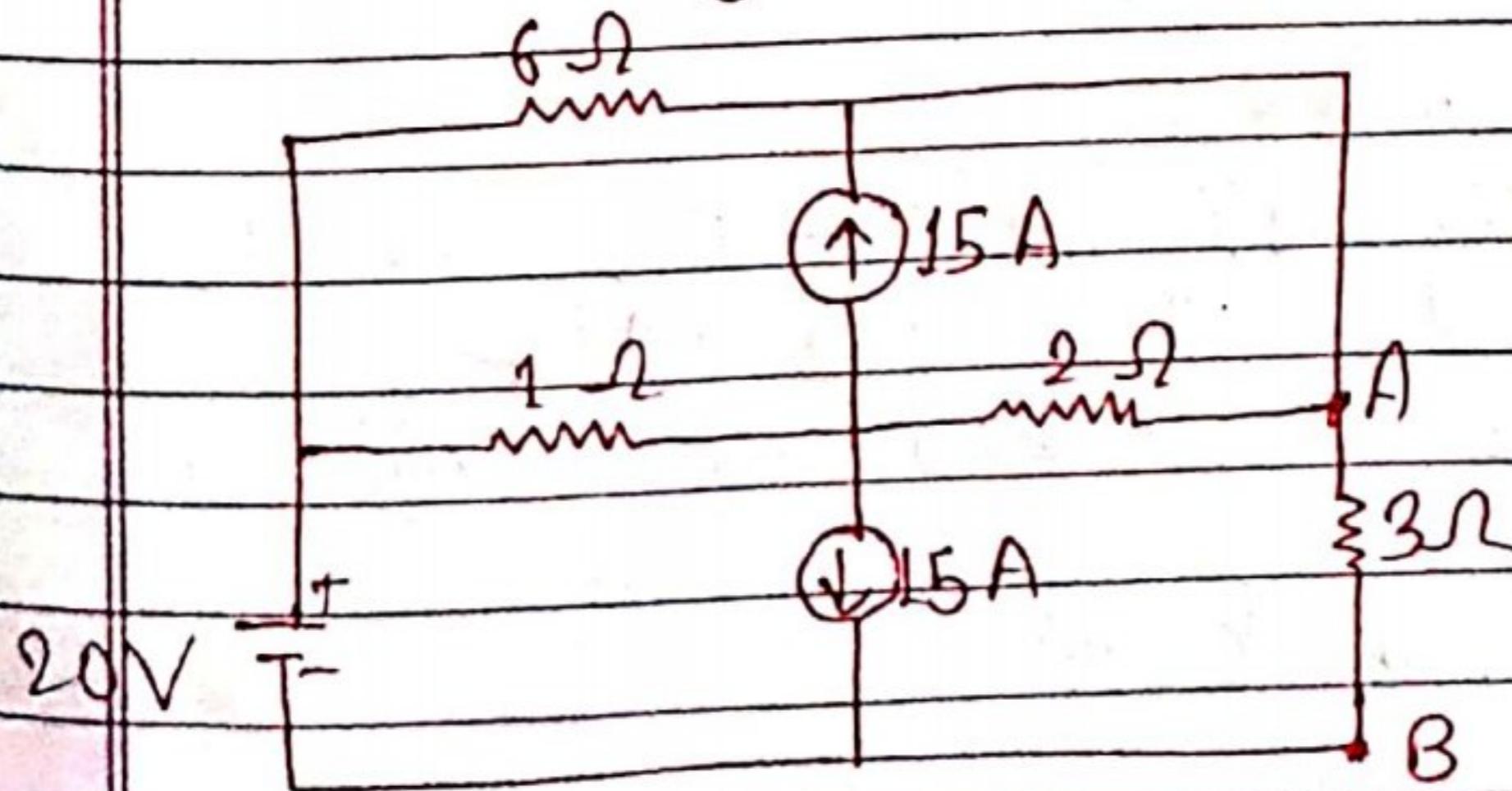Q. Use the superposition theorem to calculate the current through 3Ω resistor of the ck. shown in fig. below:



Here, Taking 20V,

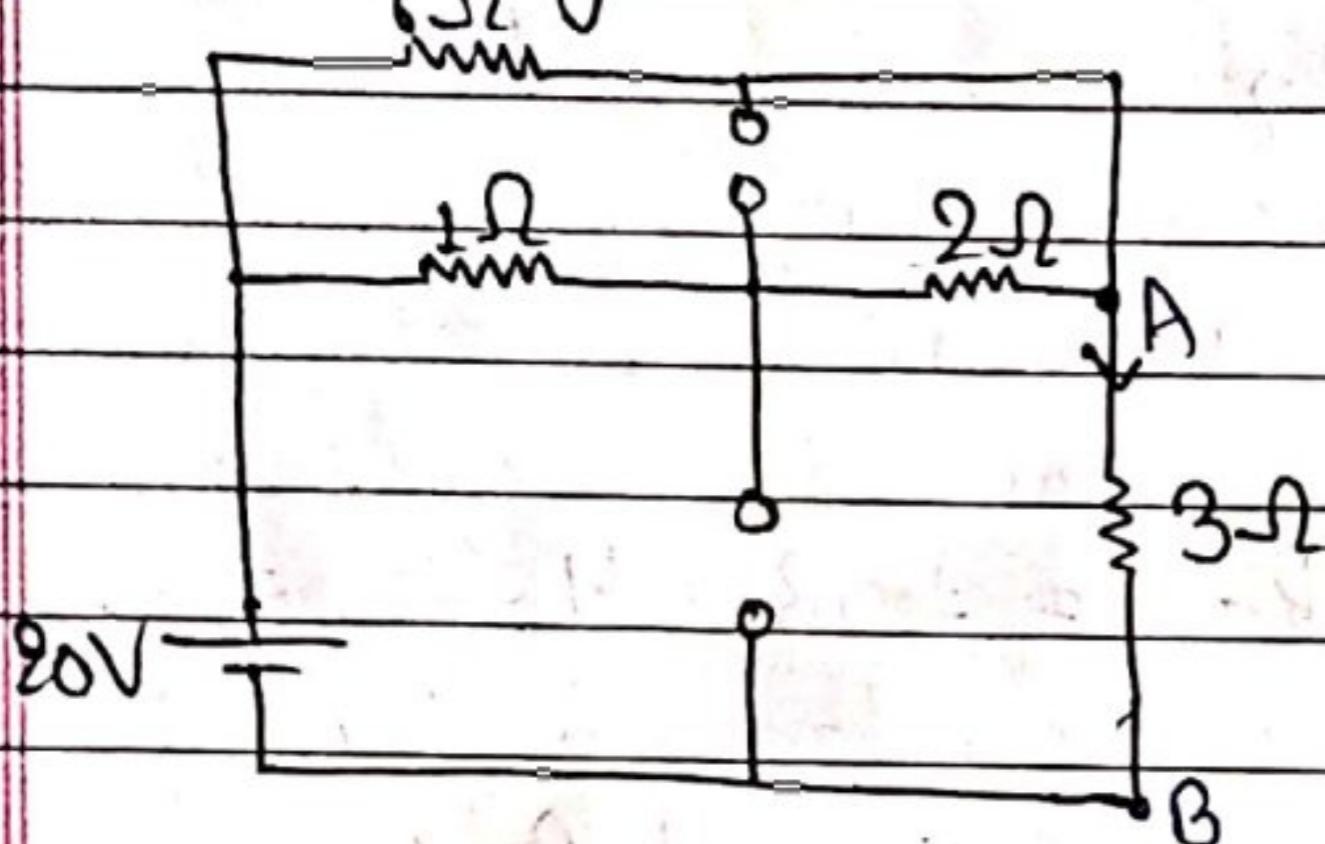

$$R_{eq} = \frac{6 \times 3}{6+3} + 3$$

$$= 5\Omega$$


$$I = \frac{V}{R_{eq}} = \frac{20}{5} = 4 \text{ Amp}$$

This I current flows through 3Ω resistor.

$$\therefore I' = 4 \text{ A } (\uparrow)$$

Now,

Step 2 Taking 15A (↑) :

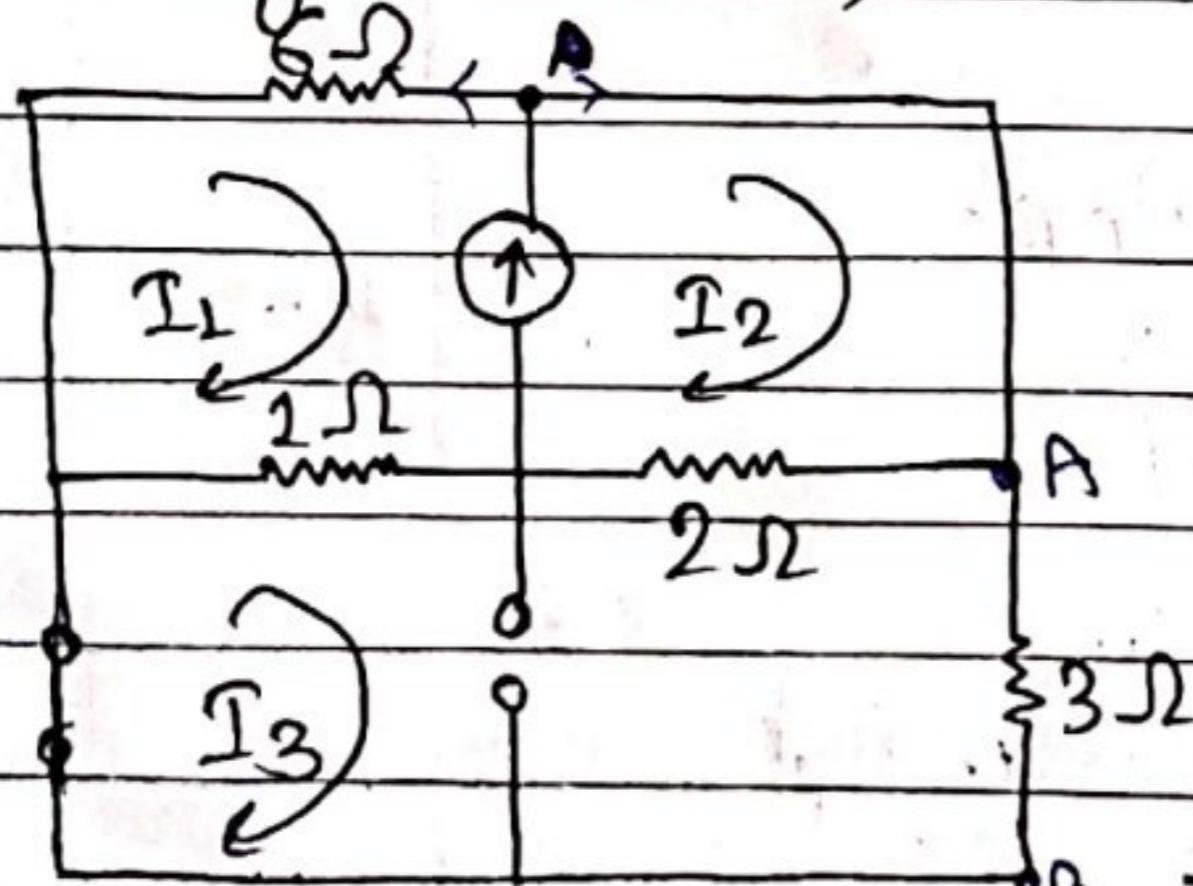

Taking node A:

$$I_L + 15 = I_2$$

$$\therefore I_1 - I_2 = -15 \quad \textcircled{1}$$

Taking common loop $\textcircled{1}$ & \textcircled{II}

$$-6I_1 - 2(I_2 - I_3) - (I_1 - I_3) = 0$$

$$\Rightarrow -6I_1 - 2I_2 + 2I_3 - I_1 + I_3 = 0$$

$$\Rightarrow -7I_1 - 2I_2 + 3I_3 = 0 \quad \textcircled{II}$$

Also, taking loop-3;

$$-3I_3 - (I_3 - I_1) - 2(I_3 - I_2) = 0$$

$$\Rightarrow -3I_3 - I_3 + I_1 - 2I_3 + 2I_2 = 0$$

$$\Rightarrow -6I_3 + I_1 + 2I_2 = 0 \quad \textcircled{III}$$

Solving $\textcircled{1}$, \textcircled{II} & \textcircled{III} ,

$$I_1 = -2 \text{ A}$$

$$I_2 = 13 \text{ A}$$


$$I_3 = 4 \text{ A}$$

Since current flowing through 3Ω resistor is I_3 .
So,

$$I'' = I_3 = 4A \quad (1)$$

Now,

~~Step 3~~ Taking $15A$ (\downarrow)

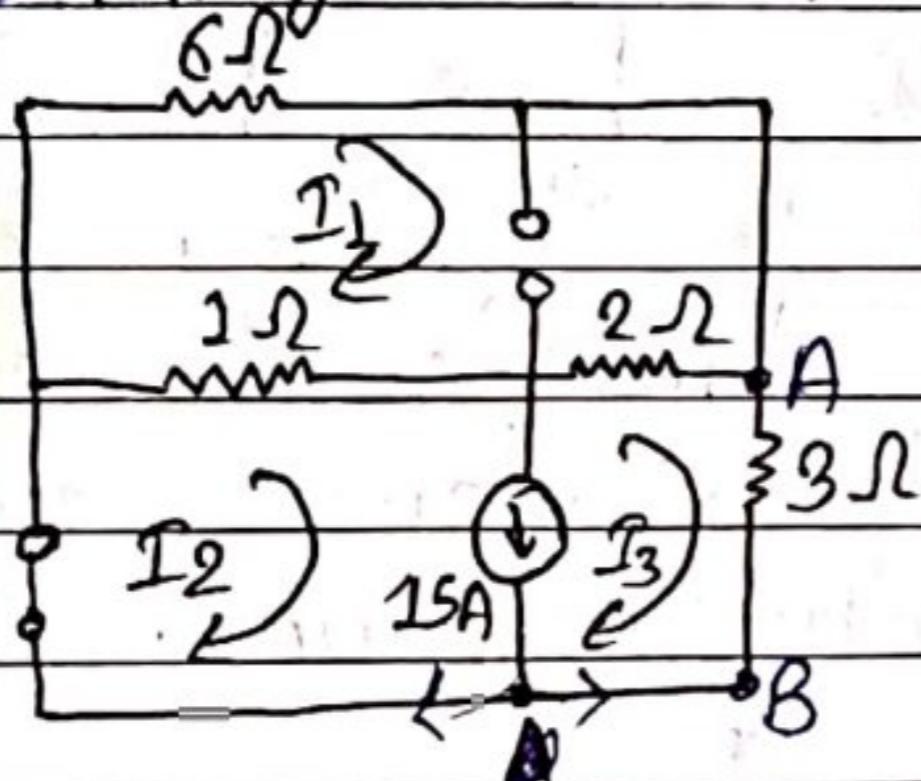

$$\text{At node A: } I_3 + 15 = I_2$$

$$\Rightarrow I_2 - I_3 = 15 \quad (1)$$

$$\begin{aligned} &\text{Taking combine loop (2) \& (3),} \\ &-3I_3 - (I_2 - I_1) - 2(I_3 - I_1) = 0 \\ &\Rightarrow -5I_3 + 3I_1 - I_2 = 0 \quad (2) \end{aligned}$$

Also, taking loop (1),

$$-6I_1 - 2(I_1 - I_3) - (I_1 - I_2) = 0$$

$$\Rightarrow -9I_1 + I_2 + 2I_3 = 0 \quad (3)$$

Solving (1), (2) & (3),

$$I_1 = 1A$$

$$I_2 = 13A$$

$$I_3 = -2A$$

Since current through 3Ω resistor I_3 ,

So,


$$I''' = I_3 = 2A \quad (4)$$

$$\therefore \text{Resultant current} = I' + I'' + I''' = 4 + 4 - 2 = 6A$$

$$\therefore \text{Voltage loop} = IR = 6 \times 3 = 18V$$

Thevenin's Theorem

It states that any ckt having a number of voltage, resistance (impedance) & open output terminal can be replaced by simple equivalent ckt, consisting of single voltage source in series with resistance (impedance) where the value of voltage source is equal to the open ckt voltage across the output terminals & resistance (impedance) is equal to the resistance seen into the N/w across the output terminal.

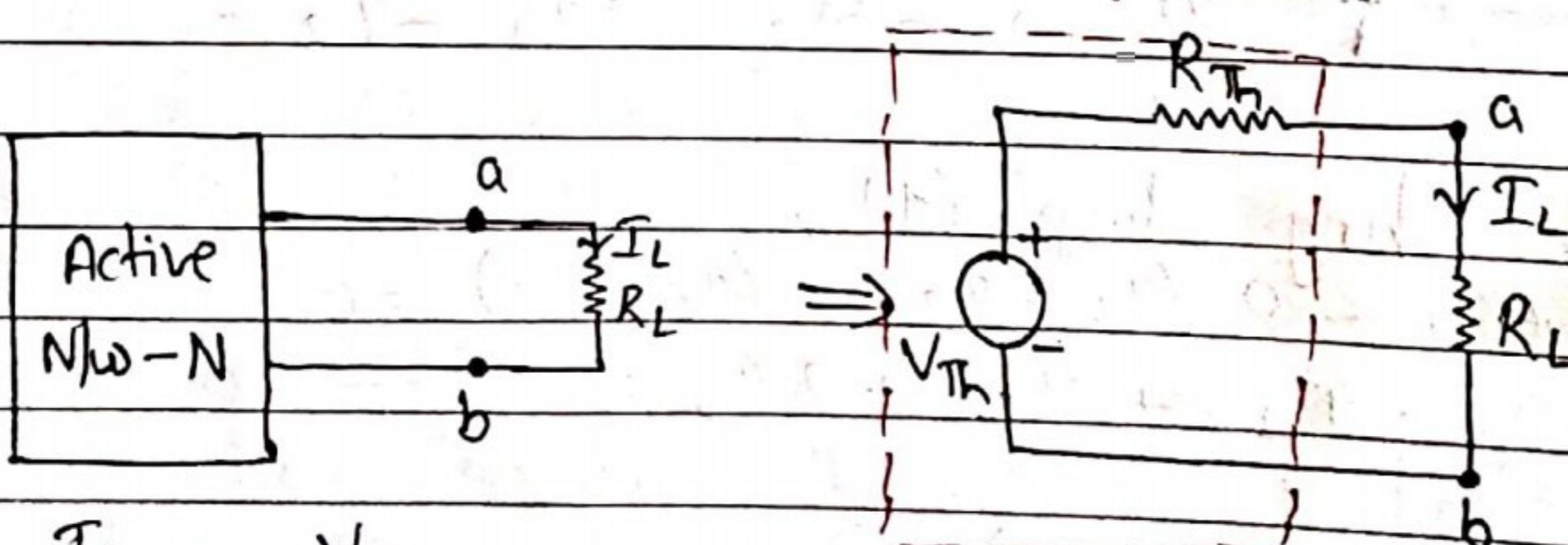

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

Thevenin's equivalent
Nw-N

Procedure

Remove the load resistance.

Calculate the voltage seen by the load.

All the voltage source - short ckt (s.c.)

" " current " " - open ckt (o.c.)

Calculate the resistance seen by the load (R_{Th}).

Thevenin's Theorem

Any linear circuit containing large number of voltages and current sources and resistances can be replaced by a simple equivalent ckt containing a single voltage source and a series resistor connected across the load.


* If resistance & current are in parallel, convert current into voltage

classmate

Date _____


Page _____

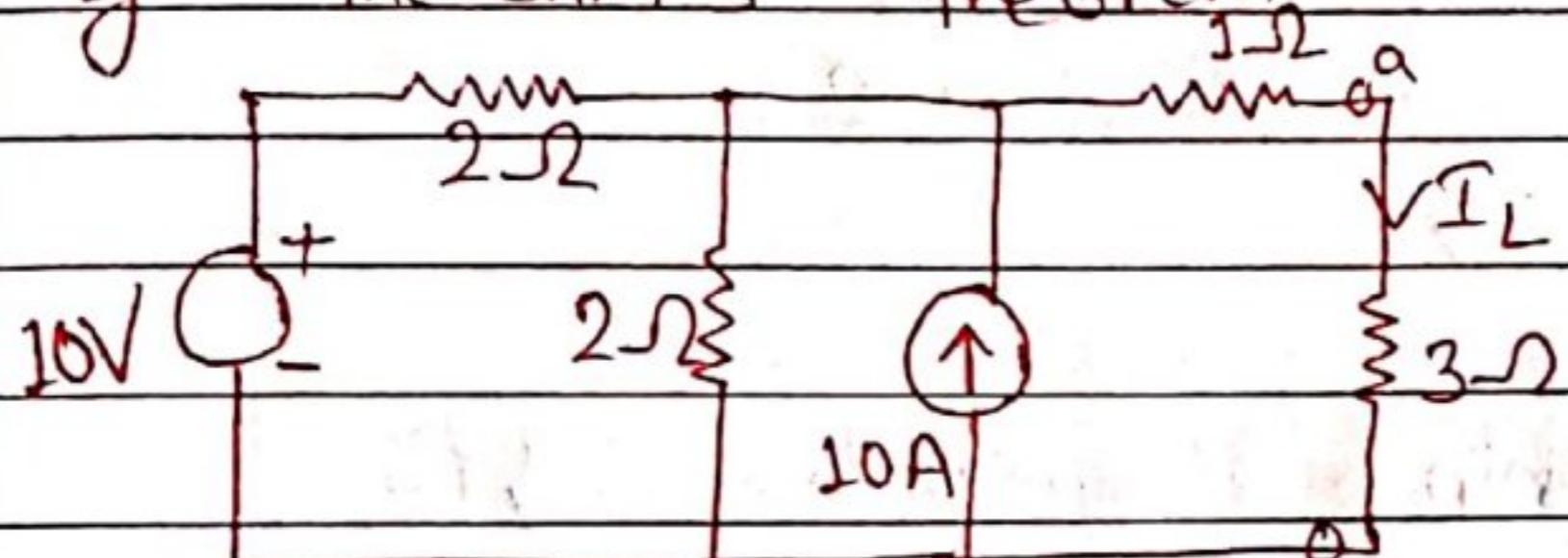Q.1 Determine the current through 3Ω resistor in the $\text{N} \text{c} \omega$ by Thevenin's theorem.



solution:



Step - 1 : finding the R_{Th} :

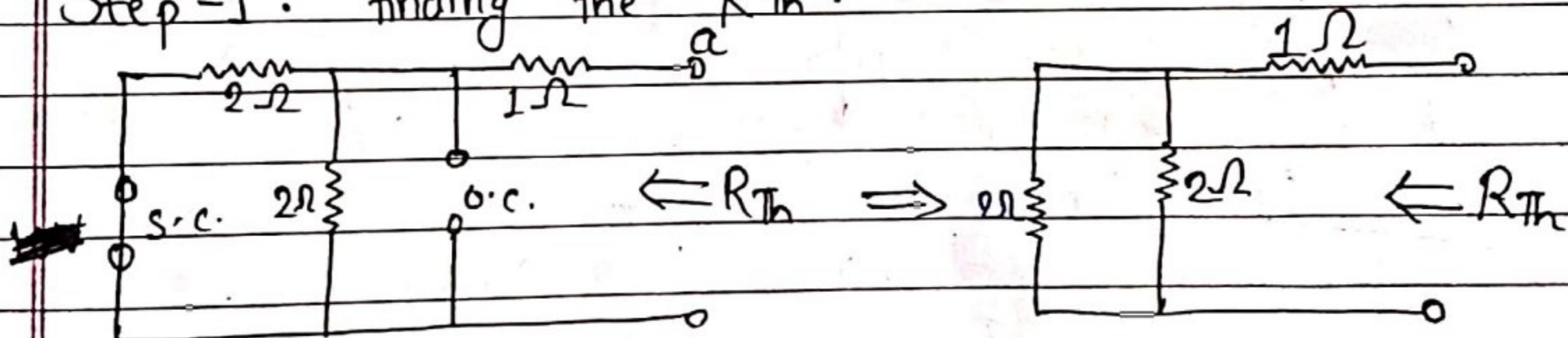

$$R_{Th} = (2//2) + 1 = 2\Omega$$

$$\therefore R_{Th} = 2\Omega$$

Step - 2 : finding the V_{Th} :

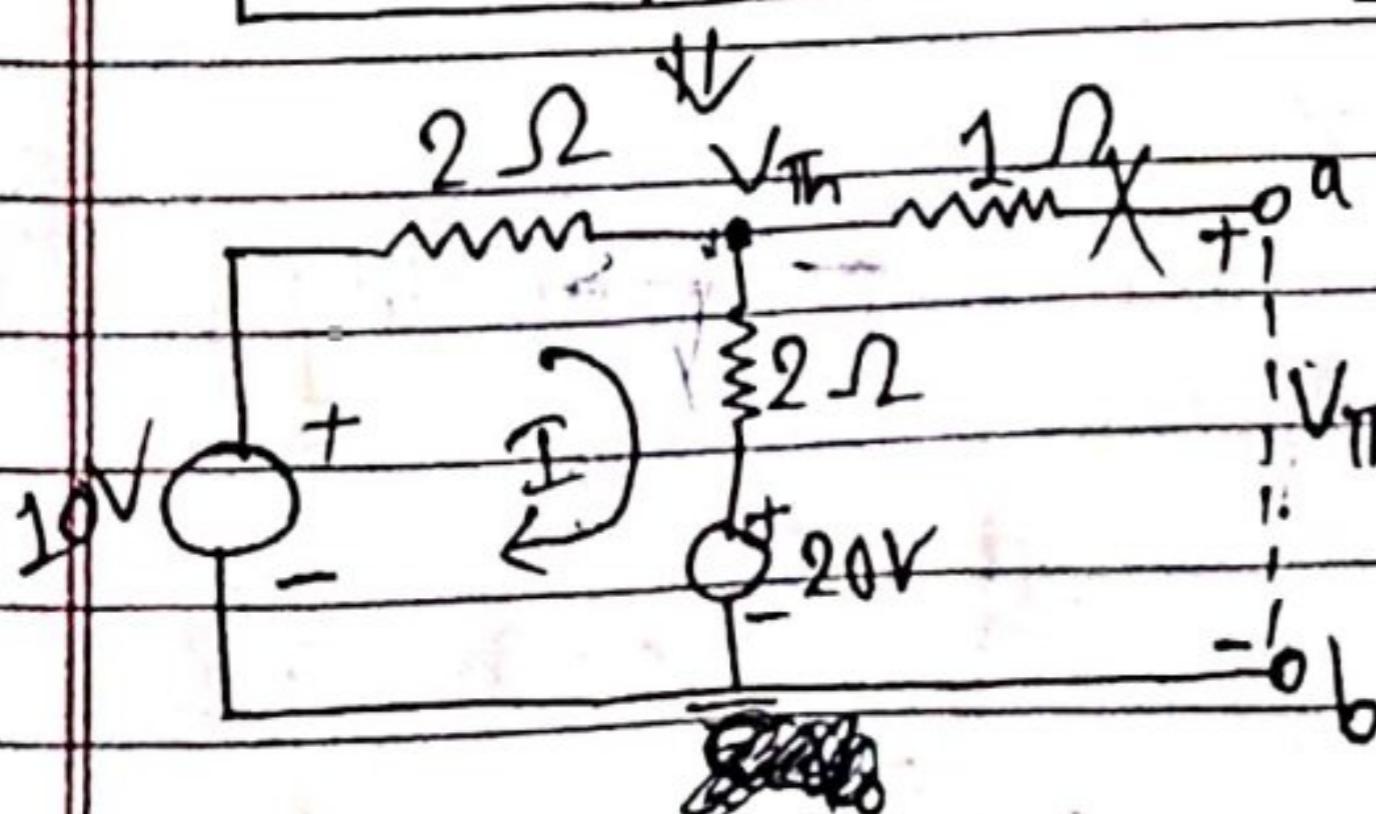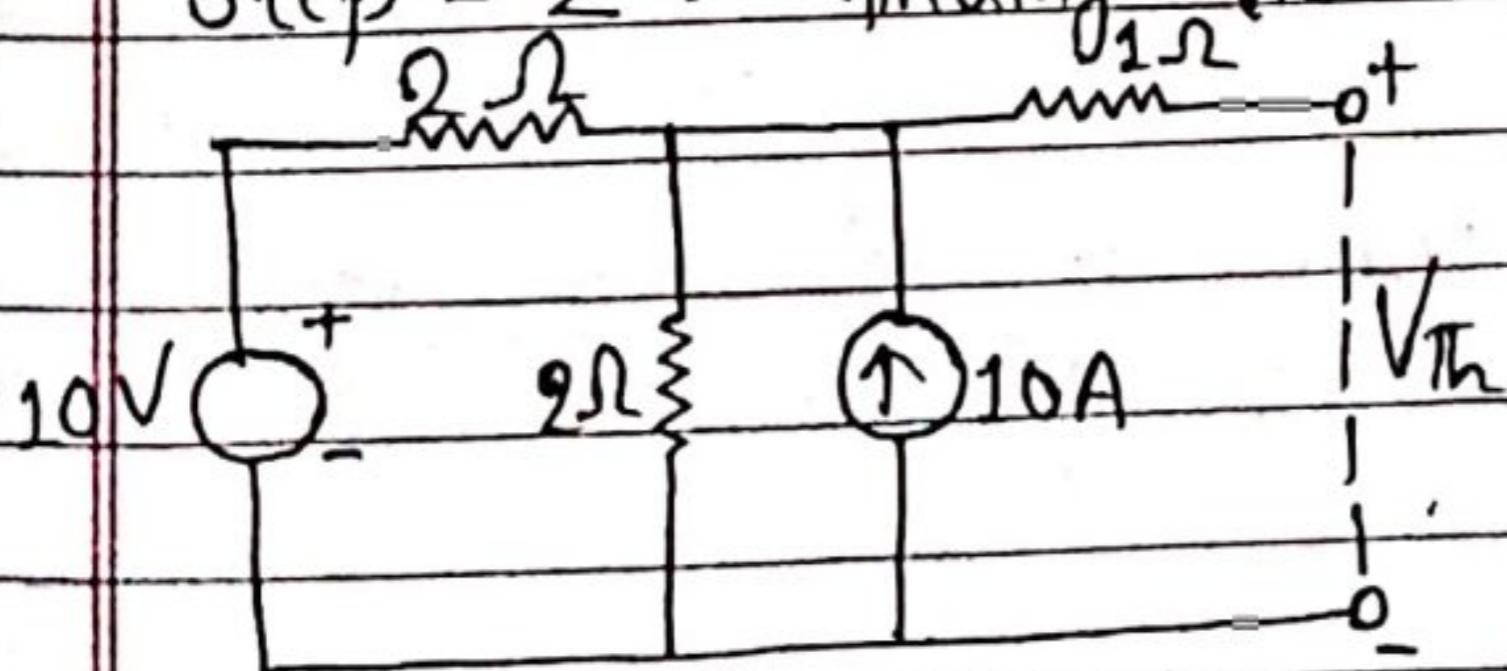

Consider mesh LHS:

$$10V - 2I_1 - 2I_2 - 20 = 0$$


$$\Rightarrow I_1 = -2.5 \text{ amp}$$

Using KVL in RHS mesh,

$$V_{Th} - 2I - 20 = 0$$

$$\therefore V_{Th} = 2 \times (-2.5) + 20 \\ = 15V$$


Step-3: Thevenin's equivalent ckt

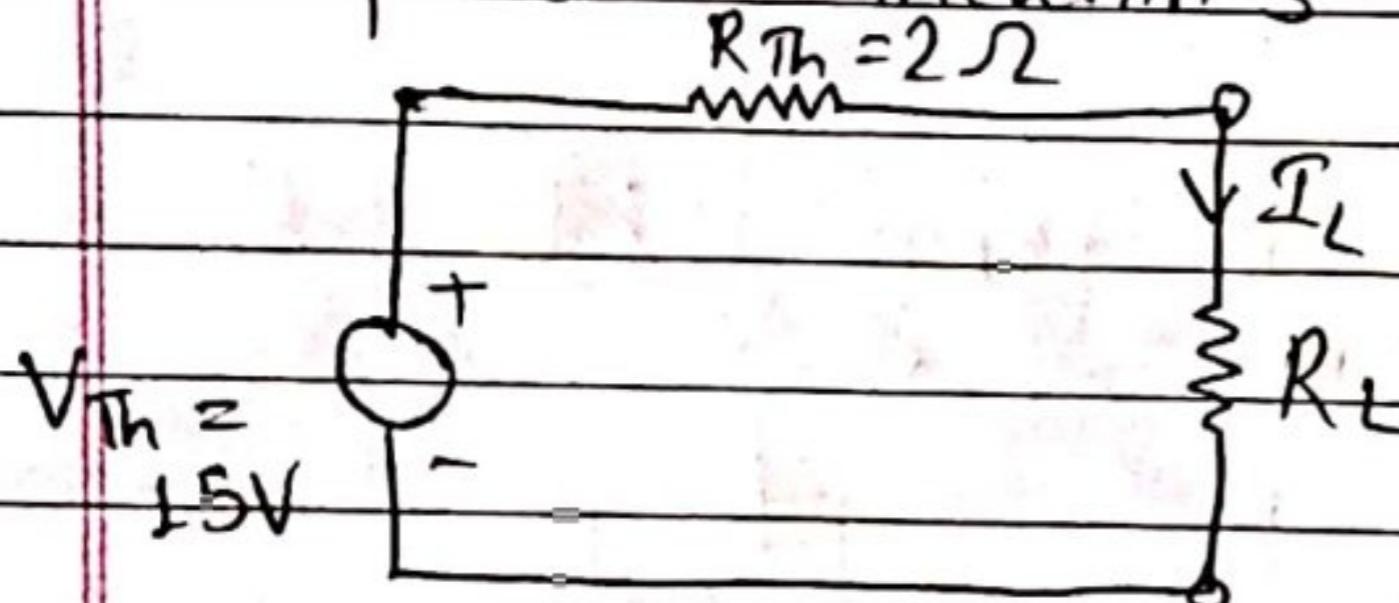

$$\text{So, } I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{15}{2+3}$$


$$\therefore I_L = 3 \text{ amp}$$

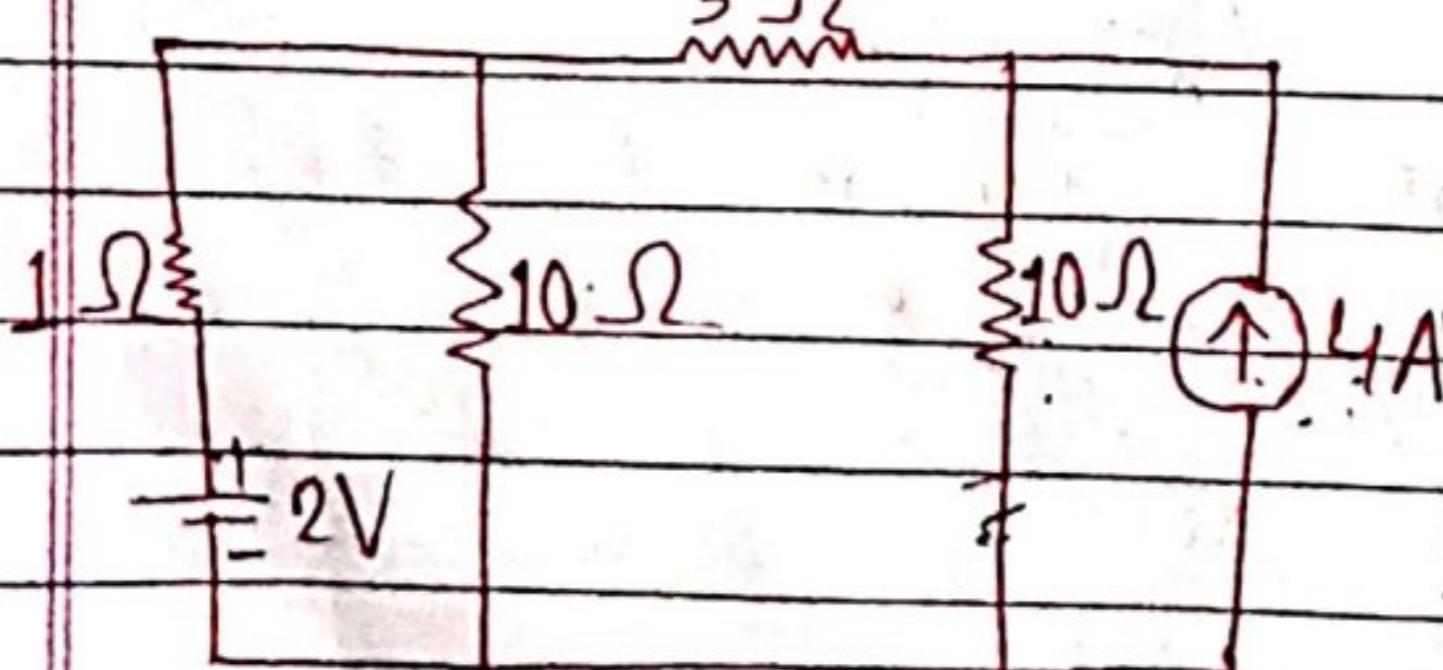Q.2) Use the Thevenin's theorem, find the current through 5Ω resistor in the ckt.




(source transformation can be done when resistors are in parallel)

$$V = IR = 4 \times 10 = 40V$$

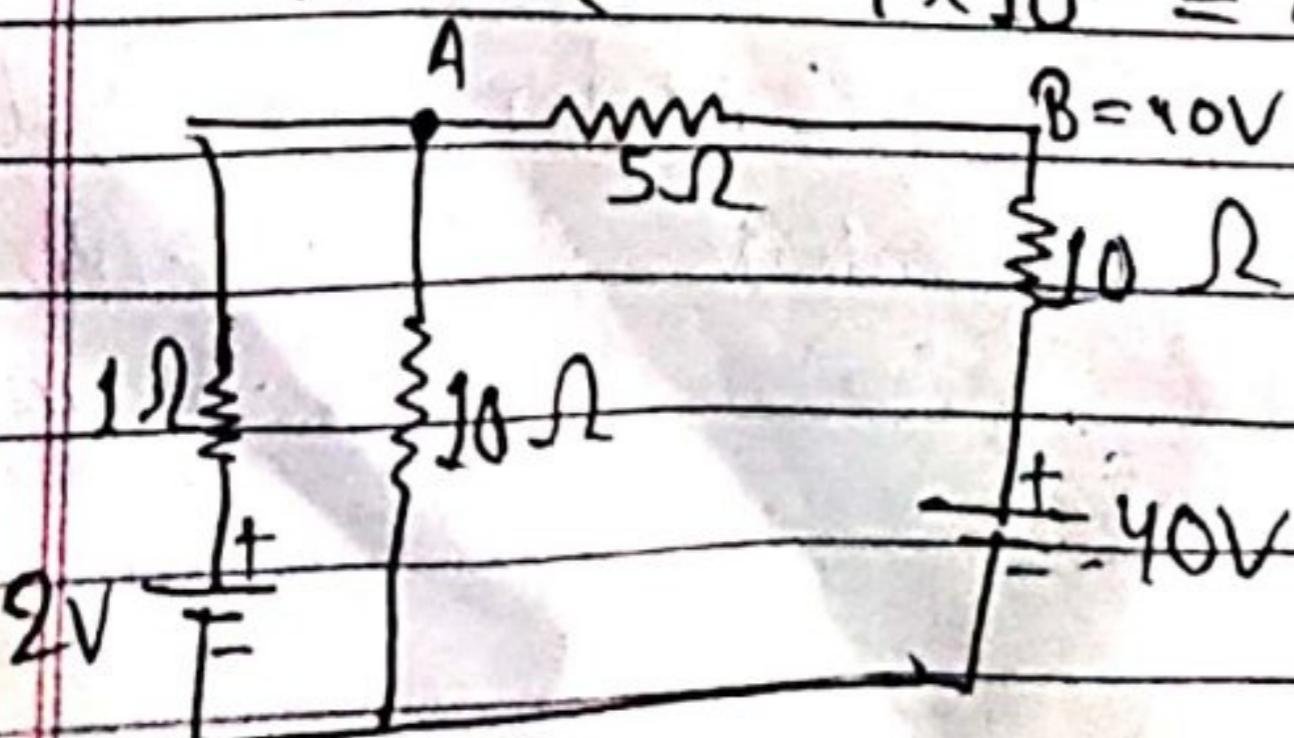


Step-1: finding R_{Th} :

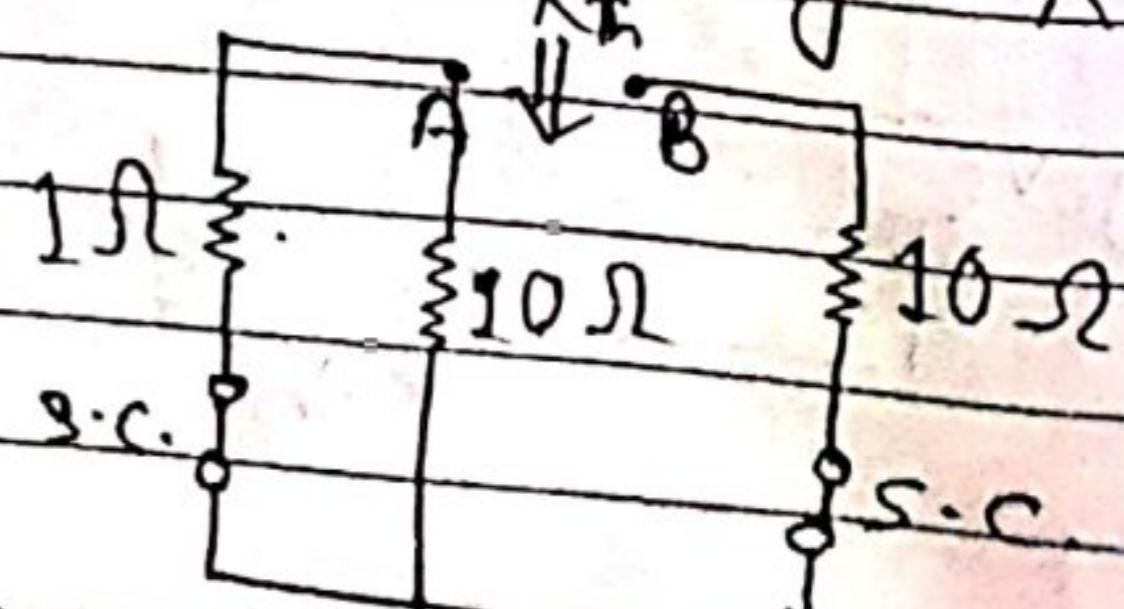

$$R_{Th} = 1 \parallel 10 + 10\Omega$$

$$= 10 \cdot 9 \Omega$$

Step -2 : finding V_{Th} :

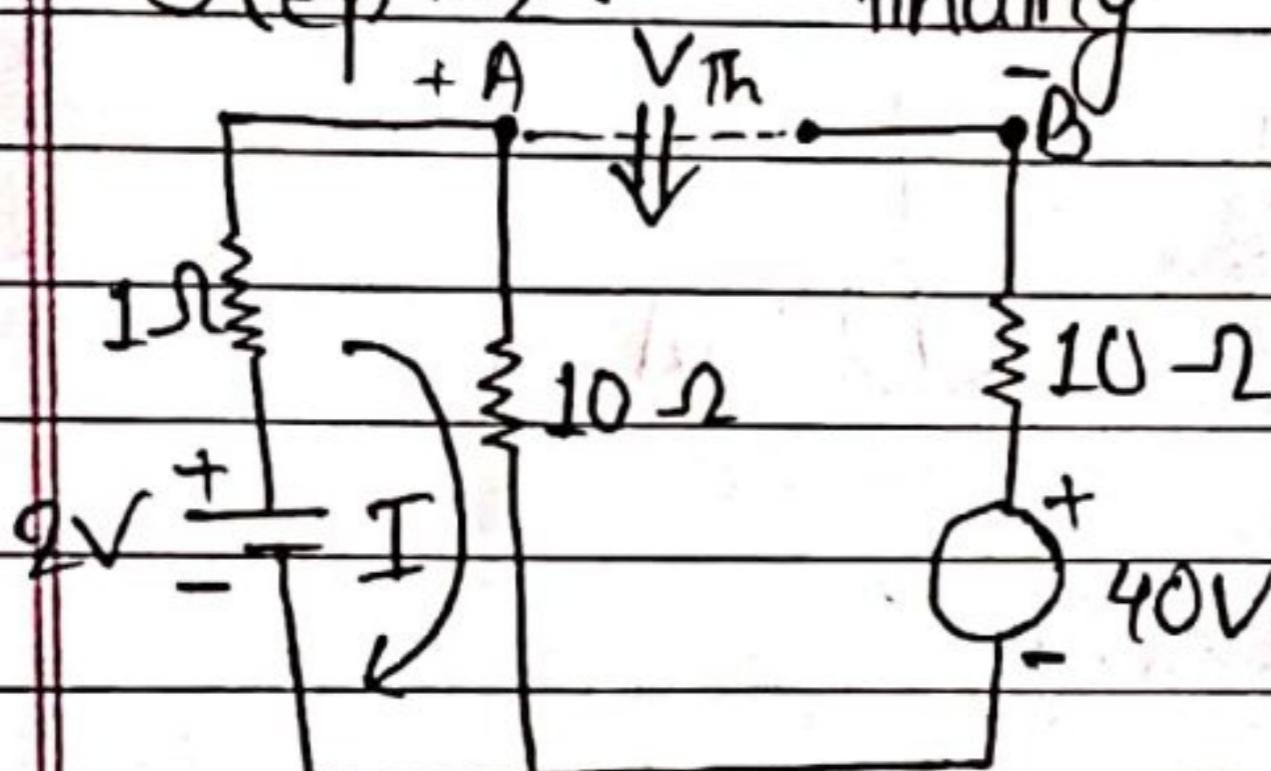

Consider LHS mesh:

$$2 - 1I - 10I = 0$$

$$\Rightarrow I = 0.18A$$

$$V_A = IR = 0.18 \times 10 = 1.8V$$

$$V_{AB} = V_B - V_A$$

$$= 40 - 1.8$$


$$= 38.2V$$

$$\therefore V_{AB} = V_{Th} = 38.2V$$

Step -3 :

Find the Thevenin's equivalent ckt:

$$R_{Th} = 10 \cdot 9 \Omega$$

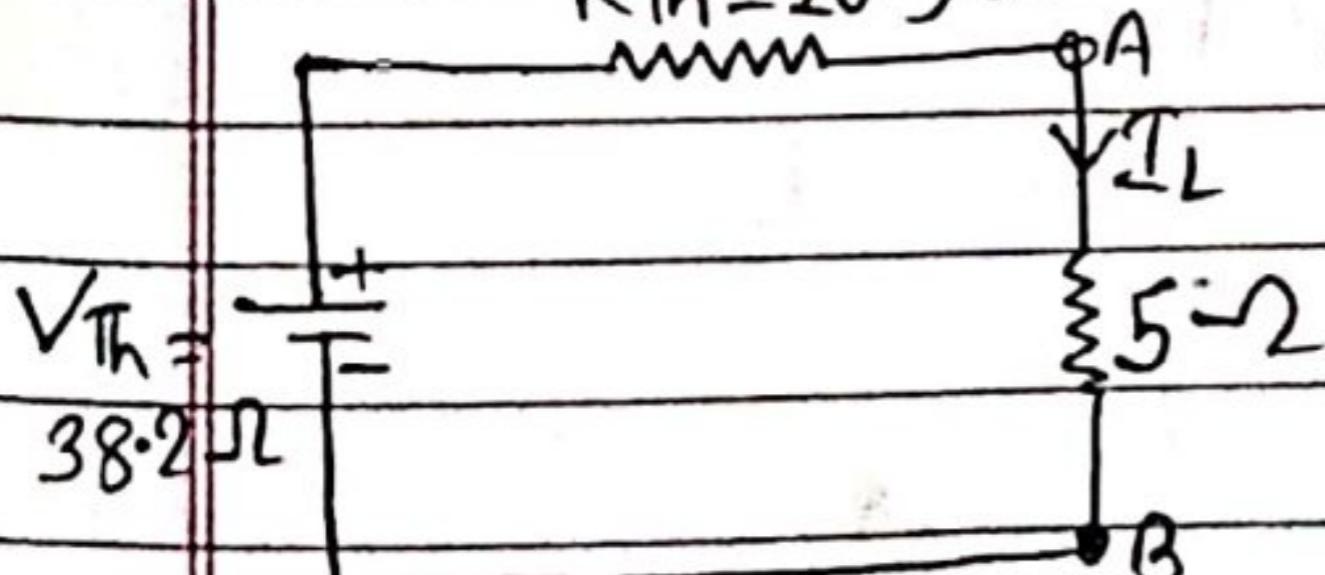


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$


$$= \frac{38.2}{10.9 + 5}$$

$$= 2.40 \text{ amp}$$

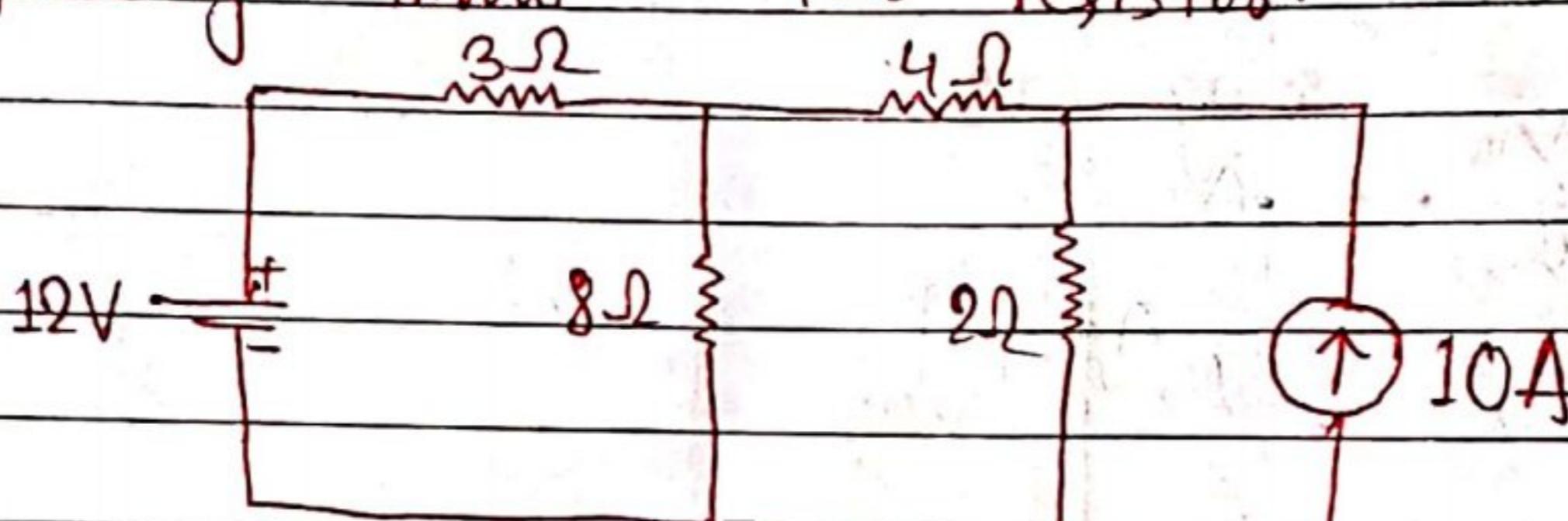Q.3) Use Thevenin's theorem to calculate the current flowing through 4Ω resistor.




Step - 1 : Finding the R_{Th} :

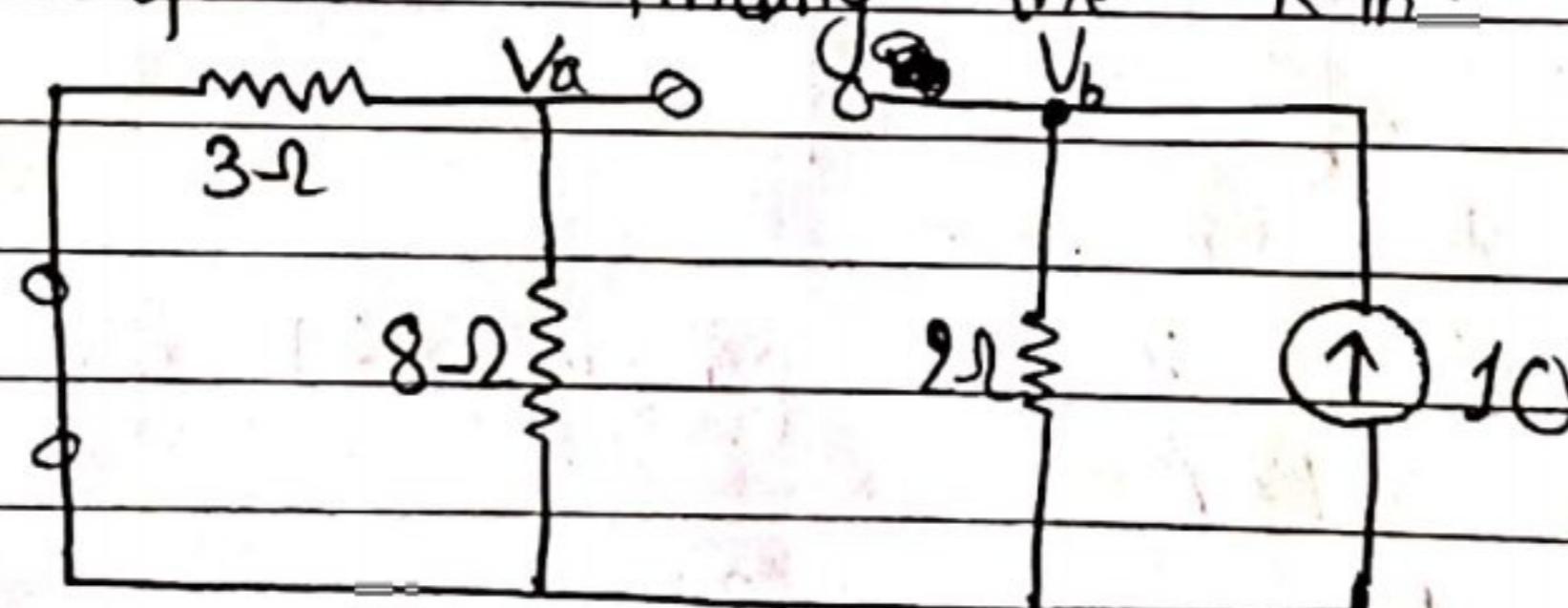

$$\begin{aligned} R_{Th} &= (3||8) + 2 \\ &= \frac{3 \times 8}{3+8} + 2 \\ &= 4.18 \Omega \end{aligned}$$

Step - 2 : finding the V_{Th} :

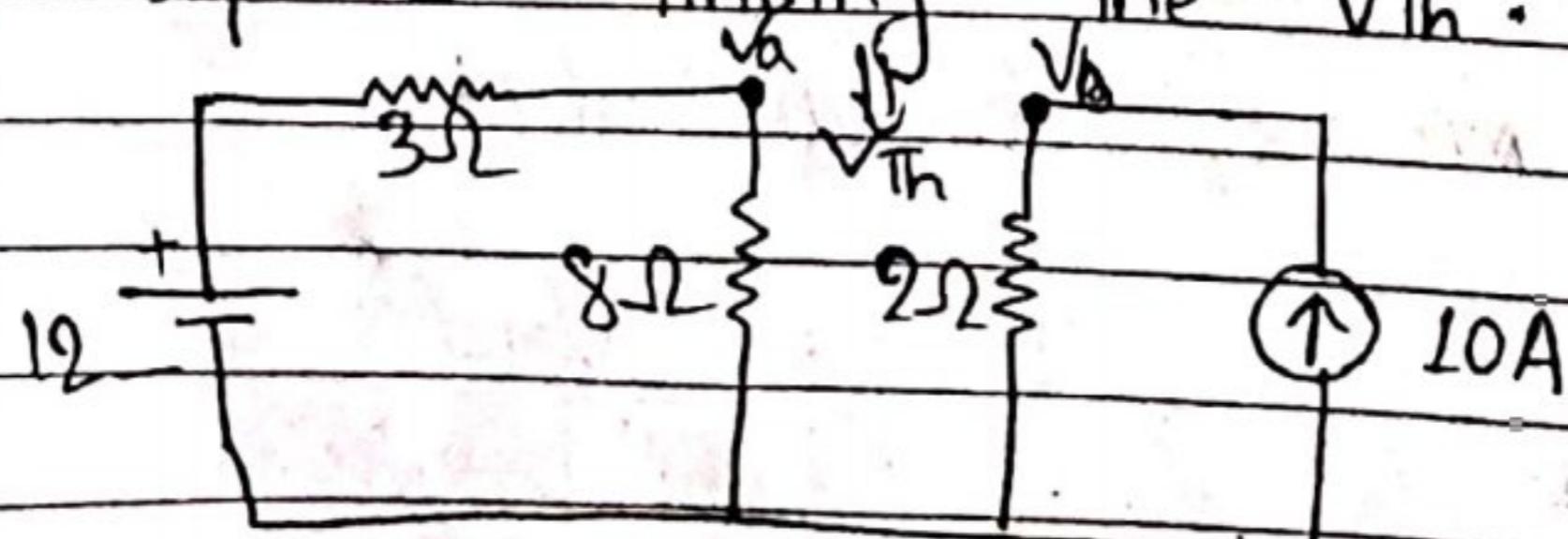

$$\frac{V_a - 12}{3} + \frac{V_b}{8} = 0$$

$$\Rightarrow 8V_a - 96 + 3V_b = 0$$


$$\Rightarrow V_a = 8.72V$$

$$\frac{V_b}{2} = 10$$

$$\Rightarrow V_b = 20V$$


$$\therefore V_{Th} = V_b - V_a \\ = 20 - 8.72 \\ = 11.28 \text{ V}$$

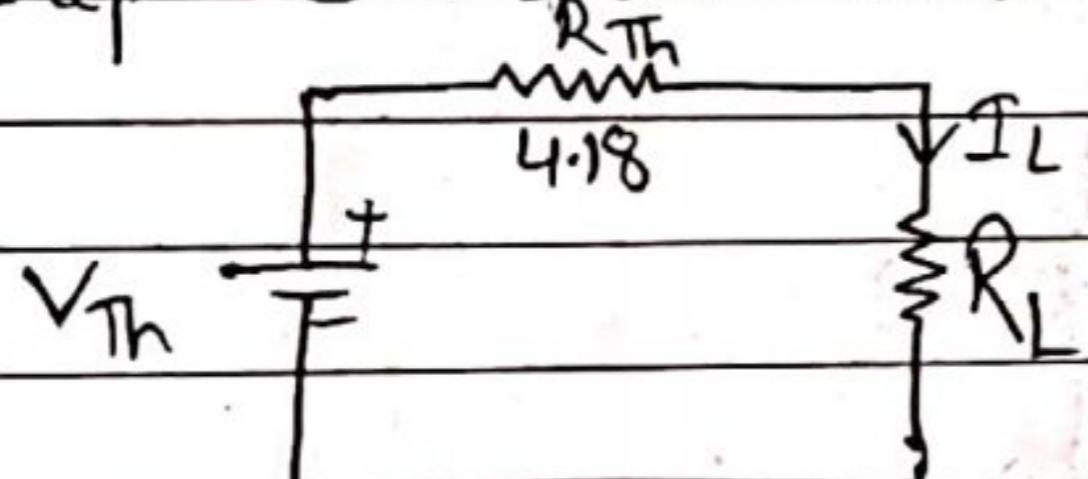Step - 3: Draw thevenin's equivalent ckt,




$$\therefore I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{11.28}{4.18 + 4} = 1.37 \text{ A}$$

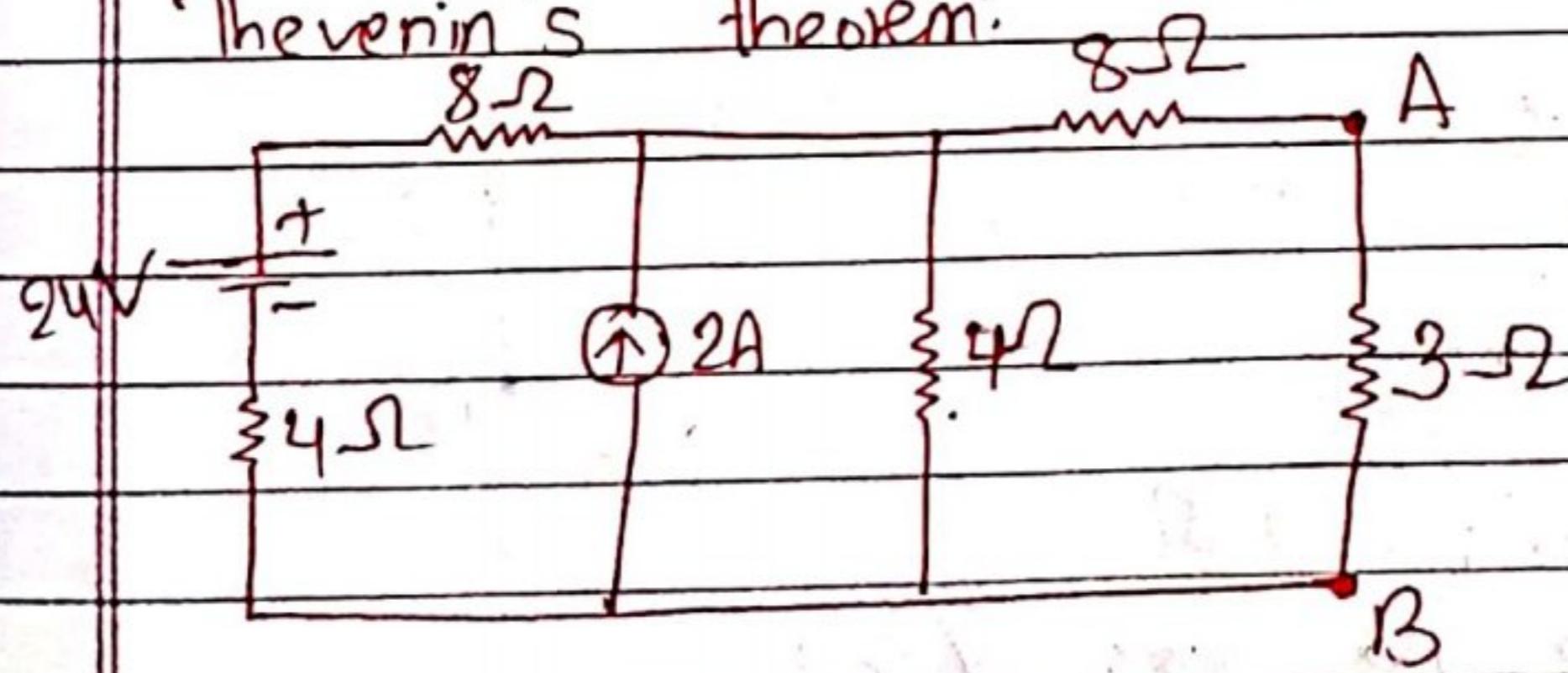
Q.4) Calculate the current through 3Ω resistor using the
Thevenin's theorem:



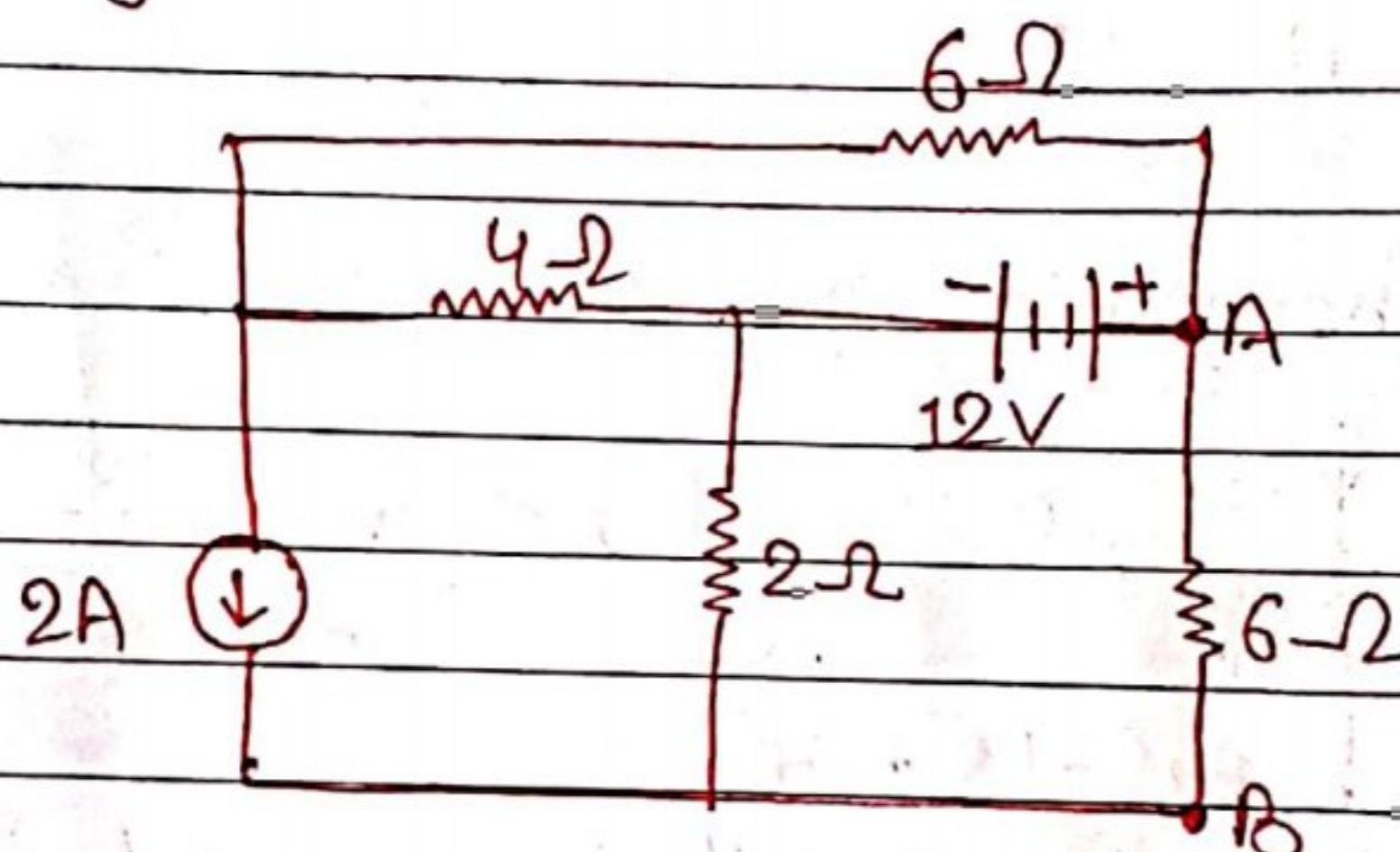~~Q.5~~ Use Thevenin's theorem, find the current flowing through 6Ω resistor in the network:




Step -1: Finding R_{Th} :

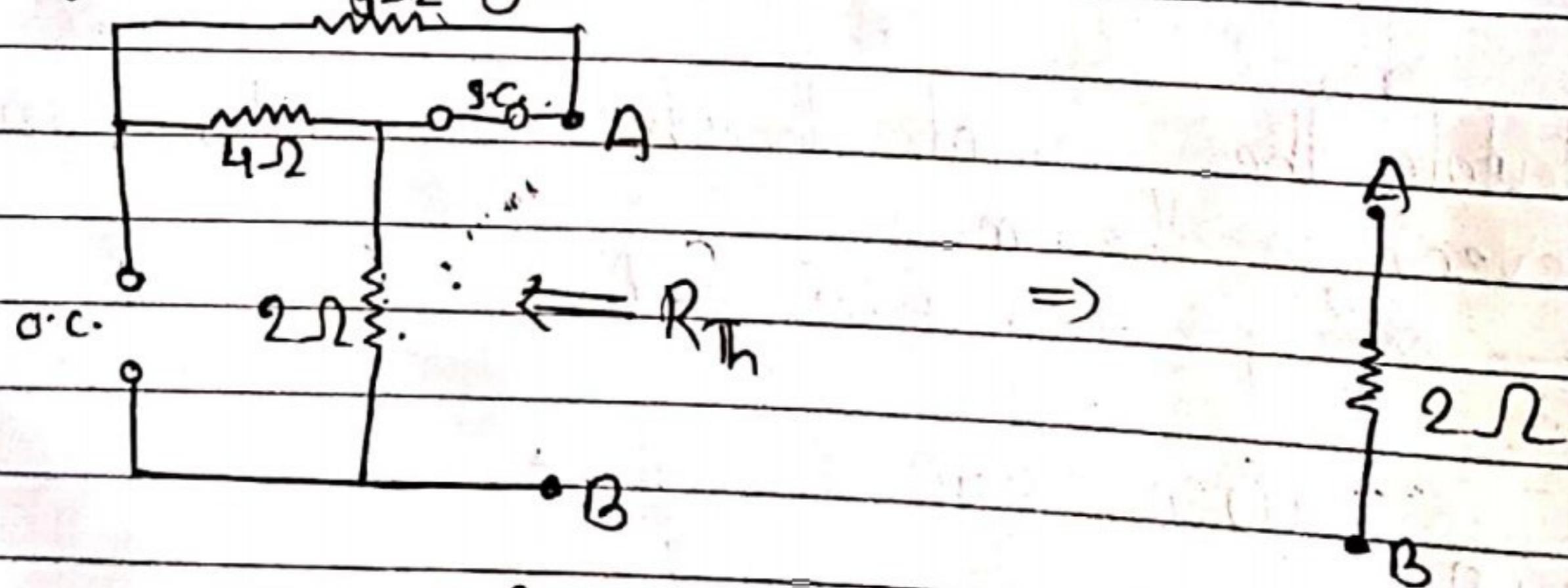

$$\therefore R_{Th} = 2\Omega$$

Step -2: Finding the ~~for~~ V_{Th} :

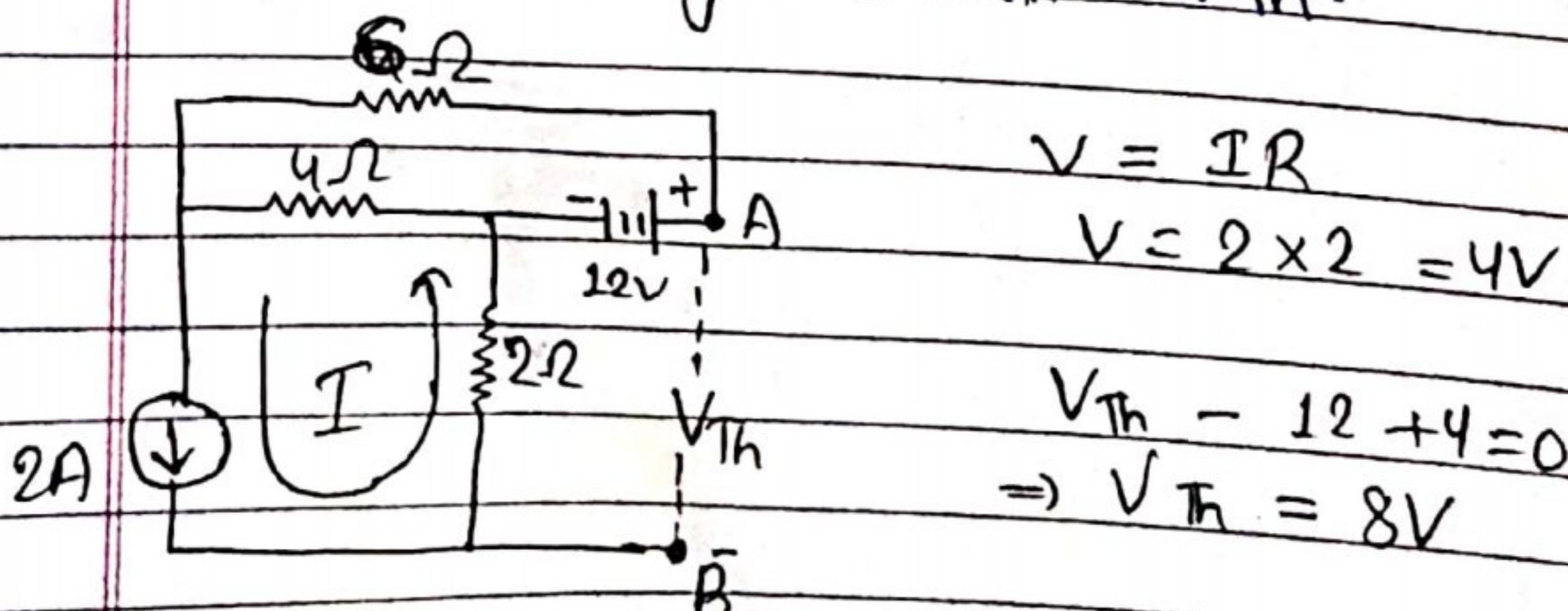


$$V = IR$$

$$V = 2 \times 2 = 4V$$

$$\begin{aligned} V_{Th} - 12 + 4 &= 0 \\ \Rightarrow V_{Th} &= 8V \end{aligned}$$


Step - 3: Thevenin's equivalent ckt:

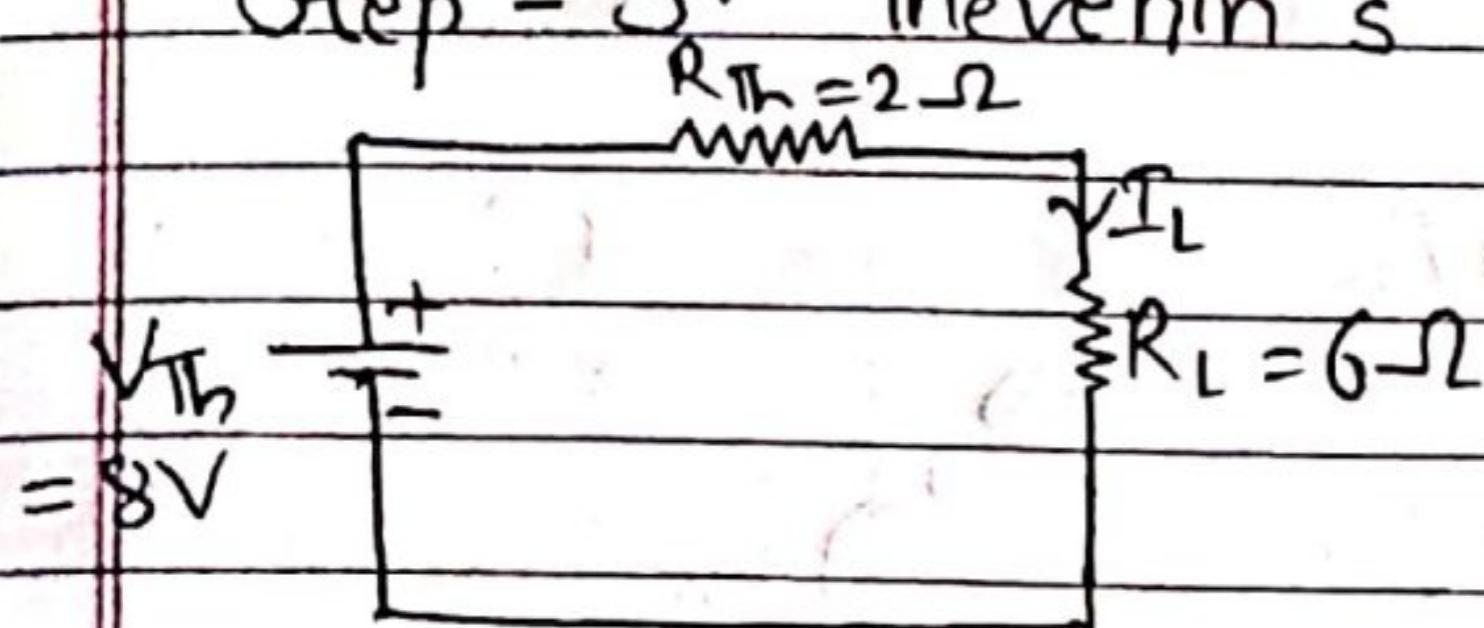


$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{8}{2 + 6}$$

$$\therefore I_L = 1 \text{ amp}$$

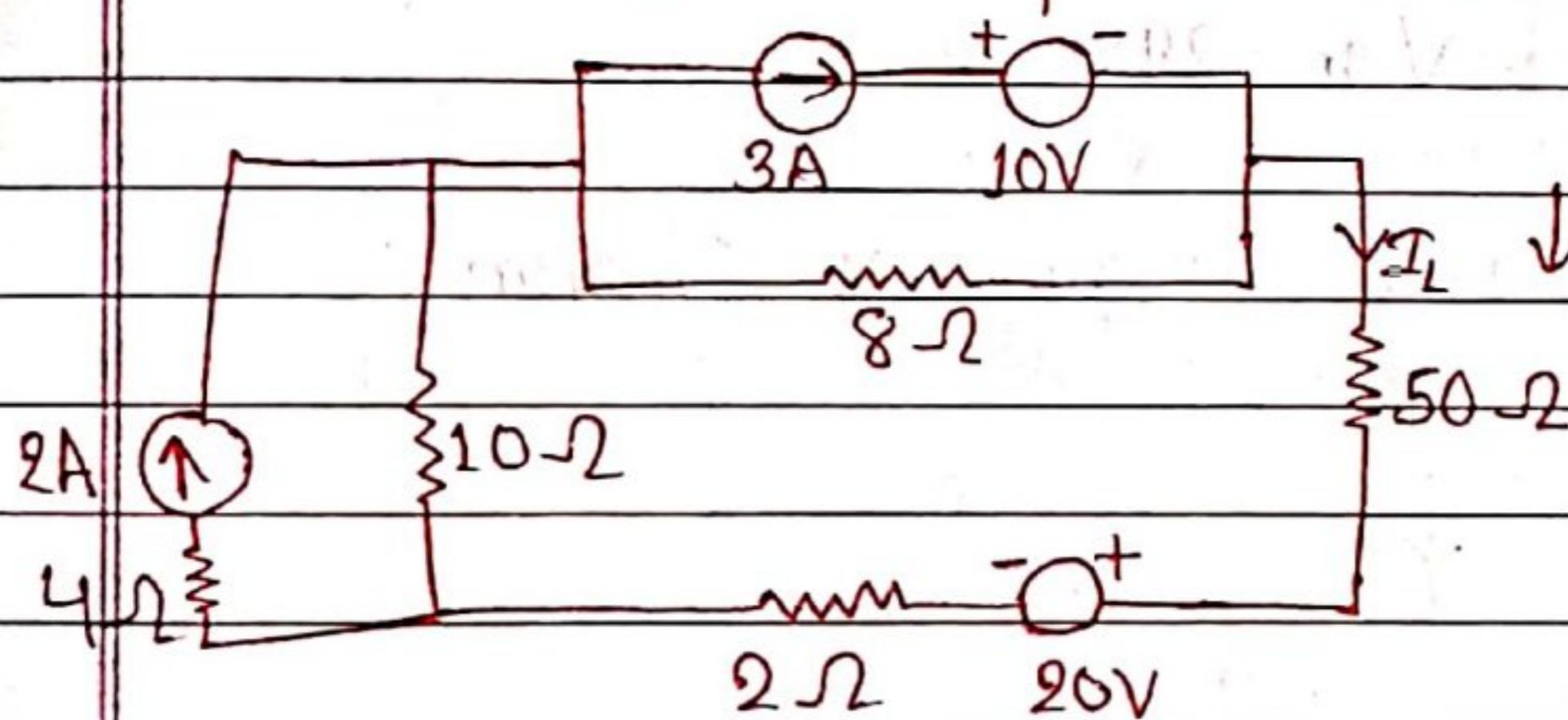Q.6) For the ckt shown in fig 'A' compute the load current (I_L) using the Thevenin's theorem and determine the value of load for which power transfer is maximum.




Here, Step - I :- finding R_{Th} :

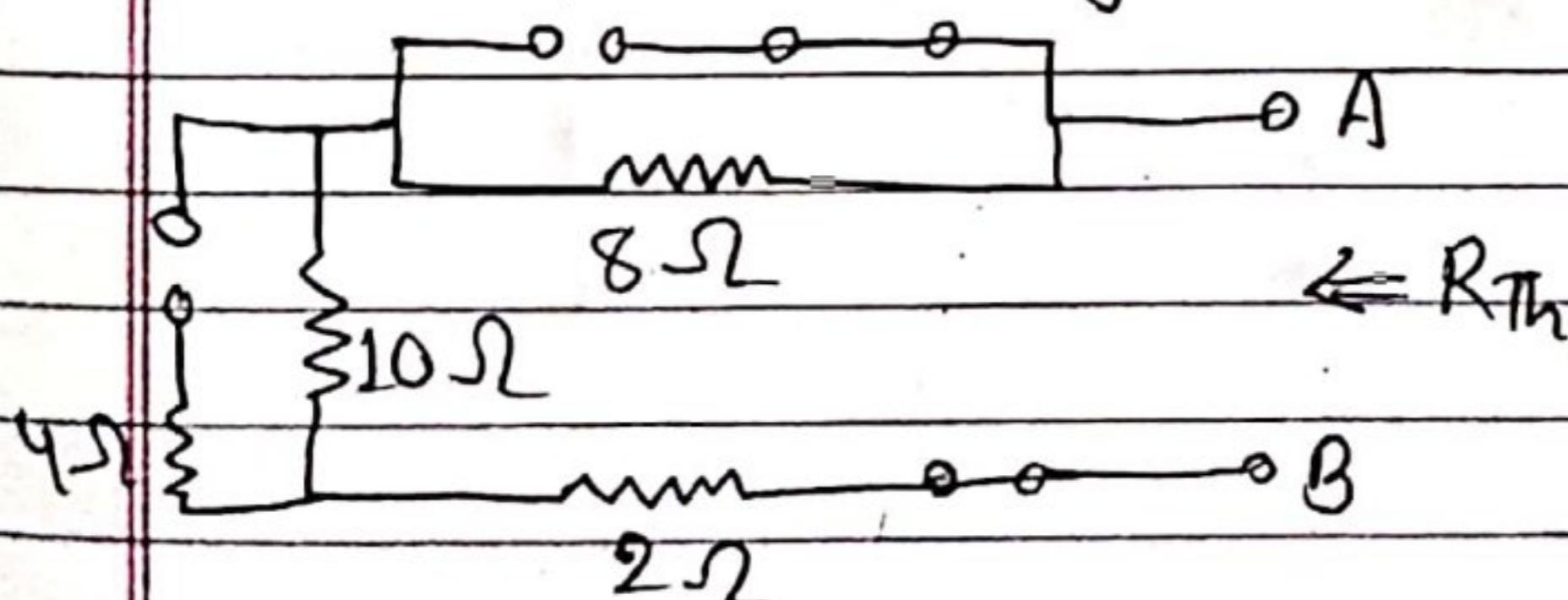

$$R_{Th} = 8\Omega + 10\Omega + 2\Omega$$

$$= 20\Omega$$

Step - II: finding V_{Th} :

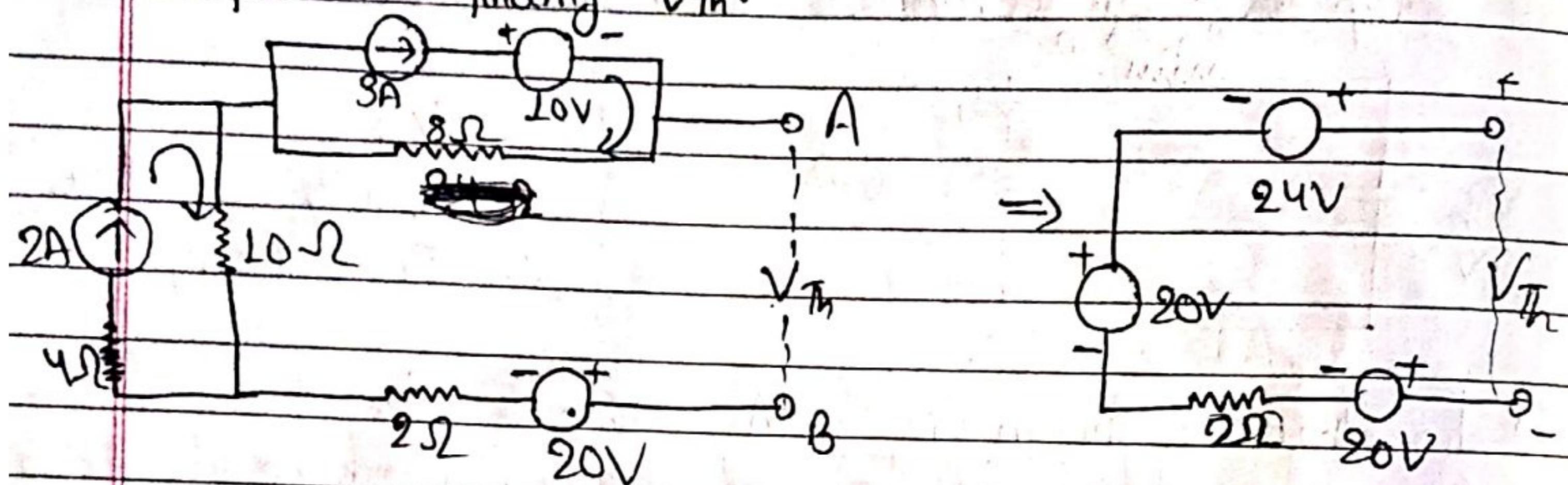


$$V_{Th} = 24 - 20 + 20 = 0$$

$$\Rightarrow V_{Th} = 24V$$

Step - 3: Thevenin's equivalent Theorem

$$R_{Th} = 20 \Omega$$

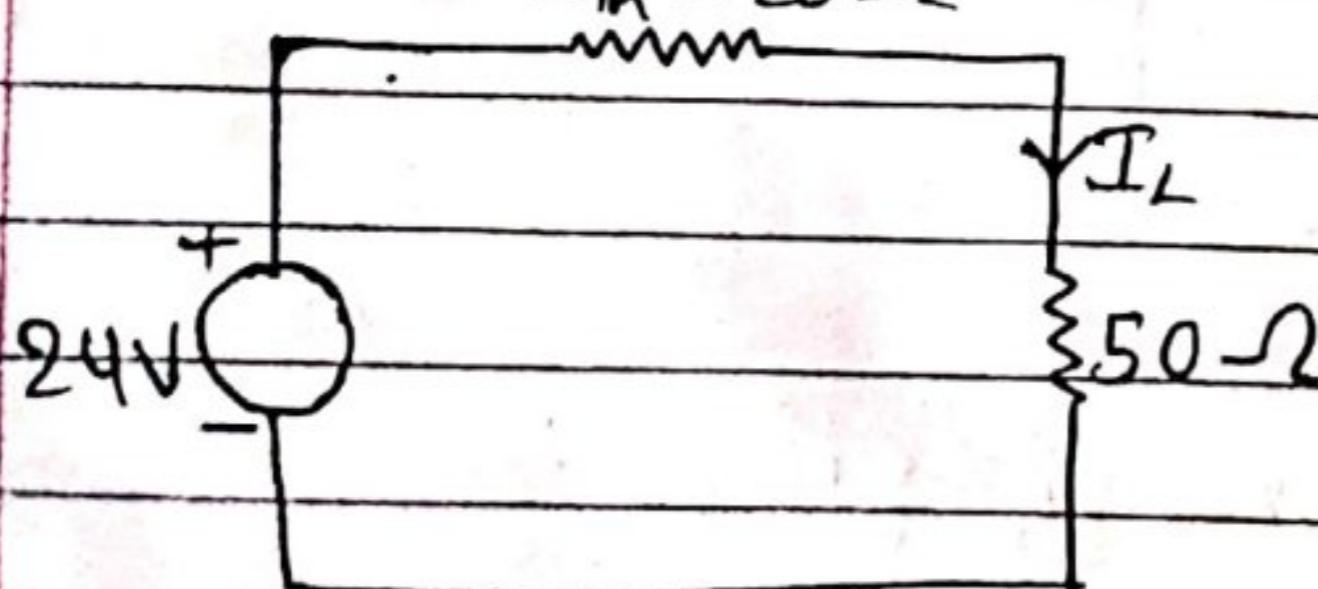

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$


$$= \frac{24}{20 + 50}$$

$$= 0.34A$$


$$P_{max} = (0.34)^2 \times 50$$

$$= 5.78 \text{ watt}$$

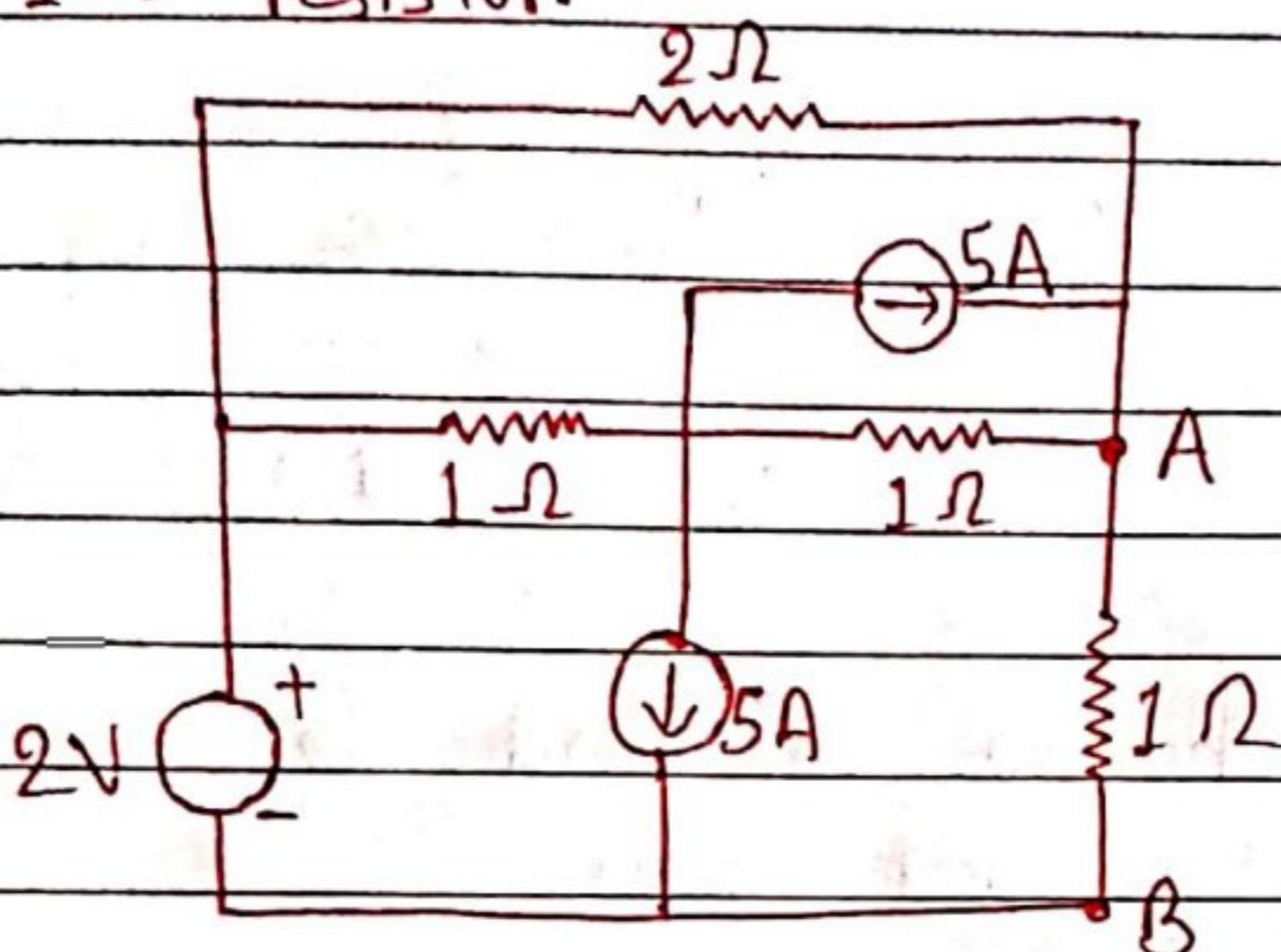Q.7) By Thevenin's Theorem find the load current (I_L) through 1Ω resistor.




Here, Step - I:

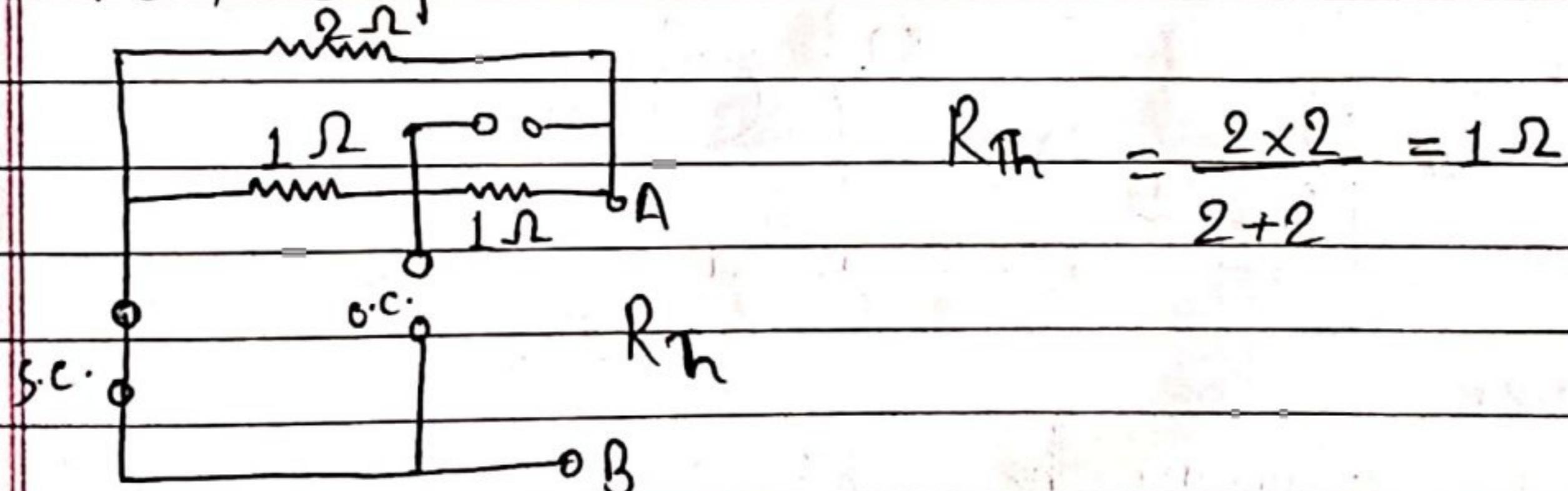

$$R_{th} = \frac{2 \times 2}{2+2} = 1\Omega$$

Step - II: finding V_{th} :

Node - a:

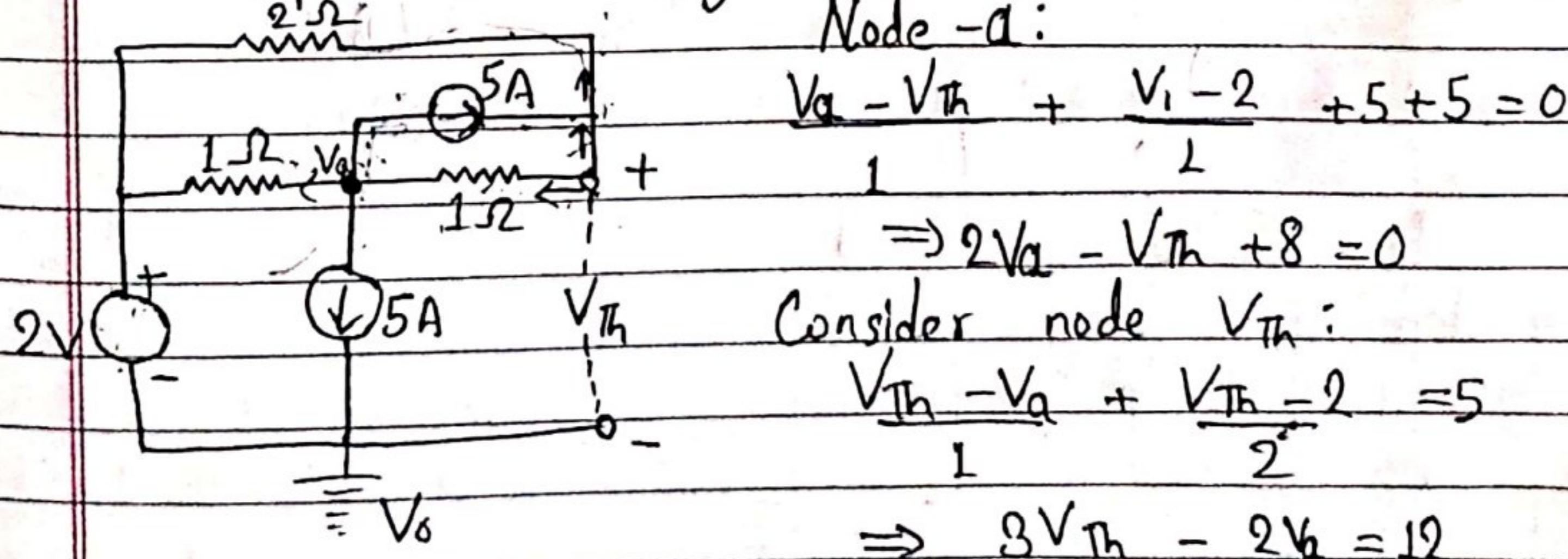

$$V_a - V_{th} + \frac{V_0 - 2}{1} + 5 + 5 = 0$$

$$\Rightarrow 2V_a - V_{th} + 8 = 0$$

Consider node V_{th} :


$$\frac{V_{th} - V_a}{1} + \frac{V_{th} - 2}{2} = 5$$

$$\Rightarrow 3V_{th} - 2V_a = 12$$

$$V_{th} = 2V$$

$$V_a = -3V$$

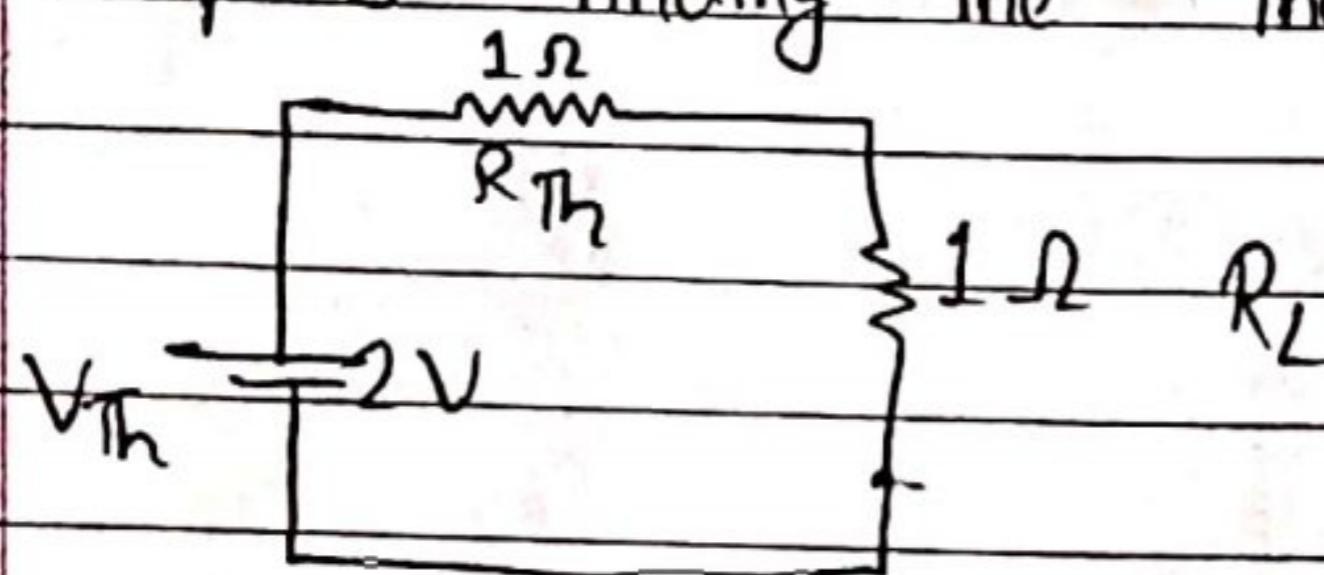
Step - 3: Finding the Thevenin's eq. ckt:



$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{2}{1+1}$$


$$\therefore I_L = 1A$$

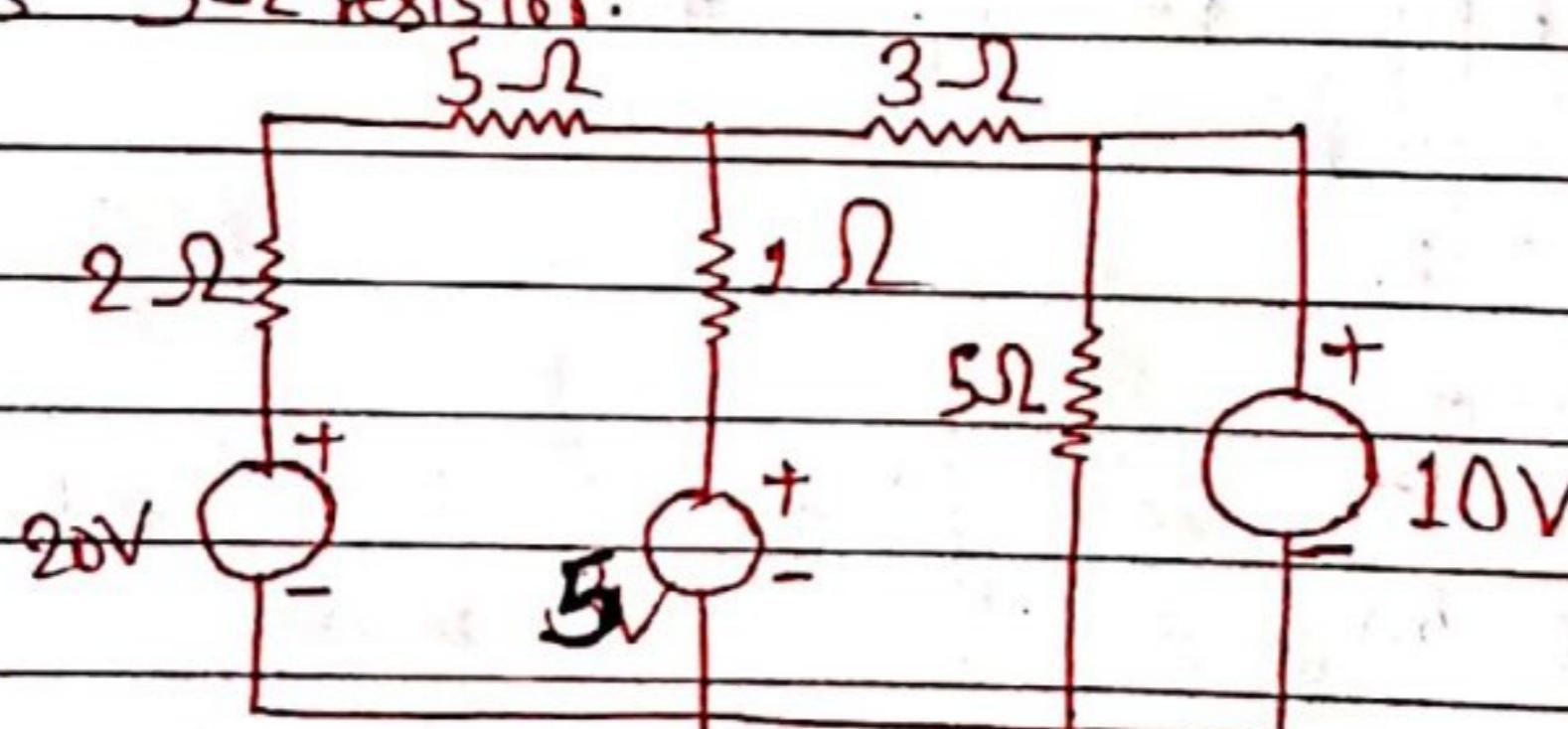Q. 8) State the Thevenin's Theorem and find the load current across 3Ω resistor.



Here,


Step - I : finding the R_{Th} :

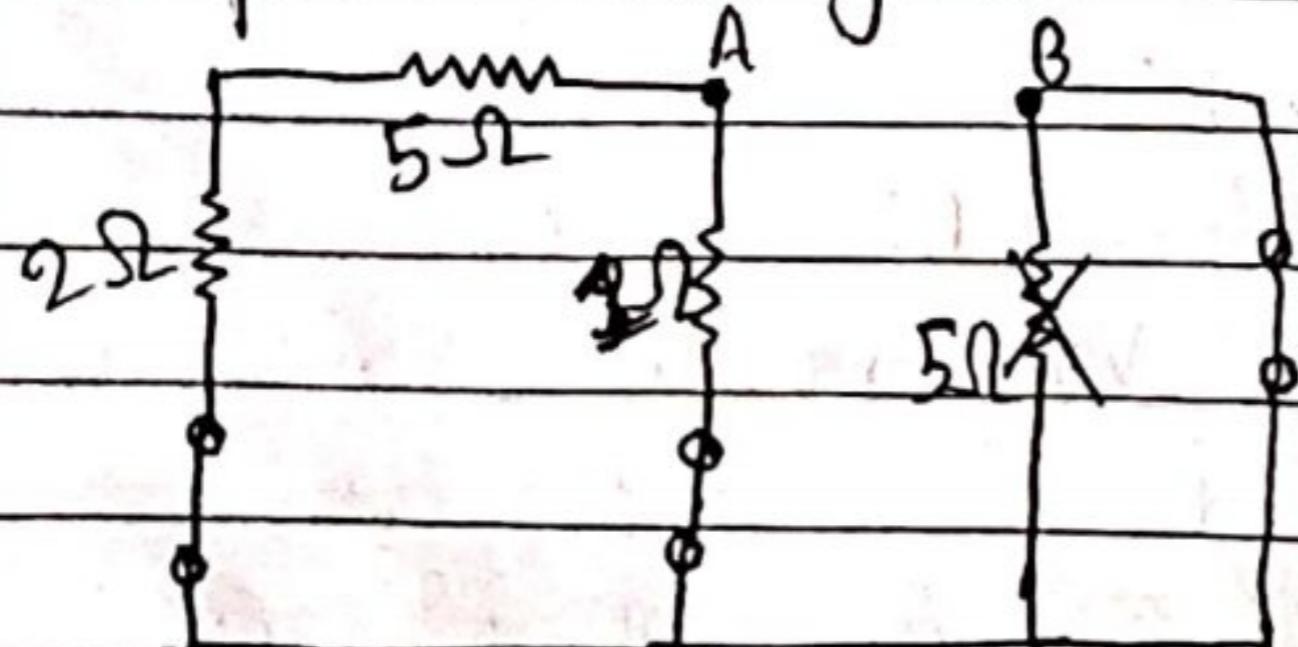

$$R_{Th} = 7 \parallel 1$$

$$= 0.875 \Omega$$

Step - II : finding V_{Th} :

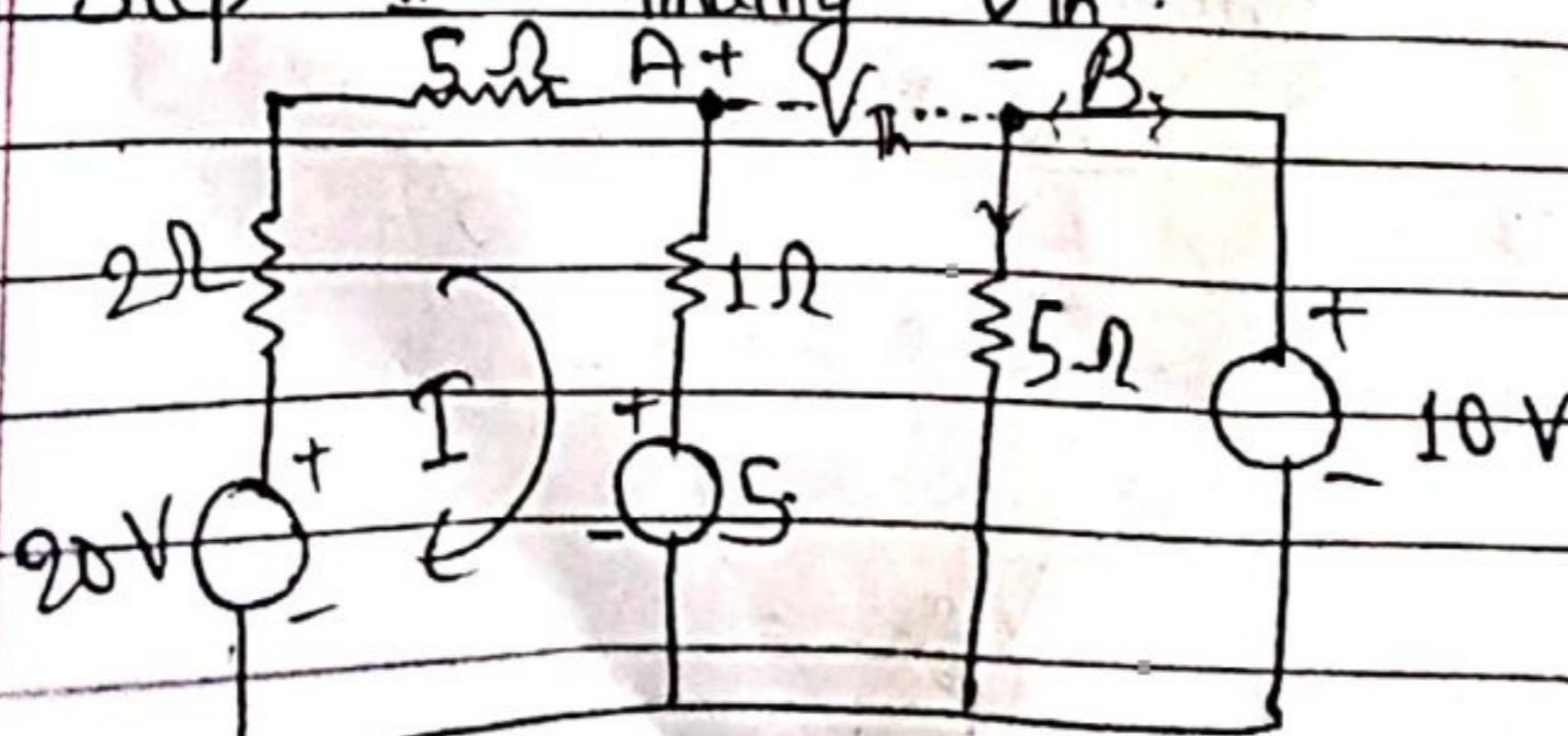

Consider LHS mesh:

$$20 - 2I - 5I - I - 5 = 0$$

$$\Rightarrow 15 = 8I$$

$$\Rightarrow I = 1.875A$$

$$V_A = 20 - 7 \times 1.875$$

$$= 20 - 13.125$$

$$= 6.875V$$

$$V_B = 10V$$


$$\therefore V_{Th} = V_B - V_A$$

$$= 10 - 6.875$$

$$= 3.125V$$

Step-3: Finding the Thevenin's eq. ckt:

$$R_{Th} = 0.875\Omega$$

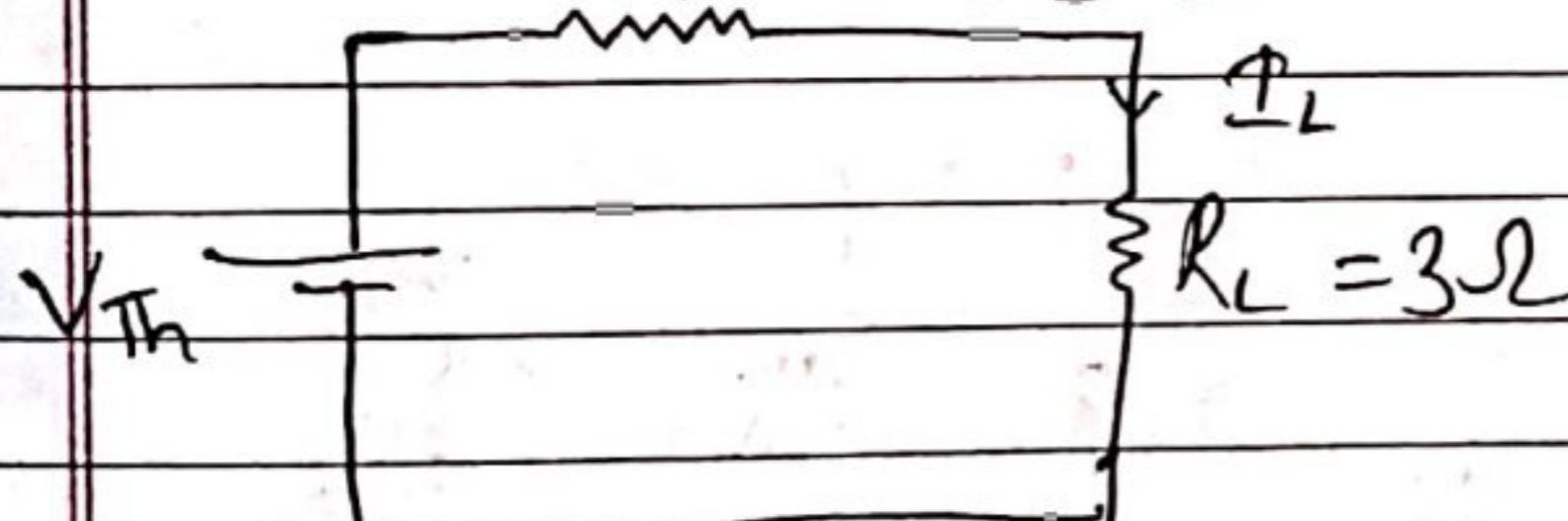

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{3.125}{0.875 + 3}$$

$$\therefore I_L = 0.806A$$

→ Any two terminal linear circuit containing a large no. of voltage and/or current sources and resistors can be replaced by a simple equivalent ckt containing a single current source in parallel with a resistor.

~~(Q.9)~~

Norton's Theorem

It states that "Any circuit with the voltage source, resistance (impedance) and open output terminal can be replaced by single current source in parallel with single resistance, where the value of current source is equal to the current passing through the short ckt output terminals and the value of current source is equal to resistance (impedance) is equal to resistance seen into the output terminal."


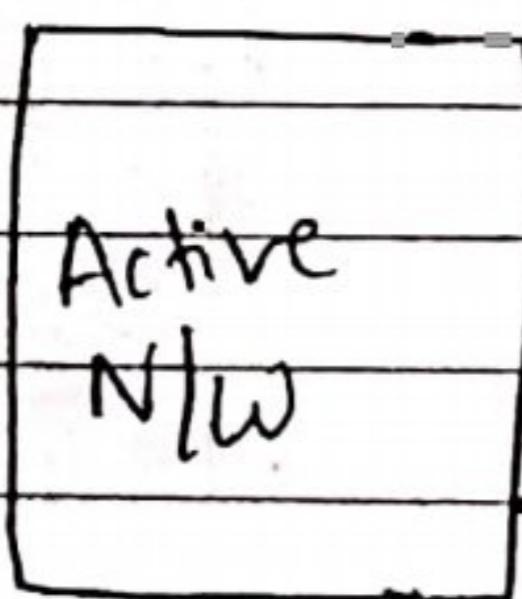


fig (a)

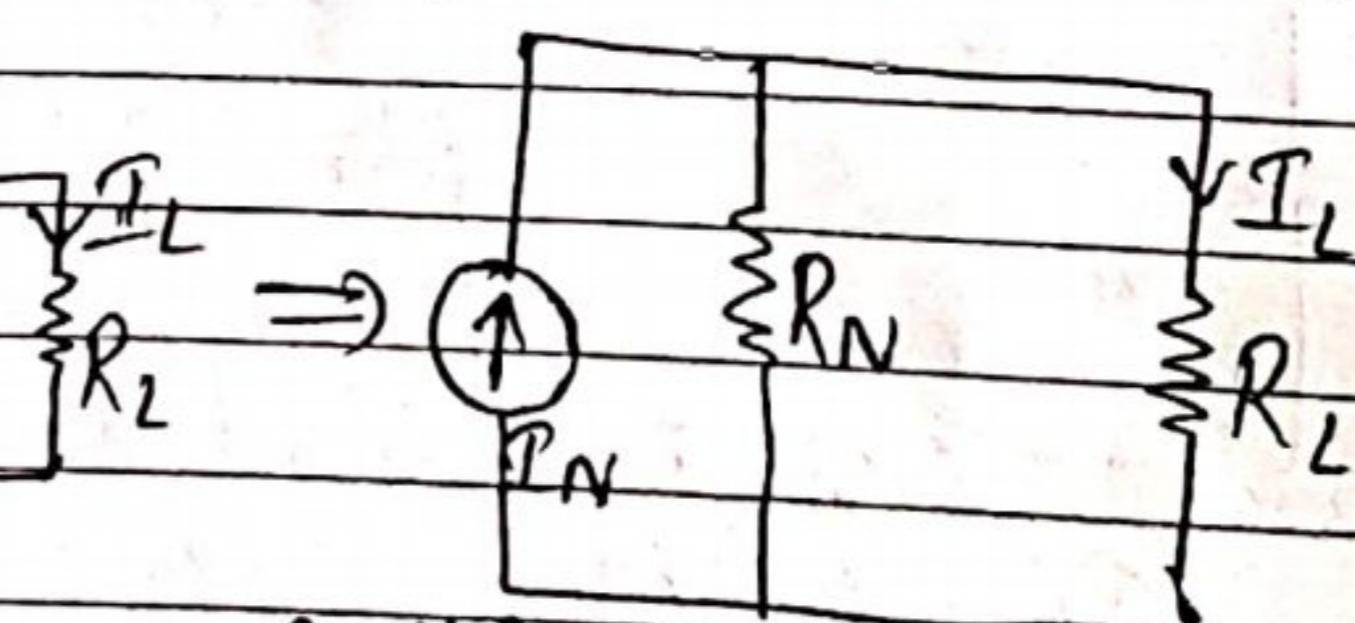

fig(b) - Equivalent N/w

or Norton's experiment


Procedure

- Short the branch through which the current is to be measured.
- Obtain the current through the short ckt branch (N/w techniques).
- Calculate the R_N (eq. Norton resistance).
- Draw the Norton's eq. ckt.
- Reconnect the branch resistance.


$$I_N = I_{S.C.}$$

$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$


Note:

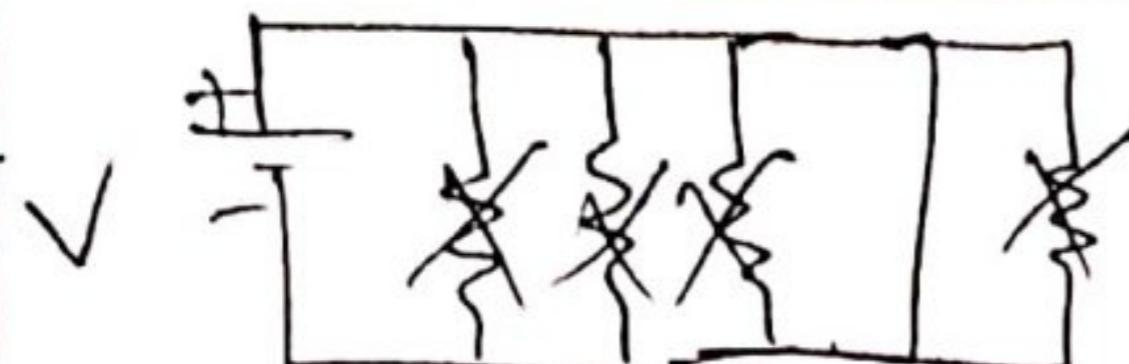

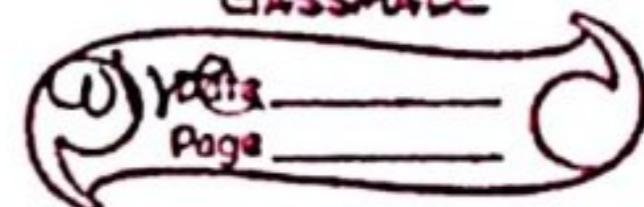11 ckt shorts when connected
with thick metallic




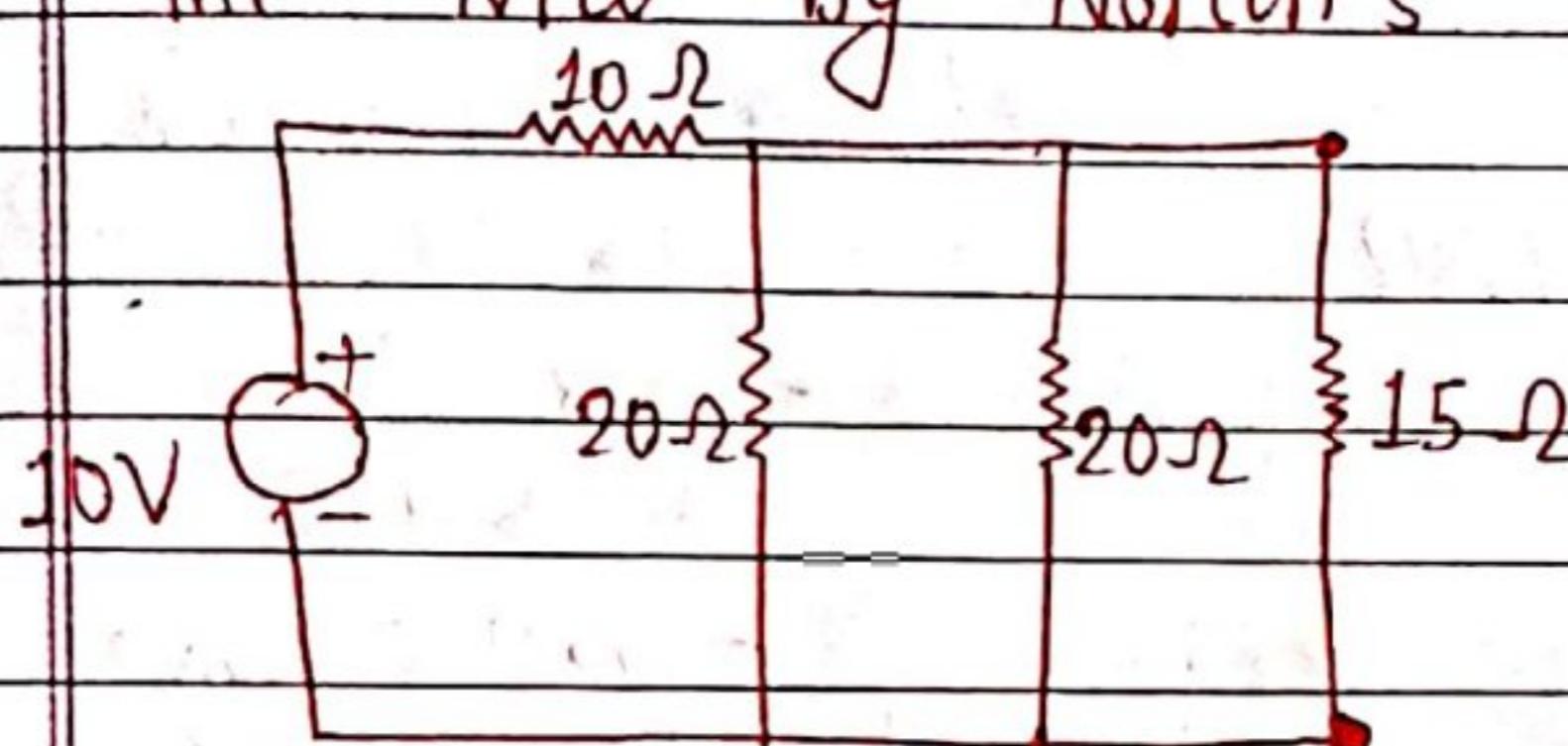Q1) Determine the current I_L through 15Ω resistor in the N/w by Norton's theorem.



solution:

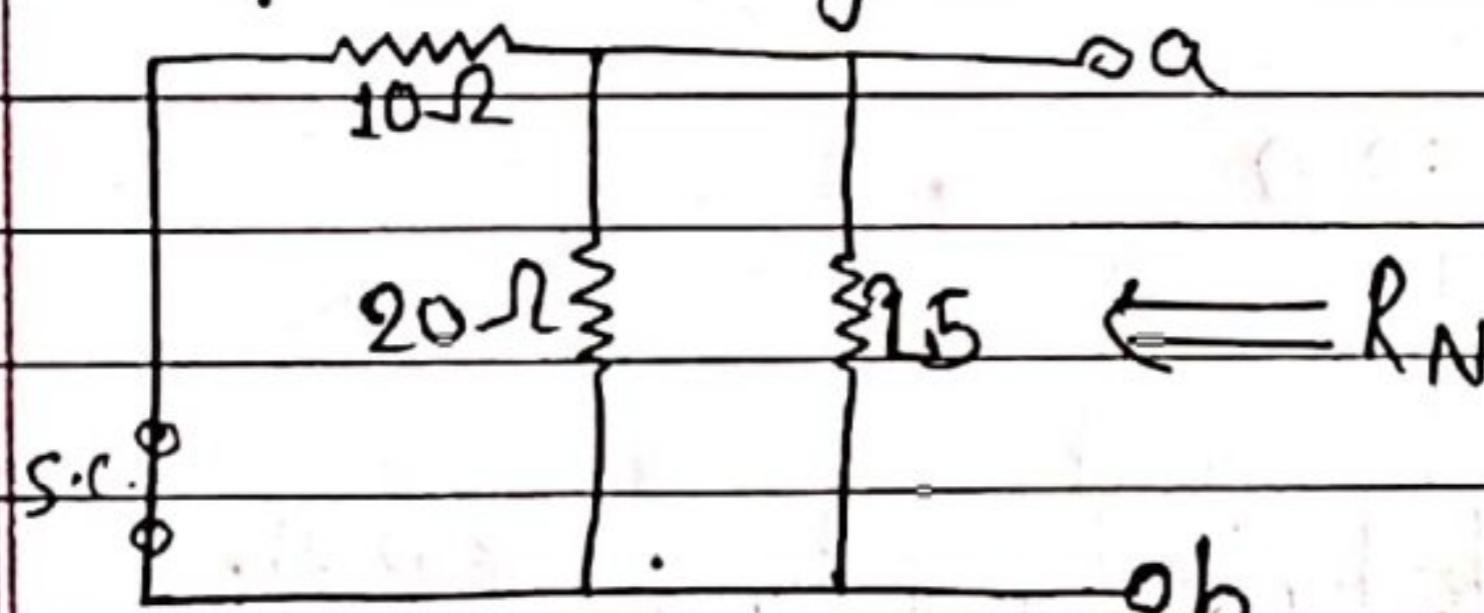Step-1: finding Norton's resistance (R_N)




$$\frac{1}{R_N} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\Rightarrow \frac{1}{R_N} = \frac{1}{10} + \frac{1}{20} + \frac{1}{20}$$

$$\Rightarrow R_N = 5\Omega$$

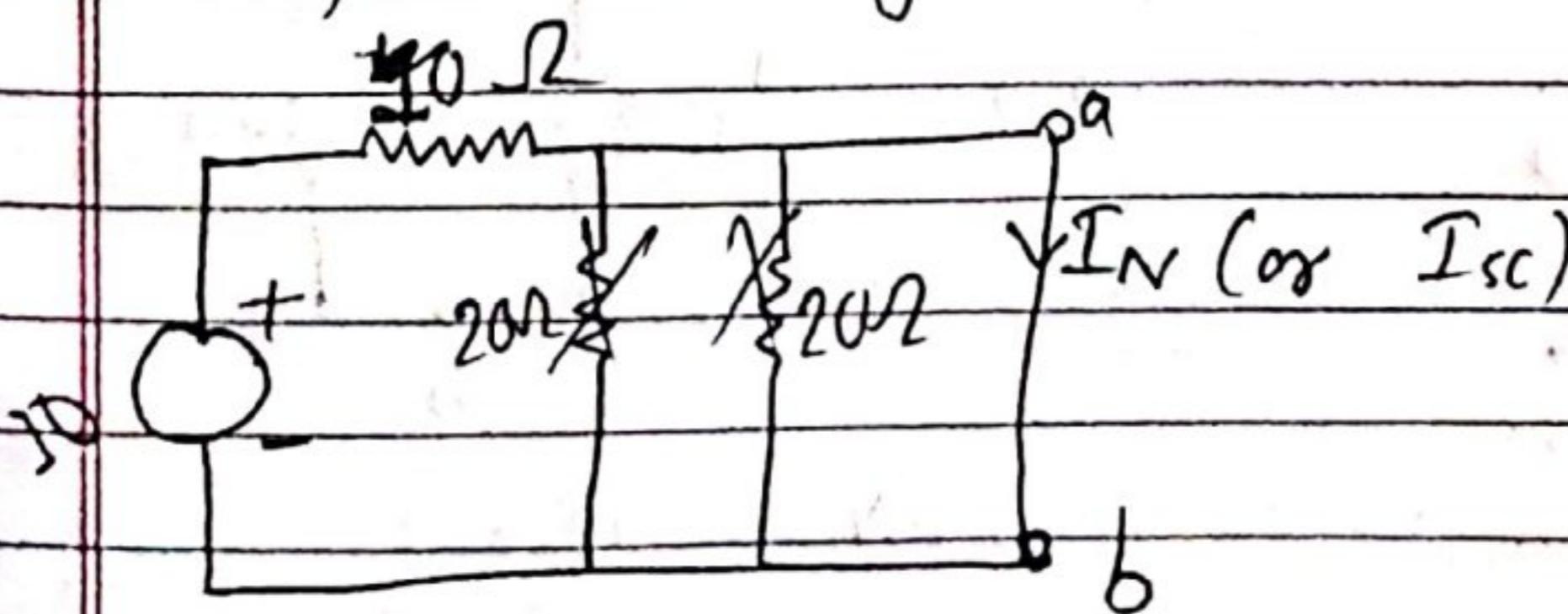
Step-2: finding the Norton's current (I_N or I_{sc})



$$I_N = \frac{V}{R} = \frac{10}{10}$$

$$\Rightarrow I_N = 1 \text{ amp}$$


Now Norton's eq. ckt:

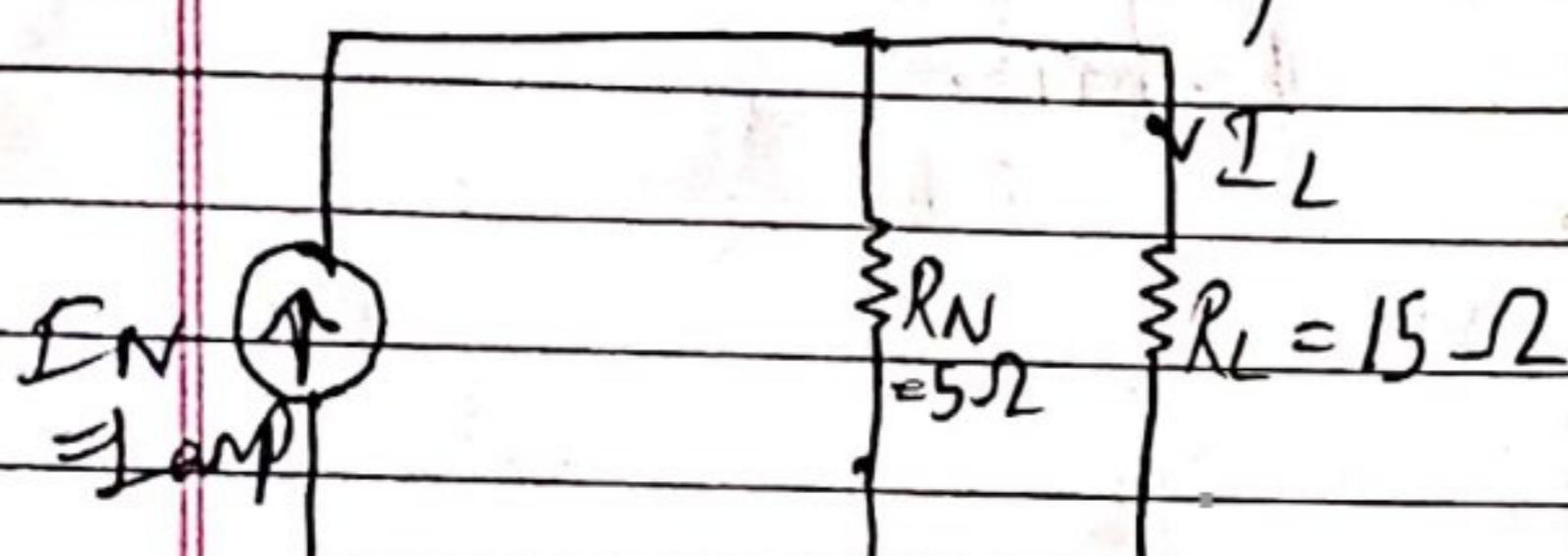



$$\begin{aligned} \mathcal{E}_L &= I_N \times R_N \\ &= 1 \times 5 \\ &= 5 \text{ V} \end{aligned}$$

$$= 0.25 \text{ amp}$$

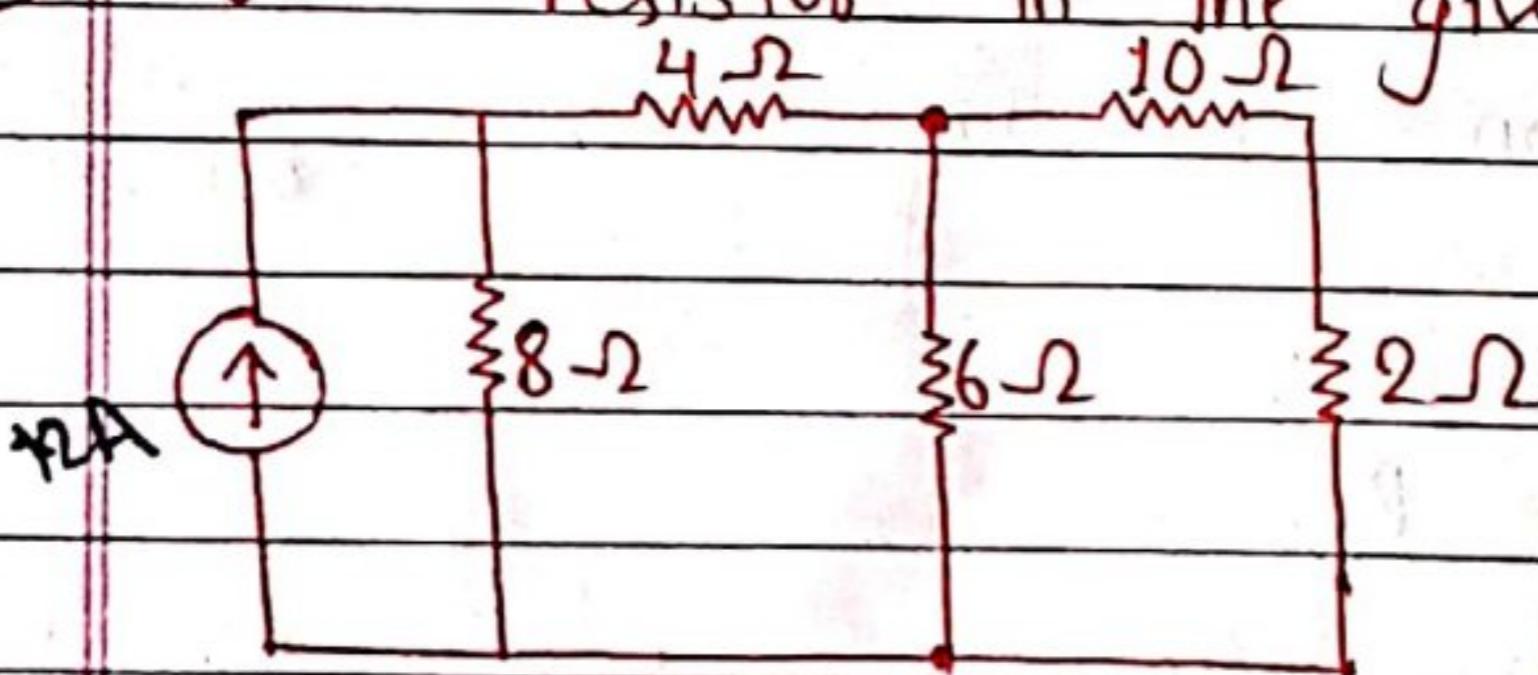~~PV~~ Q2) Use the Norton's theorem to calculate the current in 6Ω resistor in the given ckt:




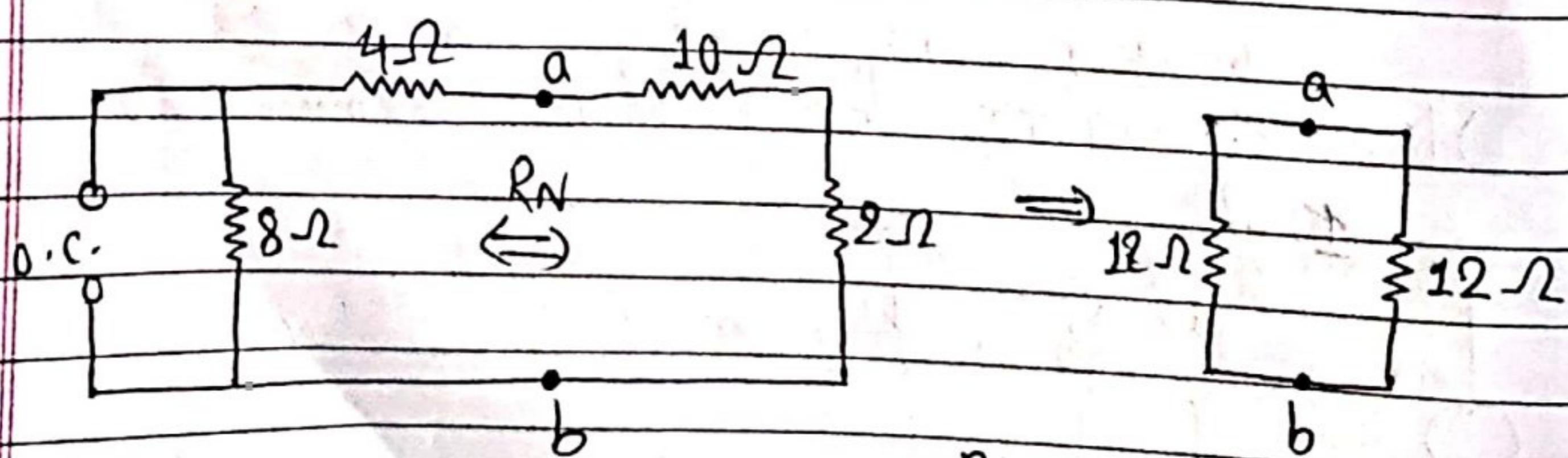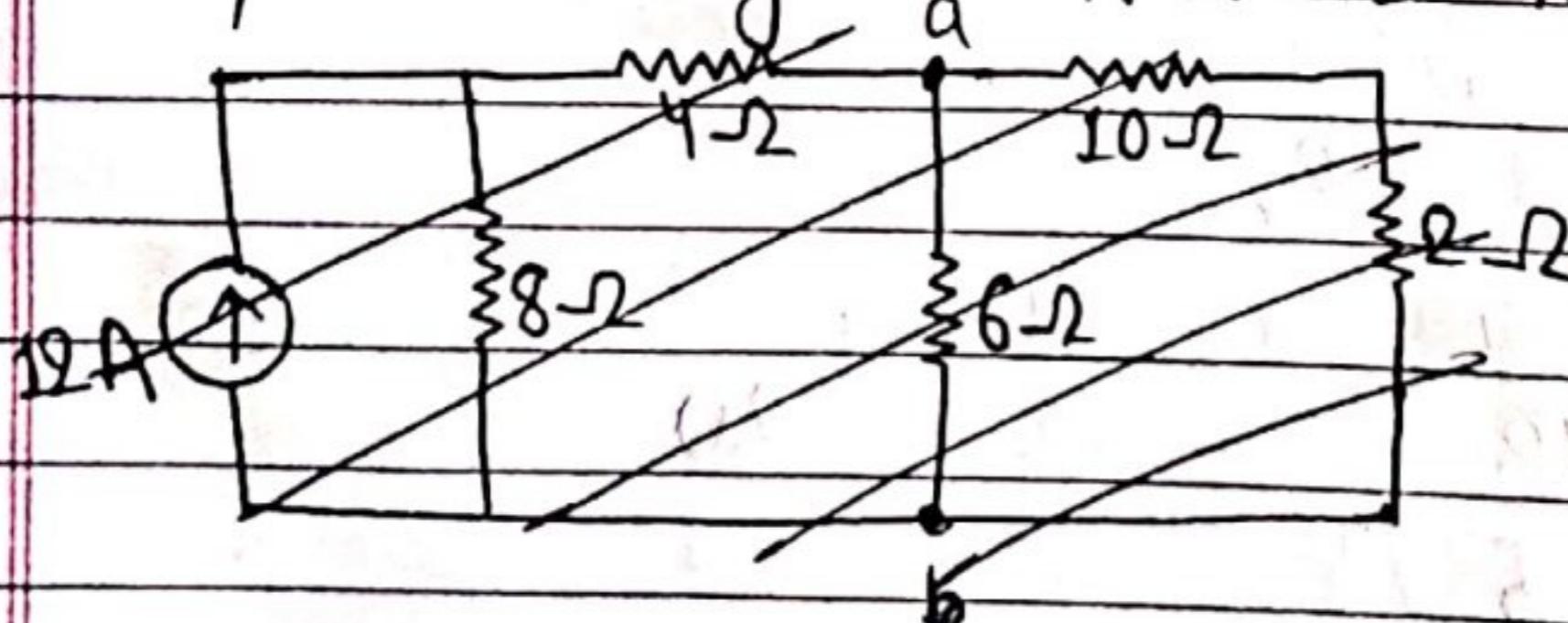Step-1: finding the Norton's resistance (R_N):




$$R_N = \frac{12 \times 12}{12 + 12} = 6\Omega$$

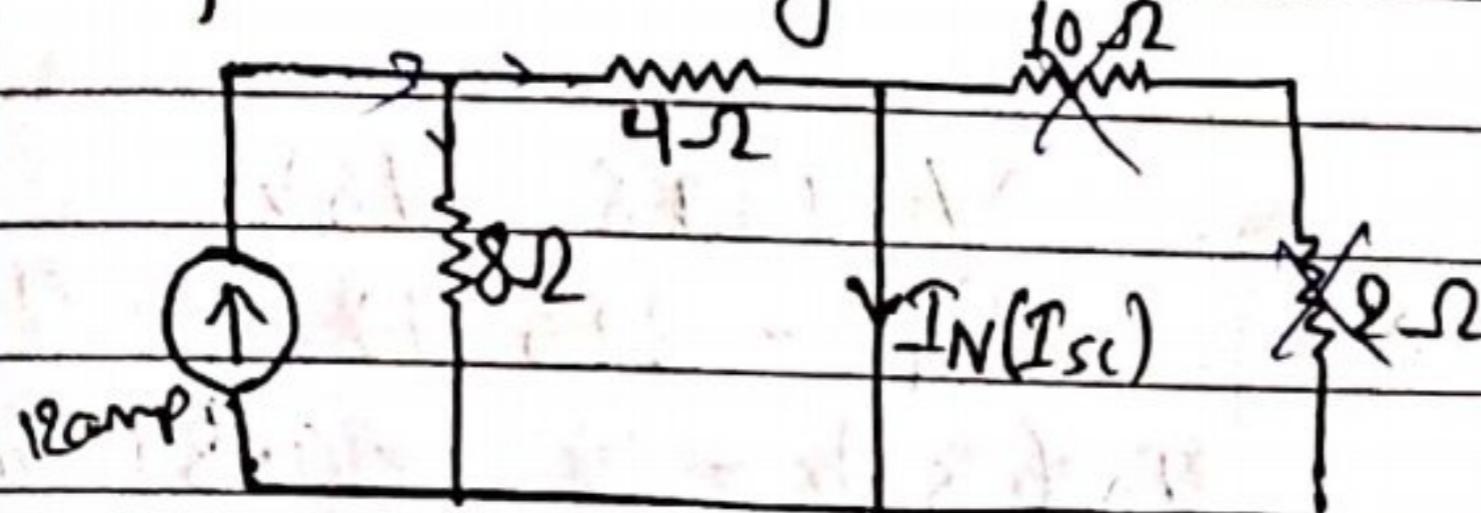Step - 2: finding the Norton's current (I_N) or I_{sc}




$$I_N = 12 \times \frac{8}{8+4} \\ = 8 \text{ amp}$$


Step - 3: Norton's equivalent ckt:

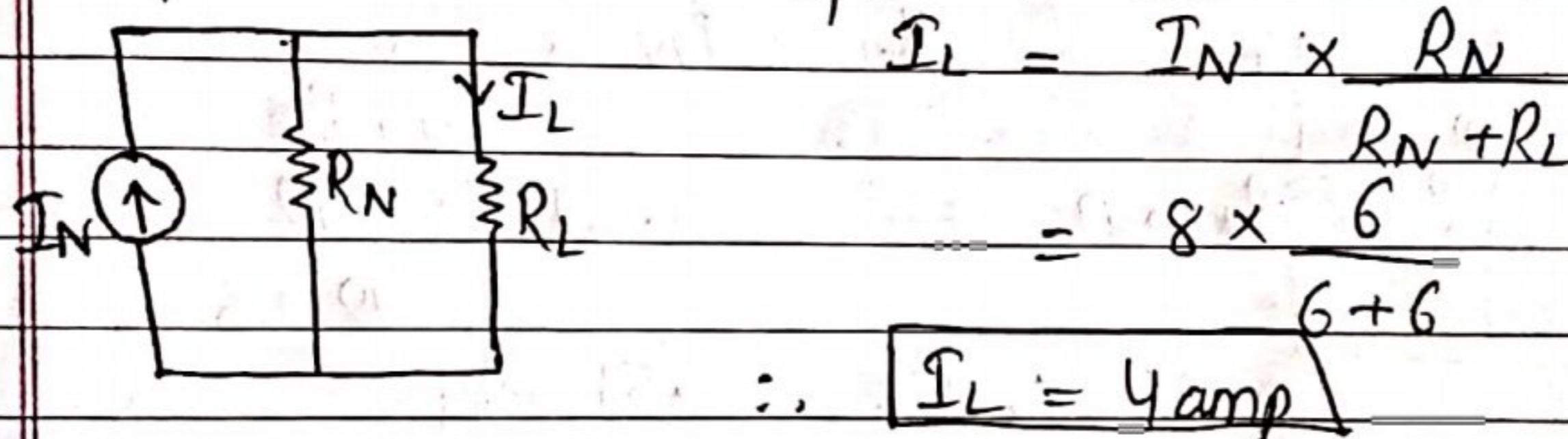

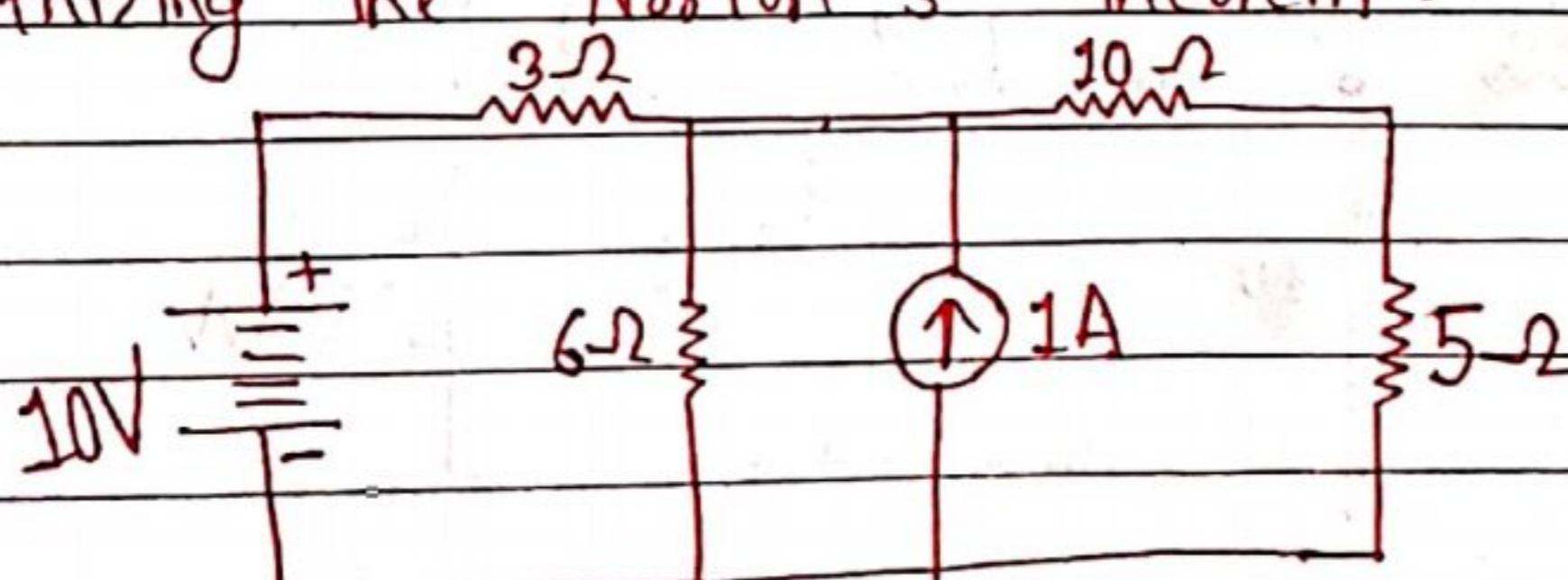Q.3: find the current in 5Ω resistor, for the given ckt
PU utilizing the Norton's theorem:




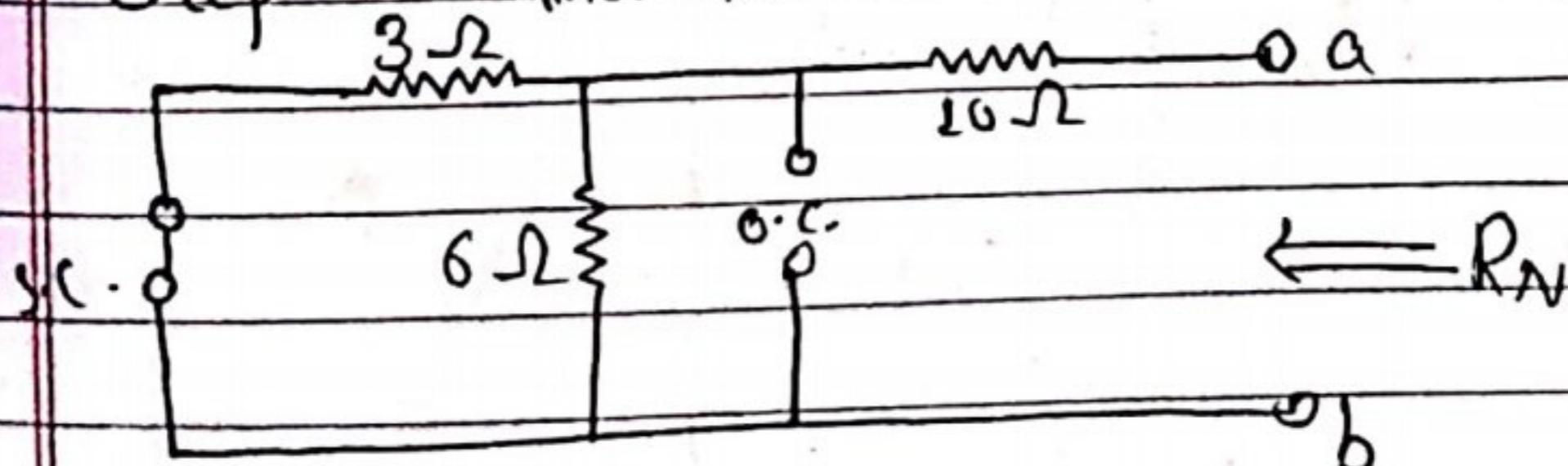Step - 1: find the R_N (Norton resistance)



$$R_N = (3//6) + 10 \\ = 19 \Omega$$

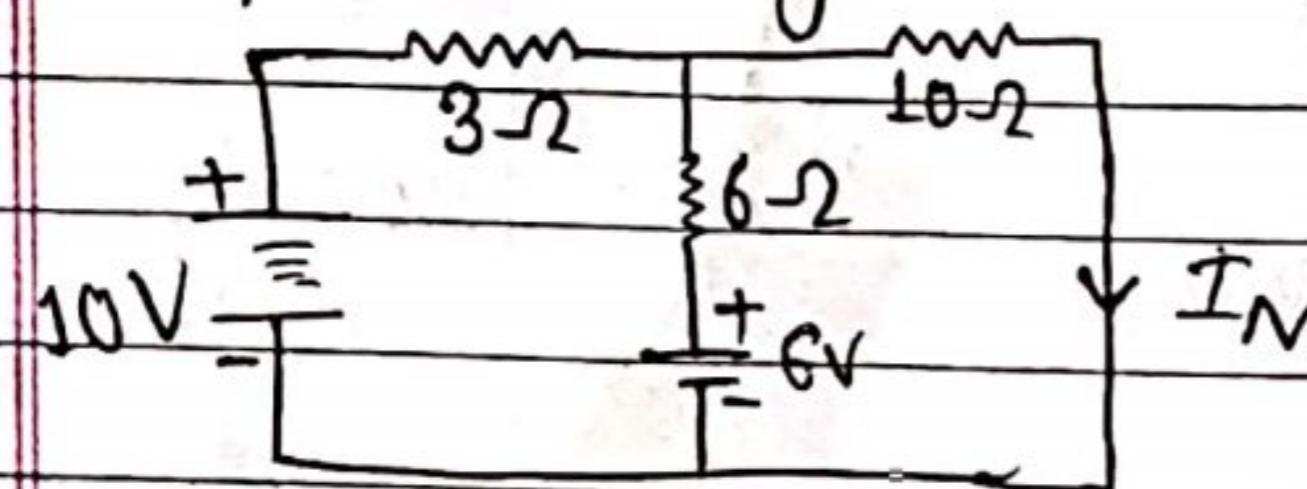Step - 2 : finding the Norton's current (I_N) or I_{SC} :




$$V = 10 + 6 = 16V$$

$$R_T = 3 + 6 + 10 = 19\Omega$$

$$I_N (I_{SC}) = \frac{16}{19} = 0.84 \text{ amp}$$

Step - 3: Norton's eq. ckt:

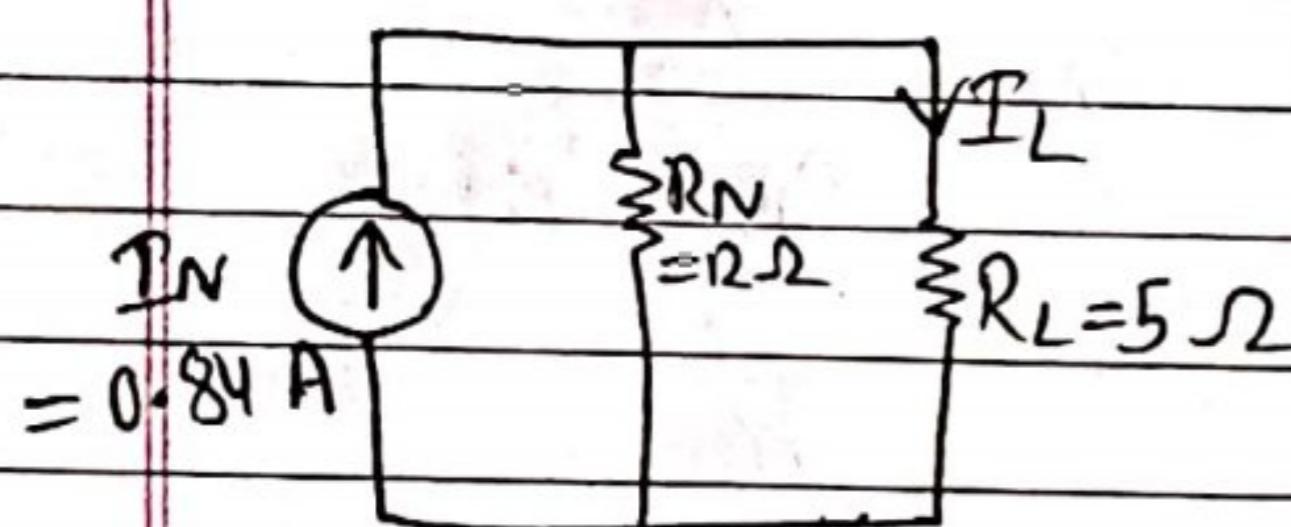


$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$



$$= 0.84 \times \frac{12}{12 + 5}$$

$$\therefore I_L = 0.59 \text{ amp}$$

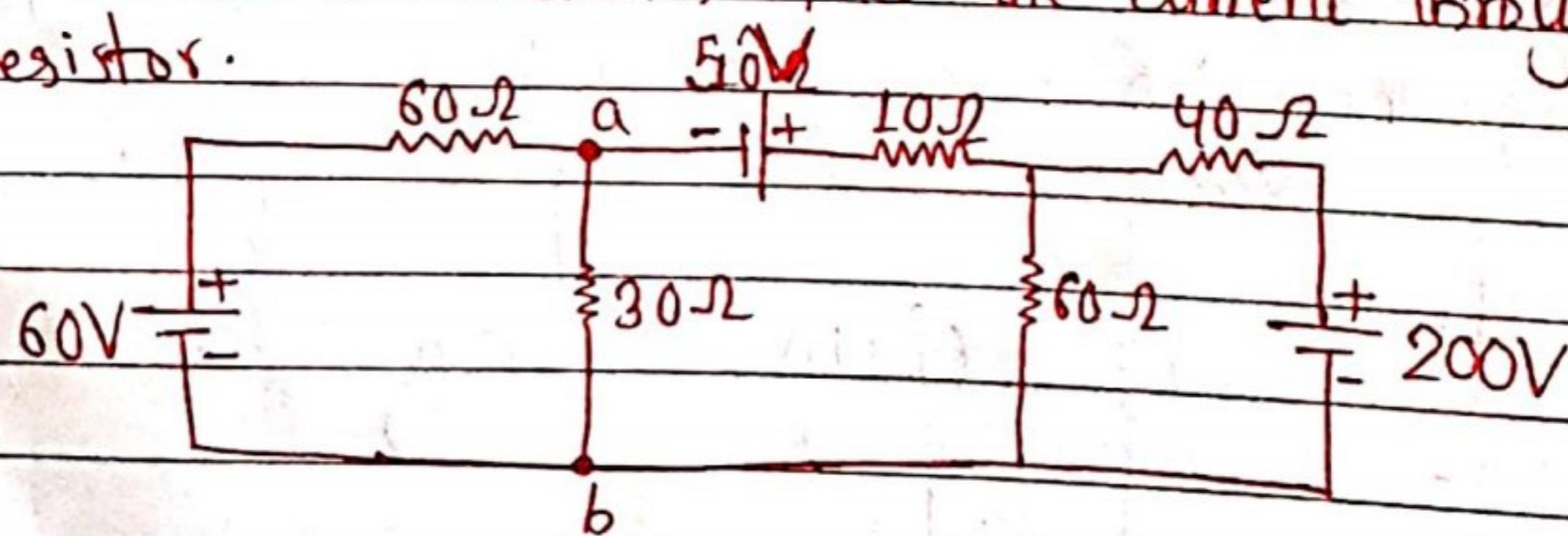Q. 4) By Norton's Theorem, find the current through 30Ω resistor.




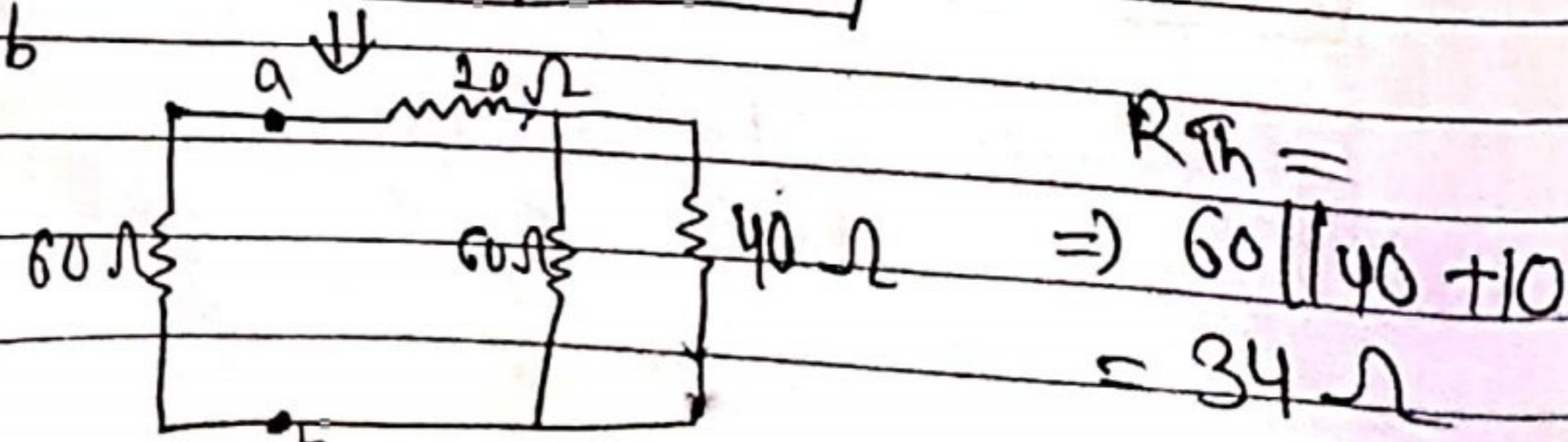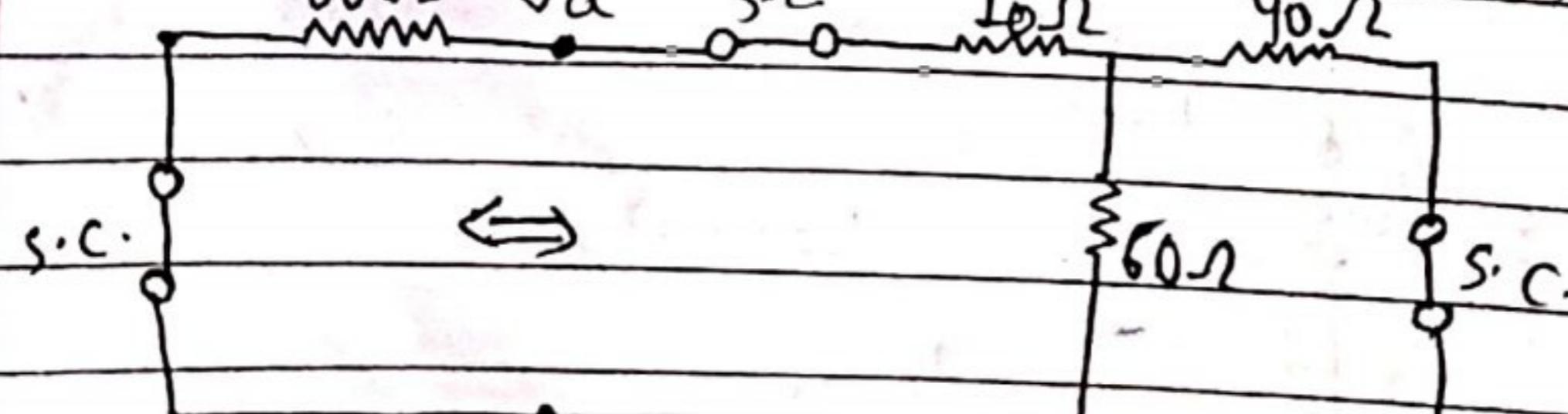Step - 1: finding the R_N (Norton's resistance)



$$\begin{array}{c}
 \text{a} \\
 \text{---} \\
 | \quad | \\
 60\Omega \quad 34\Omega \\
 | \quad | \\
 \text{b}
 \end{array}
 \quad
 \begin{aligned}
 & 60 \parallel 34 \\
 & = 21.70\Omega
 \end{aligned}$$

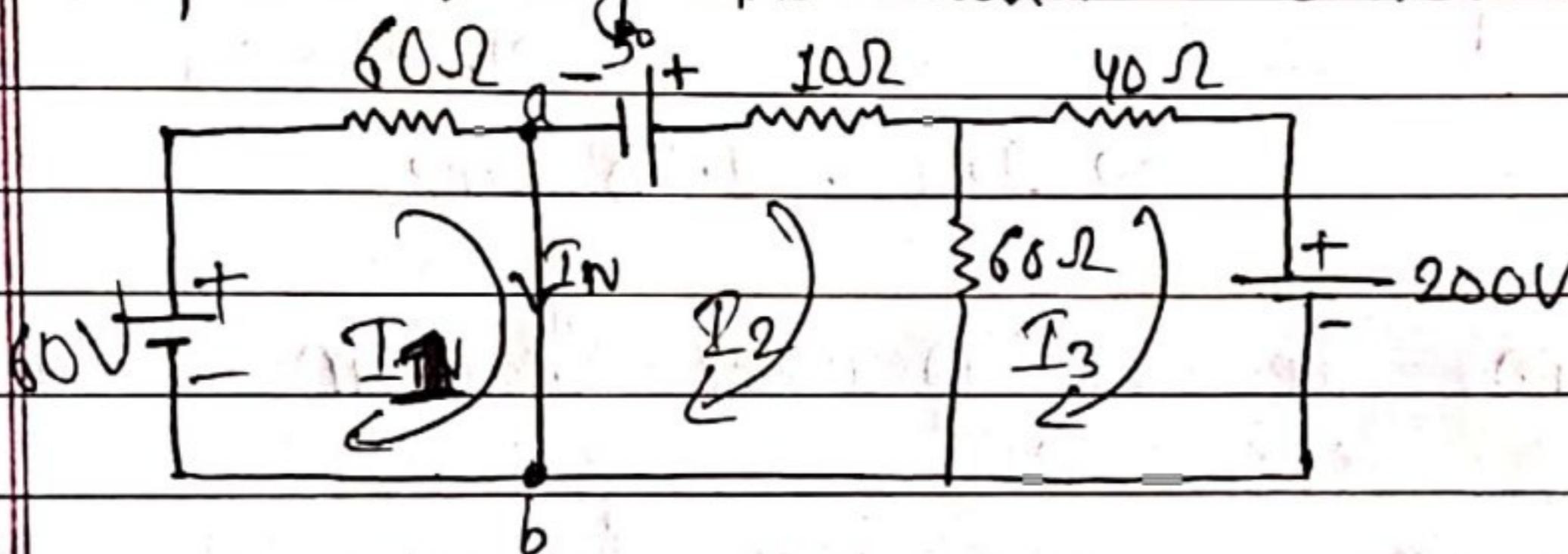Step-2: finding the Norton's current (I_N or I_{sc})



Loop-1 or mesh-1:

$$60 - 60I_1 = 0$$

$$\Rightarrow I_1 = 1 \text{ amp} \quad \textcircled{1}$$

Loop-2:

$$50 - 10I_2 - 60(I_2 - I_3) = 0$$

$$\Rightarrow 50 - 70I_2 + 60I_3 = 0$$

$$\Rightarrow 70I_2 - 60I_3 = 50 \quad \textcircled{2}$$

Loop-3:

$$-200 - 60(I_3 - I_2) - 40I_3 = 0$$

$$\Rightarrow -100I_3 + 60I_2 = 200 \quad \textcircled{3}$$

Solving,

$$I_1 = 1 \text{ amp}$$

$$\therefore I_N = I_1 - I_2$$


$$I_2 = -2.05 \text{ amp}$$

$$= 1 - (-2.05)$$

$$I_3 = -3.23 \text{ amp}$$

$$\therefore I_N = 3.05 \text{ amp}$$

Step-3 : Norton's eq. ckt :

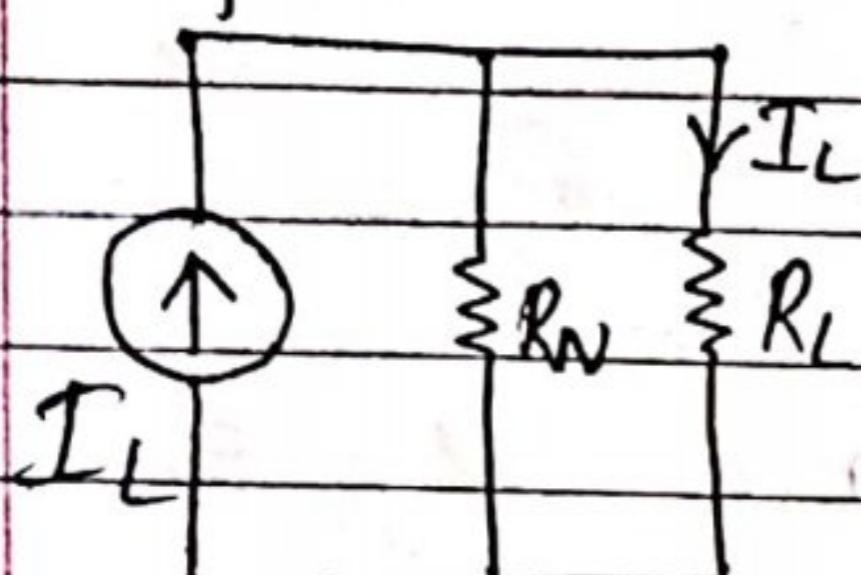

$$\begin{aligned} P_L &= I_N \times R_N \\ &\quad R_N + R_L \\ &= 3.05 \times 21.70 \\ &\quad 21.70 + 30 \end{aligned}$$


$$\Rightarrow I_L = 1.28 \text{ amp}$$

~~most imp~~

Maximum Power Transfer Theorem [MPT]:

~~vw imp
definition~~

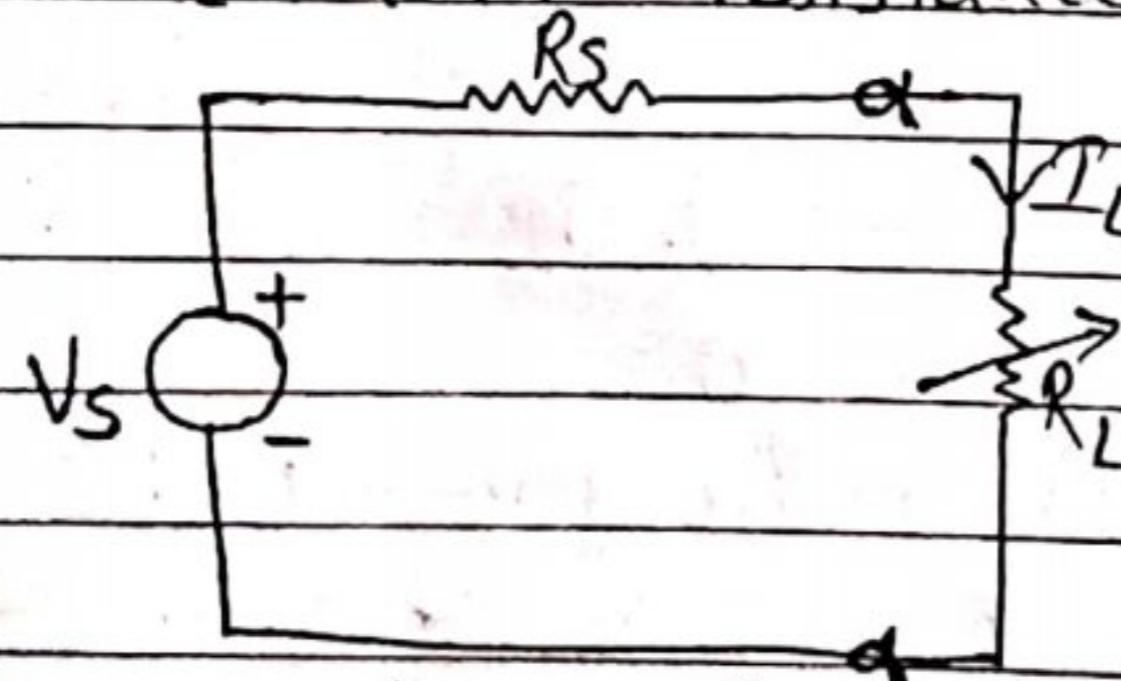The maximum power transfer theorem states that the max^m power is delivered from source to ~~load~~^{bad}, when load resistance equal to source resistance. Assume that the load resistance is variable.



load current in the ckt :

$$I_L = \frac{V_s}{R_s + R_L}$$

Power delivered to the load (R_L)

$$P_L = I_L^2 \cdot R_L = \left[\frac{V_s}{R_s + R_L} \right]^2 \cdot R_L$$

$$\therefore P_L = \frac{V_s^2 \cdot R_L}{[R_s + R_L]^2} \quad \textcircled{1}$$

To determine the value of R_L , the maximum power to be transferred to the load:

We have to set the first derivative of the above eqⁿ w.r.t. the R_L .

i.e. $\frac{d P_L}{d R_L} = 0$ [P_L is max^m]

$$\therefore \frac{d P_L}{d R_L} = \frac{d}{d R_L} \left[\frac{V_s^2 \cdot R_L}{(R_s + R_L)^2} \right]$$


$$\Rightarrow 0 = V_s^2 \left[\frac{(R_s + R_L)^2 - 2 R_L (R_s + R_L)}{(R_s + R_L)^4} \right]$$

i.e. $(R_s + R_L)^2 - 2 R_L (R_s + R_L) = 0$

$$\text{or } R_s^2 + R_L^2 + 2 R_s R_L - 2 R_L R_s - 2 R_L^2 = 0$$

$$\text{or } R_s^2 - R_L^2 = 0$$

$$\Rightarrow R_s = R_L$$

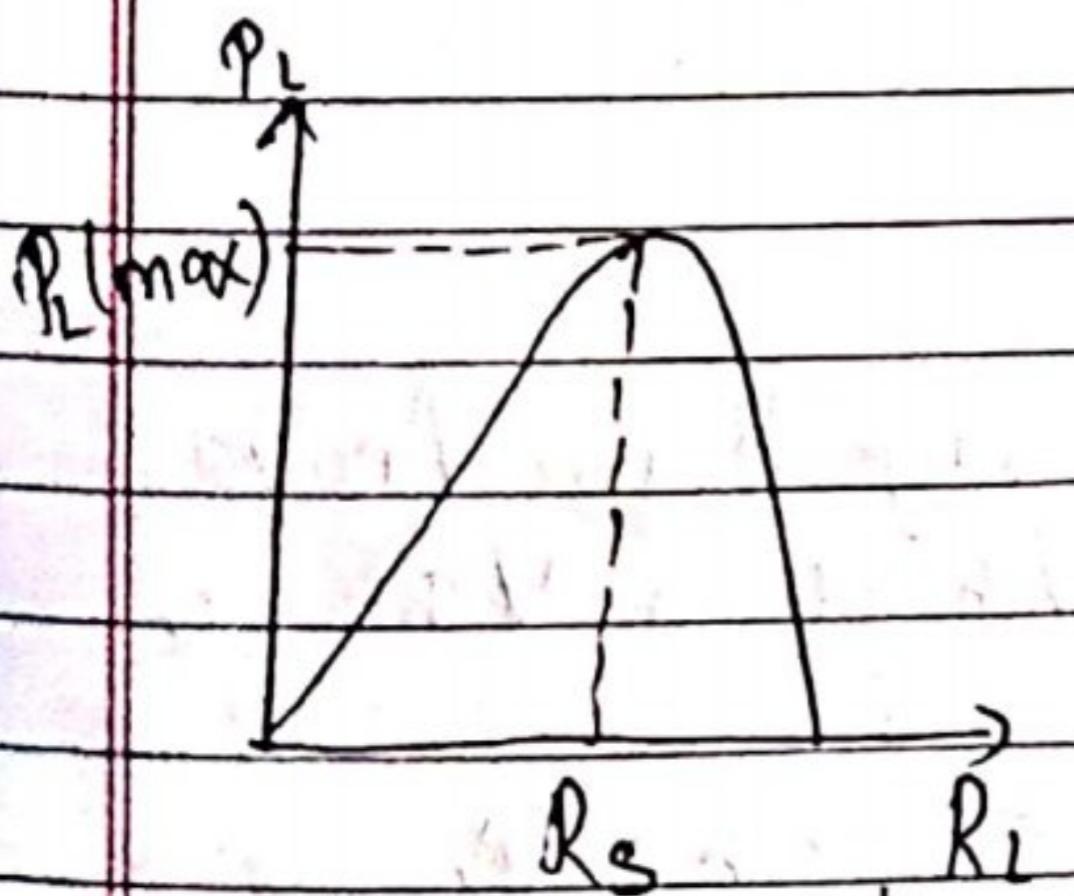


fig(a): variation of power with load resistance

So, the max^m power will be transferred to the load when load resistance equal to source resistance. So the max^m power


$$\begin{aligned} P_L(\max) &= \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2} \\ &= \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2} \\ &= \frac{V_s^2 \cdot R_L}{4 R_L^2} \quad [R_s = R_L] \end{aligned}$$

$$\therefore \text{Max}^m \text{ power } [P_L \max] = \frac{V_s^2}{4 R_L}$$

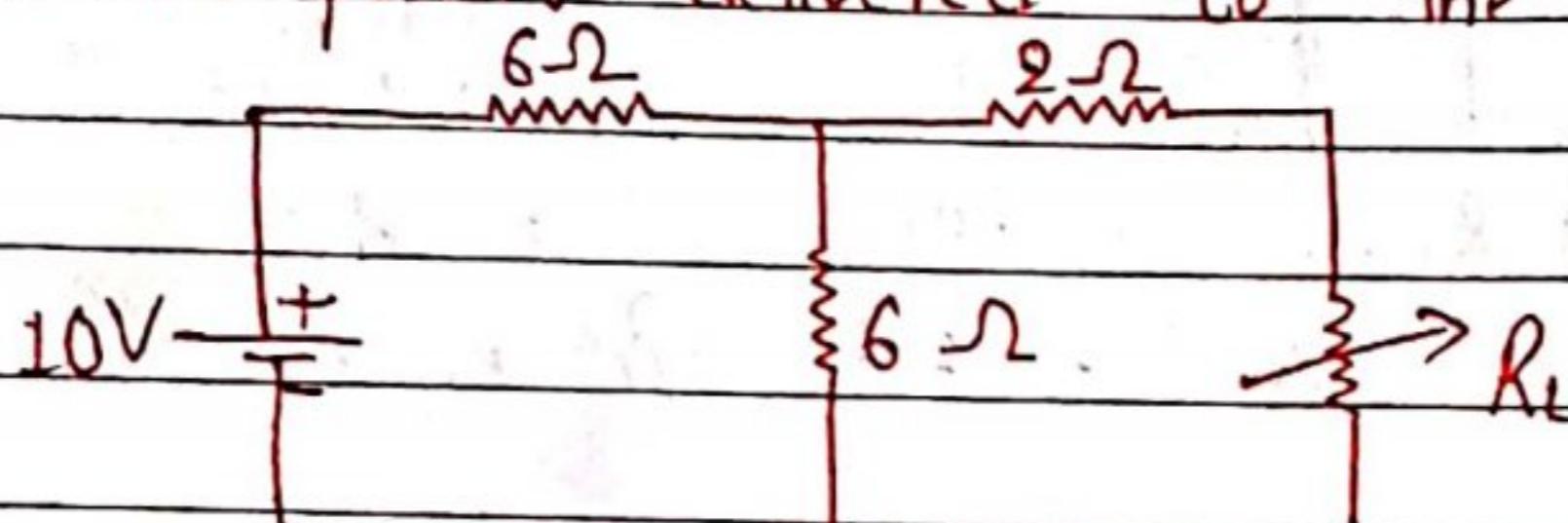- Q. In a N/w shown in fig below, determine
 (a) value of load resistance to give a max^m power transfer
 (b) the power delivered to the load.




Step - 1: finding the R_{Th} :

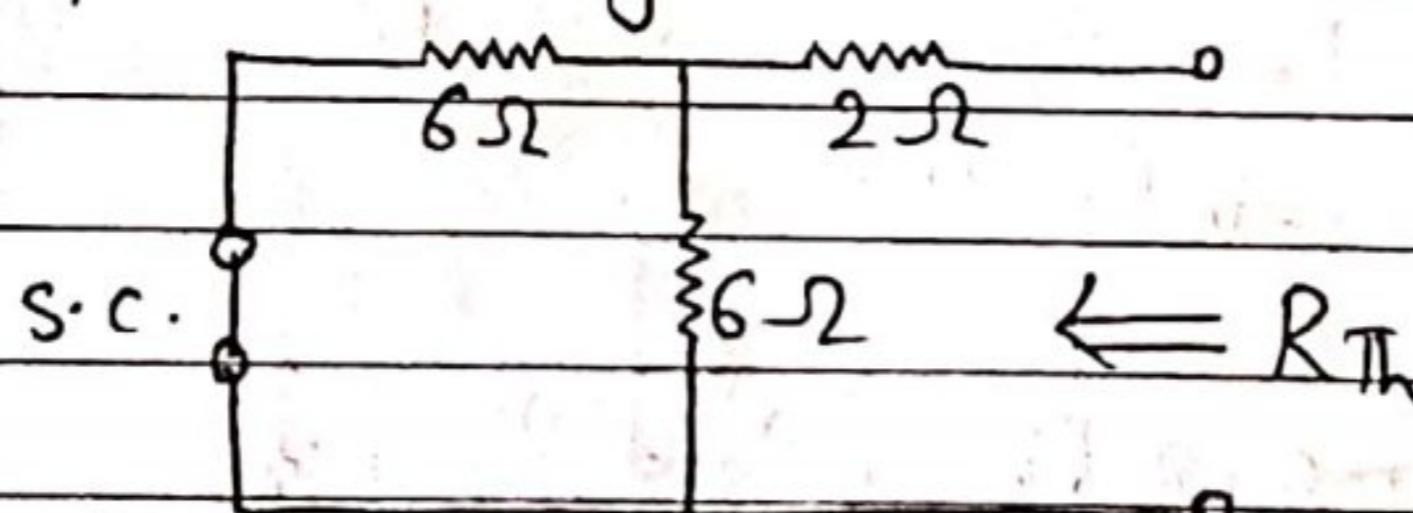

$$R_{Th} = (6 \parallel 6) + 2 = \frac{36}{12} + 2 \\ \therefore R_{Th} = 5 \Omega$$

Step - 2: finding the V_{Th} :

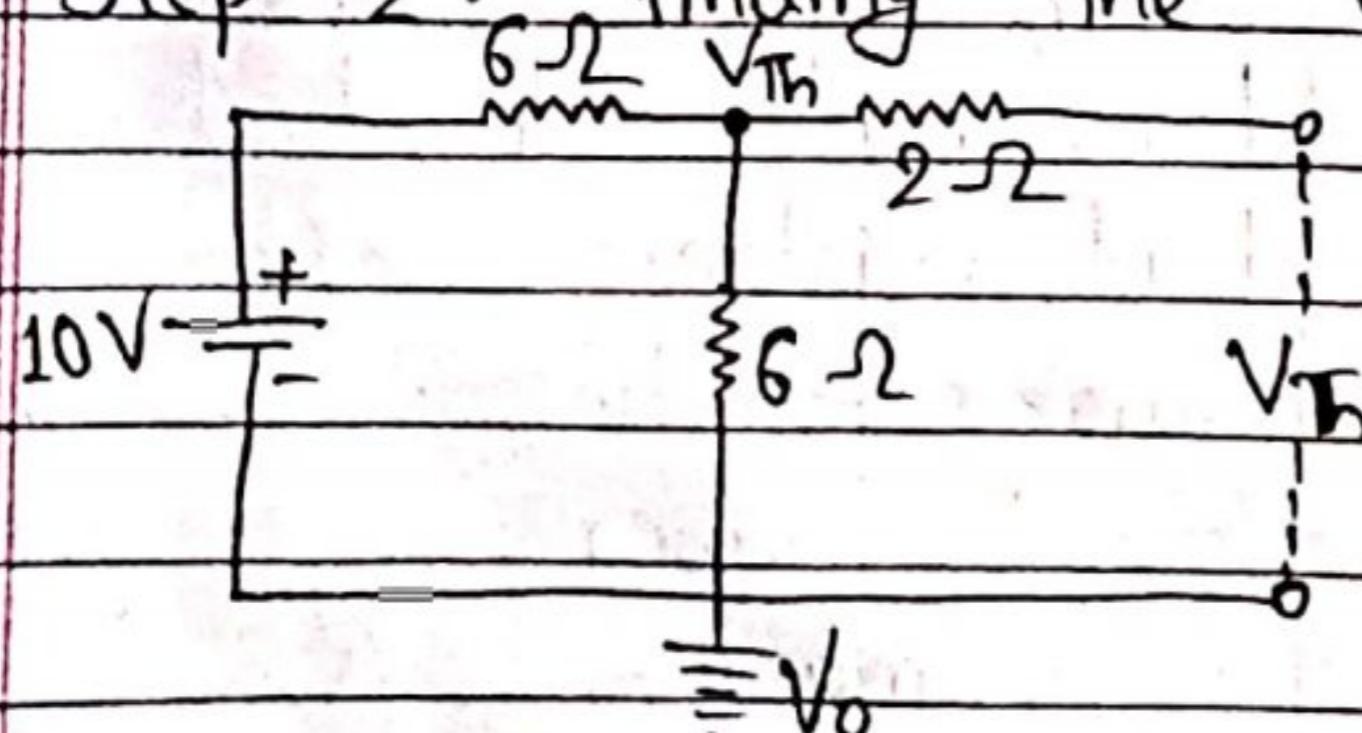

Using Nodal Analysis:


$$\frac{V_{Th} - 10}{6} + \frac{V_{Th}}{6} = 0 \\ \Rightarrow V_{Th} = 5V$$

Taking LHS mesh,

$$10V - 6I_1 - 6I_1 = 0$$

$$\text{or } 10 = 12I_1$$

$$\Rightarrow I_1 = 0.833 \text{ amp.}$$

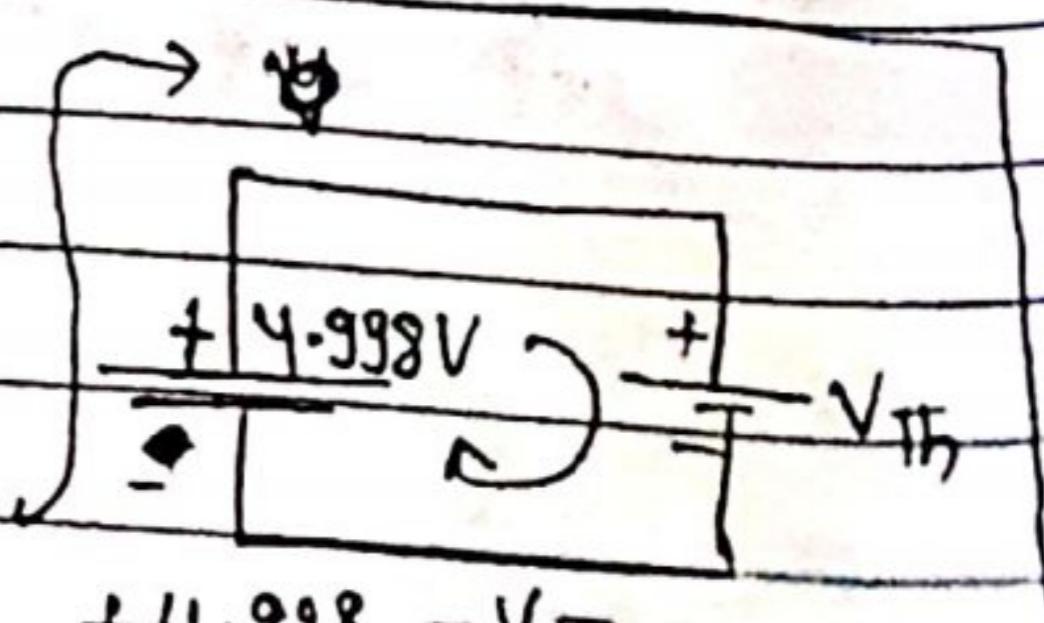

$$+4.998 - V_{Th} = 0$$

$$V_{Th} = 4.998V$$

(a) Max^m power to transfer:

$$R_L = R_{Th} = 5\ \Omega \text{ (max^m power)}$$

$$(b) \text{ If } P_L \text{ max} = I_L^2 \cdot R_L$$


$$= \frac{V_s^2}{(R_s + R_L)^2} \cdot R_L$$

$$P_L \text{ max} = \frac{V_s^2}{4R_L} \quad (R_s = R_L)$$


$$= \frac{5^2}{4 \times 5} \quad [\because V_s = V_{Th}]$$


$$\therefore P_L \text{ max} = 1.25 \text{ watt}$$

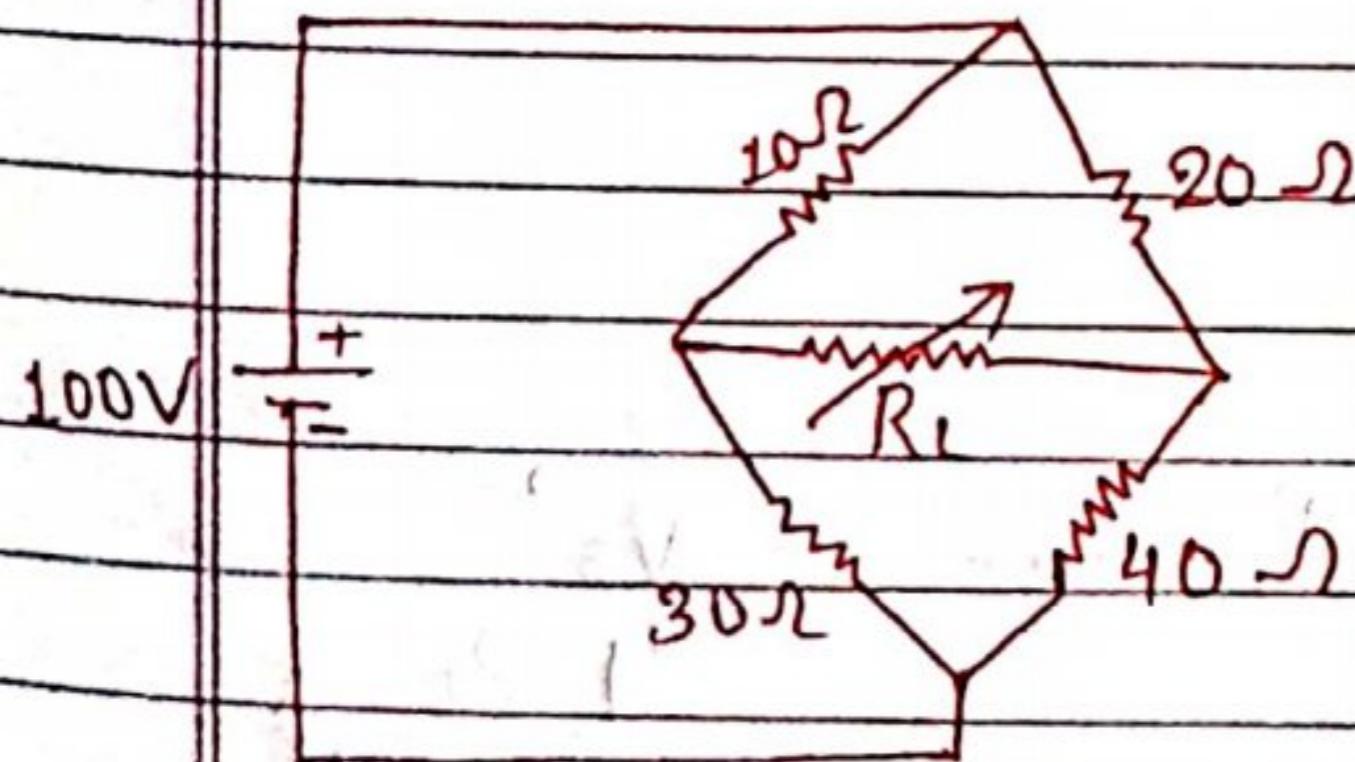Q. Determine the load resistance to receive the max^m power from the source, also find the max^m power delivered to the load in the ckt shown in fig.



Step-1: finding the R_{Th} :

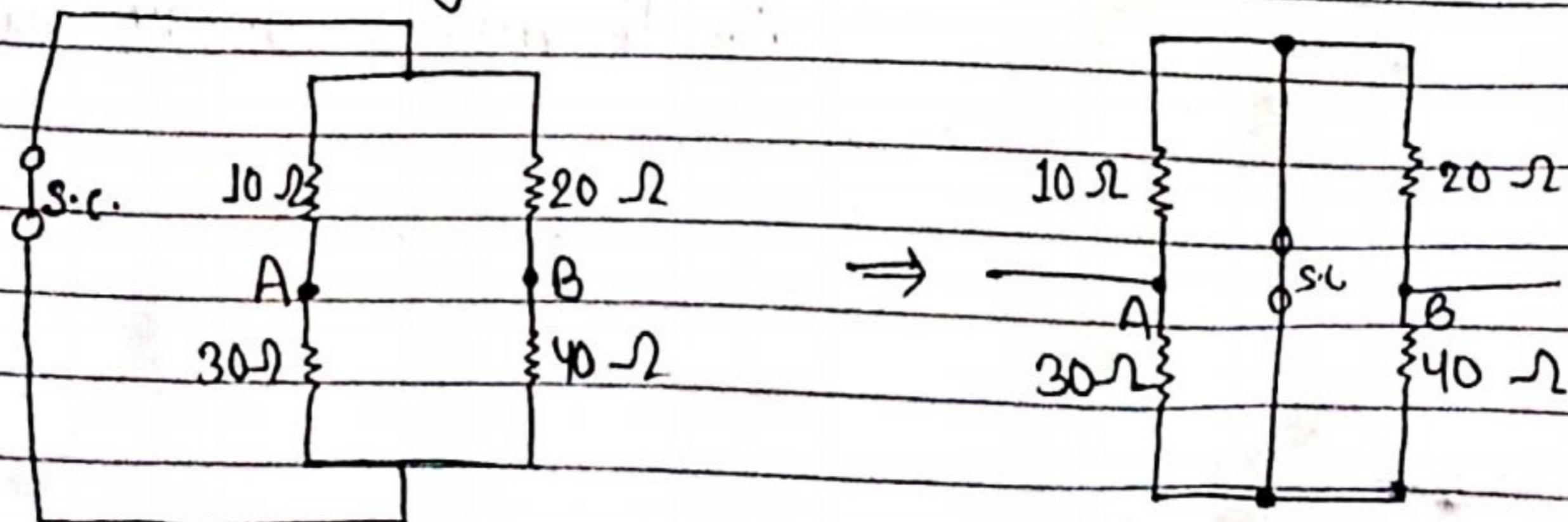


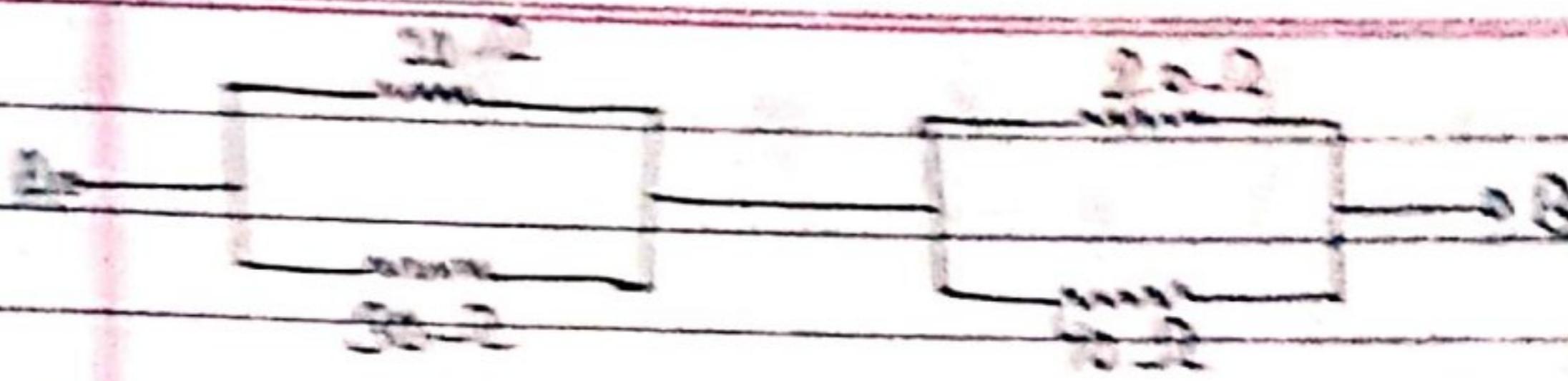

$$R_L = (10/30) + (20/30) \\ = 20.83 \Omega$$

Sop-2: Ending in the Vt.:

$$\sqrt{d} = 100 \times 10 = 25\sqrt{}$$

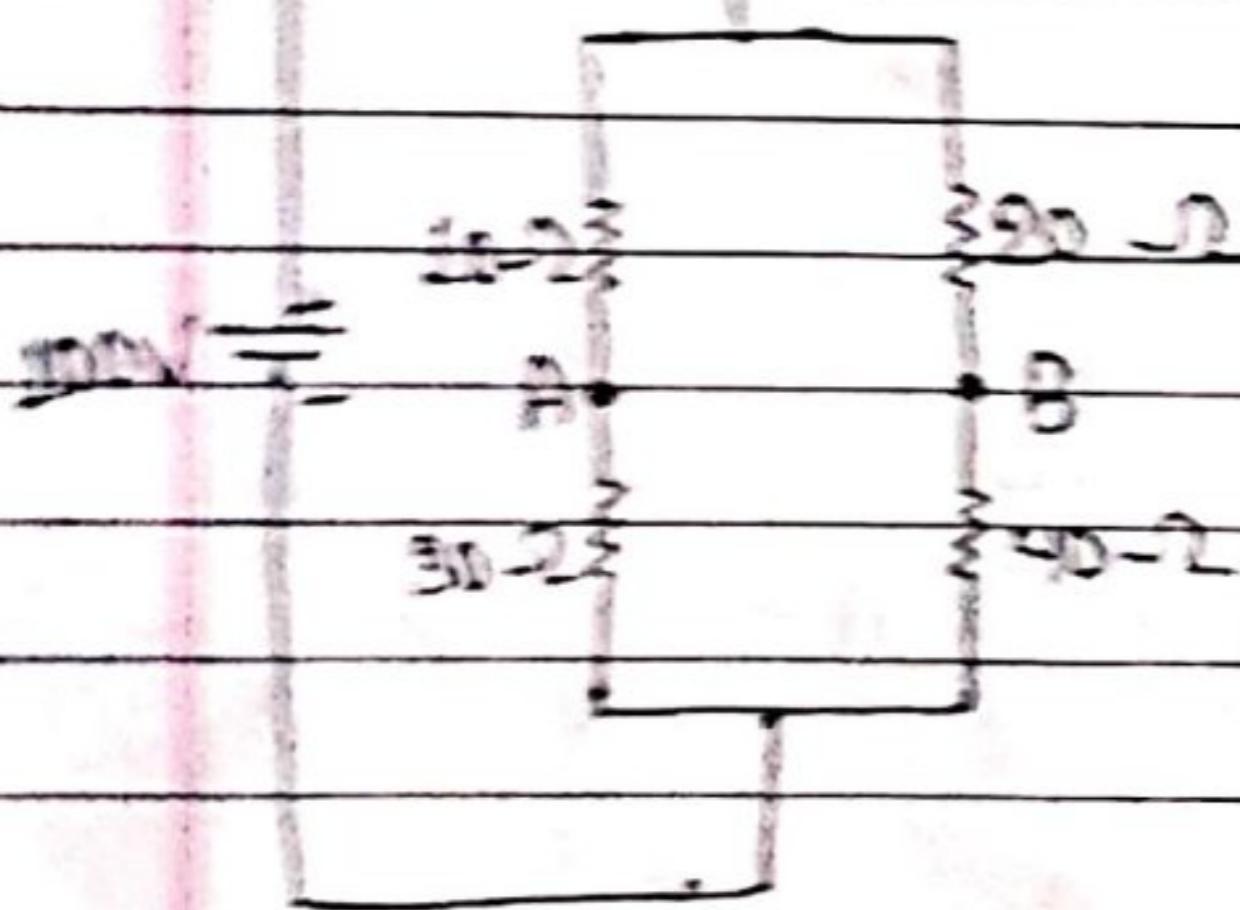

$$V_E = 100 \times \frac{20}{20+40} = 33.33$$


$$\therefore V_{AB} = \sqrt{8} - \sqrt{2}$$

$$= 33.33 - 25$$

$$\Rightarrow V_{AB} = 8.33V$$

10

$$R_F = 20 \cdot 33 - 72$$

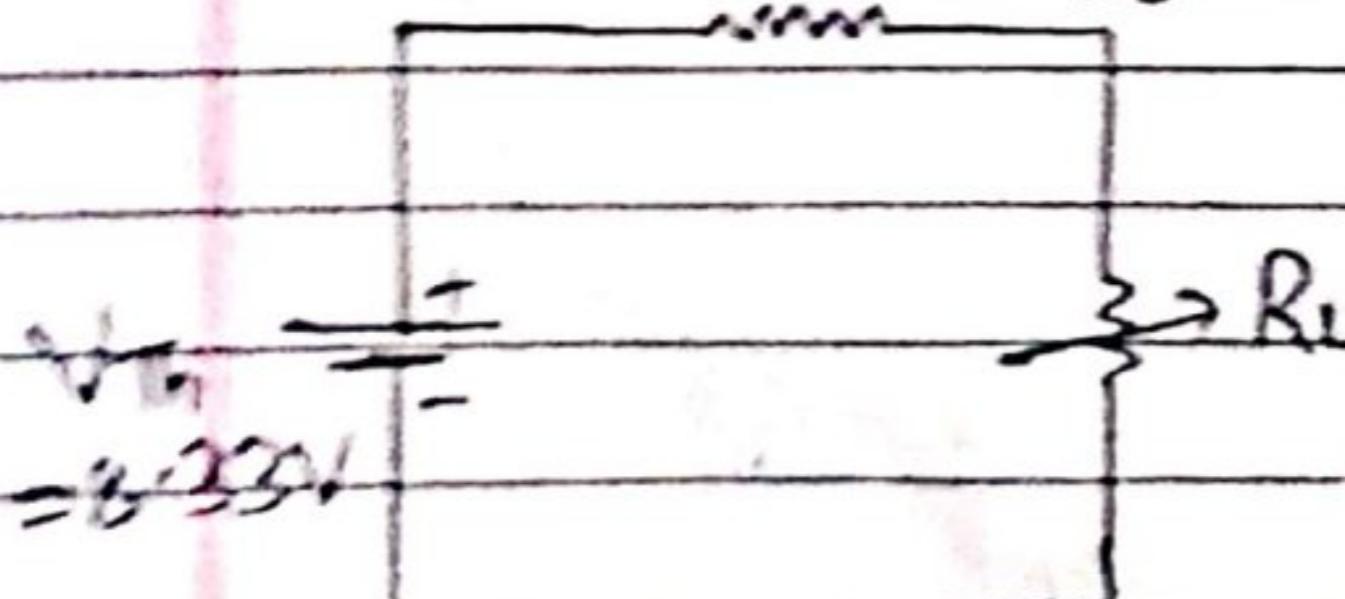

$$\dot{P}_{\max} = V_s^2$$



$$\frac{4 R_L}{(8 \cdot 33)^2}$$

$$\therefore P_{\max} = \frac{4 \times 20.83}{1000} \text{ watt}$$

Q. Find the maximum power that can be delivered to the resistor in the ckt below:


2019

fall

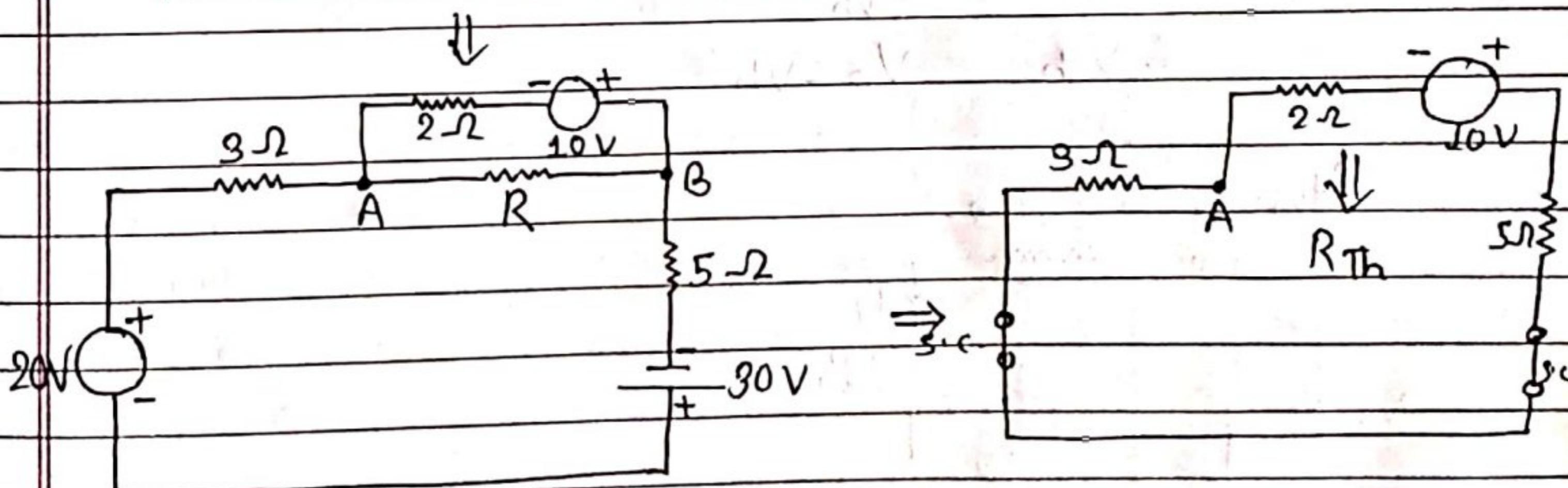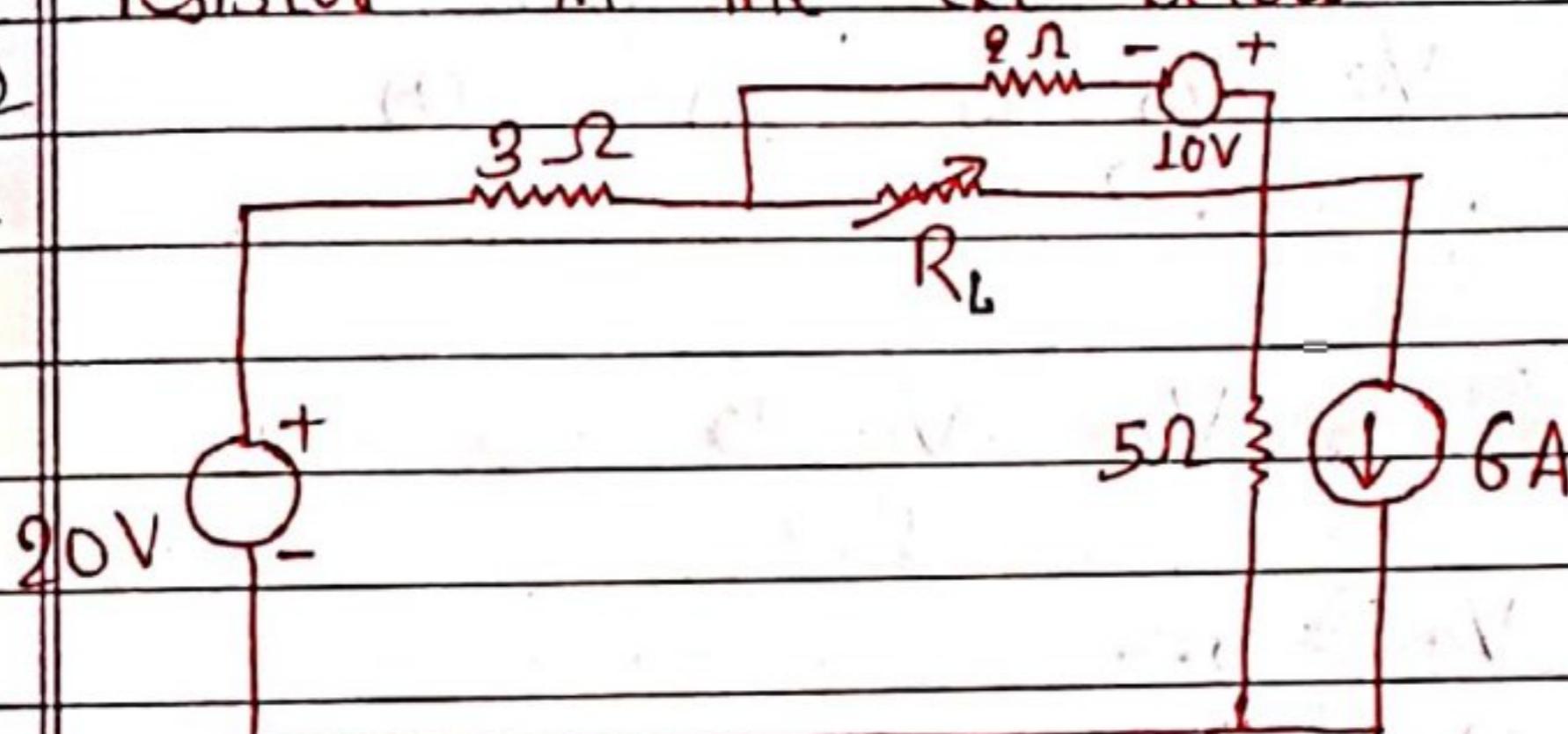

$$R_{Th} = (5+3) \parallel 2 = 1.6 \Omega$$

Now,

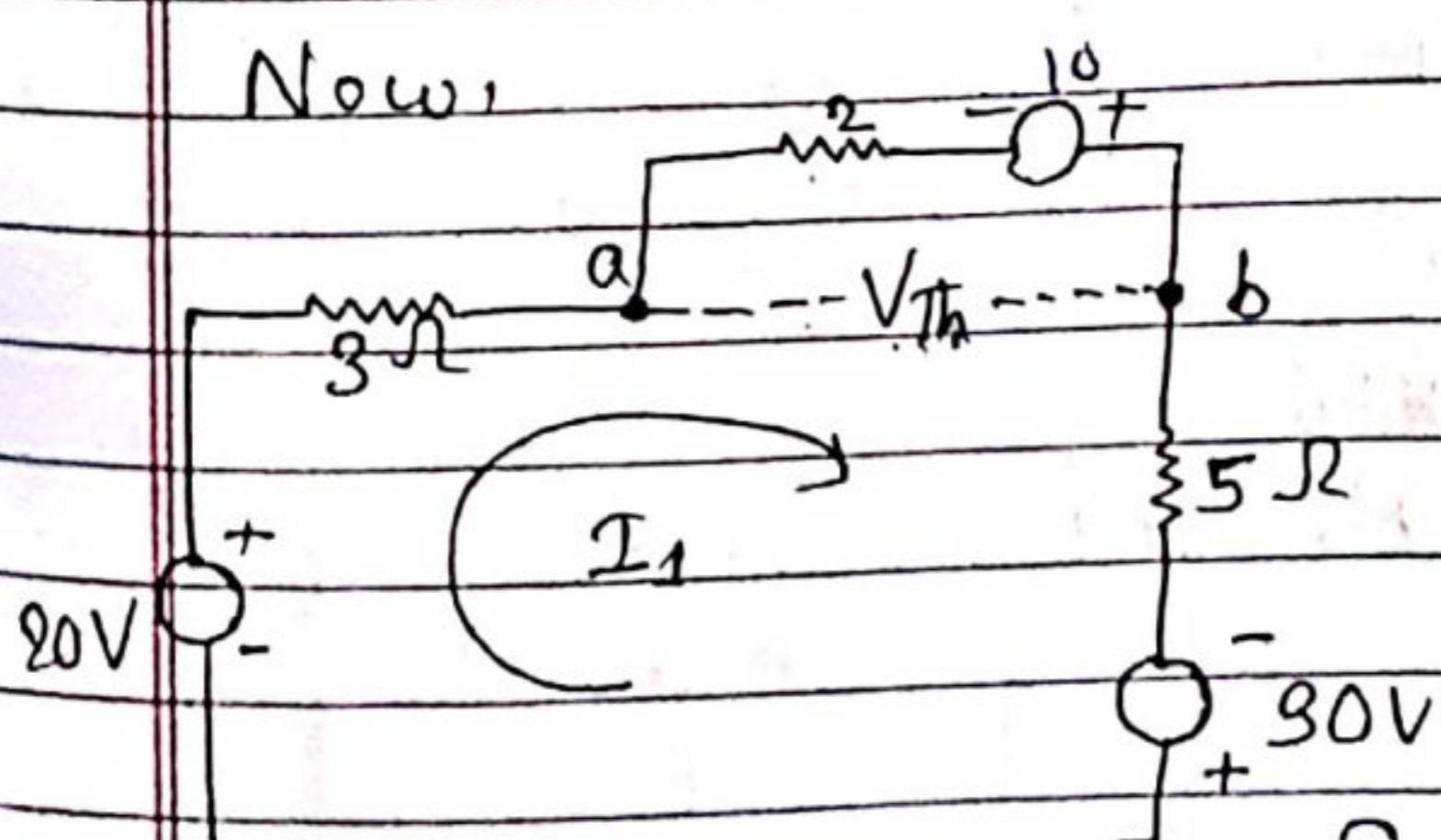

Considering mesh analysis:

$$20V - 3I_1 - 2I_1 + 10 = 0$$

$$-5I_1 + 30 = 0$$

$$60 - 10I_1 = 0$$

$$60 = 10I_1$$

$$\Rightarrow I_1 = 6 \text{ Amp}$$

$$\text{So, } V_{Th} - 2I_1 + 10 = 0$$

$$\text{So, } V_{Th} = -10 + 2 \times 6$$

$$\Rightarrow V_{Th} = 2V$$

or using Nodal Analysis,

$$\frac{V_a - 20}{3} + \frac{V_a - V_b + 10}{2} = 0 \quad \textcircled{1}$$

$$\frac{V_b + 30}{5} + \frac{V_b - V_a - 10}{2} = 0 \quad \textcircled{11}$$


Solving, $V_a = \dots$

$$V_b = \dots$$

$$\therefore V_{Th} = V_a - V_b$$

Now,

$$R_m = R_s$$

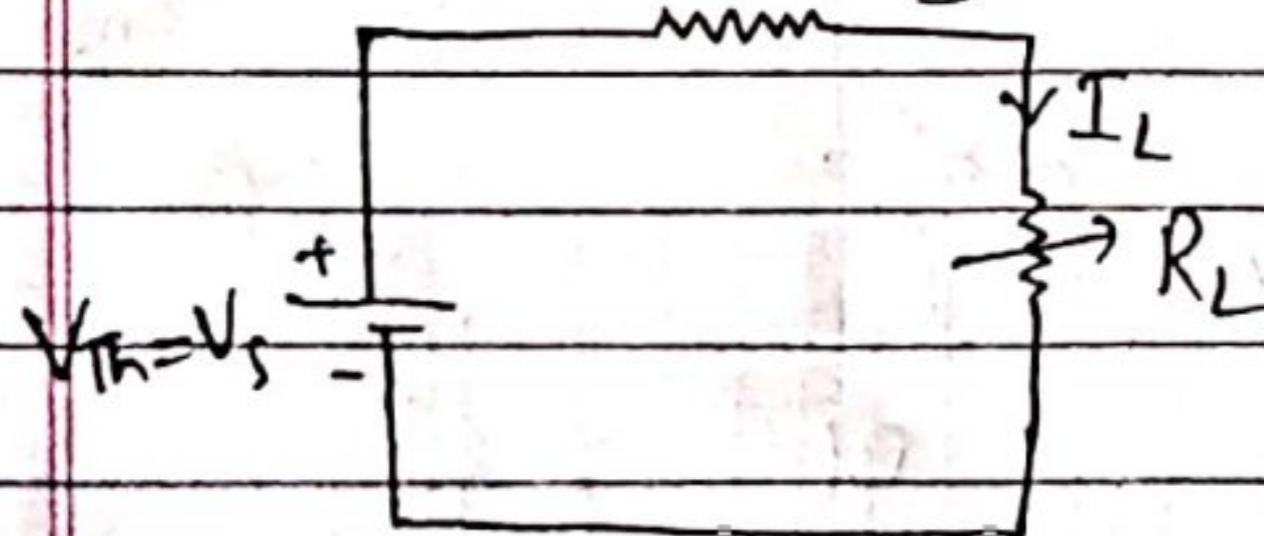

$$P_{L\max} = \frac{V_s^2}{4R_L}$$

$$= \frac{2^2}{4 \times 1.6}$$

$$\therefore P_{L\max} = 0.625 \text{ watt}$$