

DC Circuit Analysis

classmate

Date _____


Page _____

N/w elements may be classified into four groups:


- ① Active & passive elements
- ② Unilateral & bilateral elements
- ③ Linear & Non linear elements
- ④ Lumped & distributed elements

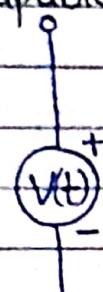1. # Active & Passive Elements :-

^{Active Elements} Energy source (voltage & current source) are active element capable of delivering power to some external device.




voltage source

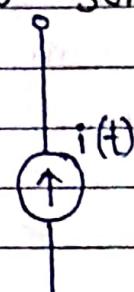


current source

Passive Elements

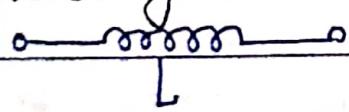Passive elements are those which are capable of only receiving the power. E.g. inductor, capacitor or resistor.



L

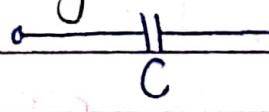

C



R

2. # Unilateral & bilateral elements :-

Unilateral elements are those whose properties change with the direction of its operation. E.g. diode \rightarrow ,

transistor



Bilateral elements are those which properties are same in either direction. Example: transmission line.

Linear & Non-Linear elements

An element is said to be linear, if it satisfies the linear voltage - current relationship. That means, the current through the element is multiplied by some constant & they result in multiplication of voltage across the element by the same constant.

Example: The current passing through the resistors is directly proportional to the voltage applied through it.

$$\begin{array}{c} V \propto I \\ V = IR \end{array} \quad \frac{I \propto P}{x(t)} \quad \boxed{\text{Linear system}} \quad \frac{O/P}{y(t)}$$

In other words, a system is linear if the superposition theorem holds good. For input & output relation

$$x_1 \rightarrow y_1 \quad x_2 \rightarrow y_2 \\ ax_1 + bx_2 \rightarrow ay_1 + by_2 \leftarrow \text{Superposition theorem}$$

Non-linear elements:

→ They are those which does not satisfy this relation.

Lumped & distributed elements:

The elements which are separated physically are known as lumped elements. E.g. three elements R, L & C are lumped.

Distributed el. are those which are not separable for analytical purpose. E.g. a transmission line has distributed resistor, inductor & capacitor along its length.

3.6 Circuit Analysis

Circuit elements [RIC] & their characters:

- X (ckt) ① Resistance parameter
 ② Inductance parameter
 ③ Capacitance parameter

1) Resistance Parameter :-

When the current flowing through the circuit material, the free electron moves through the material & collide with the atoms. This collision causes e^- lose some energy. This loss of energy per unit charge is the drop in potential ~~comes~~ across the material. The amount of energy lost by the e^- is related to the physical properties of material. There collision is restrict the moment of e^- . This property of material to restrict the flow of e^- is called resistance denoted by 'R' & unit is ohm (Ω).

fig @ symbol for resistance

According to ohm's law, the current is directly prop. to the voltage & inversely prop. to the total resistance of the circuit so

$$I = \frac{V}{R} ; \quad i = \frac{v}{R}$$

we can write the above eqⁿ in terms of charge as under.

$$V = R \frac{dq}{dt}$$

$$i = \frac{V}{R} = G \cdot v \quad \text{when, } \frac{1}{R} = G$$

conductance of the conductor

** The unit of the conductance is mho (Ω^{-1}) or siemen (S) or ohm^{-1} .

$$P = VI ; P = IR \cdot I = I^2 R$$

$$P = I^2 R$$

Energy lost in time 't' is given by

$$W = \int_0^t P \cdot dt$$

$$\text{So, } W = Pt = I^2 Rt$$

$$\Rightarrow [W = I^2 Rt] \rightarrow \text{Joules}$$

2) Inductance Parameter:

By definition, the inductance is the 1H when current through the coil change at the rate of 1A per sec induced 1 Volt across the coil.

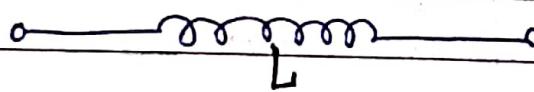


fig. (b) symbol of inductor

* Current - Voltage relation:

$$v = L \frac{di}{dt}$$

where v = voltage through the inductor in volts
 i = current through the inductor in ampere.

Re-writing above eqⁿ:

$$di = \frac{1}{L} v dt$$

Integrating both sides,

$$\int_{i(0)}^{i(t)} di = \frac{1}{L} \int_0^t v dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v dt$$

$$i(t) = \frac{1}{L} \int_0^t v dt + i(0)$$

initial current passing through inductor on coil

The power absorbed by inductor is

$$P = vi \\ = Li \frac{di}{dt} \text{ watt}$$

$$[v = L \frac{di}{dt}]$$

The energy accepted by inductor is


$$W = \int_0^t P dt = \int_0^t P dt = \int_0^t li \cdot \frac{di}{dt} dt \\ = \int_0^t li \cdot di = L \int_0^t i dt$$

Note:
 $t=0$
 $i=0$

$$\therefore W = \frac{1}{2} L i^2$$

~~Problems~~

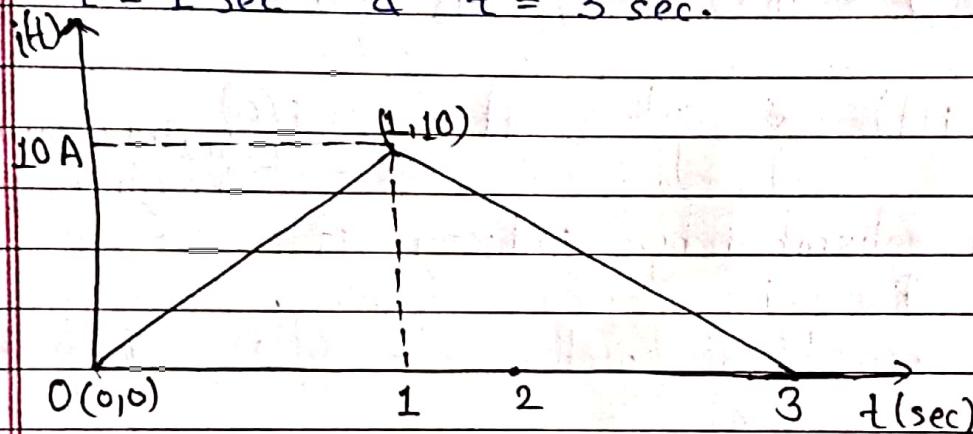Q: A current having a variation as shown in fig (a) below & applied to pure inductor having the value of 2H, calculate the voltage across the inductor at a time $t = 1 \text{ sec}$ & $t = 3 \text{ sec}$.



$$0 \leq t \leq 1 \rightarrow 1^{\text{st}} \text{ boundary cond}$$

$$1 \leq t \leq 3 \rightarrow 2^{\text{nd}} \text{ boundary cond}$$

For 1st boundary cond :

$$y - y_1 = \frac{y_2 - y_1}{x_2 - x_1} (x - x_1)$$

$$y - 0 = \frac{10 - 0}{1 - 0} (x - 0)$$

$$y = 10x$$

$$i(t) = 10t$$

$$i = 10t$$

$$\frac{di}{dt} = 10$$

$$v = L \cdot \frac{di}{dt}$$

$$= 2 \times 10$$

$$\therefore v = 20 \text{ Volts}$$

For 2nd boundary cond :

$$1 \leq t \leq 3$$

$$x_1 = 1, y_1 = 10, x_2 = 3, y_2 = 0$$

$$y - 10 = \frac{0 - 10}{3 - 1} (x - 1)$$

$$y - 10 = -5x + 5$$

$$y = -5x + 15$$

$$i(t) = -5t + 15$$

$$\frac{di}{dt} = -5$$

$$v = L \cdot \frac{di}{dt} = 2 \times (-5)$$

$$= -10V$$

jmp short note

Colour Coding


Carbon composition resistor are very small in size. It is difficult to print value in resistor. That cannot be read by naked eyes. Therefore, colour bands are printed on one end of resistor casting. This system of representing the register value is called colour coding.

The first and the second band represent the first & second significant digit of resistance value respectively. The third band is multiplier. Sometimes the third band is golden or silver color. Then this colour represent the multiplying factor of 0.1 and 0.01 resp. The fourth band represent the register tolerance.

Formula

BBRÖY of Great Britain
has a very good wife

Colour	Significant digit	Multiplier	Tolerance
Black	0	$10^0 = 1$	-
Brown	1	$10^1 = 10$	-
Red	2	$10^2 = 100$	-
Orange	3	10^3	-
Yellow	4	10^4	-
Green	5	10^5	-
Blue	6	10^6	-
Violet	7	10^7	-
Gray	8	10^8	-
White	9	10^9	-
Golden	-	0.1	$\pm 5\%$
Silver	-	0.01	$\pm 10\%$
No colour	-		$\pm 20\%$

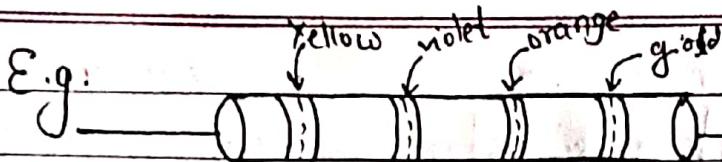

$$47 \times 10^3 \pm 5\% \quad (2.3)$$

$$= 47 + 2.3 = 49.3 \text{ k}\Omega$$

$$= 47 - 2.3 = 44.7 \text{ k}\Omega$$

Q: A resistor has colour band sequence green, blue, orange and gold. Find the range in which its value must lie depending upon the manufacture tolerance to suit a circuit.

$$\begin{matrix} G & B & O & g \\ = 4.5 \end{matrix}$$

solution:

1 st significant	2 nd significant	Multiplier	Tolerance
Green	Blue	Orange	Gold
5	6	10^3	$\pm 5\%$

$$56 \times 10^3 \pm 5\%$$

$$= 56k \pm 2.8$$

$$= 56 + 2.8$$

$$= 58.8 \text{ k}\Omega$$


Series and Parallel Compilation of Resistance

1) Conductor in Series

2) Conductor in Parallel

1. Conductor in Series

$$V = IR \quad \text{--- (i)}$$

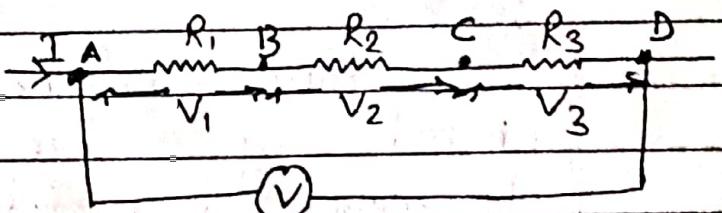

$$V = \text{sum of } (V_1 + V_2 + V_3)$$

Pd across R_1, R_2 & R_3

$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3 \quad \text{--- (ii)}$$

From eqⁿ (i) & (ii),


$$IR = IR_1 + IR_2 + IR_3$$

$$IR = I(R_1 + R_2 + R_3)$$

$$[R = R_1 + R_2 + R_3]$$

2. Conductor in Parallel

$$I = \frac{V}{R} \quad \text{--- (i)}$$

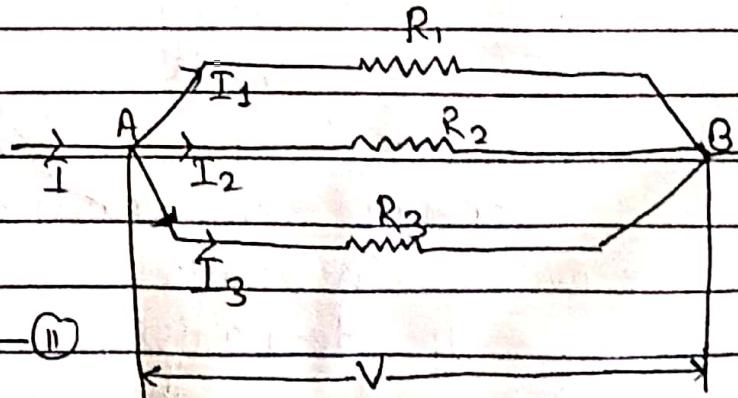

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad \text{--- (ii)}$$

From eqⁿ (i) & (ii),

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Concept of Power, Energy & its Calculations:

Energy is the capacity for doing work. Energy is nothing but store work. Energy may exist in many form as mechanical, chemical, electrical & so on.

Power is the rate of change of energy. It is denoted by either P or \dot{P} . If the certain amount of energy is used over a certain unit of time then,

$$P = \frac{\text{Energy}}{\text{time}} = \frac{w}{t}$$

$$P = \frac{dw}{dt}$$

where dw = change in energy
 dt = change in time

$$P = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt}$$

$$\therefore P = V \times I = \text{watt}$$


Energy is measured in joule, time in sec & power in watt.

By definition,



One watt is the amount of power generated when one joule of energy is consumed in 1 sec. Thus, the number of joule consume in 1 sec is always equal to the number of watts. Amount of power less than 1 watt are usually express in fraction of watt. In the field of electronics via milliwatt (mw) & microwatt (uw). In electrical phased, kilowatt & megawatt (mw) are

common units. Radio & tv station also use large amount of power to transmit the signal.

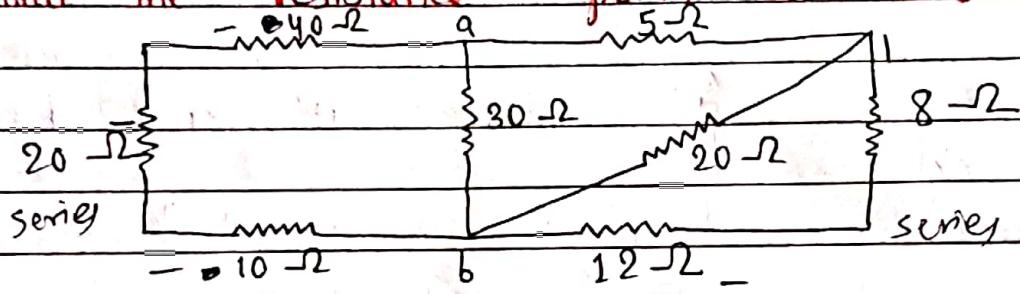Q. 2) Find the resistance between terminals a - b.



Solution:

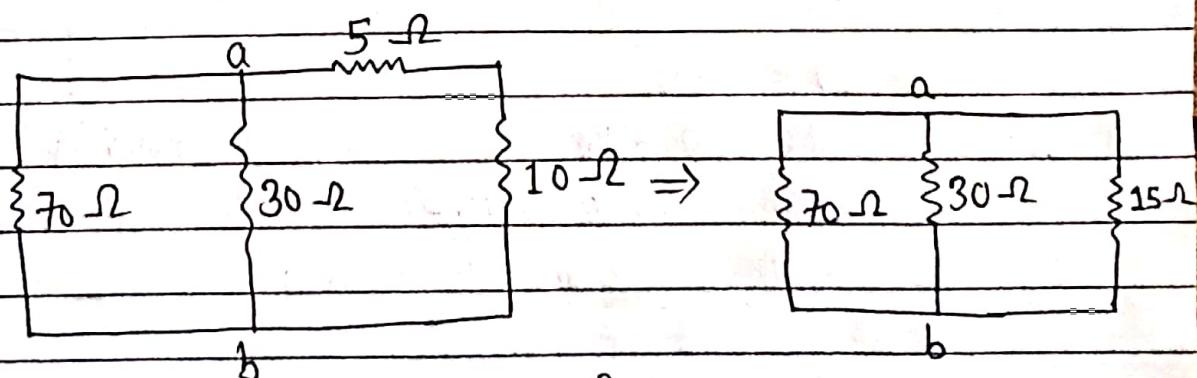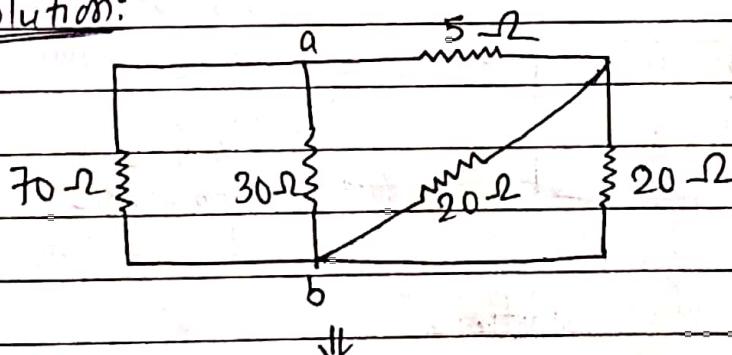

$$\frac{1}{R} = \frac{1}{70} + \frac{1}{30} + \frac{1}{10} = \frac{31}{210}$$

$$\therefore R = 6.77 \Omega$$

Short and open ckt:

1) Short ckt

a) shorts, in a series circuit


b) shorts, in a parallel ckt

2) Open ckt

(a) open in series ckt

(b) open in parallel ckt

1) Short ckt

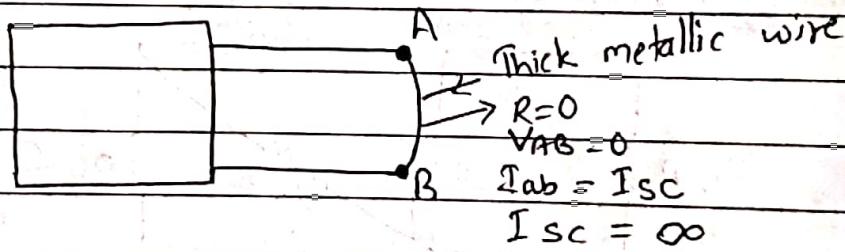

2) for short ckt condition.


$$V = 20V$$

$$R_T = R_1 + R_2 + R_3$$

$$= 5 + 10 = 15\Omega$$

$$I = \frac{V}{R} = \frac{20}{15} = 1.33 \text{ amp}$$
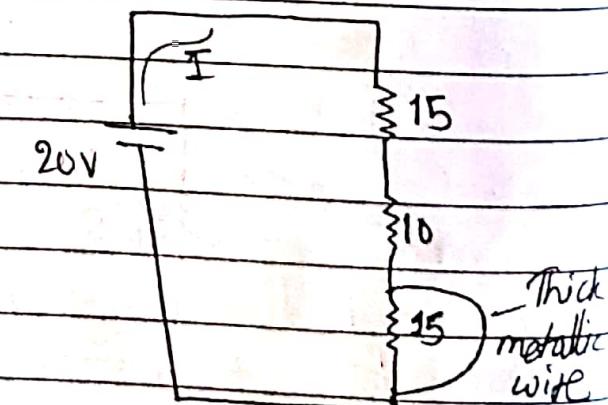
$$P = I^2 R = (1.33)^2 \times 15 \\ = 26.66 \text{ watt}$$



Normal condition,

$$V = 20V$$

$$R_T = R_1 + R_2 + R_3$$


$$= 5 + 10 + 15$$

$$= 30\Omega$$

$$I = \frac{V}{R_T} = \frac{20}{30} = 0.67 \text{ amp}$$


$$P = I^2 R = (0.67)^2 \times 30 \\ = 13.26 \text{ watt}$$

b) Short circuit in parallel circuit:

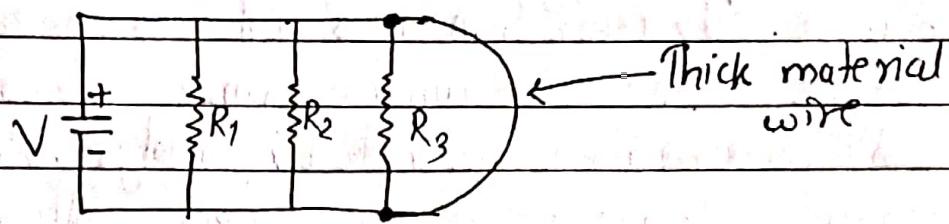


2) Open ckt


a) Opens, in a series circuit

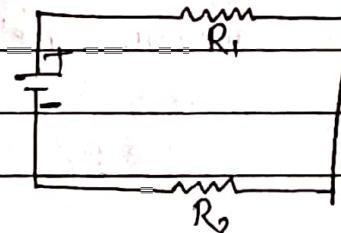

b) Opens, in a parallel ckt

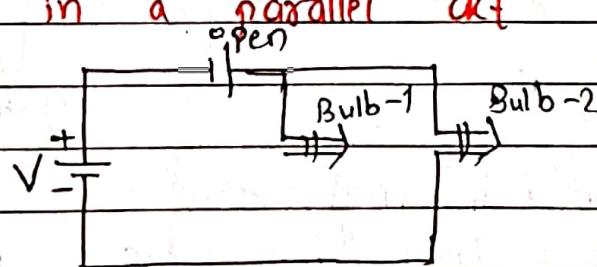


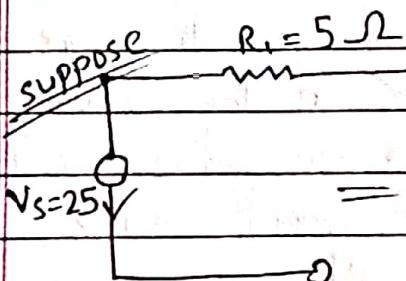
Source Conversion [Source Transformation]



$$V = 25$$

$$R_1 = 5 \Omega$$

$$I = \frac{V}{R} = \frac{25}{5} = 5A$$

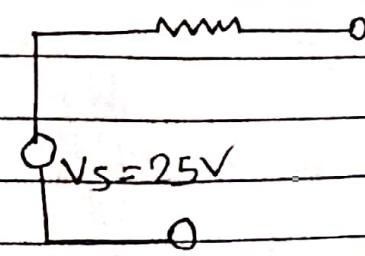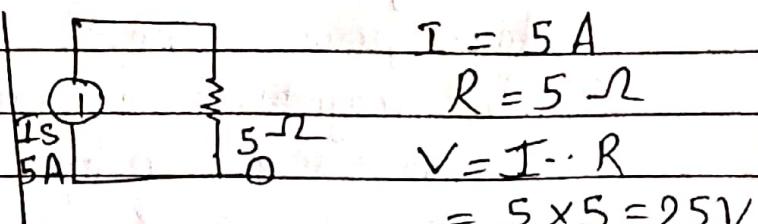

→ Basically, energy source are either voltage source or current source. Sometimes it is necessary to convert voltage source to current source & current source to voltage source in network analysis. Any practical voltage source consist of an ideal voltage source in a series with an internal resistance (impedance). Similarly, a practical current source consist of ideal current source in parallel with internal resistance (impedance) as shown below in fig a & b.

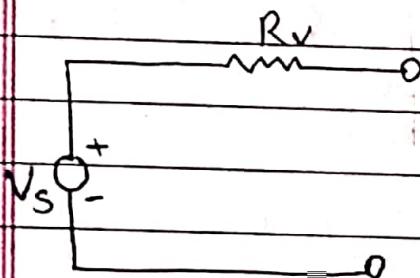


fig (a)

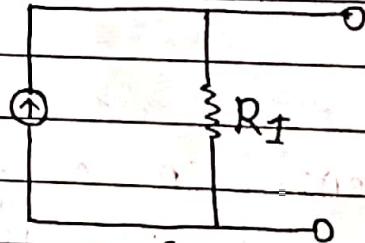


fig (b)

where, R_v = Internal resistance of voltage source (V_s)

R_I = Internal resistance of current source (I_s)

Any Source, whether it be a current source or voltage source derives current through its load resistance & the magnitude of current depend on the value of load resistance. In fig. c & d represents the practical voltage source & a practical current source connected to the same load resistance (R_L)

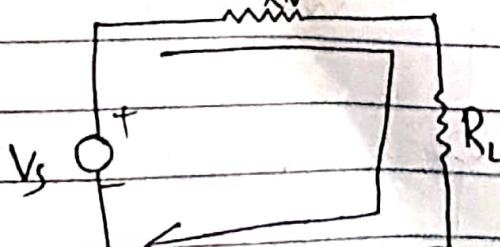


fig (c)

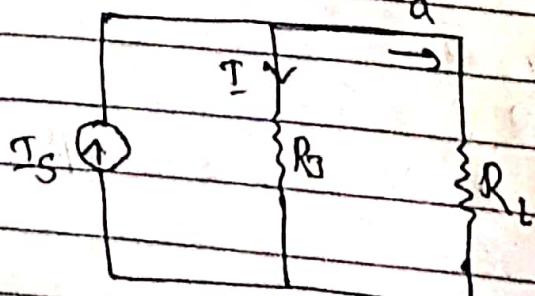


fig (d) b

The load current can be calculated by using Kirchoff's voltage law.

From fig (c),

$$I_v = \frac{V_s}{R_s + R_l} \quad \text{--- (1)}$$

From fig (d), the load current can be calculated by using Kirchoff's current law as

$$I_l = I_s = \frac{R_s}{R_s + R_l} \quad \text{--- (2)}$$

The above two source are said to be equal when they produce equal amount of current & voltage to the equal load resistance.

$$I_v = I_l$$

$$\frac{V_s}{R_v + R_l} = \frac{I_s \cdot R_l}{R_s + R_l} \quad \text{--- (3)}$$

The current source, the voltage across the terminal a.b,

$$V_s = I_s \cdot R_l$$

Substituting V_s value in eqⁿ (3),

$$\frac{I_s \cdot R_l}{R_v + R_l} = \frac{I_s \cdot R_l}{R_s + R_l}$$

$$R_v + R_l = R_s + R_l$$

$$\therefore R_v = R_s$$

Therefore, any practical voltage source having an ideal voltage (V_s) & internal series resistance (R_v) can be replaced by a current source $I = V_s / R_v$

in parallel with an internal resistance $R_s = R_v$.

Energy Sources

Voltage & current sources:-

- a) Ideal voltage & ideal current source
- b) Independent or dependent voltage & current source

a) Ideal voltage & ideal current source:

* Ideal voltage source:-

An ideal voltage source is one that maintains a constant terminal voltage no matter how much current is drawn from it.

E.g.

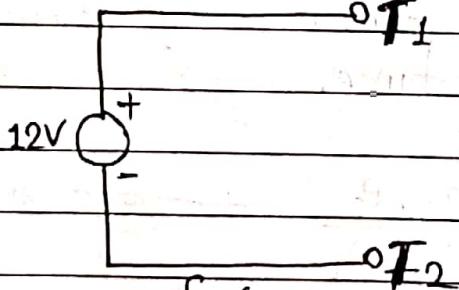


fig (a)

Terminal T₁ & T₂, whether we connect 1 MΩ or 1 kΩ resistor across all terminals. In practice, it is difficult to construct an ideal voltage source. It is a fact that all the real voltage source have some internal resistance that causes terminal voltage to be decreased if the current drawn large.

* Ideal current source:-

Ideal current source is the one that supplies the same current to any resistance connected across its terminals. However, it is difficult to construct such current source because it has some internal resistance that increases the

current. If is the resistance connected across the terminals is made too large.

b) Independent voltage & current source:

whose voltage and current doesn't depends on other ckt. variable.


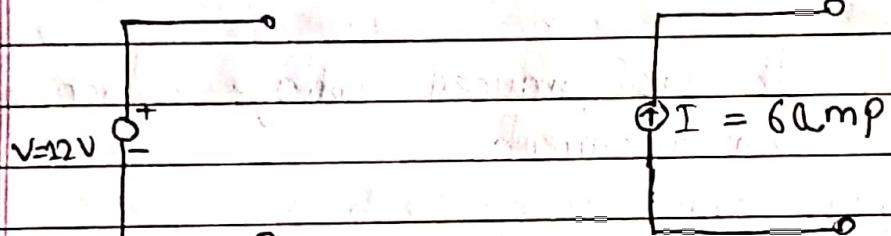


fig (a)

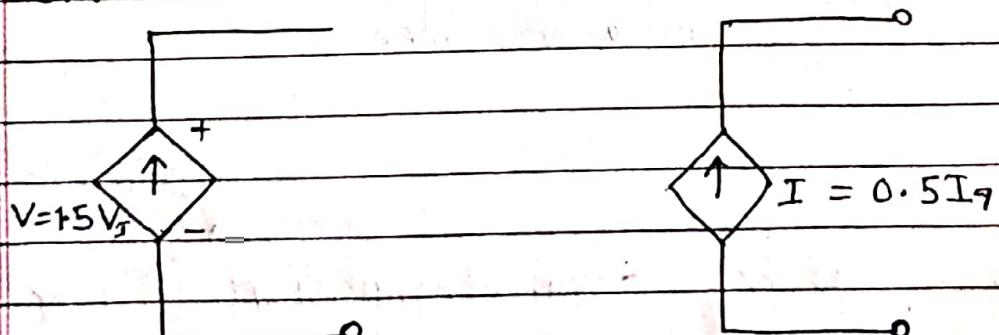A dependent voltage and current source is that whose voltage & current depends on the other ckt. variable.



Here are four types of dependent Sources:

① Voltage - dependent voltage source (VDVs)


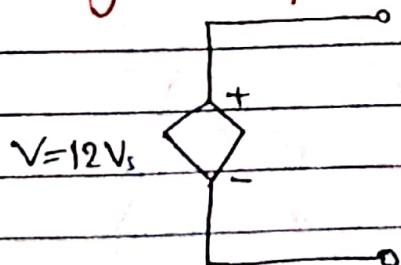


fig @


It produce voltage which depends on the voltage.

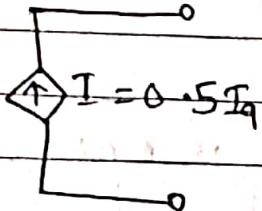② Current-dependent current source (CDCS):




It produced current that depends on the current source.

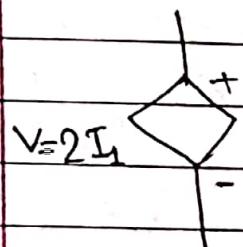③ Currents-dependent voltage source (CDVS):



It is produced voltage which depends on a current.


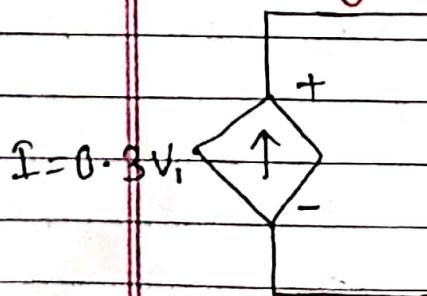
④ Voltage-dependent Current Source (VDVS):




It produce a current which depends on a variable.

short note - 5 marks
numerical - 7 marks

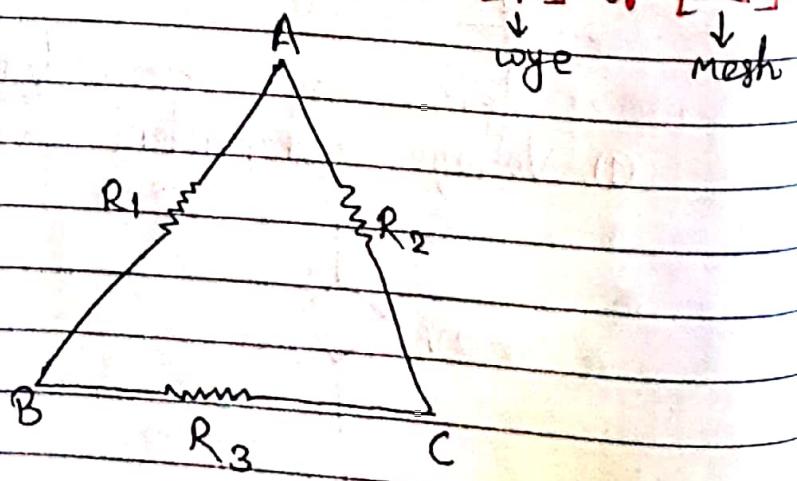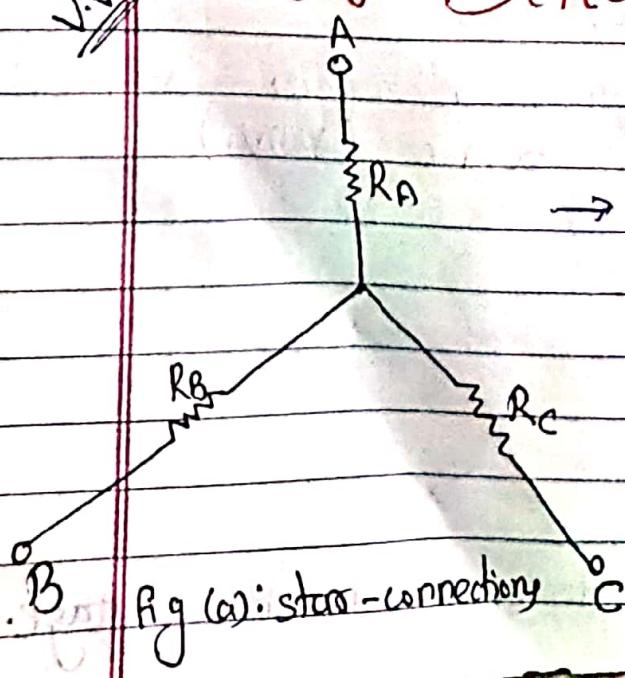~~Star-Delta Transformation~~ [Y] or [Δ]:



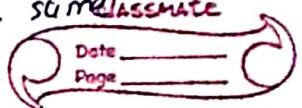These two arrangements will be electrically same if the resistance as measured bet' any pair of terminals is the same in both the arrangement.



Star Connections :-

Now, consider the star-connections ckt, the register from the terminal AB, BC and CA.

$$R_{AB} (Y) = R_A + R_B$$

$$R_{BC} (Y) = R_B + R_C$$

$$\& R_{CA} (Y) = R_C + R_A$$

Delta Connections :-

Resistance seen from the terminal AB, BC & CA (R₁ is parallel with series of R₂ & R₃).

$$R_{AB} (\Delta) = R_1 \parallel (R_2 + R_3)$$

$$= \frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{BC} (\Delta) = R_3 \parallel (R_1 + R_2)$$

$$= \frac{R_3 \times (R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{CA} (\Delta) = R_2 \parallel (R_1 + R_3)$$

$$= \frac{R_2 \times (R_1 + R_3)}{R_1 + R_2 + R_3}$$

Now,

if we equate the resistance of star to delta (Δ) ckt:

$$R_A + R_B = \frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3} \quad \text{--- (1)}$$

$$R_B + R_C = \frac{R_3 \times (R_1 + R_2)}{R_1 + R_2 + R_3} \quad \text{--- (1)}$$

$$R_c + R_A = \frac{R_2 \times (R_1 + R_3)}{R_1 + R_2 + R_3} \quad \textcircled{III}$$

Subtracting eqⁿ (II) from (I) & adding eqⁿ (III),

~~$R_A + R_B - R_B - R_C - R_C + R_A =$~~

$$\begin{aligned} R_A + R_B - R_B - R_C &= \frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3} - \left[\frac{R_3 \times (R_1 + R_2)}{R_1 + R_2 + R_3} \right] + \left[\frac{R_2 \times (R_1 + R_3)}{R_1 + R_2 + R_3} \right] \\ &+ R_C + R_A \end{aligned}$$

$$\text{on 2 } R_A = \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} - \frac{R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3} + \frac{R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3}$$

$$\text{on 2 } R_A = \frac{R_1 R_2 + R_1 R_3 - R_1 R_3 - R_2 R_3 + R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3}$$

$$\text{on 2 } R_A = \frac{2 R_1 R_2}{R_1 + R_2 + R_3}$$

$$\therefore R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3} \quad \textcircled{IV}$$

Delta to star transformation
Similarly,

$$R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3} \quad \checkmark$$

$$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3} \quad \textcircled{V}$$

Delta to star
transformation

Multiplying eqⁿ (IV) & (V), we get

$$\begin{aligned} R_A \times R_B &= \frac{R_1 R_2}{R_1 + R_2 + R_3} \times \frac{R_1 R_3}{R_1 + R_2 + R_3} \\ &= \frac{R_1^2 R_2 R_3}{(R_1 + R_2 + R_3)^2} \end{aligned}$$
(VI)

Similarly,

$$\begin{aligned} R_B \times R_C &= \frac{R_1 R_3}{(R_1 + R_2 + R_3)} \times \frac{R_2 R_3}{R_1 + R_2 + R_3} \\ &= \frac{R_1 R_2 R_3^2}{(R_1 + R_2 + R_3)^2} \end{aligned}$$
(VII)

$$\begin{aligned} R_C \times R_A &= \frac{R_2 R_3}{R_1 + R_2 + R_3} \times \frac{R_1 R_2}{R_1 + R_2 + R_3} \\ &= \frac{R_1 R_2^2 R_3}{(R_1 + R_2 + R_3)^2} \end{aligned}$$
(VIII)

Now, adding eqⁿ (VI), (VII) & (VIII),

$$\begin{aligned} R_A \times R_B + R_B \times R_C + R_C \times R_A &= \frac{R_1^2 R_2 R_3}{(R_1 + R_2 + R_3)^2} + \frac{R_1 R_2 R_3^2}{(R_1 + R_2 + R_3)^2} \\ &\quad + \frac{R_1 R_2^2 R_3}{(R_1 + R_2 + R_3)^2} \\ &= \frac{R_1 R_2 R_3 (R_1 + R_2 + R_3)}{(R_1 + R_2 + R_3)^2} \\ &= \frac{R_1 \cdot R_2 \cdot R_3}{R_1 + R_2 + R_3} \end{aligned}$$
(IX)


$$R_A \cdot R_B + R_B \cdot R_C + R_C \cdot R_A = R_A \cdot R_3$$

$$R_3 = \frac{R_A \cdot R_B + R_B \cdot R_C + R_C \cdot R_A}{R_A} \quad (x1)$$

$$R_2 = \frac{R_A \cdot R_B + R_B \cdot R_C + R_C \cdot R_A}{R_B} \quad (x11)$$

$$R_1 = \frac{R_A \cdot R_B + R_B \cdot R_C + R_C \cdot R_A}{R_C} \quad (x12)$$

* Star to delta transformation:

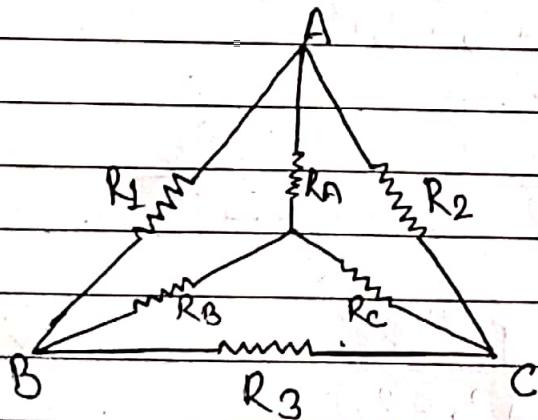

Delta to star:

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

Star to delta,



$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

Q. 1) Obtain the star connected equivalent for delta connected ckt:

PU

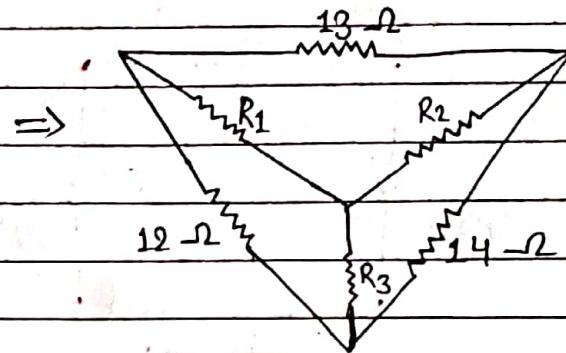
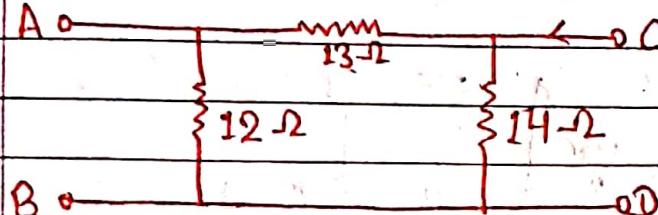


$$R_1 = \frac{12 \times 13}{12 + 13 + 14} = 4 \Omega$$

$$R_2 = \frac{13 \times 14}{12 + 13 + 14} = 4.67 \Omega$$

$$R_3 = \frac{12 \times 14}{12 + 13 + 14} = 4.31 \Omega$$

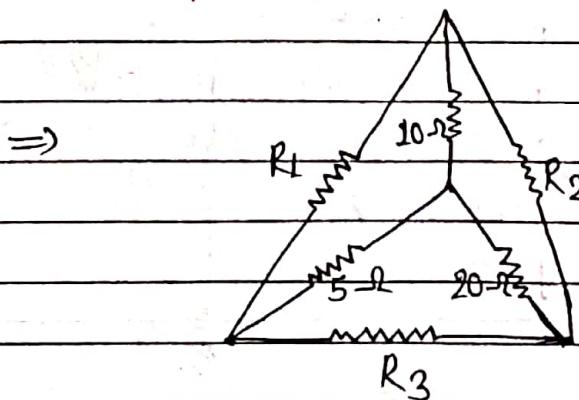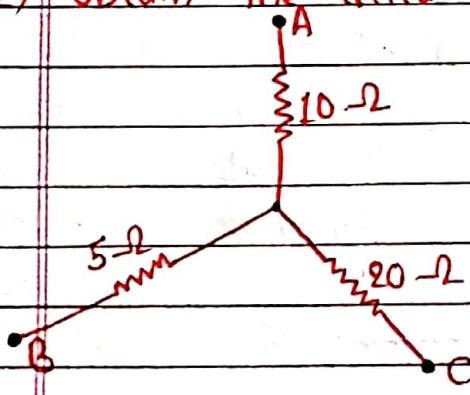Q. 2) Obtain the delta connected equivalent for star connected ckt:




$$R_1 = \frac{10 \times 5 + 5 \times 20 + 20 \times 10}{20} = 21 \Omega$$


$$R_2 = \frac{350}{5} = 70 \Omega$$

$$R_3 = \frac{350}{10} = 35 \Omega$$


finally,

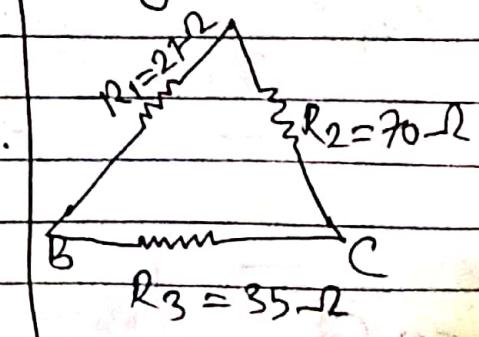

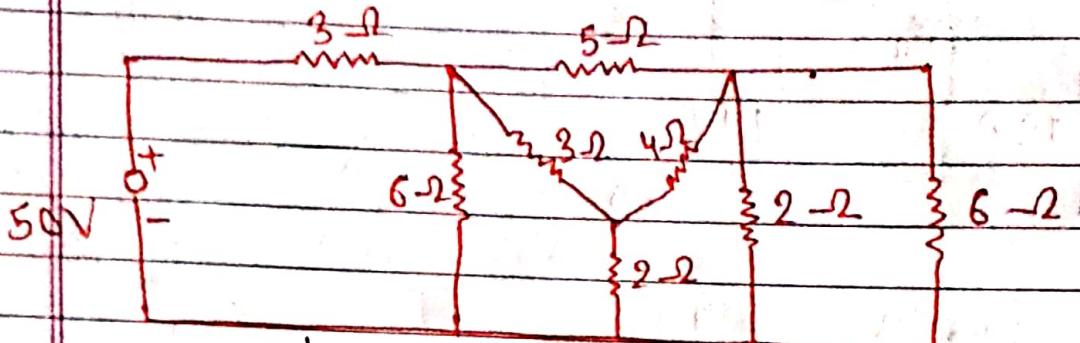Q. 3) Determine the current drawn by the ckt shown in fig.




solution:-

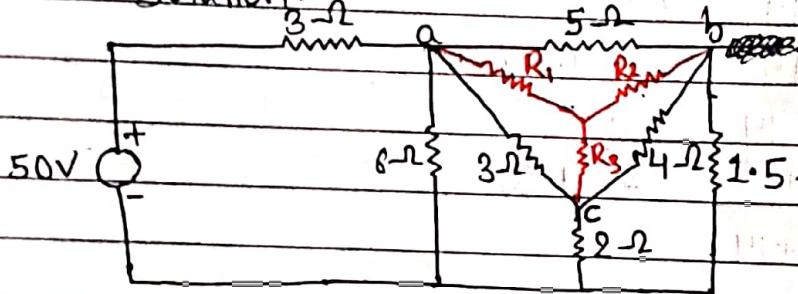

$$R_1 = \frac{5 \times 3}{3+4+5} = 1.2\Omega$$

$$R_2 = \frac{4 \times 5}{12} = 1.6\Omega$$


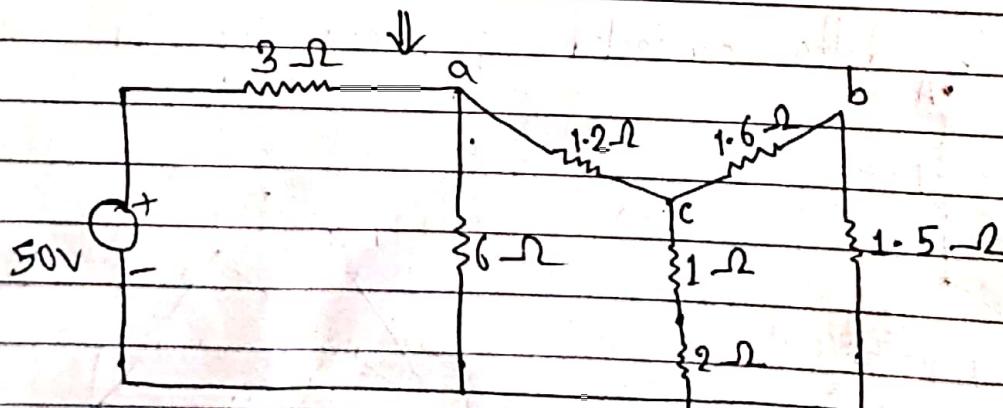
$$R_3 = \frac{3 \times 4}{12} = 1\Omega$$




$$T = V$$

$$R_T = \frac{50}{4.87}$$


$$= 10.27A$$

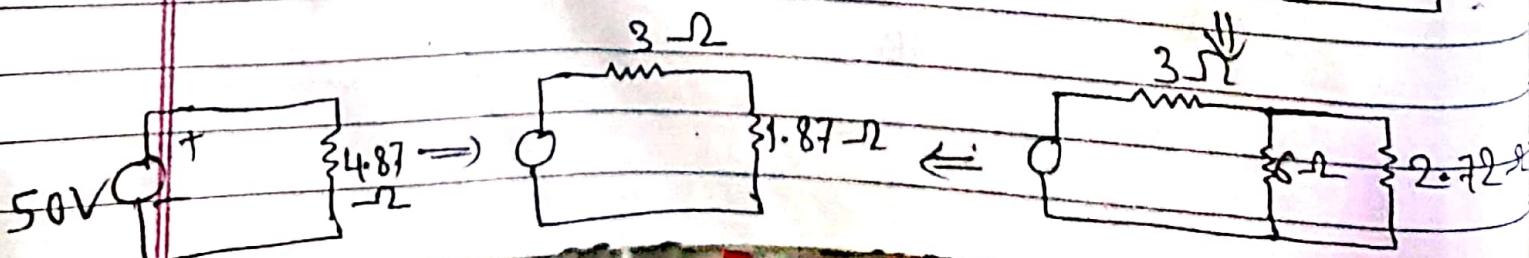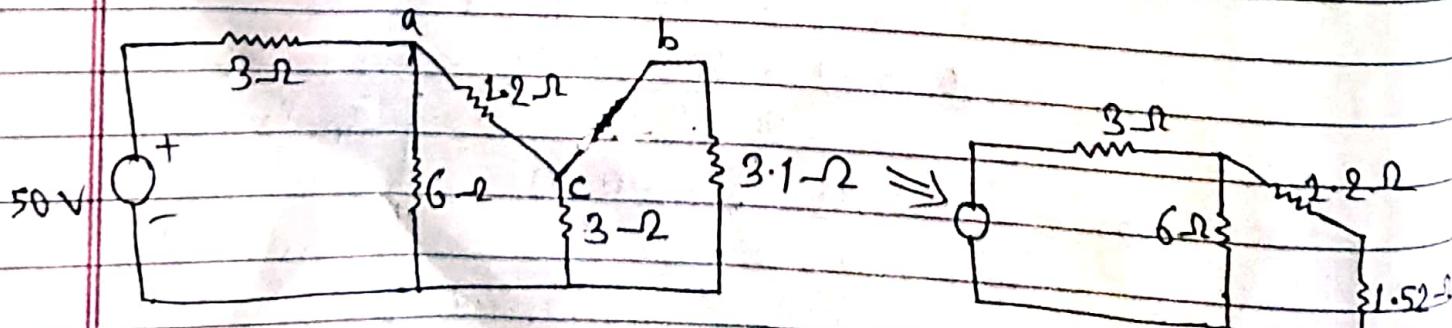

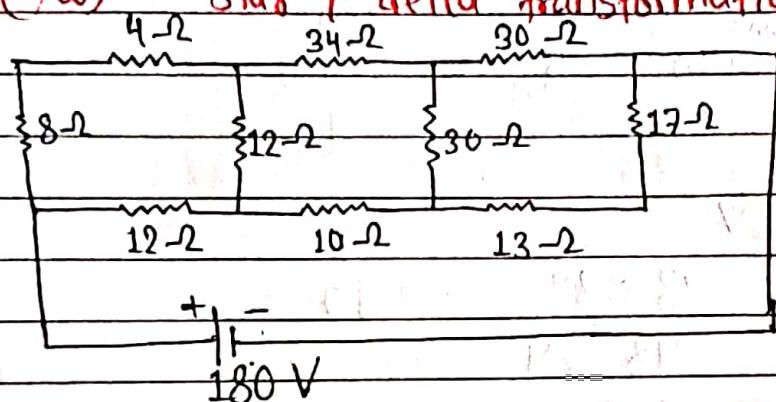Q. 4) Determine the value of current in $10\ \Omega$ resistance in network (N/w). star / delta transformation ckt is given below:



solution:

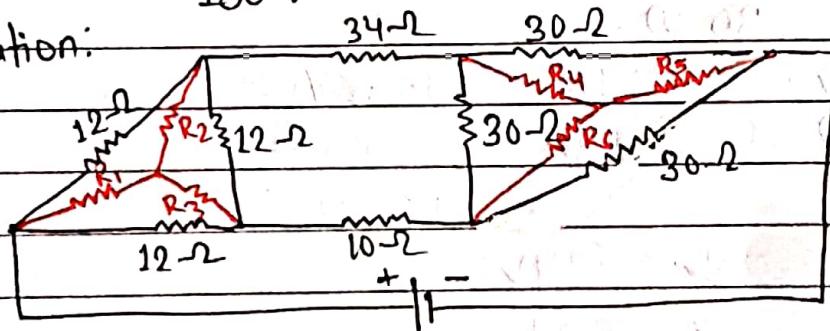

$$R_1 = \frac{12 \times 12}{12 + 12 + 12} = 4\ \Omega$$


$$R_4 = \frac{30 \times 30}{30 + 30 + 30} = 10\ \Omega$$

$$R_2 = \frac{12 \times 12}{12 + 12 + 12} = 4\ \Omega$$

$$R_5 = \frac{30 \times 30}{30 + 30 + 30} = 10\ \Omega$$

$$R_3 = \frac{12 \times 12}{12 + 12 + 12} = 4\ \Omega$$

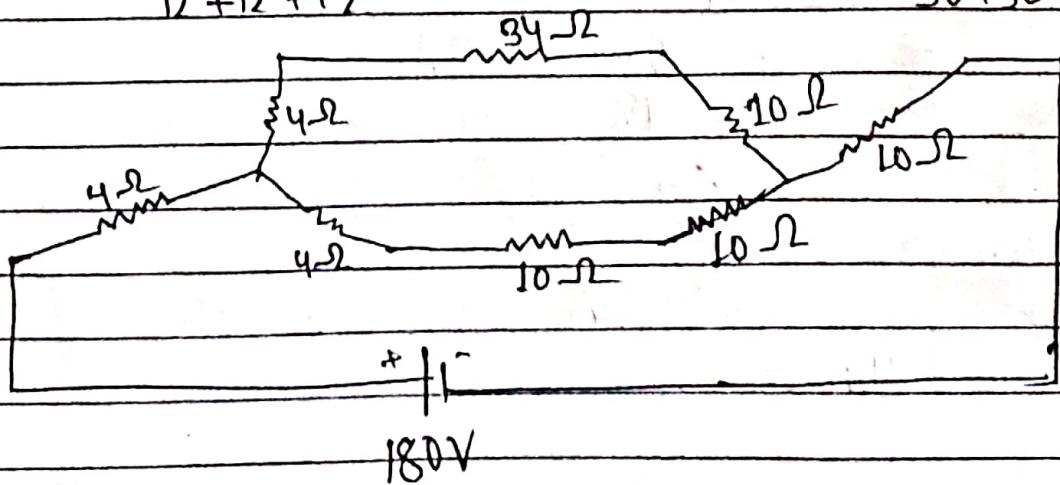
$$R_6 = \frac{30 \times 30}{30 + 30 + 30} = 10\ \Omega$$



$$V = IR$$

$$I = \frac{V}{R}$$

classmate
Date: 10/10/2023
Page: 10

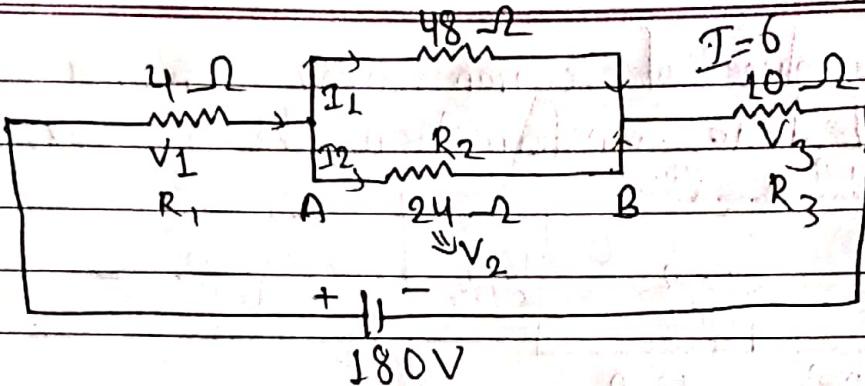

$$R_T = 4 + \frac{48 \times 24}{48+24} + 10$$

$$\therefore R_T = 30 \Omega$$

$$\therefore I = \frac{V}{R} = \frac{180}{30} = 6 A$$

So,

$$V_1 = IR_1 = 4 \times 6 = 24 V$$

$$V_2 = IR_2 = 6 \times 24 =$$

$$V_3 = IR_3 = 6 \times 10 = 60 V$$

$$V_2 = 180 - 60 - 24 = 96 V$$

For 48Ω resistance,

$$V = I_1 R \quad [V \text{ is same in } ||]$$

$$\Rightarrow 96 = I_1 R$$

$$\Rightarrow I_1 = \frac{96}{48} = 2 A$$


$$\therefore I = I_1 + I_2$$

$$\text{or } 6 = 2 + I_2$$

$$\Rightarrow I_2 = 4 A$$

$$I_{10} = 4 A$$

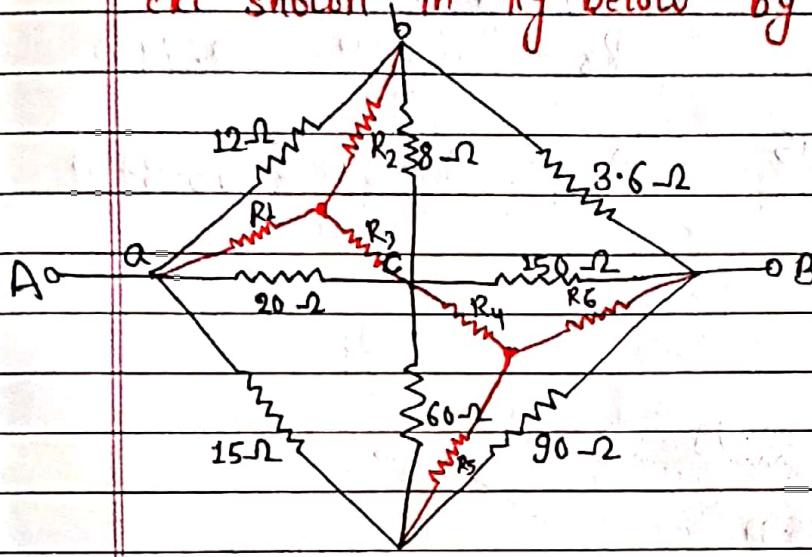Q.5) Resistance measured between terminals A and B of the ckt shown in fig below by star delta transformation:



$$R_1 = \frac{12 \times 20}{12 + 20 + 8} = 6\Omega$$

$$R_2 = \frac{12 \times 8}{12 + 20 + 8} = 2.4\Omega$$

$$R_3 = \frac{20 \times 8}{12 + 20 + 8} = 4\Omega$$


Similarly,

$$R_4 = \frac{150 \times 60}{60 + 90 + 150} = 30\Omega$$

$$R_5 = \frac{60 \times 90}{60 + 90 + 150} = 18\Omega$$



$$R_6 = \frac{150 \times 90}{60 + 90 + 150} = 45\Omega$$

From above fig.,


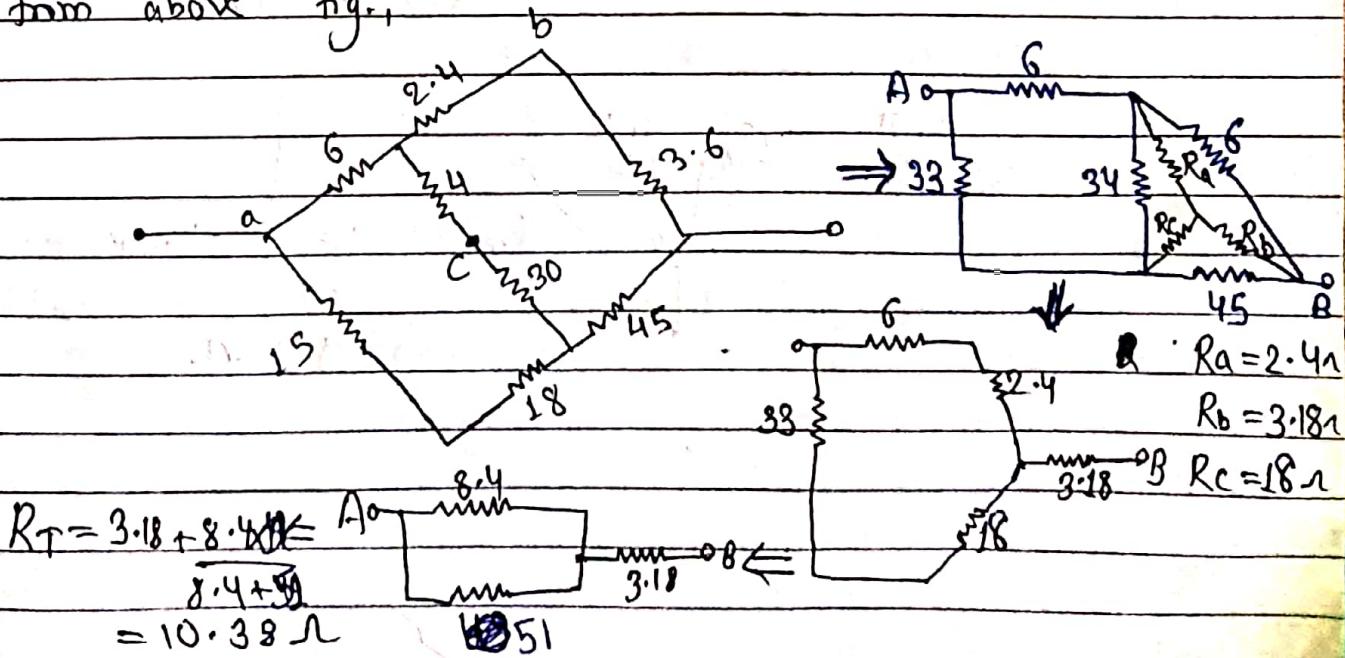



$$R_T = 3.18 + 8.4 = 10.38\Omega$$

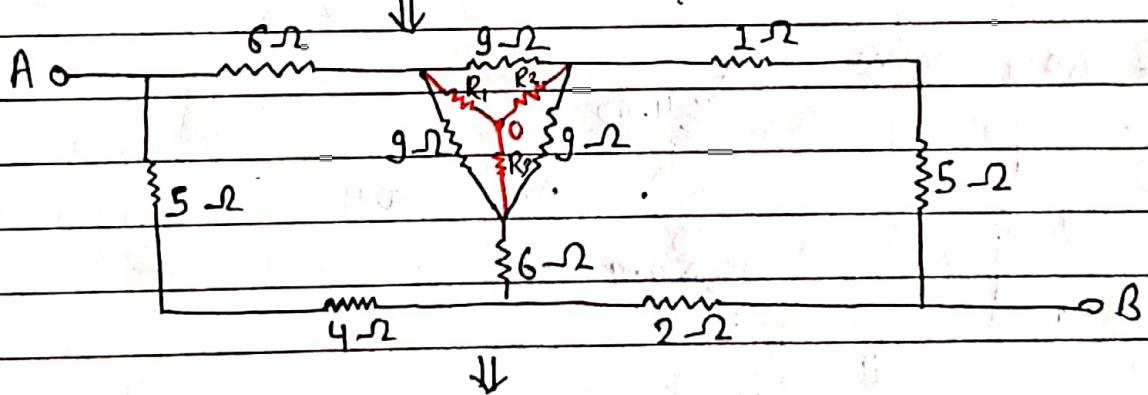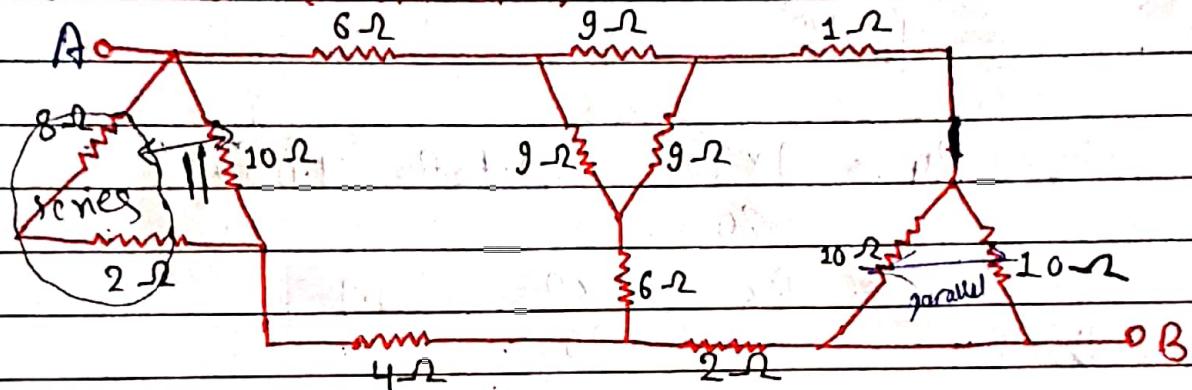Q.6) Calculate the equivalent resistance between point A & B (by star-delta transformation):



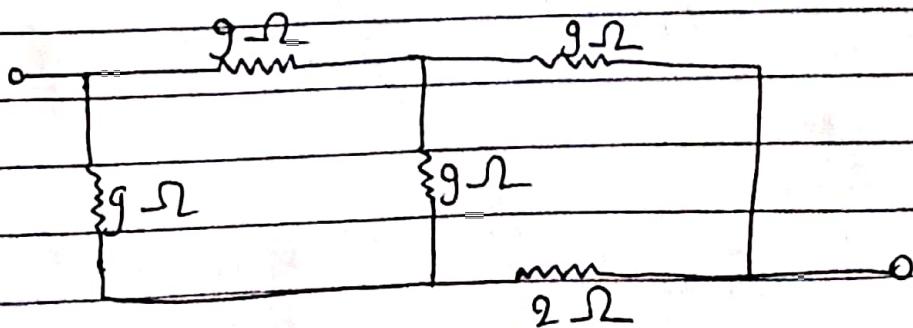
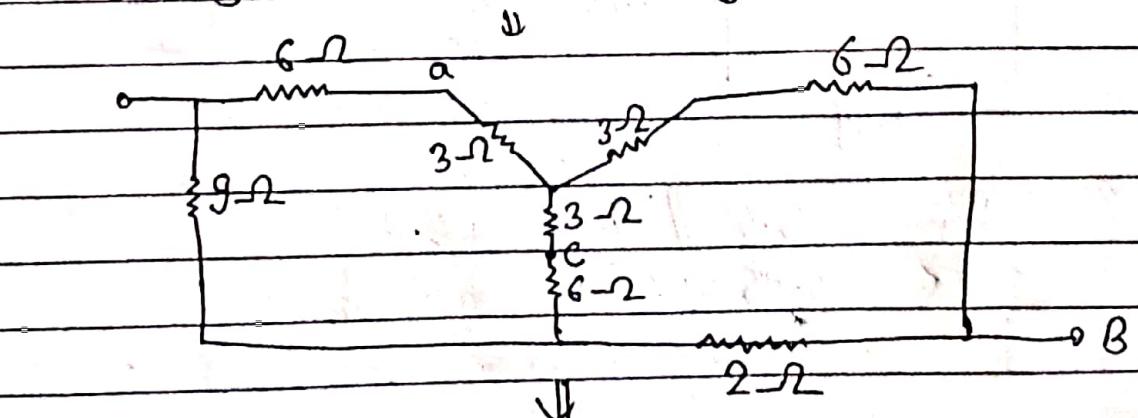
$$R_1 = \frac{9 \times 9}{9+9+9} = 3\Omega, \quad R_2 = \frac{9 \times 9}{9+9+9} = 3\Omega, \quad R_3 = \frac{9 \times 9}{9+9+9} = 3\Omega$$



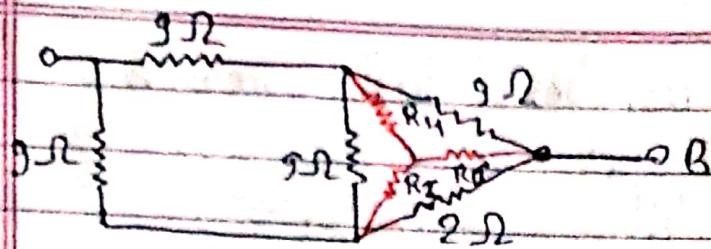

$$R_4 = \frac{9 \times 9}{20} = 4.05 \Omega$$

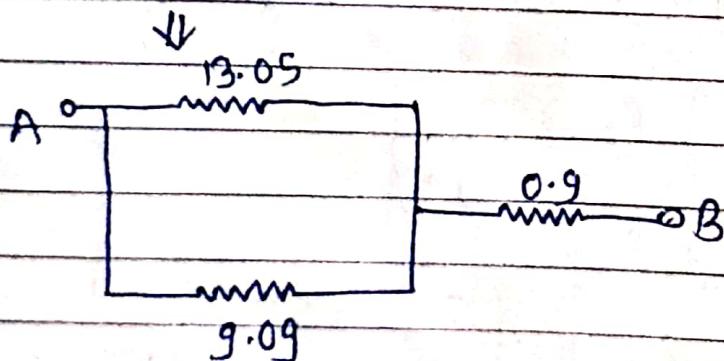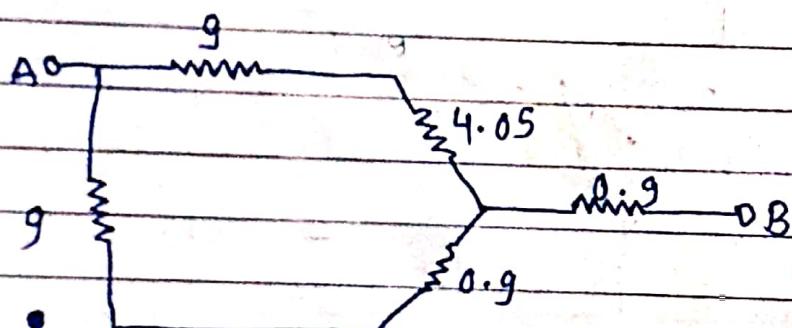~~$$R_5 = R_6 = \frac{9 \times 2}{20} = 0.9$$~~





$$R_T = 13.05 \parallel 9.09 + 0.9$$

$$= 6.26 \Omega$$

Q.7) Use the star-delta convention to find the resistance as seen from the battery terminal & hence find the current supply by the battery.

Soln :-



Star / delta eq. ckt is

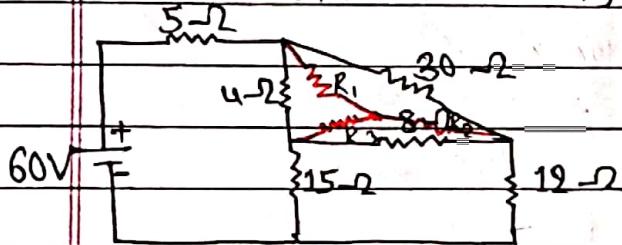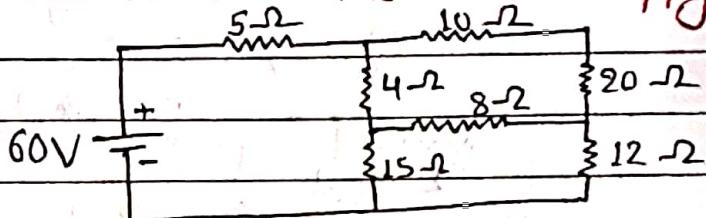

Considering star eq. to delta ckt,

$$R_1 = \frac{30 \times 4}{30 + 4 + 8} \Omega = 2.86 \Omega$$
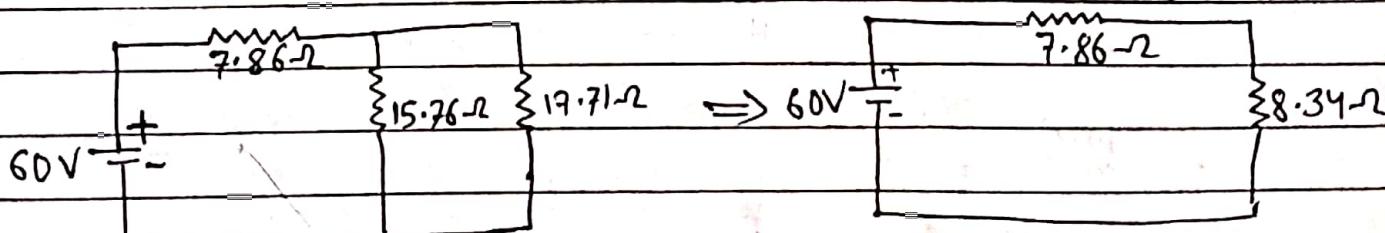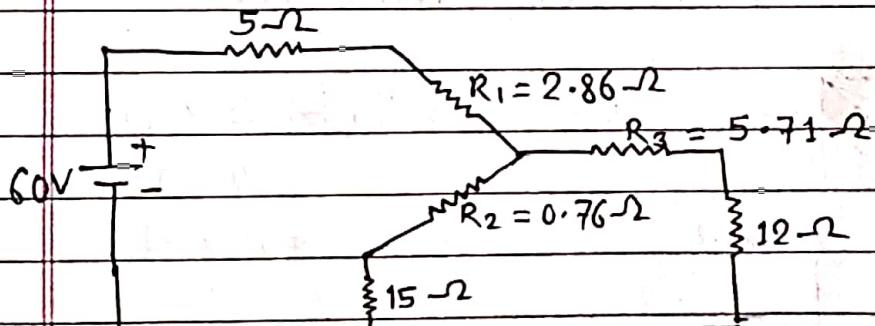
$$R_2 = \frac{4 \times 8}{4 + 8} = 0.76 \Omega, R_3 = \frac{30 \times 8}{4 + 8} = 5.71 \Omega$$




$$\therefore R_{eq} = (7.86 + 8.34) \Omega = 16.2 \Omega$$


Now,

$$\text{Current} = \frac{V}{R_{eq}} = \frac{60V}{16.2\Omega} = 3.7 \text{ ampere}$$


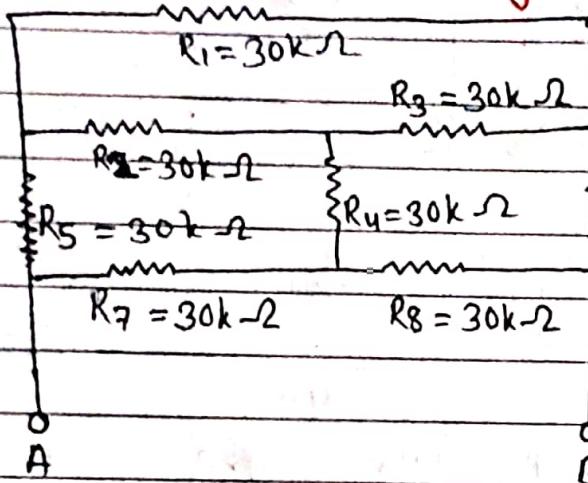
Q. 15) Find the equivalent resistance across the terminal AB for ckt shown in fig @ below:






Soln :- Considering the eq. star ckt,

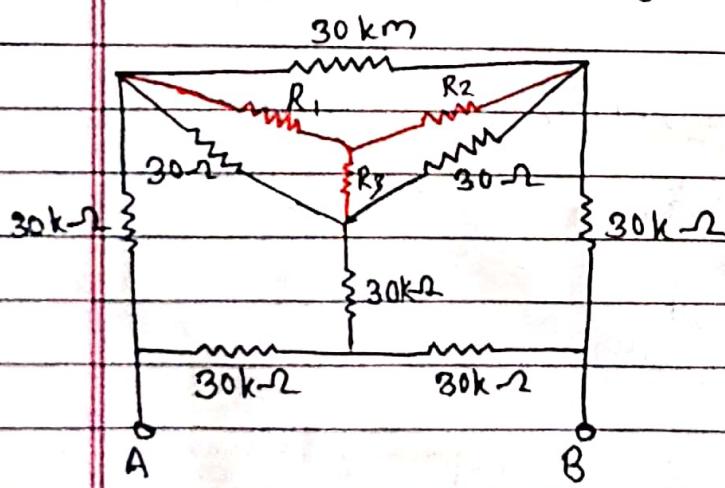
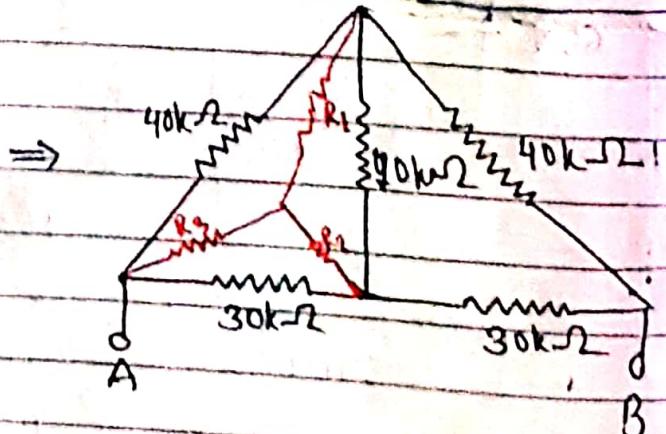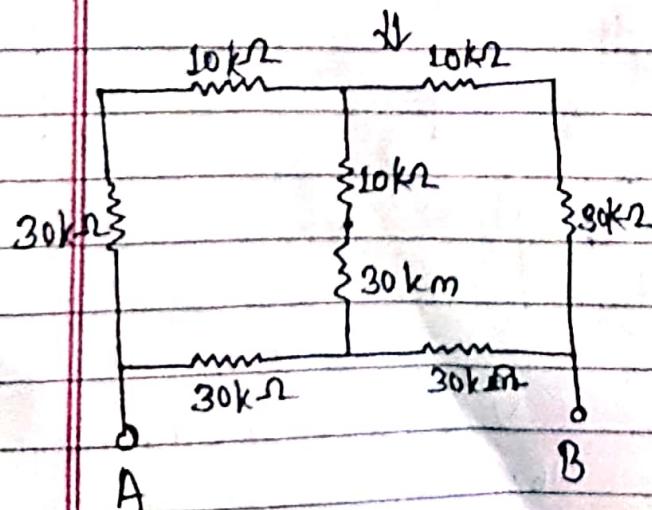
$$R_1 = R_2 = R_3 = \frac{30 \times 30}{30 + 30 + 30} = 10\text{k}\Omega$$



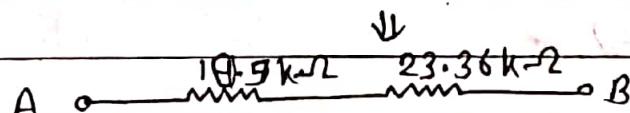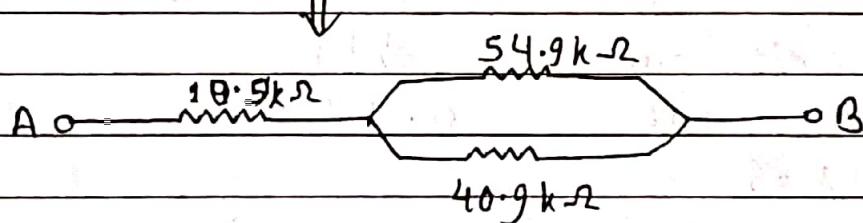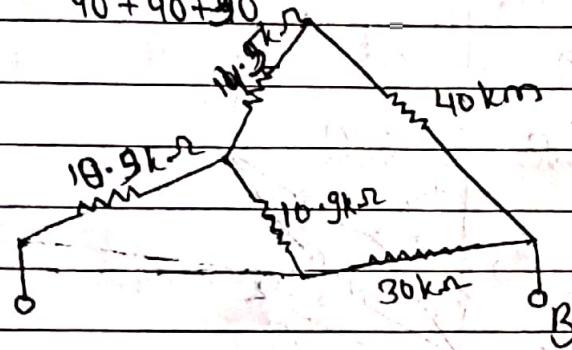
$$R_1 = \frac{40 \times 40}{40+40+30} \text{ k}\Omega = 14.5 \text{ k}\Omega ; R_2 = R_3 = \frac{30 \times 40}{40+40+30} = 10.9 \text{ k}\Omega$$




$$\therefore \text{Req} = (10.9 + 23.36) \text{ k}\Omega \\ = 34.26 \text{ k}\Omega$$

Q.12 Find the equivalent resistance:

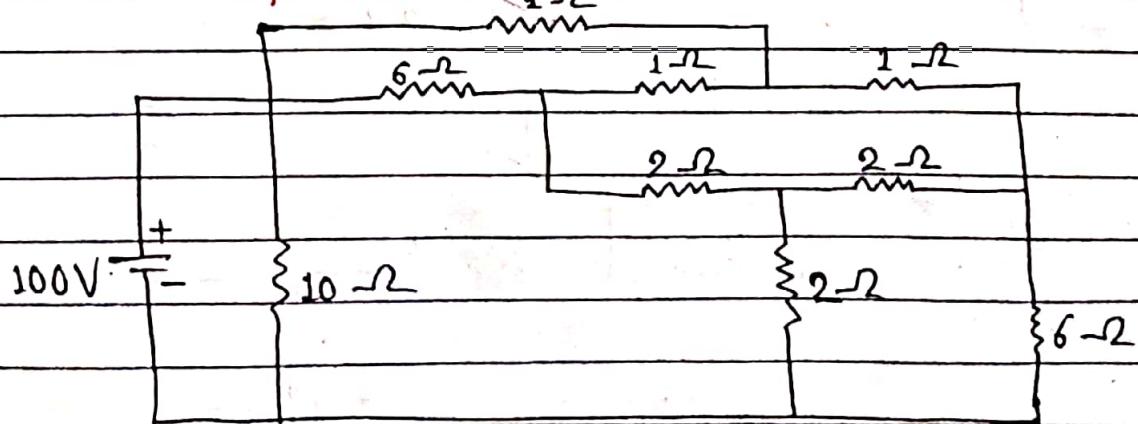



solution:

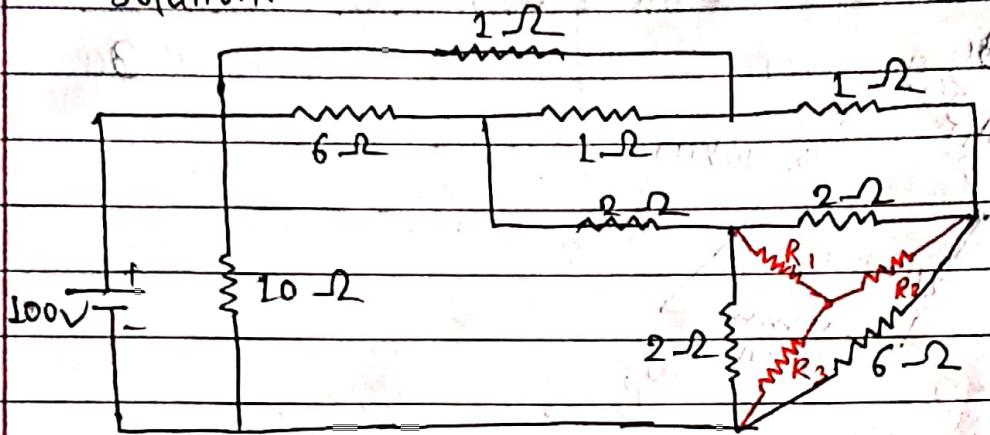


Considering the eq. star ckt:

$$R_1 = \frac{2 \times 2}{2+2+6} \Omega = 0.4 \Omega$$
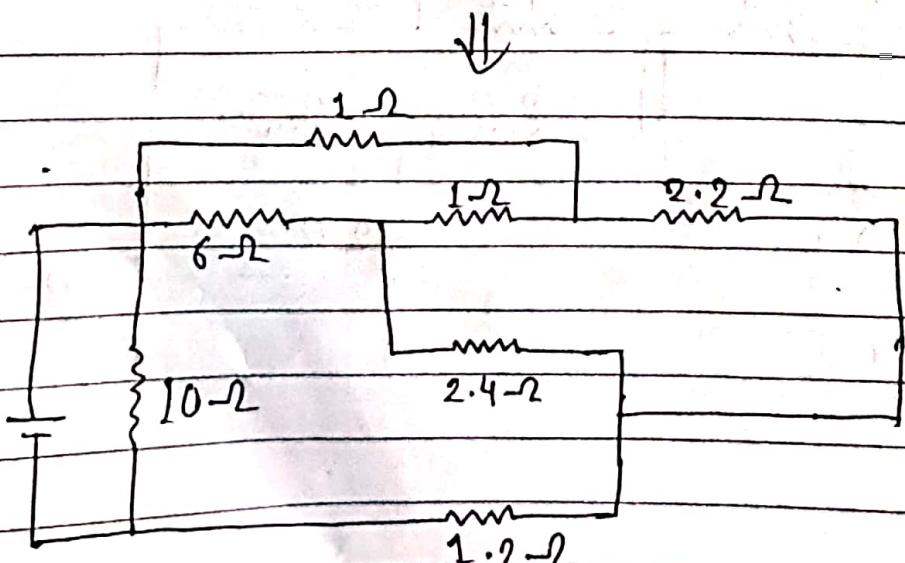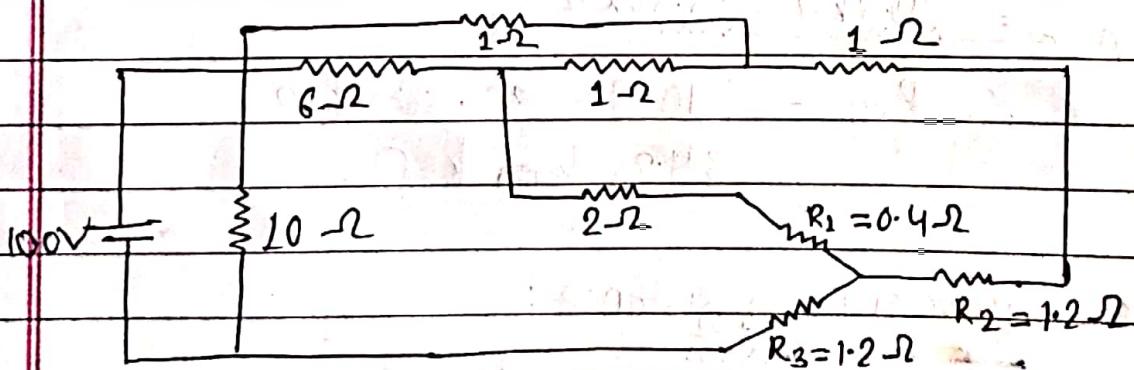
$$R_2 = R_3 = \frac{2 \times 6}{2+2+6} \Omega = 1.2 \Omega$$




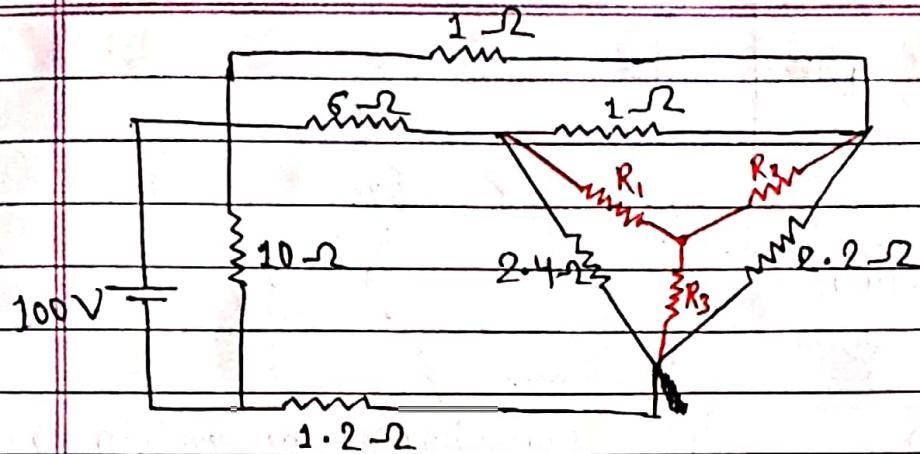




Considering the equivalent star ckt,

$$R_1 = \frac{1 \times 2.4}{2.4 + 2.2 + 1} \Omega = 0.43\Omega$$

$$R_2 = \frac{1 \times 2.2}{2.4 + 2.2 + 1} \Omega = 0.39\Omega$$
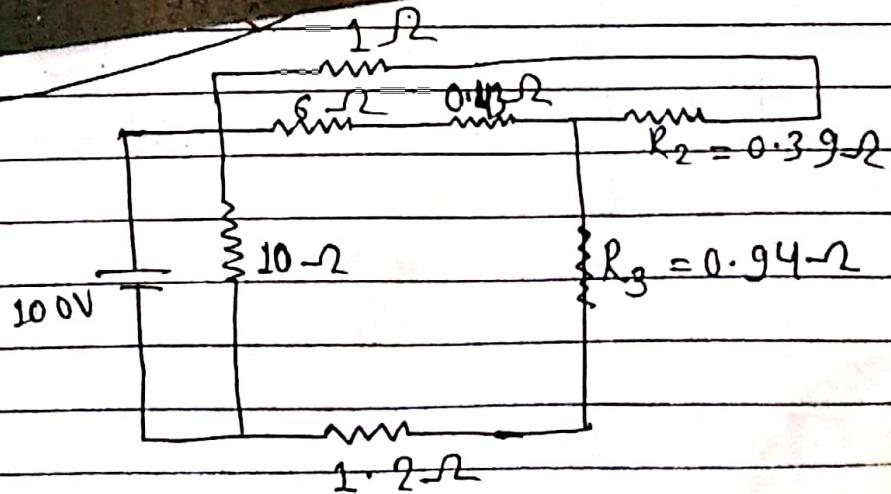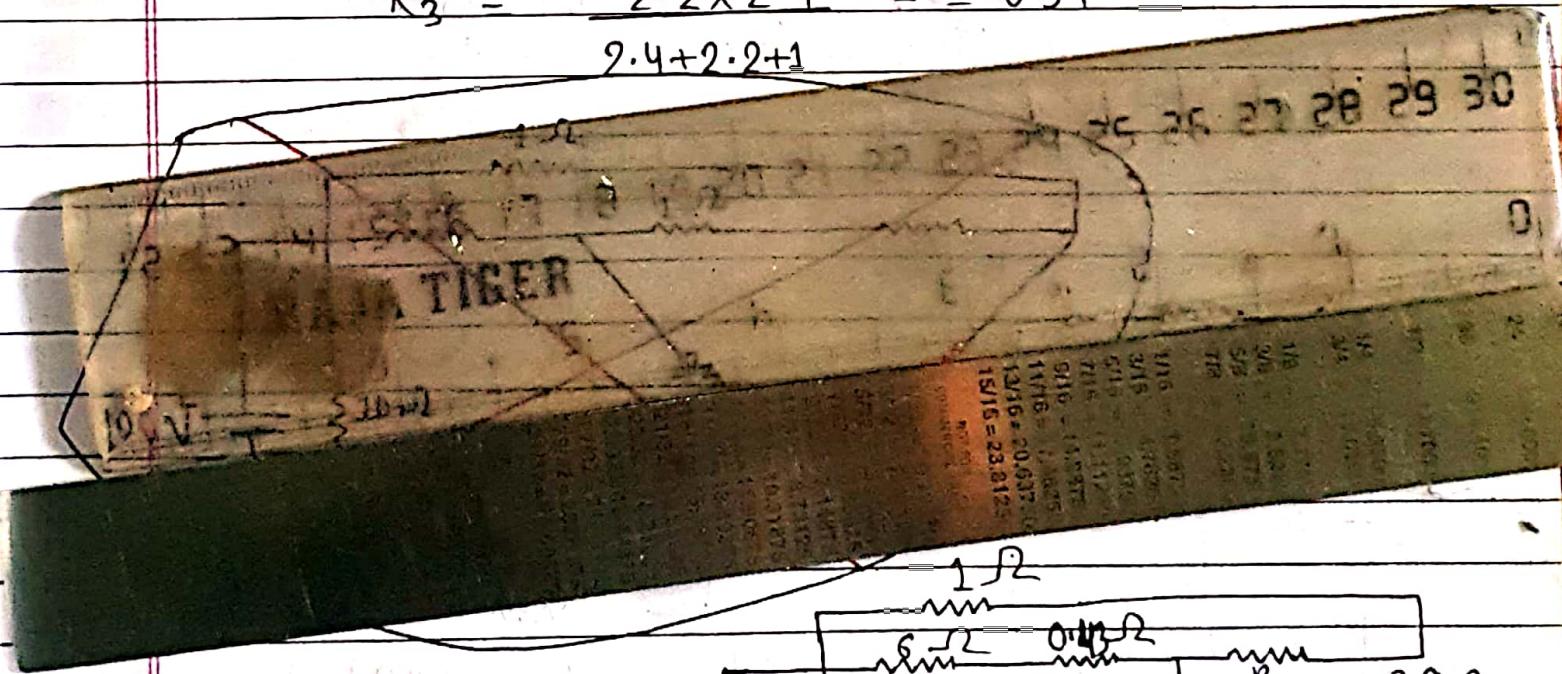
$$R_3 = \frac{2.2 \times 2.4}{2.4 + 2.2 + 1} \Omega = 0.94\Omega$$



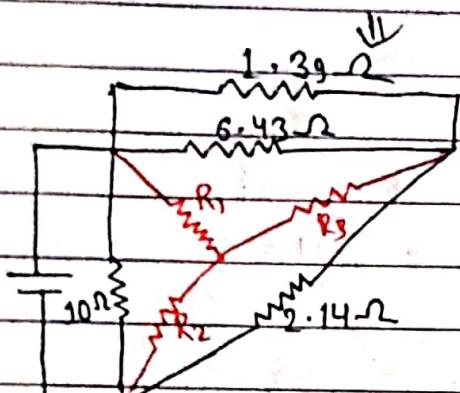
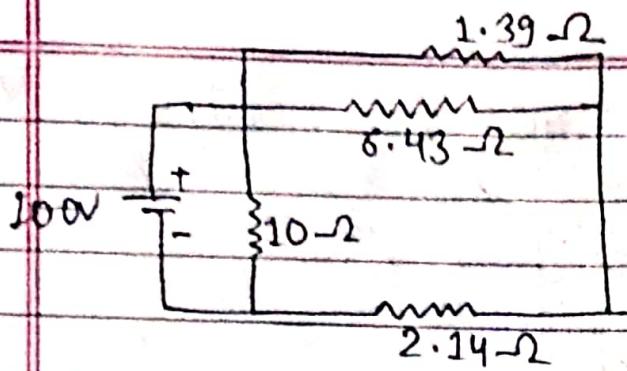


Considering the eq. star ckt,

$$R_1 = \frac{10 \times 6.43}{10 + 6.43 + 2.14} \Omega = 3.46 \Omega$$

$$R_2 = \frac{10 \times 2.14}{10 + 6.43 + 2.14} \Omega = 1.15 \Omega$$

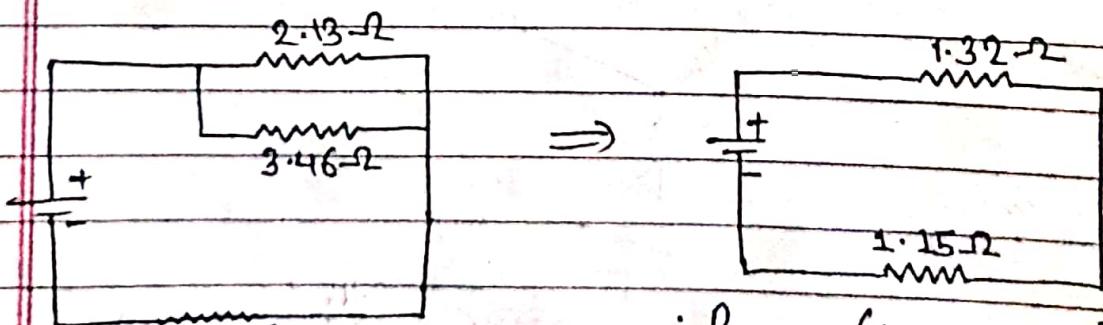
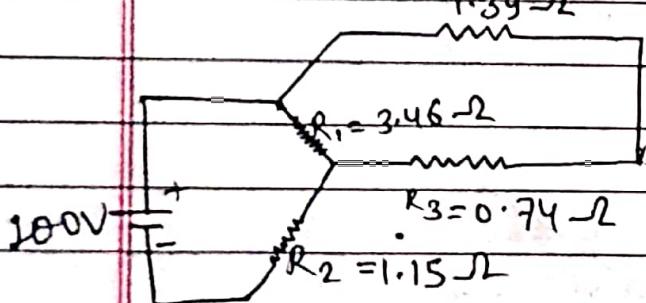
$$R_3 = \frac{6.43 \times 2.14}{10 + 6.43 + 2.14} \Omega = 0.74 \Omega$$



$$\therefore R_{eq} = (1.15 + 1.32) \Omega = 2.47 \Omega$$

Q.8 Find R_{AB} by using star to delta conversion techniques:



PV

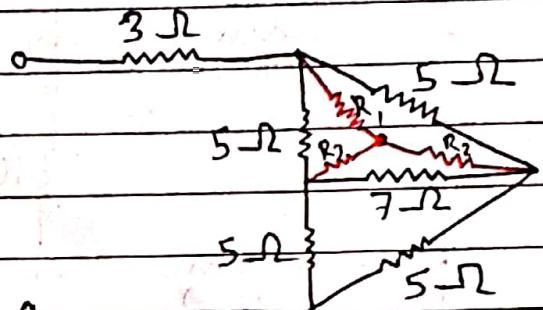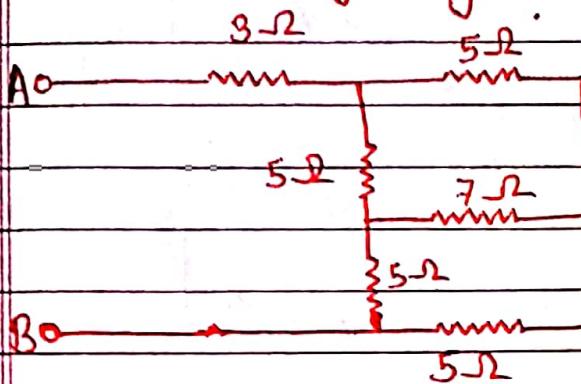

$$R_1 = \frac{5 \times 7}{5+5+7} = \frac{35}{17} \Omega = 2.06 \Omega$$

$$R_2 = R_3 = \frac{5 \times 7}{5+5+7} = \frac{35}{17} \Omega = 2.06 \Omega$$


W

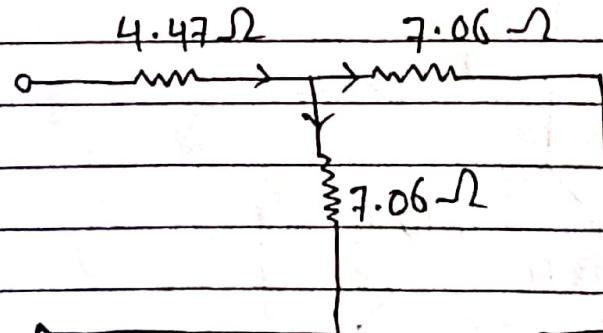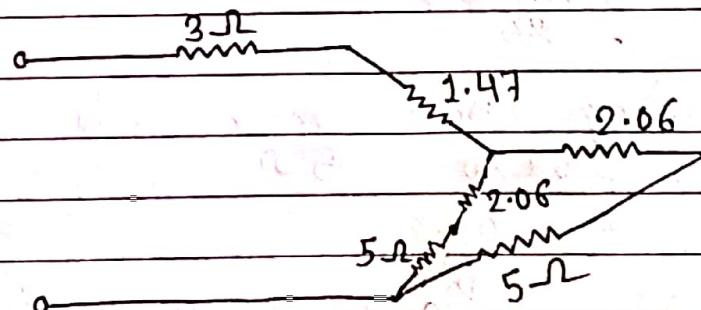


$$\therefore R_T = 4.47 + 3.52 = 7.99 \Omega$$

Q. 9) Convert the following delta Δ N/ω to star (\star) N/ω .

PU

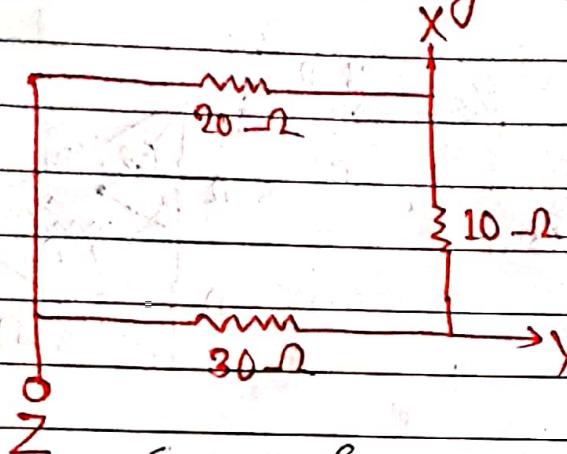

From figure above

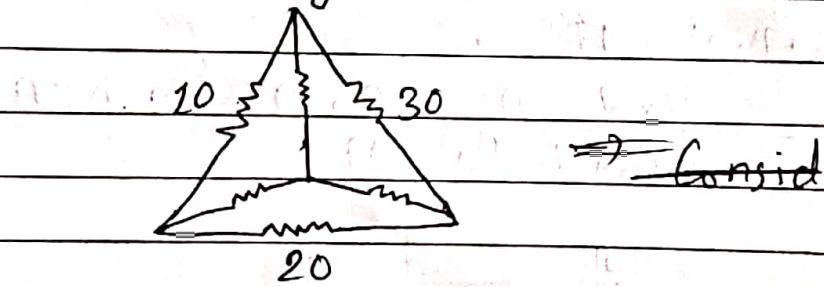


Converting above mesh into star network,


$$R_1 = \frac{10 \times 30}{60} = 5 \Omega, R_2 = \frac{20 \times 30}{60} = 10 \Omega$$

$$R_3 = \frac{10 \times 20}{60} = 3.33 \Omega$$

$$\left\{ 5 \Omega \right.$$

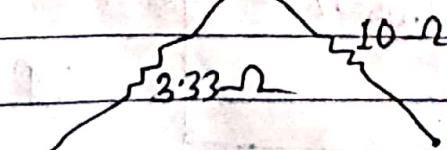


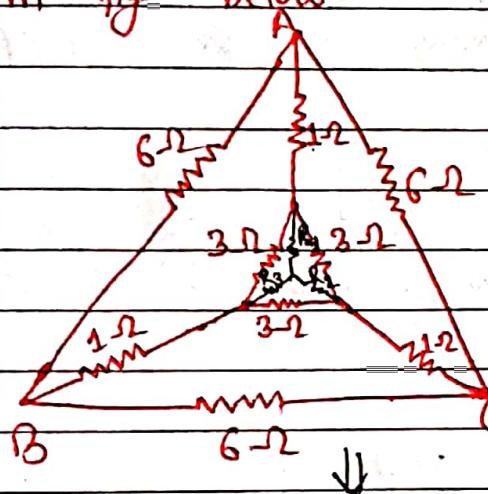
Q. 10) Determine the resistance betⁿ point A & B N/w shown in fig. below:



Considering the eq. star ckt;

$$R_1 = \frac{3 \times 3}{3+3+3} = 1\Omega$$

$$R_1 = R_2 = R_3 = 1\Omega$$

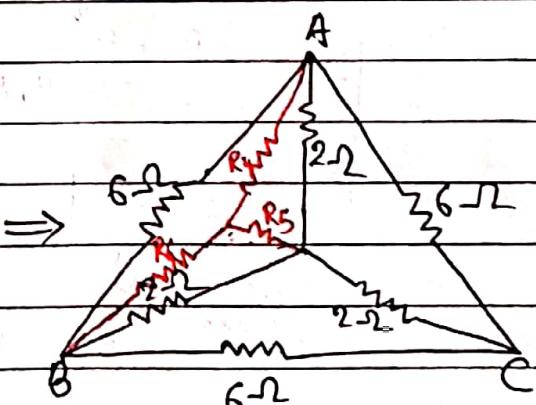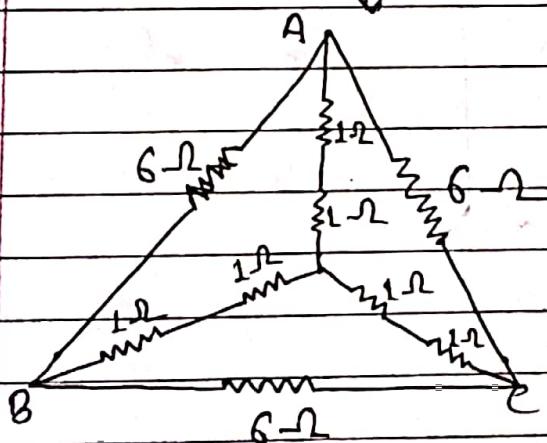




Considering the eq. star ckt;

$$R_4 = \frac{6 \times 2}{6+2+2} = \frac{12}{10} = 1.2\Omega$$

$$R_5 = \frac{2 \times 2}{10} = 0.4\Omega$$
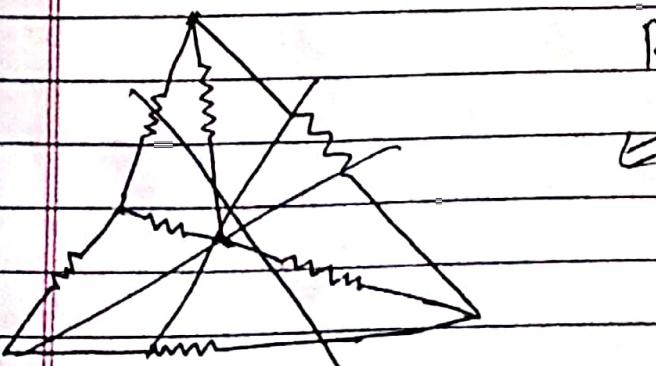
$$R_6 = \frac{6 \times 2}{10} = 1.2\Omega$$



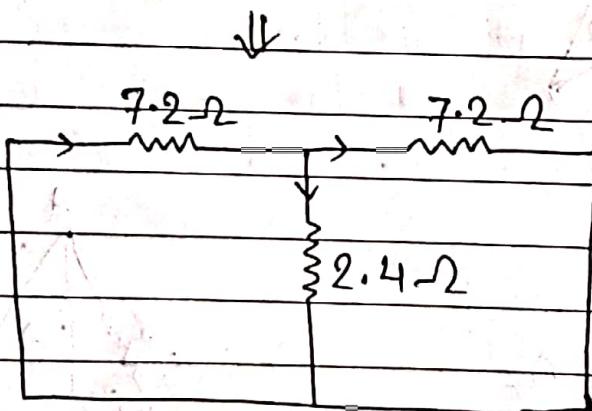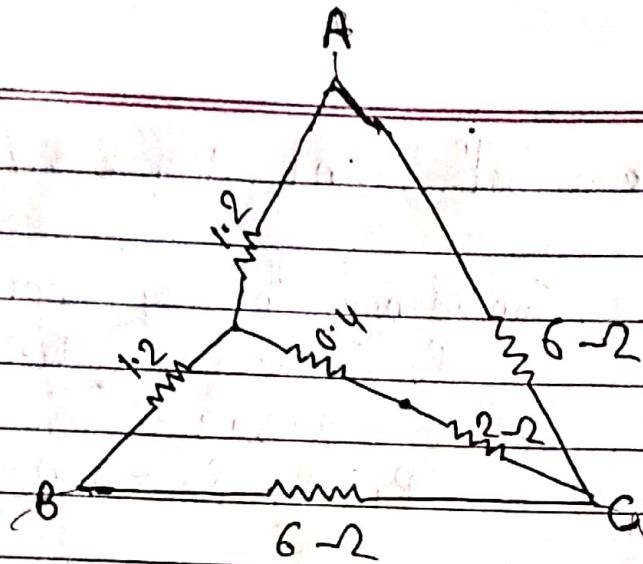


$$R_T = 7.2 + \frac{7.2 \times 2.4}{7.2 + 2.4}$$
$$= 9 \Omega$$

Kirchhoff's Current & Voltage law

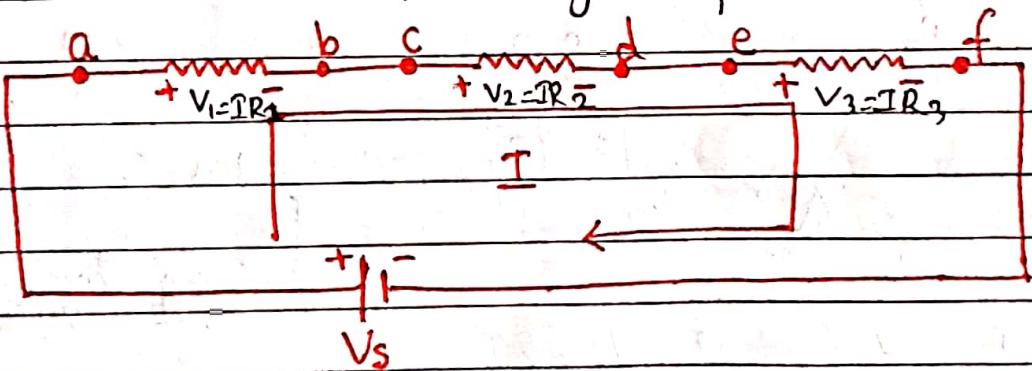1) Kirchhoff's Voltage Law:-

It states that, algebraic sum of the voltage around any closed path in a circuit is always zero (0). In any circuit, the voltage drop across the registers always have polarity opposite to the source polarity. When the current is passing through the resistor, there is loss of energy & therefore voltage drops. In any element, the current flow from higher potential to lower potential.




It is customary to take the direction of current I indicate in fig. above. It leaves the +ve terminal of the voltage source & enter into -ve terminal as the current passes in the circuit, ~~sum~~ of the voltage drops around the loop is equal to the total voltage in that loop. The voltage at a point a, c & e are more than the voltage at points b, d & f.

So,

$$V_s = V_1 + V_2 + V_3$$

Eg. 1:

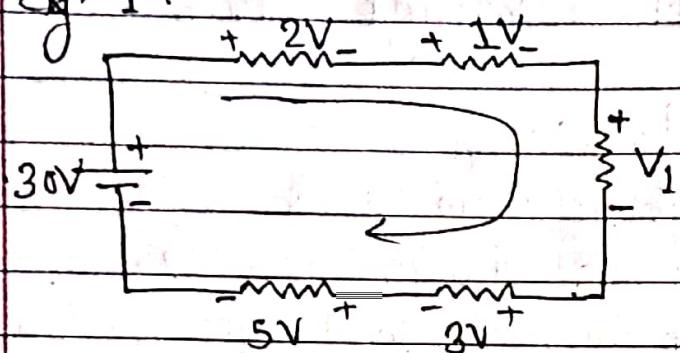

$$V_s = V_1 + V_2 + V_3 + V_4 + V_5$$


$$\therefore 30 = 2 + 1 + V_1 + 3 + 5$$

$$\therefore V_1 = 19V$$

Eg. 2) The given ckt in fig @ below find

@ The current I

b) The voltage across 30Ω

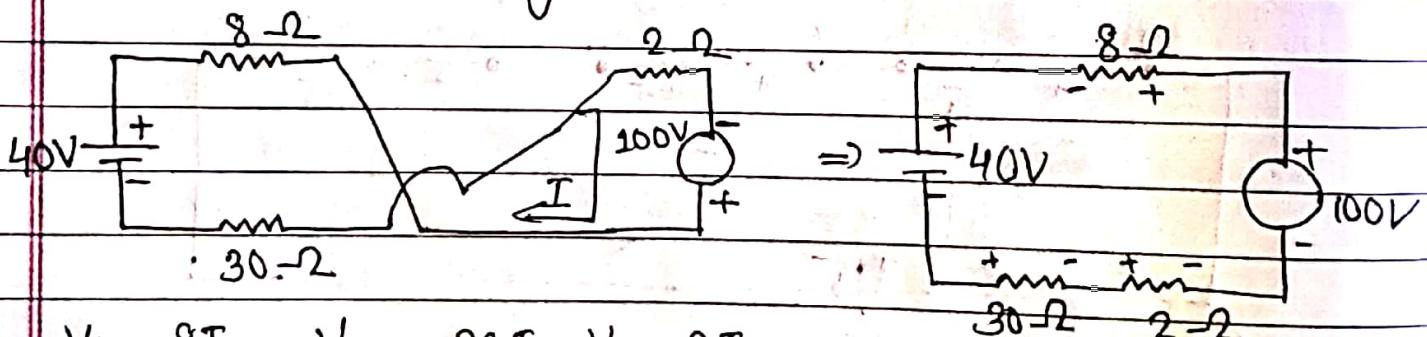

$$V_8 = 8I, V_{30} = 30I, V_2 = 2I$$

Kirchoff's voltage law,


$$100 = 8I + 30I + 2I + 40 \\ \Rightarrow I = 1.5A$$

$$V_{30} = 30 \cdot I = 30 \times 1.5 = 45V$$

Voltage division :-

$$I = \frac{V_3}{R_1 + R_2 + R_3 + \dots + R_m}$$
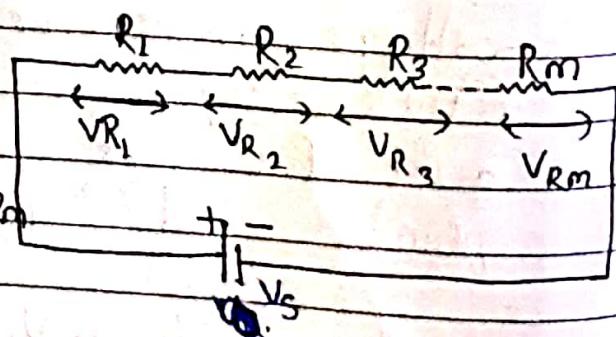
$$V_{R_1} = IR_1, V_{R_2} = IR_2, V_{R_3} = IR_3, \dots, V_{R_m} = IR_m$$



$$\therefore V_{Rm} = V_s \cdot \frac{R_m}{R_1 + R_2 + R_3 + \dots + R_m}$$

$$R_1 + R_2 + R_3 + \dots + R_m$$

$$V_m = \frac{R_m}{R_T} \cdot V_s$$


where, V_m = voltage across m^{th} resistor

R_m = resistance across the voltage is to be determined

R_T = total series resistance

E.g. 1) What is the voltage across the $10\ \Omega$ resistor in fig. b)


$$V_{10} = ?$$

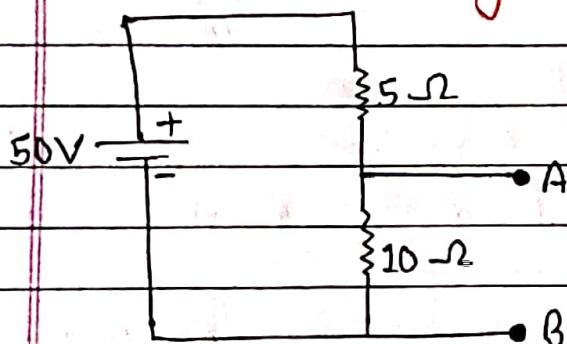

$$V_m = \frac{R_m}{R_T} \cdot V_s$$

$$V_{10} = \frac{10}{15} \times 50$$

$$= 33.33\ \text{V}$$

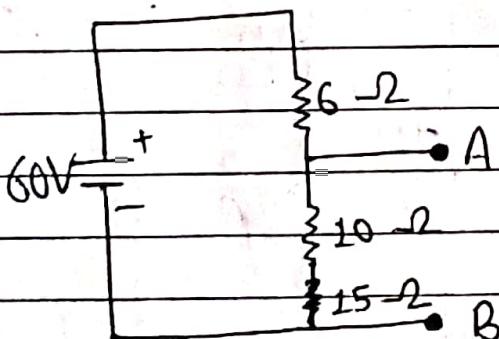


$$V_{AB} = \frac{(10 + 5)}{6 + 10 + 15} \times 60$$

$$= 48.39\ \text{V}$$

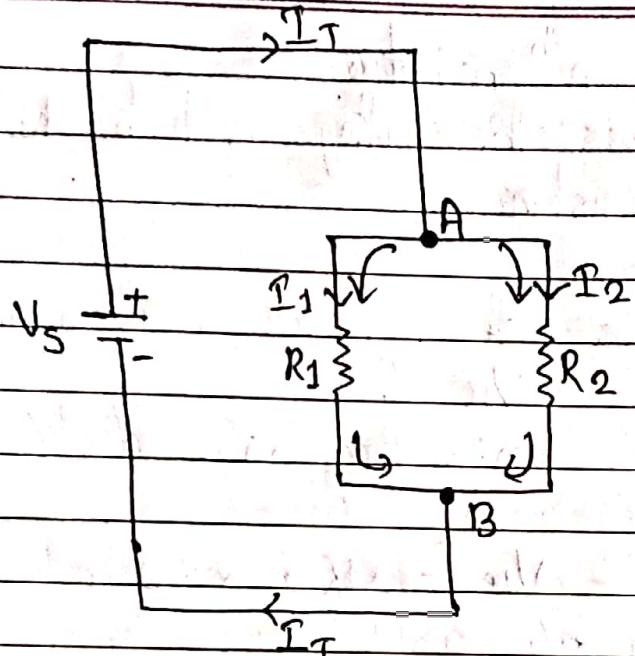2) Kirchoff's Current Law :-

It states that, the sum of currents entering into any point is equal to the sum of the currents leaving that points. The point may be interconnection of two or more branches. In parallel circuit, node consists of two or more branches. Therefore the total current entering into the node is equal to the current leaving that node.



Consider the node A

$$I_T = I_1 + I_2$$

Consider the node B

$$I_1 + I_2 = I_T$$

Q. Determine the current in all registers in the circuit shown in fig. below:

$$I_T = I_1 + I_2 + I_3$$

$$\text{or, } 50 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\text{or, } 50 = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\text{or, } 50 = V \left(\frac{1}{2} + \frac{1}{1} + \frac{1}{5} \right)$$


$$\Rightarrow V = 29.4V$$

So,



$$I_1 = \frac{V}{R_1} = \frac{29.4}{2} = 14.7A$$

$$I_2 = \frac{V}{R_2} = \frac{29.4}{1} = 29.4A$$
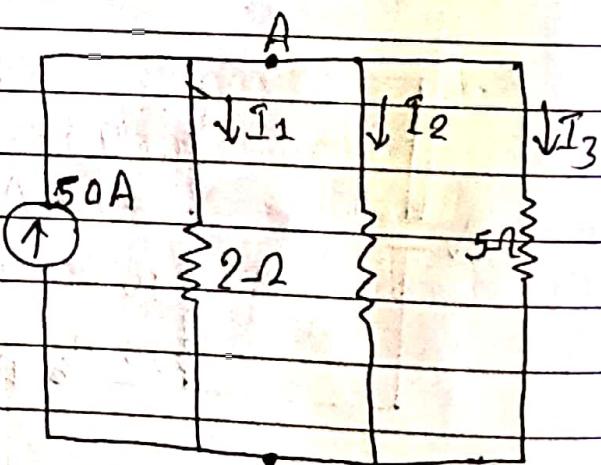
$$I_3 = \frac{V}{R_3} = \frac{29.4}{5} = 5.88A$$



Current divisions

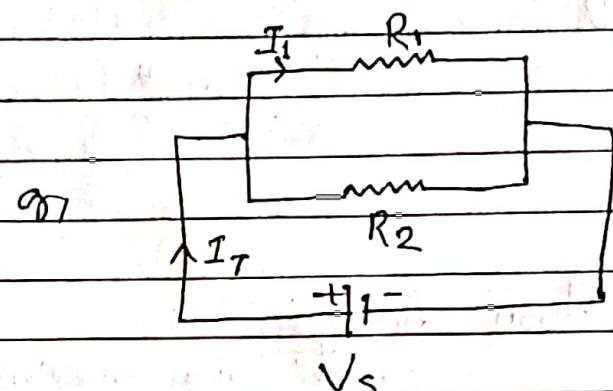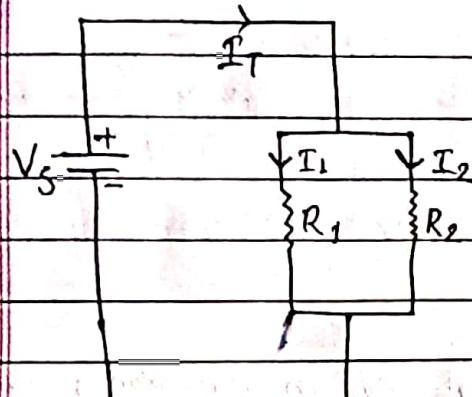

The voltage applied to each of resistor is $= V_s$
The current passing through each of resistor is given by

$$I_1 = \frac{V_s}{R_1} \quad \text{--- (i)} \quad \therefore V_s = I_1 \cdot R_1$$

$$I_2 = \frac{V_s}{R_2} \quad \text{--- (ii)} \quad \therefore V_s = I_2 \cdot R_2$$

The total resistance of the given ckt :

$$R_T = \frac{R_1 R_2}{R_1 + R_2} \quad \text{--- (iii)}$$

Total current

$$I_T = \frac{V_s}{R_T} \quad \text{--- (iv)}$$

$$\therefore I_1 = I_T \cdot \frac{R_2}{R_1 + R_2}$$

$$I_T = \frac{V_s}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$I_T = \frac{V_s \cdot (R_1 + R_2)}{R_1 R_2}$$

$$I_T = \frac{V_s \cdot (R_1 + R_2)}{R_1 R_2}$$

$$= \frac{I_2 \cdot R_2 (R_1 + R_2)}{R_1 R_2}$$

$$I_T = \frac{I_1 \cdot R_1 (R_1 + R_2)}{R_1 R_2}$$


$$I_T = \frac{I_2 (R_1 + R_2)}{R_1}$$

$$I_T = \frac{I_1 (R_1 + R_2)}{R_2}$$


$$\therefore I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$

Sign Conversion :-

①

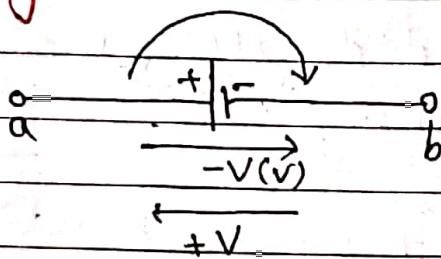

②

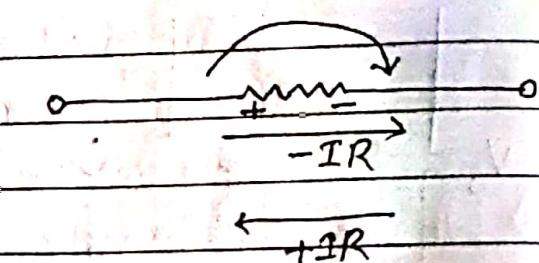~~www2mp~~

Mesh Analysis

↳ used only in planar circuit; not in non-planar ckt.


Mesh is defined as a loop which does not contain any other loops within it.

1) Mesh Analysis

Step 1: Check whether the ckt is planar or not.

Step 2: Select the mesh current (loop current).

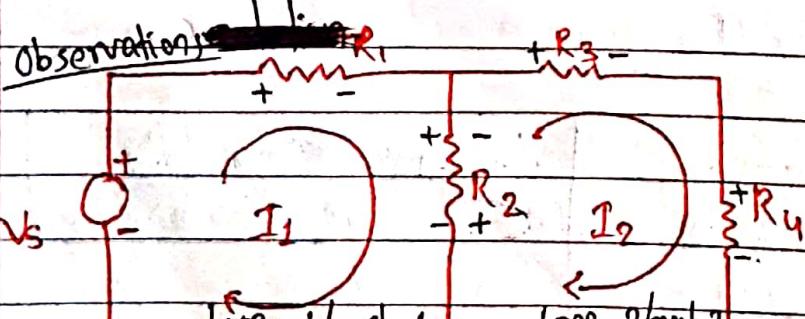Step 3: Finally, write the Kirchhoff's Voltage Law eq? in terms of unknown & solving leads to final



solution:

Consider the loop-1

$$+V_s - I_1 R_1 - R_2 [I_1 - I_2] = 0$$


$$\Rightarrow I_1 R_1 + R_2 [I_1 - I_2] = V_s \quad \text{--- (1)}$$

Consider the loop-2

$$-R_3 I_2 - R_4 I_2 - R_2 (I_2 - I_1) = 0$$

$$\Rightarrow R_3 I_2 + R_4 I_2 + R_2 (I_2 - I_1) = 0 \quad \text{--- (2)}$$

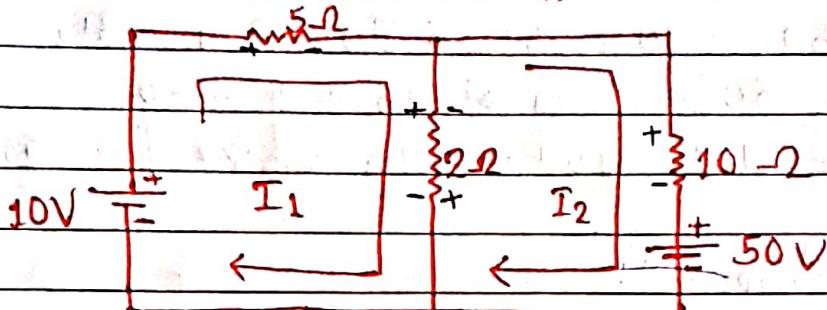Q.1) Write the mesh current I_1 & I_2 in the ckt shown in fig below & determine the currents.



solution:

Consider loop - 1:

$$10V - 5I_1 - 2(I_1 - I_2) = 0$$

$$\Rightarrow -5I_1 - 2I_1 + 2I_2 = -10V$$

$$\Rightarrow 7I_1 - 2I_2 = 10 \quad \text{--- (1)}$$

Consider the loop - 2:

$$-10I_2 - 50V - 2(I_2 - I_1) = 0$$

$$\Rightarrow 10I_1 + 2I_2 - 2I_2 = 50$$


$$\Rightarrow -2I_1 + 12I_2 = -50 \quad \text{--- (2)}$$

Solving (1) & (2),

$$I_1 = 0.25A$$

$I_2 = -4.125A$ (The current will flow in opposite direction of what we have assumed.)

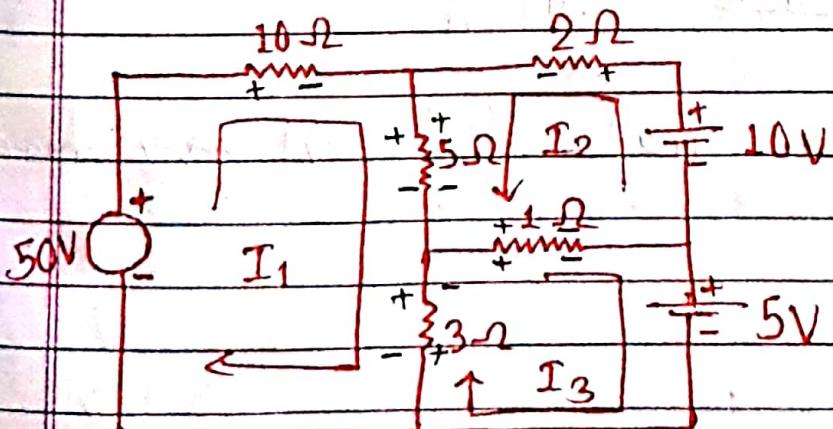Q.2) Determine the mesh currents I_1 , I_2 & I_3 in the ckt shown in fig below:



Consider loop - 1:

$$50V - 10I_1 - 5(I_1 + I_2) - 3(I_1 - I_3) = 0$$

$$\Rightarrow 50 - 10I_1 - 5I_1 - 5I_2 - 3I_1 + 3I_3 = 0$$

$$\Rightarrow 50 - 18I_1 - 5I_2 + 3I_3 = 0$$

$$\Rightarrow 18I_1 + 5I_2 - 3I_3 = 50 \quad \text{--- (1)}$$

Consider loop - 2:

$$10V - 2I_2 - 5(I_1 + I_2) - 1(I_2 + I_3) = 0$$

$$\text{on } 10 - 2I_2 - 5I_1 - 5I_2 - I_2 - I_3 = 0$$

$$\text{on } 10 - 8I_2 - 5I_1 - I_3 = 0$$

$$\Rightarrow 5I_1 + 8I_2 + I_3 = 10 \quad \text{--- (2)}$$

Consider loop - 3:

$$-5V - 3(I_3 - I_1) - 1(I_2 + I_3) = 0$$

$$\text{on } -5 - 3I_3 + 3I_1 - I_2 - I_3 = 0$$

$$\text{on } -5 - 4I_3 + 3I_1 - I_2 = 0$$

$$\Rightarrow -3I_1 + I_2 + 4I_3 = -5 \quad \text{--- (3)}$$


Solving (1), (2) & (3),

$$I_1 = 4.12 \quad 3.30 \text{ A}$$

$$I_2 = 1.92 \quad -0.997 \text{ A}$$

$$I_3 = 4.82 \quad 1.47 \text{ A}$$

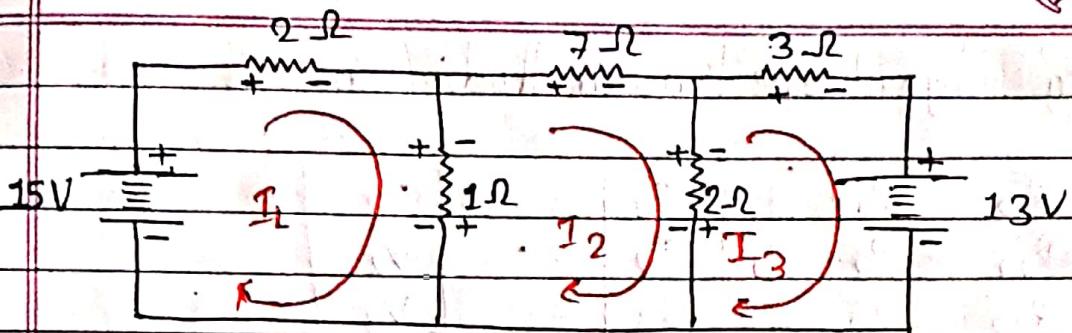²⁰¹⁵
Q.3) Calculate the mesh current of the circuit given shown
PU in fig. below:



Consider loop - 1:

$$15 - 2I_1 - 1(I_1 - I_2) = 0$$

$$\text{on } 15 - 2I_1 - I_1 + I_2 = 0$$

$$\Rightarrow 3I_2 - I_1 = 15 \quad \text{--- (1)}$$

Consider loop - 2:

$$-1(I_2 - I_1) - 2(I_2 - I_3) = 0$$

$$\text{on } -I_2 + I_1 - 2I_2 + 2I_3 = 0$$

$$\Rightarrow -I_1 + 10I_2 - 2I_3 = 0 \quad \text{--- (2)}$$

Consider loop - 3:

$$-13 - 2(I_3 - I_2) - 3I_3 = 0$$

$$\text{on } -13 - 2I_3 + 2I_2 - 3I_3 = 0$$

$$\Rightarrow 2I_2 - 5I_3 = 13 \quad \text{--- (3)}$$

Solving;

$$I_1 = 4.99 \text{ A}$$

$$I_2 = -0.622 \text{ A}$$

$$I_3 = -2.609 \text{ A}$$

Mesh eq' by Inspection method:

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

R_{11} = self resistance of mesh - ① [sum of resistance in mesh-1]

R_{22} = " " " mesh - ② [" " " " " mesh-2]


R_{33} = " " " mesh - ③ [" " " " " mesh-3]

$R_{12} = R_{21} = -$ [sum of all resistance common to mesh
① & ②]

$R_{13} = R_{31} = -$ [sum of all resistance common to mesh
① & ③]

$R_{23} = R_{32} = -$ [sum of all resistance common to mesh
② & ③]

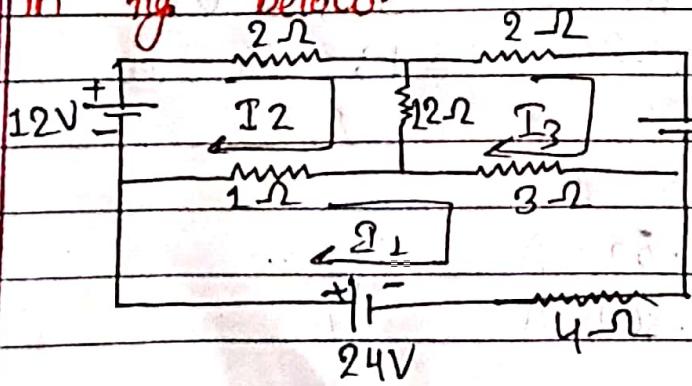Q. Determine the current ^{voltage drop} in 4-Ω branch in the circuit shown in fig below.



$$R_{11} = 1 + 3 + 4 = 8\Omega$$

$$R_{22} = 2 + 12 + 1 = 15\Omega$$

$$R_{33} = 2 + 3 + 12 = 17\Omega$$

$$R_{12} = R_{21} = -1\Omega$$

$$R_{13} = R_{31} = -3\Omega$$

$$R_{23} = R_{32} = -12\Omega$$

Above values in matrix form:

$$\begin{bmatrix} 8 & -1 & -3 \\ -1 & 15 & -12 \\ -3 & -12 & 17 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 12 \\ -10 \end{bmatrix}$$

$$V_1 = 24V$$

$$V_2 = 12V$$

$$V_3 = -10V$$


$$I_1 = 4.11A, I_2 = 2.71A, I_3 = 2.05A$$

$$V = I_1 R$$

$$= 4 \cdot 11 \times 4$$

$$= 16.44$$

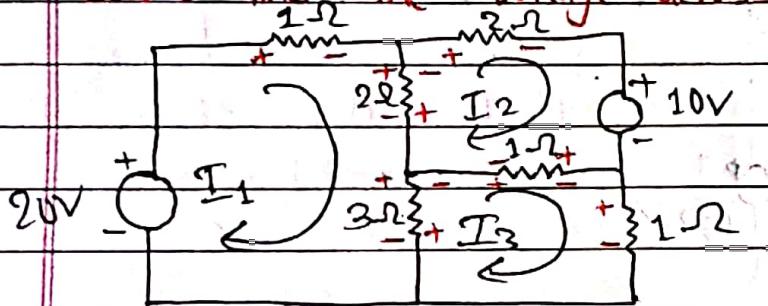- Q. Determine the mesh currents in the ckt shown in fig (a) below. Find the voltage across the 3Ω resistor.



Consider loop-1:

$$20 - I_1 - 2(I_1 - I_2) - 3(I_1 - I_3) = 0$$

$$\text{or } 20 - I_1 - 2I_1 + 2I_2 - 3I_1 + 3I_3 = 0$$

$$\text{or } 20 - 6I_1 + 2I_2 + 3I_3 = 0$$

$$\Rightarrow 6I_1 - 2I_2 - 3I_3 = 20 \quad \text{--- (1)}$$

Consider loop-2:

$$-10 - 1(I_2 - I_3) - 2(I_2 - I_1) - 2I_2 = 0$$

$$\text{or } -I_2 + I_3 - 2I_2 + 2I_1 - 2I_2 = 10$$

$$\Rightarrow 2I_1 - 5I_2 + I_3 = 10 \quad \text{--- (2)}$$

Consider loop-3:

$$-I_3 - (I_3 - I_2) - 3(I_3 - I_1) = 0$$

$$\text{or } I_2 - 2I_3 - 3I_3 + 3I_1 = 0$$

$$\Rightarrow 3I_1 - 5I_3 = 0 \quad \text{--- (3)}$$

Solving:


$$I_1 = 5.92 \text{ A}$$

$$I_2 = 0.746 \text{ A}$$

$$I_3 = 3.28 \text{ A}$$

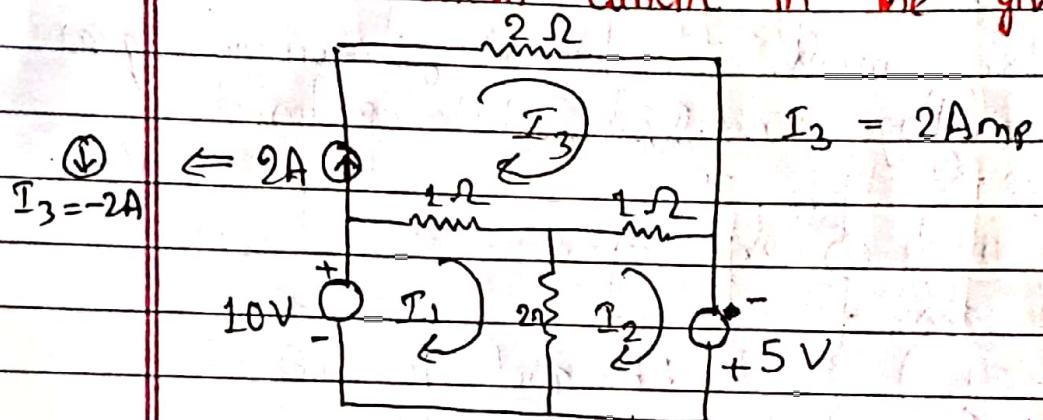2) Mesh Analysis with current sources:

PV 2012 Q. Find the mesh current in the given fig below:



$$\textcircled{1} \quad I_3 = -2 \text{ Amp}$$

$$I_3 = 2 \text{ Amp}$$

$$\therefore I_3 = 2 \text{ A}$$

Consider loop - 1:

$$10V - 1(I_L - I_3) - 2(I_1 - I_2) = 0$$

$$\text{on } 3I_1 - 2I_2 = 10 + 2 = 12$$

$$\therefore 3I_1 - 2I_2 = 12 \quad \text{--- (1)}$$

Consider loop - 2:

$$5V - 2(I_2 - I_1) - 1(I_2 - I_3) = 0$$

$$\text{on } 5 - 2I_2 + 2I_1 - I_2 + 2I_3 = 0$$

$$\Rightarrow 2I_1 - 3I_2 + 2I_3 = 0 \quad \text{--- (2)}$$

Solving:


$$I_1 = 10 \text{ A} ; I_2 = 8 \text{ A}$$

3) Super mesh Analysis:


Suppose any branch in network has a current source than it is slightly difficult to apply Mesh analysis. One way to overcome this difficulty is by applying the super mesh technique. Here we have choose a kind of super mesh.

"A super mesh is constituted by two adjacent loops that have common current source."

Observation

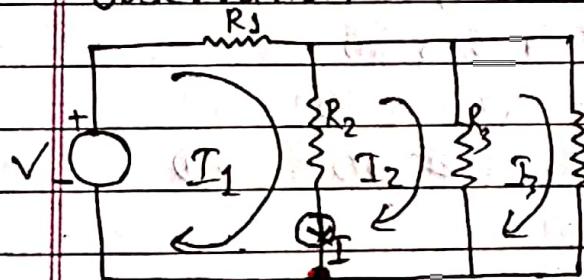

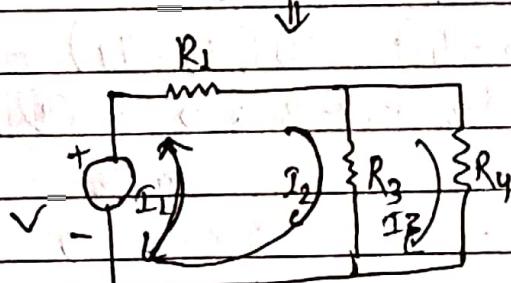solution: Write the combine eqⁿ of loop-1 & loop-2.




Consider loop -3 :


$$-R_4I_3 - R_3(I_3 - I_2) = 0 \quad (II)$$

Other eqⁿ: $I + I_2 = I_1$
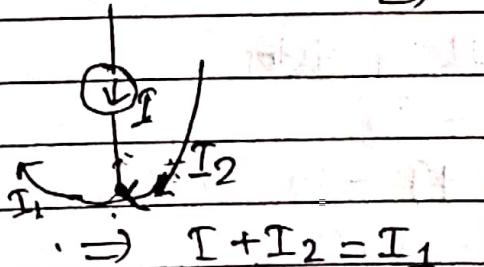
$$\Rightarrow I_1 - I_2 = I \quad (III)$$



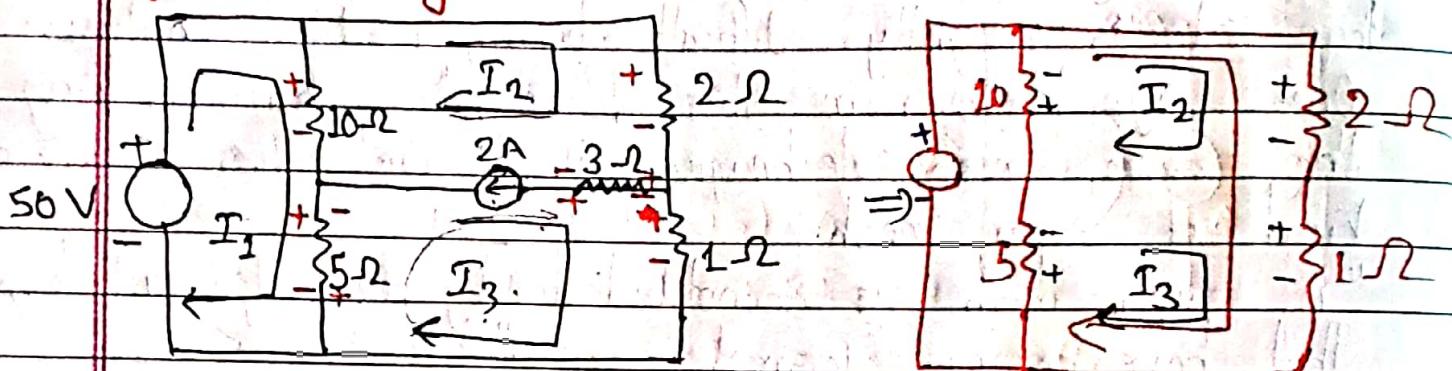1) Q. Determine the current in a 5Ω resistor in the network given in fig. below.



Consider loop -1:

$$50V - 10(I_1 - I_2) - 5(I_1 - I_3) = 0$$

$$\text{or } 50 - 10I_1 + 10I_2 - 5I_1 + 5I_3 = 0$$

$$\Rightarrow 15I_1 - 10I_2 - 5I_3 = 50$$

$$\Rightarrow 3I_1 - 2I_2 - I_3 = 10 \quad \text{(i)}$$

Combine eqⁿ of loop -2 & loop -3:

$$-2I_2 - 1I_3 - 5(I_3 - I_1) - 10(I_2 - I_1) = 0 \quad \text{(ii)}$$

$$\Rightarrow -15I_1 + 12I_2 + 6I_3 = 0 \quad \text{(ii)}$$

Other eqⁿ:

$$2 + I_3 = I_2 \Rightarrow I_2 - I_3 = 2 \quad \text{(iii)}$$

$$I_1 = 19.99$$

$$I_2 = 17.33$$

$$I_3 = 15.33$$

Current in 5Ω resistor

$$= I_1 - I_3$$

$$= 19.99 - 15.33$$

$$= 4.66 \text{ A}$$

Q2. Use the concept of mesh analysis to find the mesh current in a given circuit.

Consider loop -1:

$$5 - 2(I_1 - I_2) - 1(I_1 - I_2) = 0$$

on $5 - 9I_1 + 9I_2 - I_1 + I_2 = 0$

$$\Rightarrow 3I_1 - 2I_2 - I_3 = 5 \quad \text{--- (1)}$$

Combine eqⁿ of loop-2 & loop-3;

$$50 - 2(I_2 - I_1) - 2I_3 - 1(I_3 - I_1) = 0$$

on $50 - 2I_2 + 2I_1 - 2I_3 - I_3 + I_1 = 0$

$$\text{on } -3I_1 - 2I_2 - 3I_3 = -50 \quad \text{--- (II)}$$

Other eqⁿ:

$$2 + I_2 = I_3 \quad I_2 = 2 + I_3$$


$$\Rightarrow I_2 - I_3 = -2 \quad \text{--- (III)}$$

Solving:

$$I_1 = 27.83 \text{ A}$$

$$I_2 = 25.5 \text{ A}$$

$$I_3 = 27.5 \text{ A}$$

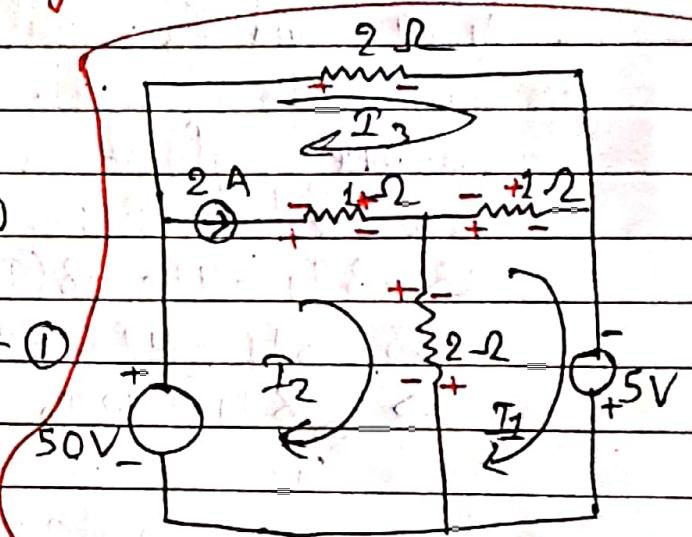

PV 2005 2008, 2012 F

- Q. Use concept of super mesh analysis, find the mesh current I_1, I_2 and I_3 .


Combine eqⁿ of

loop 1 & loop -2;

$$18 - 8I_1 - 4I_2 - 8(I_2 - I_3) = 0$$

$$\text{on } 18 - 8I_1 - 4I_2 - 8I_2 + 8I_3 = 0$$
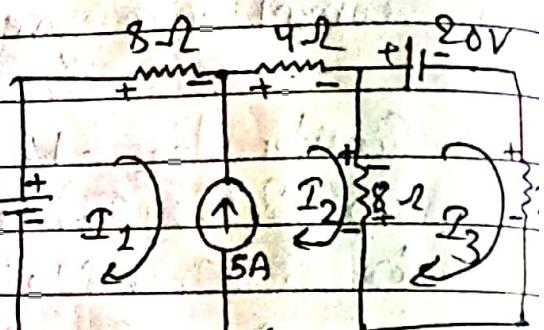
$$\Rightarrow 8I_1 + 12I_2 - 8I_3 = 18 \quad \text{--- (1)}$$



Consider loop -3:

$$-8(I_3 - I_2) - 20 - 18I_3 = 0$$

$$\text{on } -8I_3 + 8I_2 - 20 - 18I_3 = 0$$

$$\Rightarrow 8I_2 - 26I_3 = 20 \quad \text{--- (II)}$$

Other eqⁿ:

$$I_1 + I_2 = I_3$$

$$\Rightarrow 5 + I_2 = I_3$$

$$\Rightarrow I_1 - I_2 = 5 \quad \text{--- (III)}$$


Solving:

$$I_1 = 3.39 \text{ A}$$

$$I_2 = -1.61 \text{ A}$$

$$I_3 = -1.26 \text{ A}$$

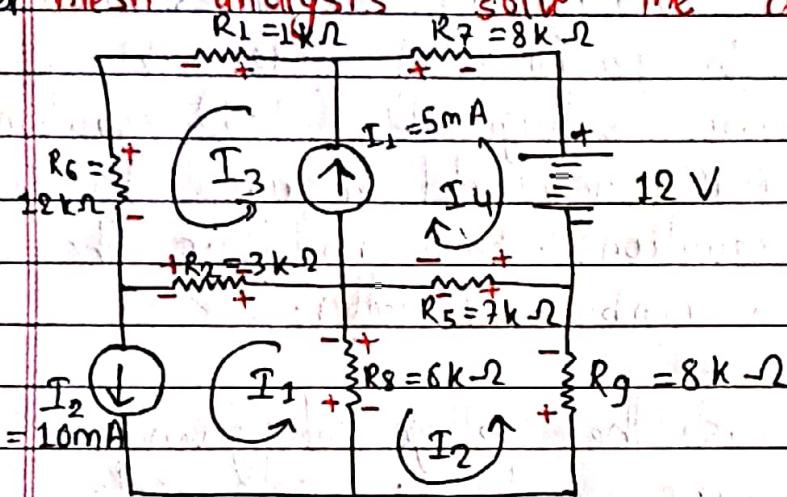4) (Q) Determine the voltage across $3\text{ k}\Omega$ resistor. Using the super mesh analysis solve the circuit shown below:



Solving:

$$I_1 = 10 \text{ mA}$$

$$I_2 = -5.34$$

$$I_3 = -19.6$$

$$I_4 = 24.6$$

Solution:

$$I_1 = 10 \text{ mA} \quad \rightarrow 0$$

Consider loop-2:

$$-8I_2 - 7(I_2 + I_4) - 6(I_2 - I_1) = 0$$

~~$$\text{on } -8I_2 - 7I_2 - 7I_4 - 6(I_2 - 10) = 0$$~~

~~$$\text{on } -8I_2 - 7I_2 - 7I_4 - 6I_2 + 60 = 0$$~~

~~$$\Rightarrow -21I_2 - 7I_4 = -60$$~~

~~$$\Rightarrow 21I_2 + 7I_4 = 60 \quad \text{--- (i)}$$~~

Combine eqⁿ of loop-3 & loop-4;

~~$$-12 - 8(7(I_4 + I_2)) - 3(I_3 - I_1) - I_3 - 12I_3 - 8I_4 = 0$$~~

~~$$\text{on } -12 - 7I_4 - 7I_2 - 3I_3 + 30 - I_3 - 12I_3 - 8I_4 = 0$$~~

~~$$\text{on } -7I_2 - 16I_3 - 15I_4 + 18 = 0$$~~

~~$$\Rightarrow 7I_2 + 16I_3 + 15I_4 = 18 \quad \text{--- (ii)}$$~~

Cons other eqⁿ:


$$I_3 + I_4 = 5 \quad \text{--- (iv)}$$

Nodal Analysis

In simple circuit containing any two nodes including the reference node. In general, N node ckt will require $(N-1)$ unknown voltage & $(N-1)$ equation. For example; a 10 nodes ckt require 9 unknown voltage and 9 equations. Each node in the ckt can be assigned a number or letter.

The node voltage is the voltage of given node with respect to one particular node called the reference node or Datum node or '0' zero potential node which can be assumed to be zero potential that's why it is also called zero potential node.

Observation:

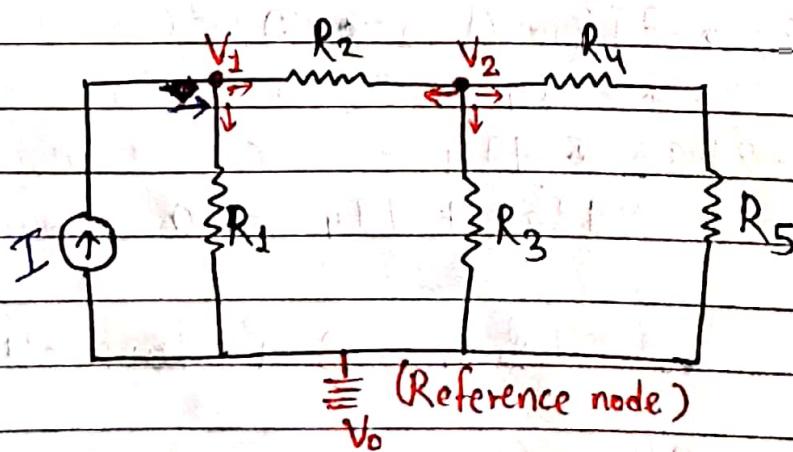

Consider Node -1:

$$I = \frac{V_1 - V_0}{R_1} + \frac{V_1 - V_2}{R_2} - \quad \oplus$$

on

$$I = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} - \quad \oplus \quad [V_0 = 0]$$

V_0 is assumed '0' always

$$\text{on } \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} = I$$

$$\Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left(\frac{1}{R_2} \right) = I - ①$$




Consider Node - 2:

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_0}{R_4 + R_5} + \frac{V_2 - V_0}{R_3} = 0$$

$$\text{on } \frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_4 + R_5} + \frac{V_2}{R_3} = 0$$

$$\text{on } -V_1 \left(\frac{1}{R_2} \right) + V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4 + R_5} \right) = 0 - ②$$


Simplification:

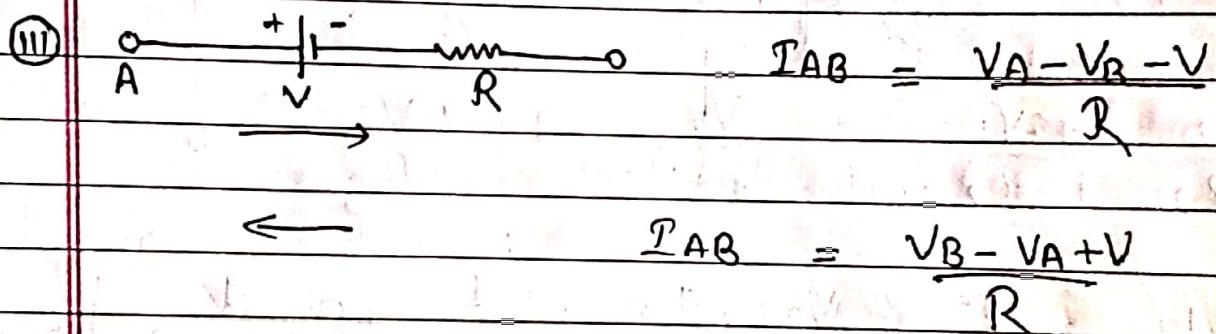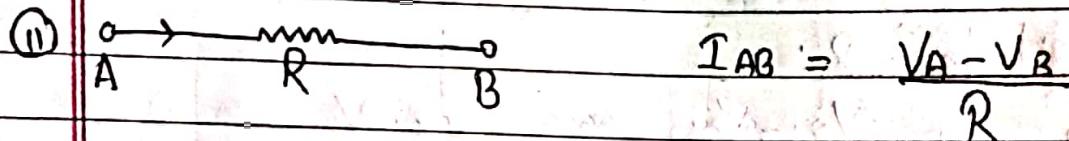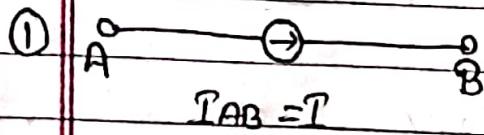



④ Nodal Analysis Procedure:

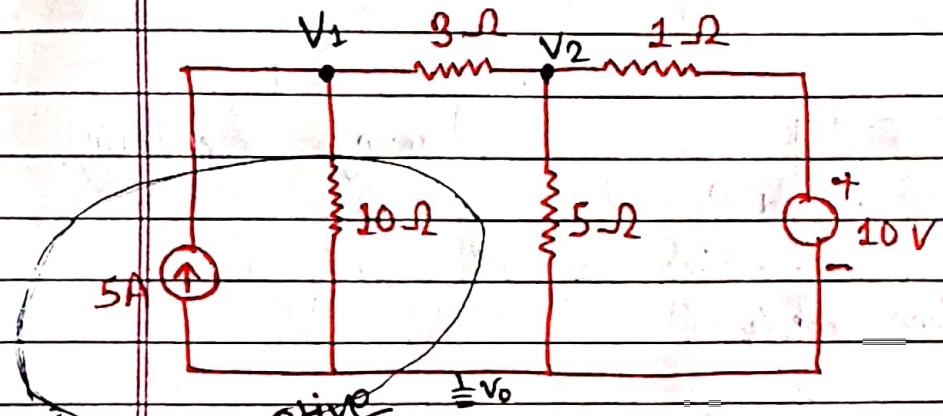- 1) Convert all the voltage source to current source & redraw the ckt diagram.
- 2) Identify all the nodes & choose a reference node.
- 3) Write the eq' for current flowing into & out of each node, with exception of reference node.
- 4) Solve the eq' to determine the node voltage & required the branch currents.


Q. Write the node voltage (v_1) and determine the current in each branch for network in fig. below:


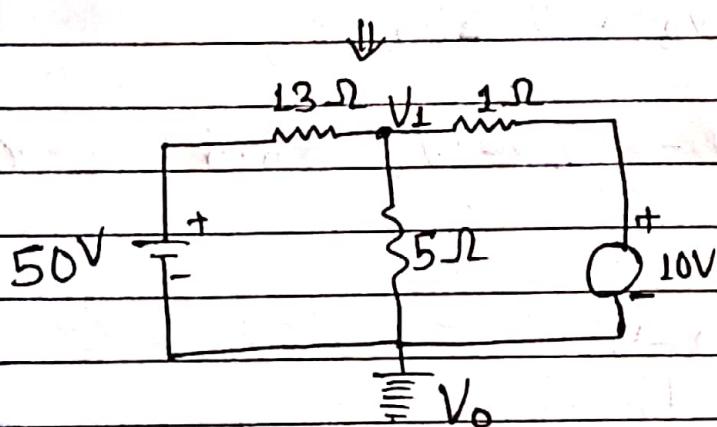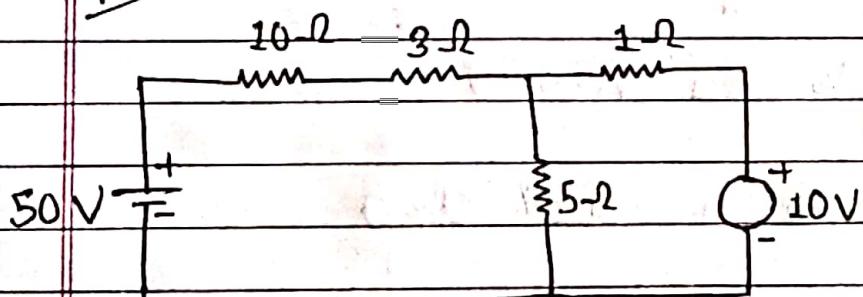
$$\text{Alternative } V = IR = 5 \times 10 = 50V$$



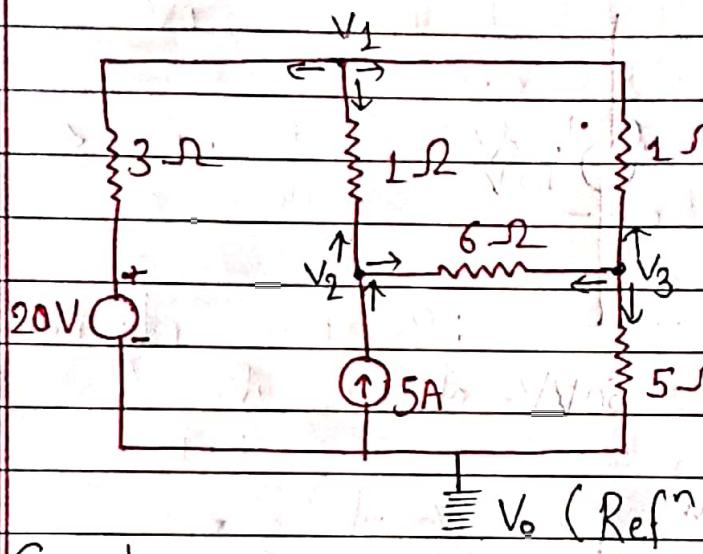Q. Use the nodal analysis to find the power dissipated in 6Ω resistor of the ckt shown in fig. below.



leaving = entering

Consider Node -1:

$$\frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{1} + \frac{V_1 - 20 - 16}{3} = 0$$

$$\text{on } V_1 - V_2 + V_1 - V_3 + \frac{V_1 - 20}{3} = 0$$

$$\text{on } V_1 (2 + 0.33) - V_2 - V_3 = 6.67 \quad \text{--- (1)}$$

Consider Node -2:

$$\frac{V_2 - V_3}{6} + \frac{V_2 - V_1}{1} = 5 \quad \text{--- (II)} \quad [\text{leaving} = \text{entering}]$$

$$\Rightarrow V_2 - V_3 + 6V_2 - 6V_1 = 30$$

$$\Rightarrow -6V_1 + 7V_2 - V_3 = 30 \quad \text{--- (II)}$$

Consider Node - 3:

$$\frac{V_3 - V_1}{1} + \frac{V_3 - V_0}{5} + \frac{V_3 - V_2}{6} = 0$$

$$\text{on } V_3 - V_1 + \frac{V_3 - V_0}{5} + \frac{V_3 - V_2}{6} - \frac{V_0}{5} = 0$$

$$\text{on } -V_1 - \frac{V_2}{6} + V_3 \left(\frac{1}{5} + \frac{1}{6} + \frac{1}{6} \right) = 0$$

$$\text{on } -V_1 - \frac{V_2}{6} + \frac{41}{30} V_3 = 0 \quad \text{--- (III)}$$

Solving,

$$V_1 = 23.12 \text{ V}$$

$$V_2 = 26.98 \text{ V}$$


$$V_3 = 20.21 \text{ V}$$

~~$\times R$~~ (highest voltage - lowest voltage)

$$P = I^2 R \Rightarrow - \frac{(V_2 - V_3)^2}{R^2} \times R = \frac{(26.98 - 20.21)^2}{6}$$

$$\therefore P = 7.64 \text{ watt}$$

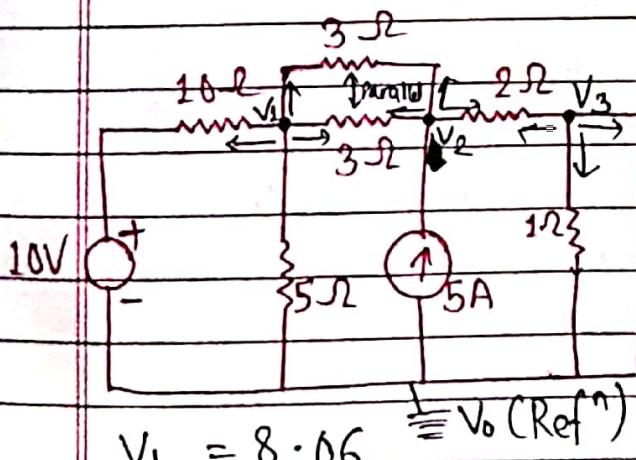
Q. Determine the voltage for each node for the ckt below:



$$V_1 = 8.06 \text{ V} \equiv V_0 (\text{Ref})$$

$$V_2 = 10.2 \text{ V}$$

$$V_3 = 3.07 \text{ V}$$

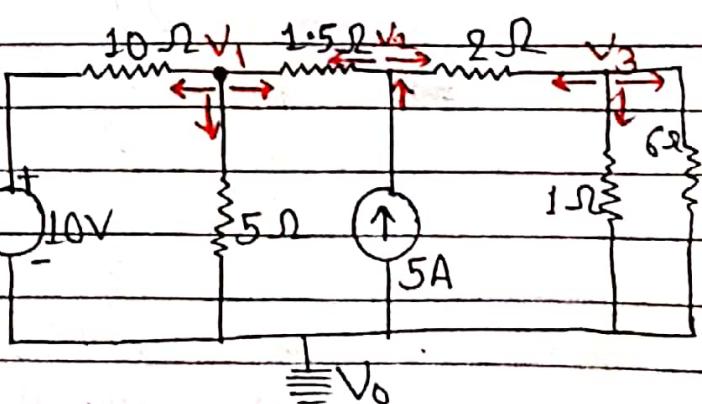

Consider node -1:

$$\frac{V_1 - 10}{10} + \frac{V_1 - V_2}{1.5} + \frac{V_1 - V_0}{5} = 0$$

$$\text{or } V_1 \left(\frac{1}{10} + \frac{1}{1.5} + \frac{1}{5} \right) - V_2 \cdot \frac{1}{1.5} = 1$$

$$\Rightarrow \frac{V_1 \cdot 29}{30} - V_2 \cdot \frac{2}{3} = 1 \quad \text{--- (I)}$$

Consider node -2:

$$\frac{V_2 - V_1}{1.5} + \frac{V_2 - V_3}{2} = 5$$

$$\text{or, } -\frac{2}{3} (V_2 - V_1) + \frac{1}{2} (V_2 - V_3) = 5$$

$$\Rightarrow -\frac{2}{3} V_1 + 1.16 \times V_2 - \frac{1}{2} V_3 = 5 \quad \text{--- (II)}$$

Consider node -3:

$$\frac{V_3 - V_2}{2} + \frac{V_3 - V_0}{6} + \frac{V_3 - V_1}{1} = 0$$

$$\Rightarrow V_2 \left(-\frac{1}{2} \right) + V_3 \left(\frac{1}{2} + \frac{1}{6} + 1 \right) = 0$$

$$\Rightarrow V_2 \cdot -\frac{1}{2} + V_3 \cdot \frac{5}{3} = 0 \quad \text{--- (III)}$$



Solving (I), (II) & (III);

$$V_1 = 8.97 \text{ V}$$

$$V_2 = 10.42 \text{ V}$$

$$V_3 = 3.13 \text{ V}$$

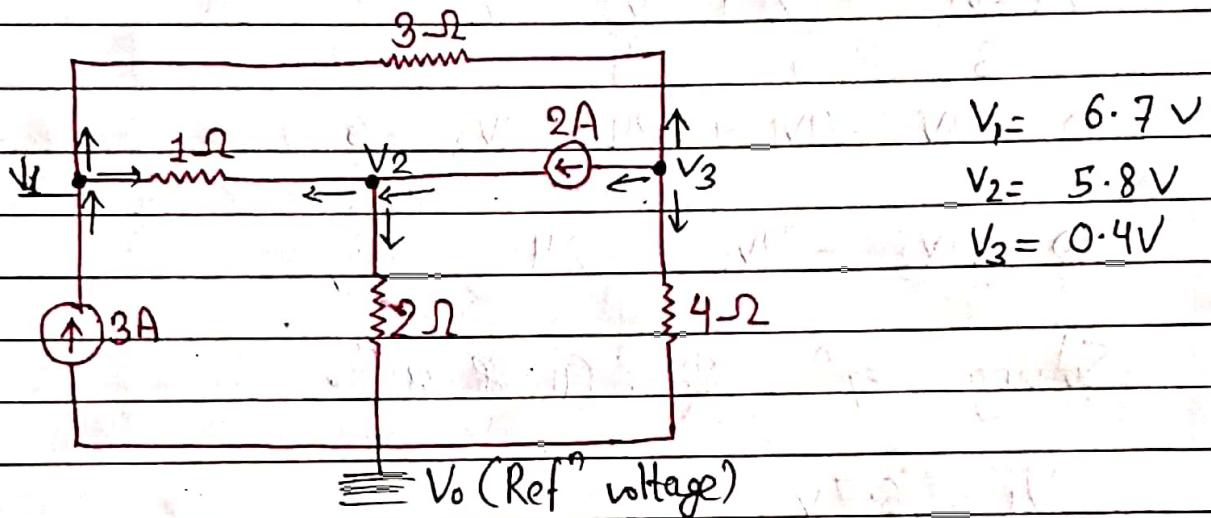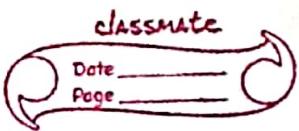Q. Use the nodal analysis to determine all the node voltage and all the element current for the network.



$$V_1 = 6.7 \text{ V}$$

$$V_2 = 5.8 \text{ V}$$

$$V_3 = 0.4 \text{ V}$$

Consider node -1:

$$\frac{V_1 - V_3}{3} + \frac{V_1 - V_2}{L} = 3 \rightarrow \textcircled{1}$$

$$\text{on } V_1 \left(\frac{1}{3} + 1 \right) - V_2 - V_3 \cdot \frac{L}{3} = 3$$

$$\text{on } V_1 \cdot \frac{4}{3} - V_2 \cdot 1 - V_3 \cdot \frac{1}{3} = 3 \quad \text{---} \textcircled{2}$$

$$\Rightarrow 4V_1 - 3V_2 - V_3 = 9 \quad \text{---} \textcircled{1}$$

Consider node -2:

$$\frac{V_2 - V_1}{L} + \frac{V_2 - V_0}{2} = 2$$

$$\Rightarrow 2V_2 - 2V_1 + V_2 = 4$$

$$\Rightarrow 3V_2 - 2V_1 = 4 \quad \text{---} \textcircled{2}$$

In node - III,

$$\frac{V_3 - V_1}{3} + 2 + \frac{V_3}{4} = 0$$

$$\Rightarrow 4V_3 - 4V_1 + 94 + 3V_3 = 0$$

$$\Rightarrow 7V_3 - 4V_1 = -94 \quad \text{--- (III)}$$


Solving eqⁿ (I), (II) & (III),

$$V_1 = 6.7V$$

$$V_2 = 5.8V$$

$$V_3 = 0.4V$$

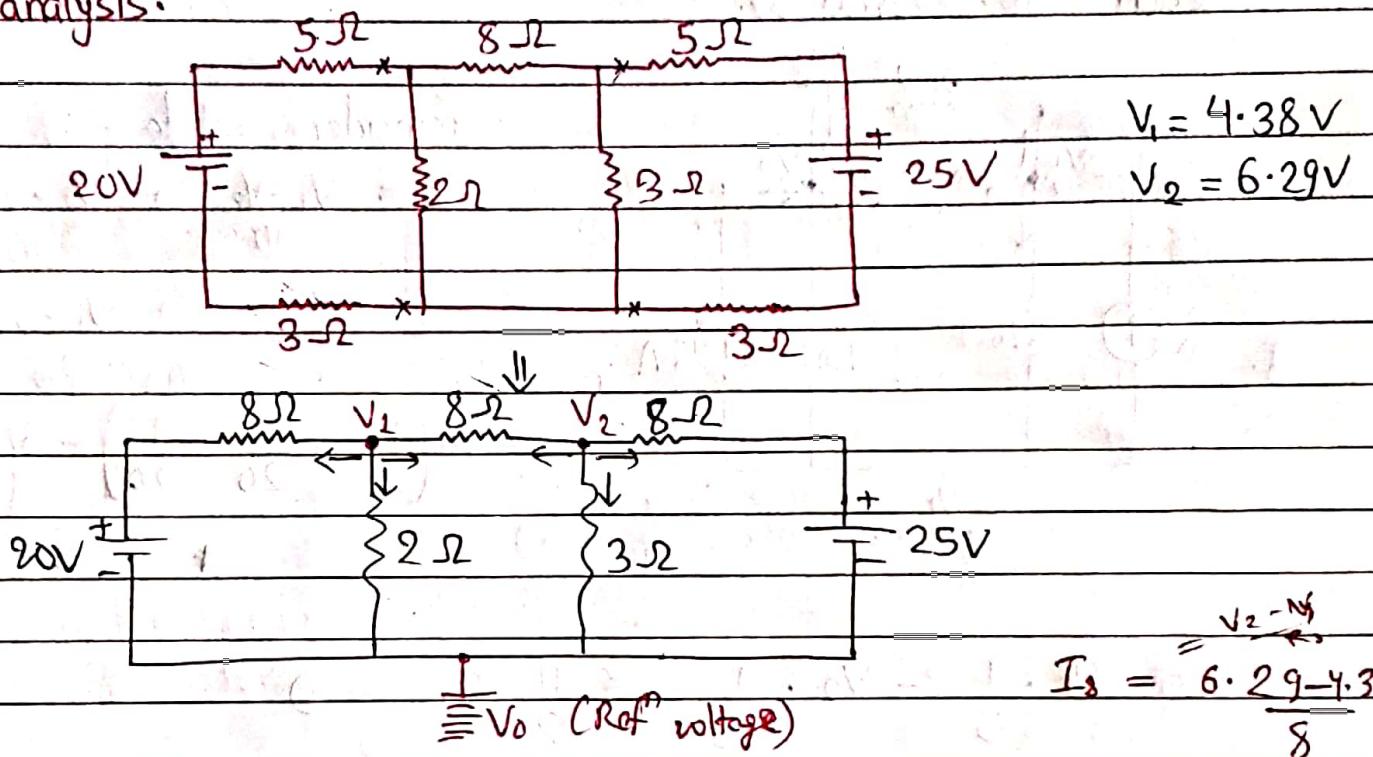Q. Find the current across the 8Ω resistor using the nodal analysis.



Consider node - 1:

$$\frac{V_1 - V_2}{8} + \frac{V_1 - V_0}{2} + \frac{V_1 - 20}{8} = 0$$

$$\frac{V_1 - V_2}{8} + \frac{V_1 - V_0}{2}$$

$$\text{on } V_1 - 20 + 4V_1 + V_1 - V_2 = 0$$

$$\Rightarrow 6V_1 - V_2 = 20 \quad \text{--- (I)}$$

In node II,

$$\frac{V_2 - V_1}{8} + \frac{V_2}{3} + \frac{V_2 - 25}{8} = 0$$

$$\Rightarrow 3V_2 - 3V_1 + 8V_2 + 3V_2 - 75 = 0$$

$$\Rightarrow 14V_2 - 3V_1 - 75 = 0 \quad \text{--- (II)}$$


Solving,

$$V_1 = 4.38V$$

$$V_2 = 6.29V$$

2019
Q.

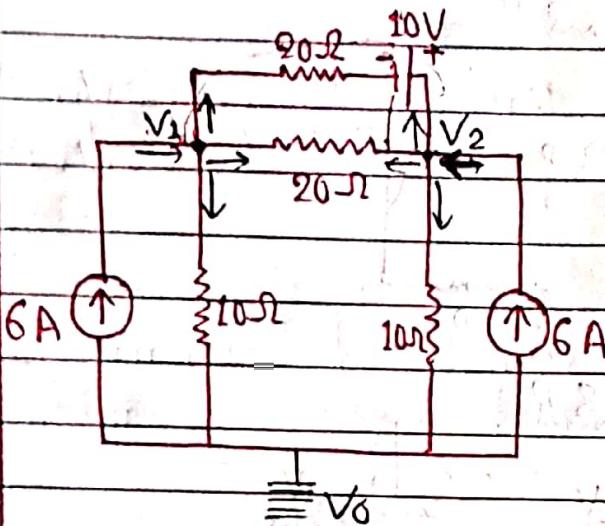Using nodal analysis method, find the current through each $10\ \Omega$ resistor.



Consider Node - 1:

$$6 = \frac{V_1 - V_0}{10} + \frac{V_1 - V_2}{20}$$

$$+ \frac{V_1 - V_2 + 10}{20}$$

$$\therefore V_1 \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{20} \right) - V_2 \left(\frac{1}{20} + \frac{1}{20} \right) = 6 - \frac{1}{2}$$

$$\Rightarrow V_1 \cdot \frac{1}{5} - V_2 \cdot \frac{1}{10} = \frac{11}{2} \quad \textcircled{1}$$

Consider Node - 2:

$$6 = \frac{V_2 - V_0}{10} + \frac{V_2 - V_1}{20} + \frac{V_2 - V_1 - 10}{20} \quad \textcircled{11}$$

~~$$6 = V_2 \left(-\frac{1}{10} - \frac{1}{20} \right) + V_2 \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right) - \frac{1}{2}$$~~

~~$$\Rightarrow V_2 \left(-\frac{3}{20} \right) + V_2 \left(\frac{1}{4} \right) = \frac{13}{2} \quad \textcircled{11}$$~~

Solving $\textcircled{1}$ & $\textcircled{11}$,

$$V_1 = 58.33V$$

$$V_2 = 61.67V$$


Now,

$$(I_{10})' = \frac{58.33}{10} = 5.83A$$

$$(I_{10})'' = \frac{61.67}{10} = 6.16A$$

Super Node Analysis

Suppose a network has a single voltage source in any branch, then it is difficult to apply the nodal analysis, one way to overcome this difficulty is to apply supernode techniques. In this method, the two adjacent nodes that are connected by a voltage source are reduced to a single node & then the eq's are formed by applying the Kirhoff's current law as usual. This is explained with the help of fig. below:

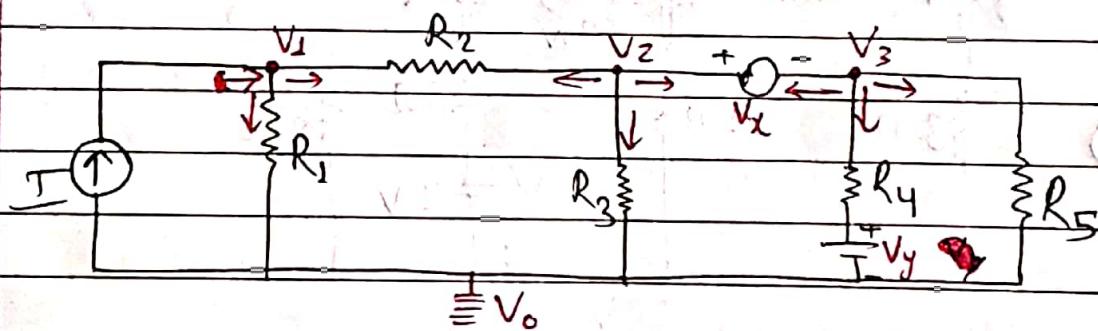

Applying KCL at node -1:

$$I = \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_o}{R_1} \quad \text{--- (1)}$$

Due to the presence of voltage source V_x in both node -2 & node -3, it is slightly difficult to find out the current. The super node techniques can conveniently be applied in this case. Accordingly, we can write the combined eq for node -2 & node -3 as under:


$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_o}{R_3} + \frac{V_3 - V_o}{R_5} + \frac{V_3 - V_y}{R_4} = 0 \quad \text{--- (2)}$$

Other eqⁿ:

$$V_2 - V_3 = V_x \quad \text{--- (III)}$$

from above three eqⁿ's, we find the three unknown voltage.

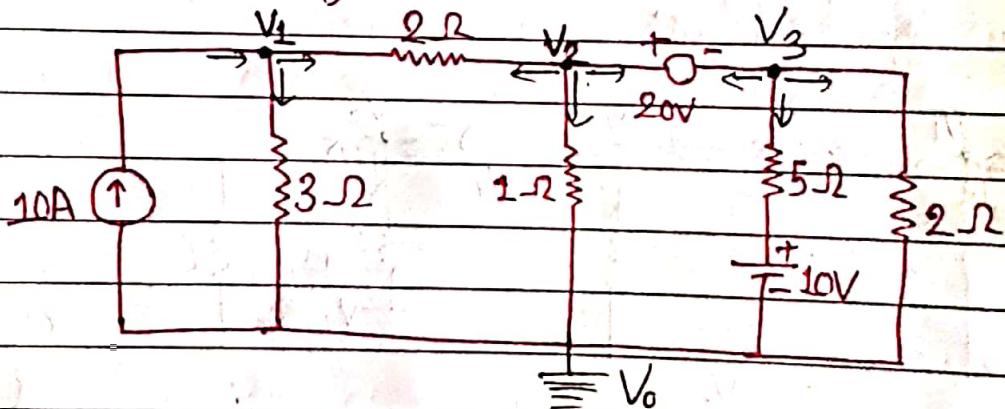- Q. Determine the current in 5Ω resistor for the ckt shown in fig. below:



Consider node -1:

$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_0}{3} = 10 \quad \text{--- (1)}$$

$$\text{on } V_1 \left(\frac{1}{2} + \frac{1}{3} \right) - \frac{V_2}{2} = 10$$

$$\text{on } \frac{5}{6}V_1 - \frac{V_2}{2} = 10 \quad \text{--- (1)}$$

Combine eqⁿ of node -2 & node -3:

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_0}{1} + \frac{V_3 - V_0}{2} + \frac{V_3 - V_0 - 10}{5} = 0$$

$$\text{on } V_1 \left(-\frac{1}{2} \right) + V_2 \left(\frac{1}{2} + 1 \right) + V_3 \left(\frac{1}{2} + \frac{1}{5} \right) = 2$$

$$\text{on } -\frac{1}{2}V_1 + \frac{3}{2} \cdot V_2 + \frac{7}{10} \cdot V_3 = 2 \quad \text{(I)}$$

Other eqⁿ:

$$V_2 - V_3 = 20 \quad \text{--- (II)}$$

Solving,

$$V_1 = 18.95 \text{ V}$$

$$V_2 = 11.58 \text{ V}$$

$$V_3 = -8.42 \text{ V}$$